

Chapter5-Synchronous Sequential Logic

Lecture7- Design of Clocked Sequential Circuits


Objectives

- Design of Clocked Sequential Circuits
- Conversion of Flip-Flops

Design Procedure

- Design starts from verbal specifications of design and results in a logic diagram or a list of Boolean functions.
- The steps to be followed are:
 - Derive a state diagram
 - Reduce the number of states
 - Assign binary values to the reduced states
 - Obtain the binary coded state table
 - Choose the type of flip flops to be used
 - Derive the simplified flip flop input equations and output equations
 - Draw the logic diagram

Design Steps

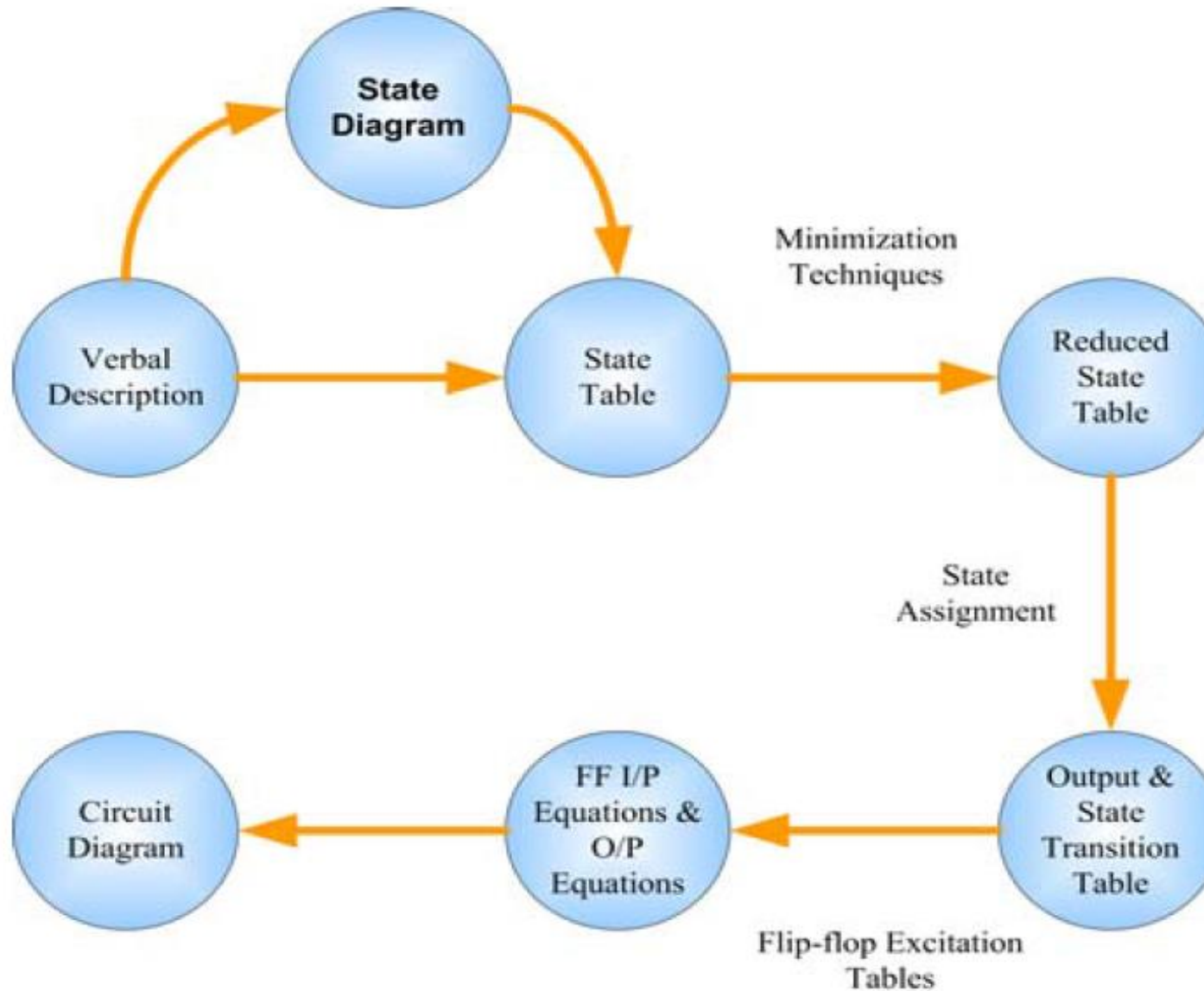

Design Example: A Sequence Detector

- Design a sequence detector (Moore FSM) that detects three or more consecutive 1's from the serial binary data.
 - From the verbal specifications of design, we derive state diagram as shown below.

 


Fig. 5-24 State Diagram for Sequence Detector

Synthesis Using D Flip Flops

- The next step is to create a state table and reduce states. No state reduction is possible in our design example.
- Make binary assignment to the four states i.e 00, 01, 10, and 11 and list Transition Table (Binary Coded State Table).
- Choose the type of flip-flops i.e two D flip flops to represent four states, and label their outputs as A and B.
- There is one input, x, and one output, y, representing the input sequence and the output value respectively.
- Remember that the characteristic equation of the D flip flop is
 - $Q(t + 1) = D_Q$
 - This means that the next-state values in the state table specify the D input condition for the flip flop.

State Table for Sequence Detector

| Present State | | | Input | | Next State | | | Output |
|---------------|---|--|-------|--|------------|---|--|--------|
| A | B | | x | | A | B | | y |
| 0 | 0 | | 0 | | 0 | 0 | | 0 |
| 0 | 0 | | 1 | | 0 | 1 | | 0 |
| 0 | 1 | | 0 | | 0 | 0 | | 0 |
| 0 | 1 | | 1 | | 1 | 0 | | 0 |
| 1 | 0 | | 0 | | 0 | 0 | | 0 |
| 1 | 0 | | 1 | | 1 | 1 | | 0 |
| 1 | 1 | | 0 | | 0 | 0 | | 1 |
| 1 | 1 | | 1 | | 1 | 1 | | 1 |

- Input equations can be obtained directly from the table using minterms:
 - $A(t + 1) = D_A(A, B, x) = \sum(3, 5, 7)$
 - $B(t + 1) = D_B(A, B, x) = \sum(1, 5, 7)$
 - $y(A, B, x) = \sum(6, 7)$

Boolean Minimization

- K-Maps can be used to minimize the input equations, resulting in
 - $D_A = Ax + Bx$; $D_B = Ax + B'x$; $Y = AB$

 


Fig. 5-25 Maps for Sequence Detector

- From Flip Flop Input Equations and Output Equation we can draw the logic diagram of the circuit as shown in the next slide.

Logic Diagram


 


Fig. 5-26 Logic Diagram of Sequence Detector

Timing Diagram Moore

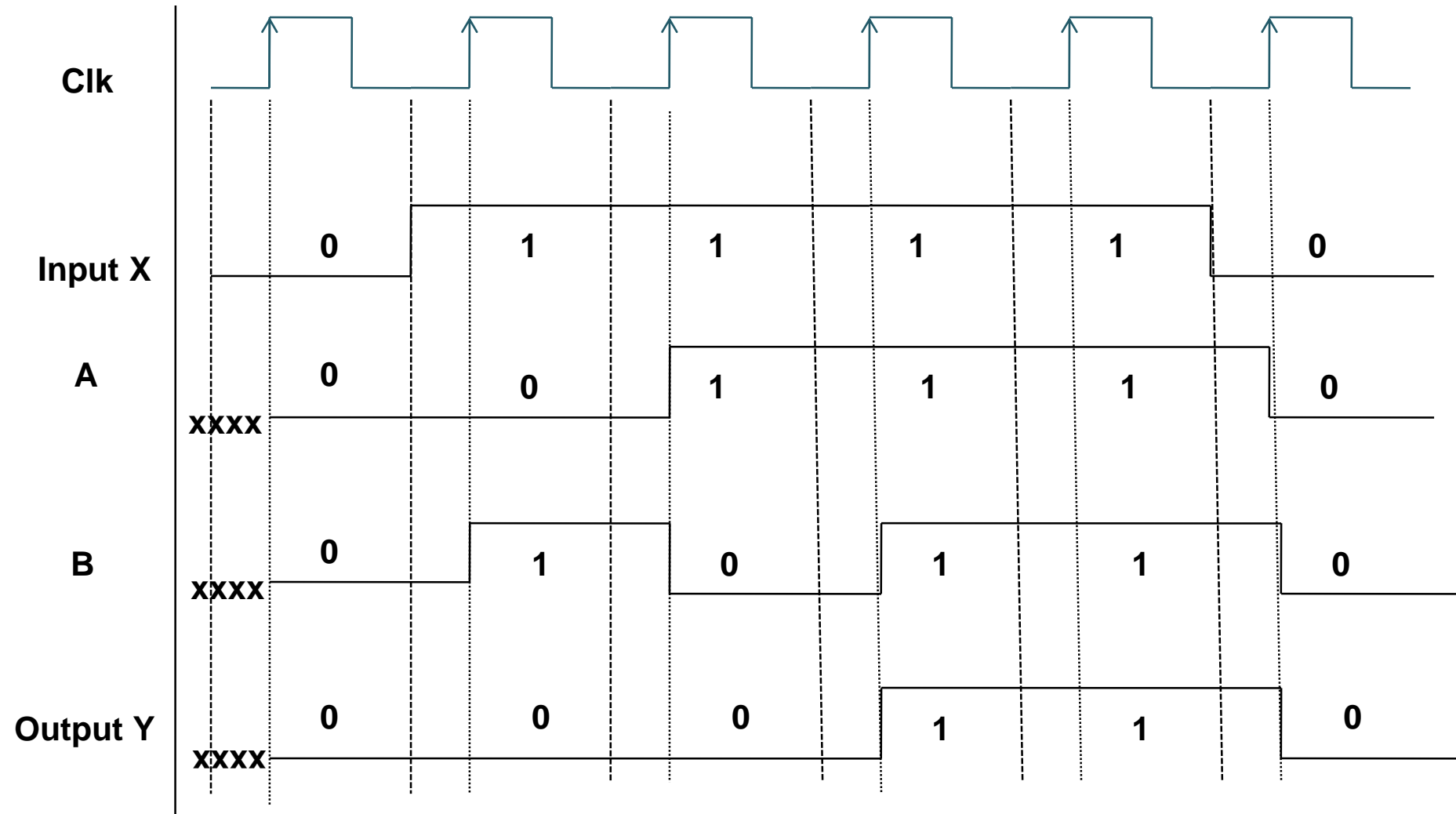Example:

Sequence detector to detect three or more consecutive 1's



$$Y=AB$$

Fall 2021

Excitation Table

- The design of sequential circuits other than D type flip flops is complicated by the fact that input equations must be derived indirectly from the state table.
 - It is necessary to derive a functional relationship between the state table and the input equations.
- During the design, we usually know the transition from present to next state but we need to find the flip flop input conditions that will cause the required transition.
 - We need a table that lists the required inputs for a given change of state, called an **excitation table**.

Excitation Tables for JK and T Flip-Flops

| JK Flip Flop | | | |
|--------------|---|----------|------------|
| J | K | $Q(t+1)$ | |
| 0 | 0 | $Q(t)$ | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | $Q'(t)$ | Complement |



| $Q(t)$ | $Q(t+1)$ | J | K |
|--------|----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

| T Flip Flop | | |
|-------------|----------|------------|
| T | $Q(t+1)$ | |
| 0 | $Q(t)$ | No change |
| 1 | $Q'(t)$ | Complement |



| $Q(t)$ | $Q(t+1)$ | T |
|--------|----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Synthesis Using JK Flip Flops

- Synthesis of circuits with JK flip flops is the same as with D flip flops except that the input equations must be evaluated from the present-state to the next-state transition derived from the excitation table.
- Consider a sequential circuit described by the state table shown in the next slide.
- Note that one extra section i.e Flip Flop Inputs has been added and we are required to derive algebraic expressions for Flip Flop Inputs as a function of present state and external inputs.

Example JK Synthesis

| Present State | | Input | Next State | | Flip-Flop Inputs | | | |
|---------------|---|-------|------------|---|------------------|----------------|----------------|----------------|
| A | B | X | A | B | J _A | K _A | J _B | K _B |
| 0 | 0 | 0 | 0 | 0 | 0 | X | 0 | X |
| 0 | 0 | 1 | 0 | 1 | 0 | X | 1 | X |
| 0 | 1 | 0 | 1 | 0 | 1 | X | X | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | X | X | 0 |
| 1 | 0 | 0 | 1 | 0 | X | 0 | 0 | X |
| 1 | 0 | 1 | 1 | 1 | X | 0 | 1 | X |
| 1 | 1 | 0 | 1 | 1 | X | 0 | X | 0 |
| 1 | 1 | 1 | 0 | 0 | X | 1 | X | 1 |

| Q(t) | Q(t+1) | J | K |
|------|--------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

JK Synthesis Logic Cont...

- By using K-maps we can minimize the flip flop input equations as under:-

$$J_A = Bx'; K_A = Bx \quad J_B = x; K_B = (A \oplus x)'$$

| | | | | | |
|-----|---|------|-----|-----|-----|
| | | Bx | | B | |
| | | 0 0 | 0 1 | 1 1 | 1 0 |
| A | 0 | | | | 1 |
| A | 1 | X | X | X | X |

$J_A = Bx'$

| | | | | | |
|-----|---|------|-----|-----|-----|
| | | Bx | | B | |
| | | 0 0 | 0 1 | 1 1 | 1 0 |
| A | 0 | X | X | X | X |
| A | 1 | | | 1 | |

$K_A = Bx$

| | | | | | |
|-----|---|------|-----|-----|-----|
| | | Bx | | B | |
| | | 0 0 | 0 1 | 1 1 | 1 0 |
| A | 0 | | 1 | X | X |
| A | 1 | | 1 | X | X |

$J_B = x$

| | | | | | |
|-----|---|------|-----|-----|-----|
| | | Bx | | B | |
| | | 0 0 | 0 1 | 1 1 | 1 0 |
| A | 0 | X | X | | 1 |
| A | 1 | X | X | 1 | |

$K_B = (A \oplus x)'$

Fig. 5-27 Maps for J and K Input Equations

JK Synthesis Logic Cont...

 


Fig. 5-28 Logic Diagram for Sequential Circuit with JK Flip-Flops

Synthesis using T flip-flops

Example: Three-bit binary counter Design. The state diagram is as shown

State Table

| Present State | | | Next State | | | Flip-Flop Inputs | | |
|---------------|-------|-------|------------|-------|-------|------------------|----------|----------|
| A_2 | A_1 | A_0 | A_2 | A_1 | A_0 | T_{A2} | T_{A1} | T_{A0} |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter

Synthesis using T flip-flops Cont...

- By using K-maps we can minimize the flip flop input equations as under:-

$$T_{A2} = A_1 A_0; \quad T_{A1} = A_0; \quad T_{A0} = 1$$

 


Fig. 5-30 Maps for 3-Bit Binary Counter

Synthesis using T flip-flops Cont...

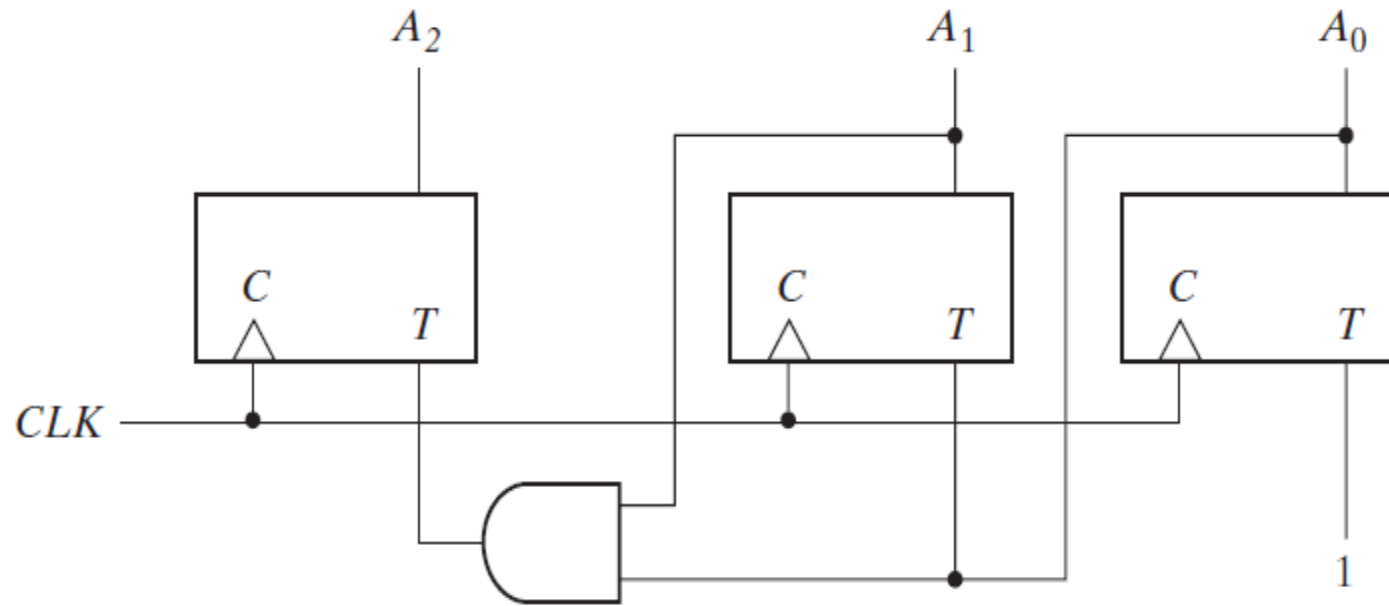


Fig. 5-31 Logic Diagram of 3-Bit Binary Counter

Design Example: A Sequence Detector

- Design a sequence detector (Mealy FSM) that detects three or more consecutive 1's from the serial binary data.
 - From the verbal specifications of design, we derive state diagram as shown below.

Problem: Design a Sequence detector to detect an overlapping sequence 1010

Design a FSM that has one input w and one output z . The machine is a sequence detector that produces $z=1$ when the previous two values of w were 00 or 11; otherwise $z=0$.


Conversion of Flip-Flops

- We can convert one flip flop to another by the following procedure.
 - List characteristic table of flip flop to be constructed.
 - From this derive excitation table of the given flip flop.
 - Derive flip flop input equations of given flip flop as a function of present state and inputs of flip flop to be designed.
 - From this we can draw the logic diagram of new flip-flop and perform hardware implementation.

Example-Conversion From D to T Flip-Flop

| T | Q(t) | Q(t+1) | D |
|---|------|--------|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

$$D = T \oplus Q(t)$$

 

Conversion from D to T Flip Flop

The End