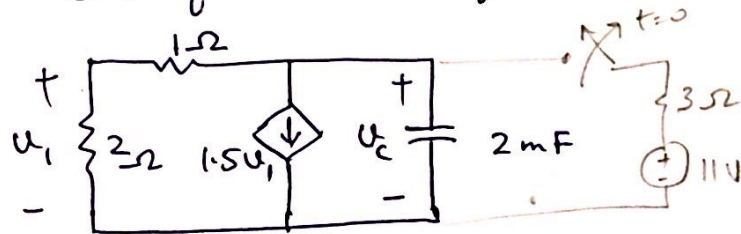


(MUST)

(Pdf)

Pract 8.7 General RC Circuit
(PP 282 8th Ed HKD)

Determine $u_c(t)$ for $t > 0$ if $u_c(0) = 11 \text{ volts}$.




Solution: The circuit is identified as a source-free RC circuit.

— Its response will be of the form

$$u_c(t) = V_{co} e^{-t/\tau} \text{ V}$$

$$\text{where } \tau = R_{eq} C_{eq}$$

— To calculate R_{eq} ?

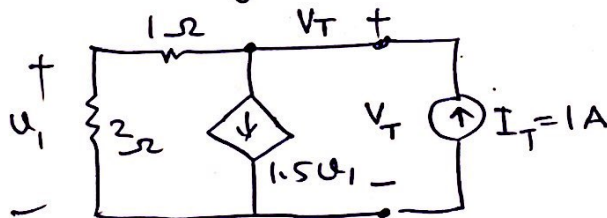

— and $R_{eq} = \frac{V_T}{I_T}$

— Writing KCL at node V_T :

$$\frac{V_T - u_1}{1} + 1.5u_1 = 1$$

$$\text{or } V_T + 0.5u_1 = 1 \quad \text{--- (1) --- contd}$$

— contd (282)

Also $V_1 = (1 - 1.5V_1) \times 2$ (KCL at top node)

$$V_1 = 2 - 3V_1$$

$$4V_1 = 2$$

$$V_1 = 0.5 \quad \text{--- (2)}$$

— Putting in (1)

$$V_T + 0.5 \times 0.5 = 1$$

$$V_T = 1 - 0.25 = 0.75$$

$$V_T = 0.75$$

— Hence $R_{eq} = \frac{0.75}{1} = 0.75 \Omega$.

— So $\tau = R_{eq}C = 0.75 \times 2 \times 10^{-3}$

$$\tau = 1.5 \times 10^{-3} \text{ s}$$

— Thus $V_c(t) = V_0 e^{-t/\tau} \text{ V}$

$$V_c(t) = 11 e^{-\frac{t}{1.5 \times 10^{-3}}}$$

$$V_c(t) = 11 e^{-\frac{10}{15} \times 10^3 t}$$

$$V_c(t) = 11 e^{-\frac{2}{3} \times 10^3 t} \text{ V}, \quad t > 0$$

Note: NOW voltage across 2Ω and 1Ω can be found by voltage division rule.

$$\text{So } V_1(t) = \frac{2}{3} \times 11 e^{-\frac{2}{3} \times 10^3 t}$$

$$\text{and } V_2(t) = \frac{1}{3} \times 11 e^{-\frac{2}{3} \times 10^3 t} \text{ Volts}$$