

# EE-421: Digital System Design

## **Multiplier on FPGA and It's Performance**

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Multiplication

# Multiplication


Multiplying **1-bit numbers** is an **AND** operation

$$0 \times 0 = 0$$

$$0 \times 1 = 0$$

$$1 \times 0 = 0$$


$$1 \times 1 = 1$$

 
 
# Multiplication

Multiplying 1-bit x N-bit is AND operation

$A \times B = P$   
 $1011 \times 0 = 0000$   
 $1011 \times 1 = 1011$



# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

$$\begin{array}{r} \phantom{x} \phantom{A_3} \phantom{A_2} \phantom{A_1} \phantom{A_0} \\ \phantom{x} \phantom{A_3} \phantom{A_2} \phantom{A_1} \phantom{A_0} \\ \phantom{x} \phantom{A_3} \phantom{A_2} \phantom{A_1} \phantom{A_0} \\ \phantom{x} \phantom{A_3} \phantom{A_2} \phantom{A_1} \phantom{A_0} \\ \phantom{x} \phantom{A_3} \phantom{A_2} \phantom{A_1} \phantom{A_0} \\ \hline \end{array}$$

# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

$$\begin{array}{rcccc} & A_3 & A_2 & A_1 & A_0 \\ X & B_3 & B_2 & B_1 & B_0 \\ \hline & A_3 B_0 & A_2 B_0 & A_1 B_0 & A_0 B_0 \end{array}$$

# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

	$A_3$	$A_2$	$A_1$	$A_0$
X	$B_3$	$B_2$	$B_1$	$B_0$
<hr/>				
	$A_3 \cdot B_0$	$A_2 \cdot B_0$	$A_1 \cdot B_0$	$A_0 \cdot B_0$
$A_3 \cdot B_1$	$A_2 \cdot B_1$	$A_1 \cdot B_1$	$A_0 \cdot B_1$	

# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

		$A_3$	$A_2$	$A_1$	$A_0$
	X	$B_3$	$B_2$	$B_1$	$B_0$
		$A_3 \cdot B_0$	$A_2 \cdot B_0$	$A_1 \cdot B_0$	$A_0 \cdot B_0$
	$A_3 \cdot B_1$	$A_2 \cdot B_1$	$A_1 \cdot B_1$	$A_0 \cdot B_1$	
$A_3 \cdot B_2$	$A_2 \cdot B_2$	$A_1 \cdot B_2$	$A_0 \cdot B_2$		



# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

		$A_3$	$A_2$	$A_1$	$A_0$
	X	$B_3$	$B_2$	$B_1$	$B_0$
		$A_3 \cdot B_0$	$A_2 \cdot B_0$	$A_1 \cdot B_0$	$A_0 \cdot B_0$
	$A_3 \cdot B_1$	$A_2 \cdot B_1$	$A_1 \cdot B_1$	$A_0 \cdot B_1$	
	$A_3 \cdot B_2$	$A_2 \cdot B_2$	$A_1 \cdot B_2$	$A_0 \cdot B_2$	
$A_3 \cdot B_3$	$A_2 \cdot B_3$	$A_1 \cdot B_3$	$A_0 \cdot B_3$		

# N-Bit x N-Bit (Unsigned) Multiplication

Consider 4-bit x 4-bit Multiplication

				$A_3$	$A_2$	$A_1$	$A_0$
			X	$B_3$	$B_2$	$B_1$	$B_0$
				$A_3 \cdot B_0$	$A_2 \cdot B_0$	$A_1 \cdot B_0$	$A_0 \cdot B_0$
			$A_3 \cdot B_1$	$A_2 \cdot B_1$	$A_1 \cdot B_1$	$A_0 \cdot B_1$	
		$A_3 \cdot B_2$	$A_2 \cdot B_2$	$A_1 \cdot B_2$	$A_0 \cdot B_2$		
+	$A_3 \cdot B_3$	$A_2 \cdot B_3$	$A_1 \cdot B_3$	$A_0 \cdot B_3$			
$P_7$	$P_6$	$P_5$	$P_4$	$P_3$	$P_2$	$P_1$	$P_0$

# N-Bit x N-Bit (Unsigned) Multiplication

## Consider 4-bit x 4-bit Multiplication


*AB<sub>i</sub> called a "partial product"* →

				$A_3$	$A_2$	$A_1$	$A_0$	
			X	$B_3$	$B_2$	$B_1$	$B_0$	
				$A_3 B_0$	$A_2 B_0$	$A_1 B_0$	$A_0 B_0$	
				$A_3 B_1$	$A_2 B_1$	$A_1 B_1$	$A_0 B_1$	
		$A_3 B_2$	$A_2 B_2$	$A_1 B_2$	$A_0 B_2$			
+	$A_3 B_3$	$A_2 B_3$	$A_1 B_3$	$A_0 B_3$				
$P_7$	$P_6$	$P_5$	$P_4$	$P_3$	$P_2$	$P_1$	$P_0$	

**Sounds familiar, Right! : Multiplication by Hand**

**How to express this multiplication in Hardware?**
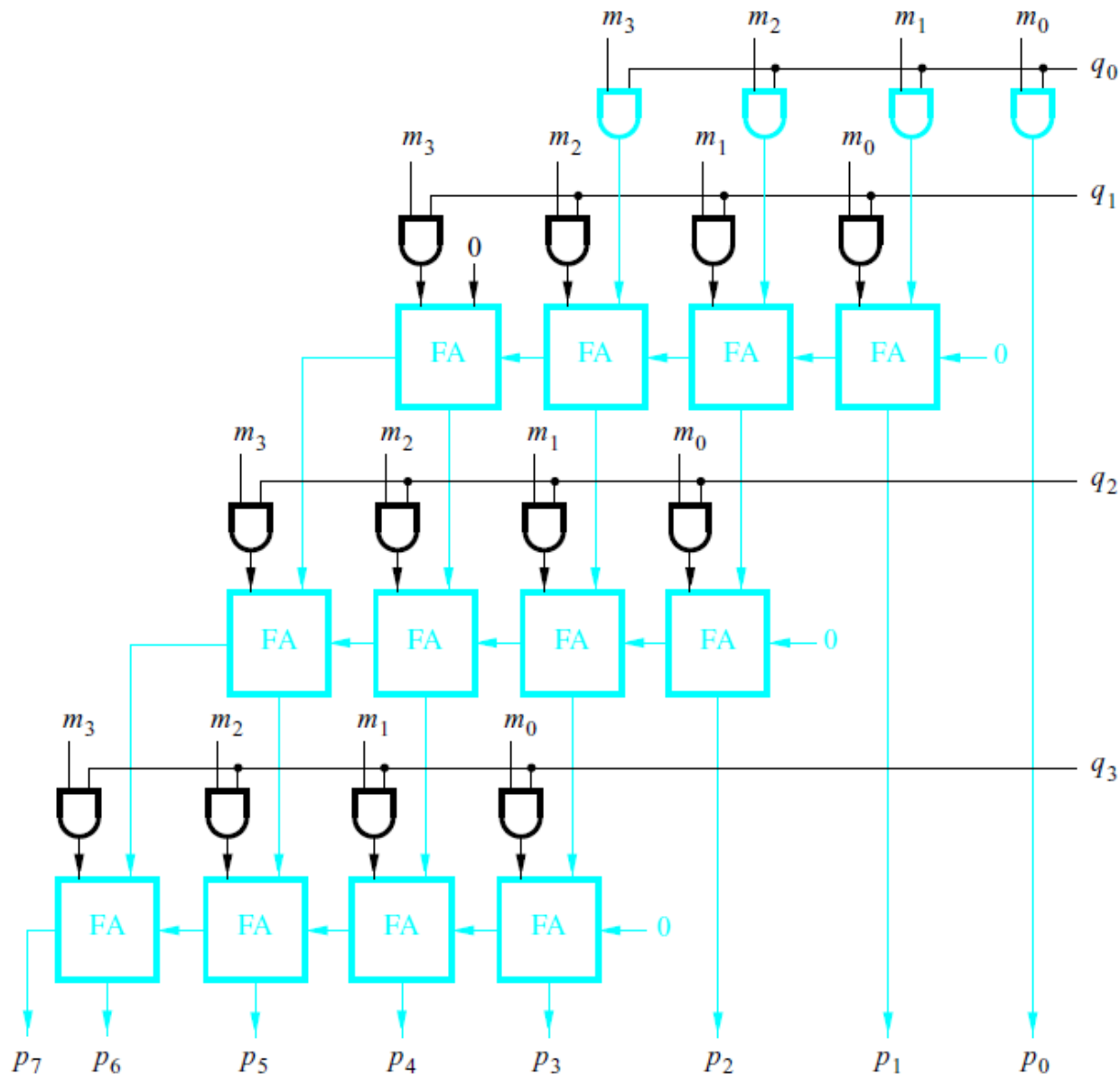
# Hardware Implementation: N-Bit x N-Bit (Unsigned) Multiplication




# Hardware Implementation: N-Bit x N-Bit (Unsigned) Multiplication

Do you see any problem in  
this circuit?

Yes, the curse of carry!


Easy Part: forming partial products

Hard Part: Adding partial products

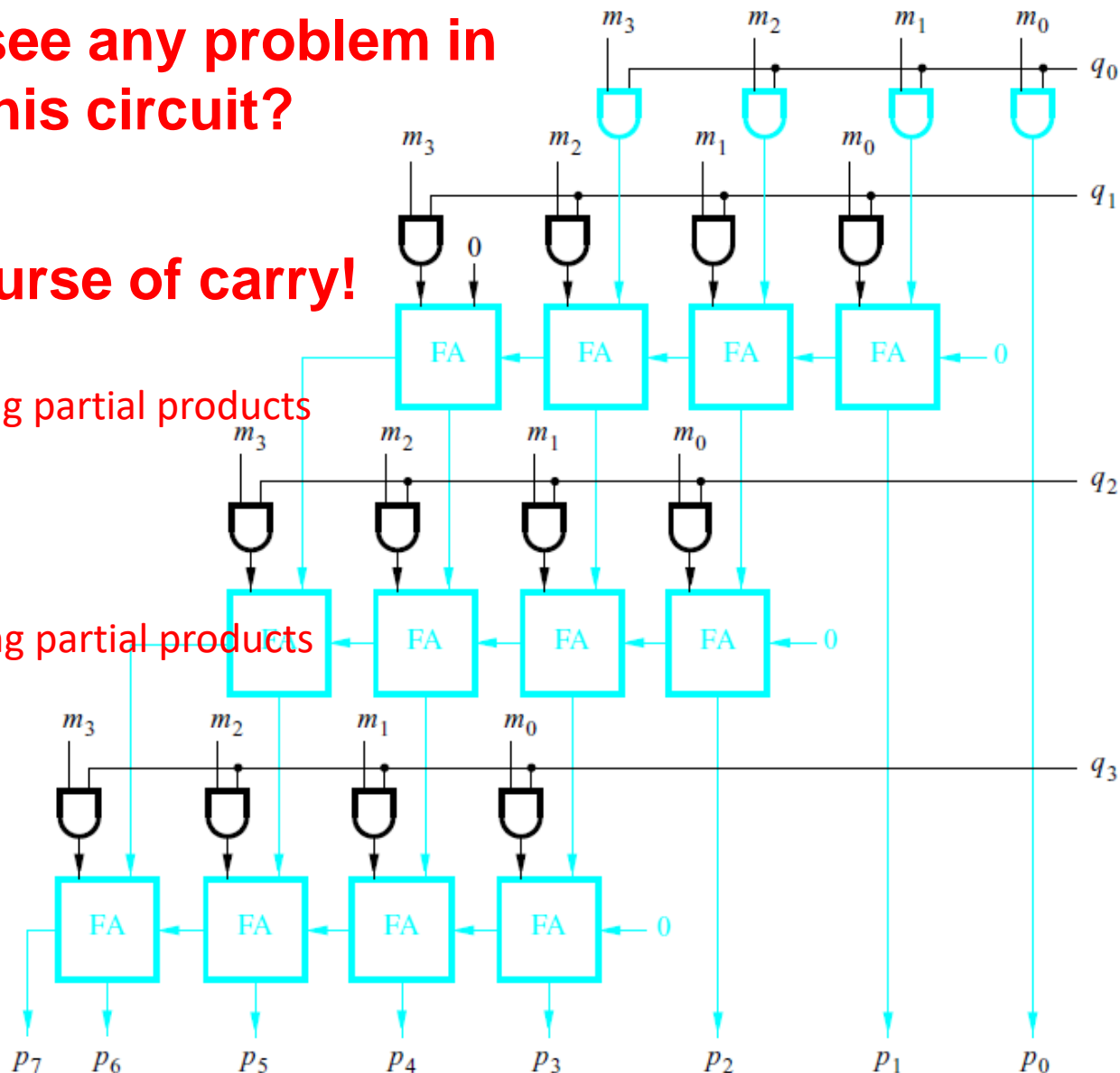


# Propagation Delay

Propagation Delay  $\sim 2N$

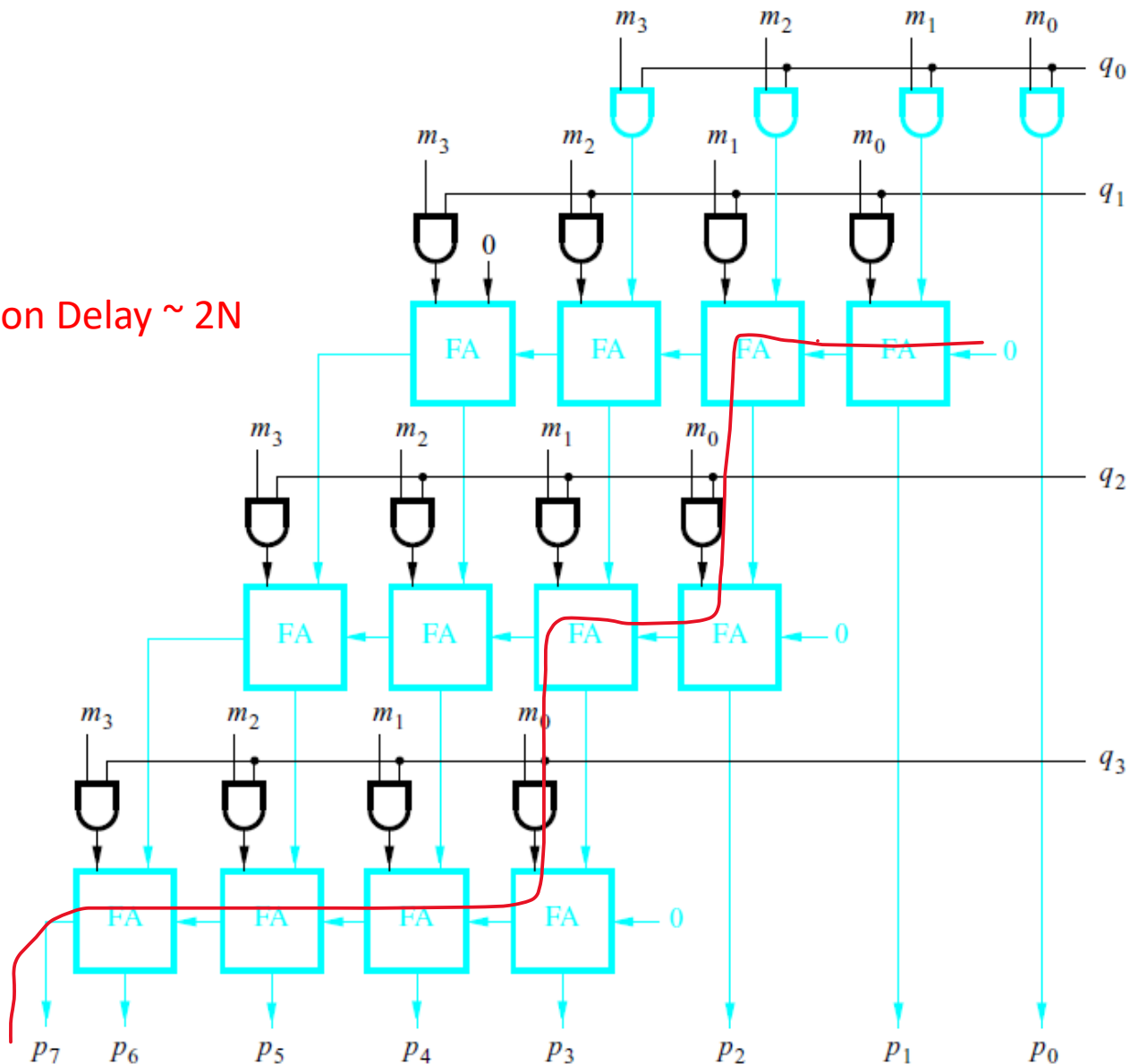
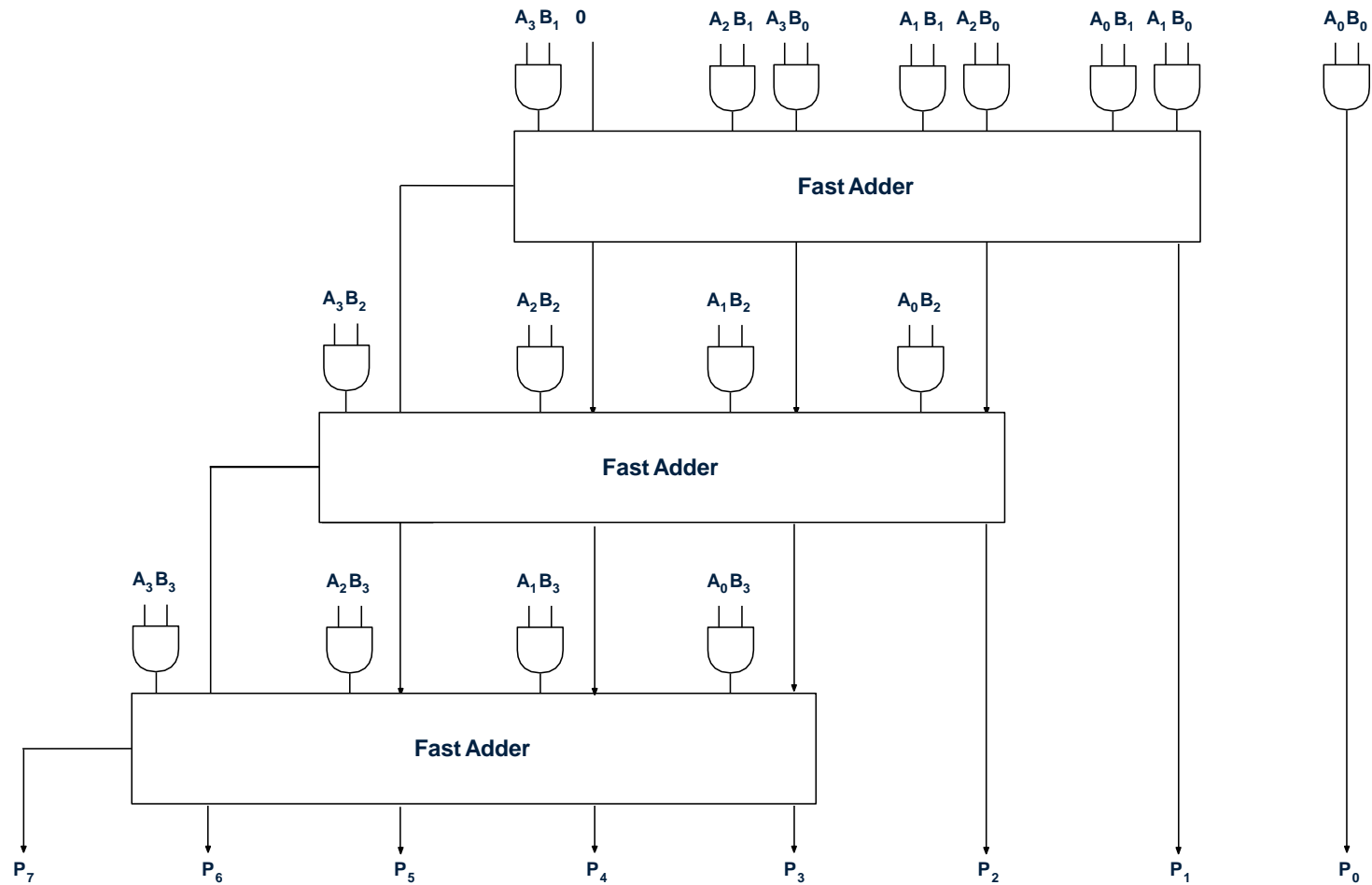
# Using Fast Adders as Discussed Previously



# FPGA Implementation of a Combinational Multiplier

- In Verilog:

$$\mathbf{P} = \mathbf{A} * \mathbf{B};$$

(make sure **P** has twice the number of bits of **A** and **B**)

- Synthesis tool will create a combinational multiplier if DSP Block inference is turned off.



# $F_{\max}$ of a Combinational Multiplier

- Measured on our Cyclone FPGA:

Multiplier Width (in bits)	$F_{\max}$ (MHz)
8 x 8	464
16 x 16	396
32 x 32	104
64 x 64	66

# THANK YOU

