



Chapter2: Boolean Algebra and Logic Gates

Lecture2- Boolean Functions, Different Representations, and Complement of a Function

Engr. Arshad Nazir, Asst Prof
Dept of Electrical Engineering
SEECS

Objectives

- Study Boolean Functions and different representations of a Boolean function
- Algebraic manipulations of Boolean functions
- Complement of a function

Boolean Functions

- A **Boolean function** is an expression described by:
 - binary variables
 - constants 0 and 1
 - logic operation symbols
- For a given value of the binary variables the result of the function can either be 0 or 1.
- An example function:
 - $F_1 = x + y'z$
 - F_1 is equal to 1 if x is equal to 1 or if both y' and z equal to 1. F_1 is equal to 0 otherwise

Function as a Truth Table

- A **Boolean function** can be represented in a **truth table**.
 - A truth table is a list of combinations of 1's and 0's assigned to the binary variables and a column that shows the value of the function for each binary combination

| x | y | z | | $F_1 = x + y'z$ |
|----------|----------|----------|--|-----------------------------------|
| 0 | 0 | 0 | | 0 |
| 0 | 0 | 1 | | 1 |
| 0 | 1 | 0 | | 0 |
| 0 | 1 | 1 | | 0 |
| 1 | 0 | 0 | | 1 |
| 1 | 0 | 1 | | 1 |
| 1 | 1 | 0 | | 1 |
| 1 | 1 | 1 | | 1 |

Function as a Gate Implementation

- A **Boolean function** can be transformed from an algebraic expression into **circuit diagram** composed of **logic gates**.
 - $F_1 = x + y'z$
 - The logic-circuit diagram for this function is shown below:



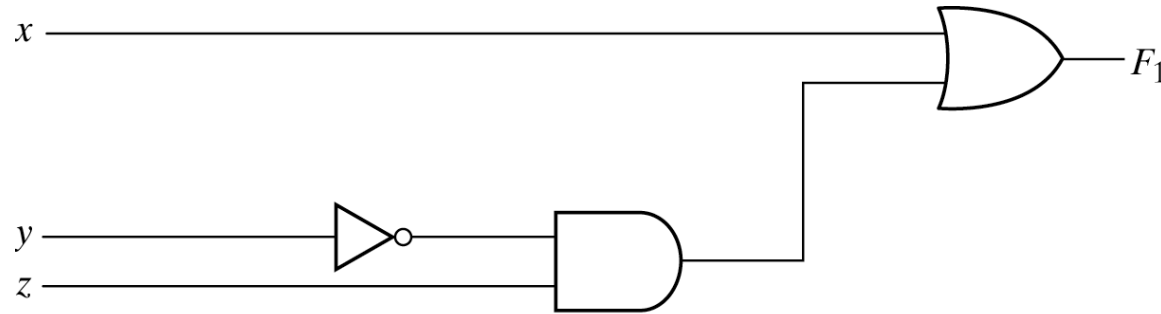


Fig. 2-1 Gate implementation of $F_1 = x + y'z$

Gate Implementation (Examples)

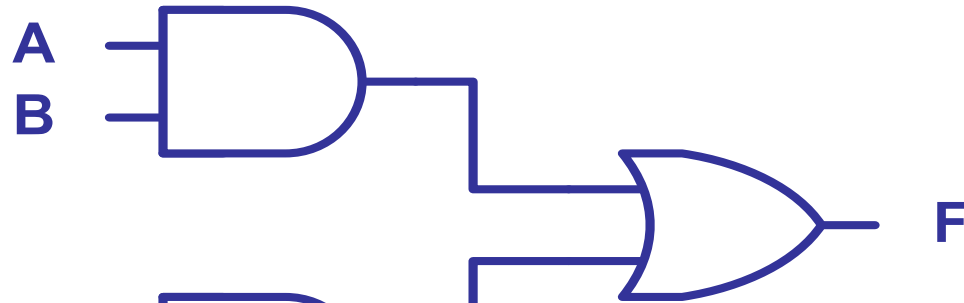


$$F = AB + AC$$

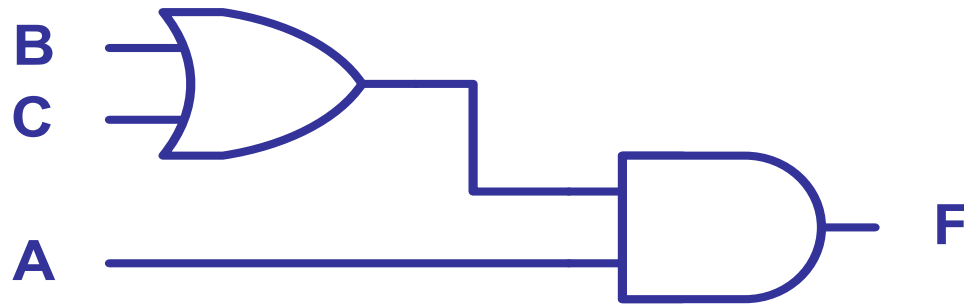


$$F = A(B + C)$$

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Gate Implementation (Examples)

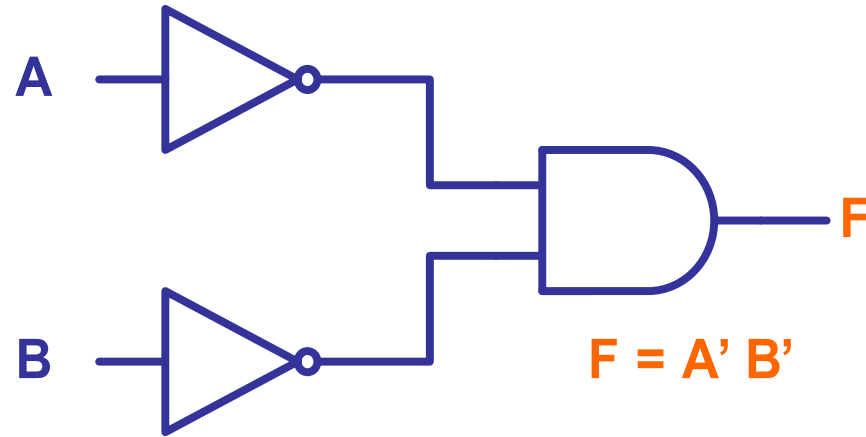

$$F = A' B'$$

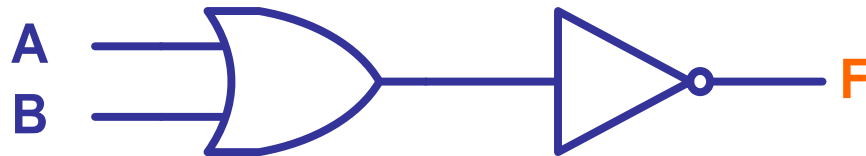

$$F = (A + B)'$$

| A | B | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


Functions Minimization

- Functions in algebraic form can be represented in various ways.
 - Remember the postulates and theorems that allow us to represent a function in various ways.
- We must keep in mind that the algebraic expression is representative of the gates and circuitry used in a hardware piece.
 - We want to be able to minimize circuit design to reduce cost, power consumption, and package count, and to increase speed.
- By manipulating a function using the postulates and theorems, we may be able to minimize an expression.

Non-Minimized Function

- The following is an example of a non-minimized function:

➤ $F_2 = x'y'z + x'yz + xy'$

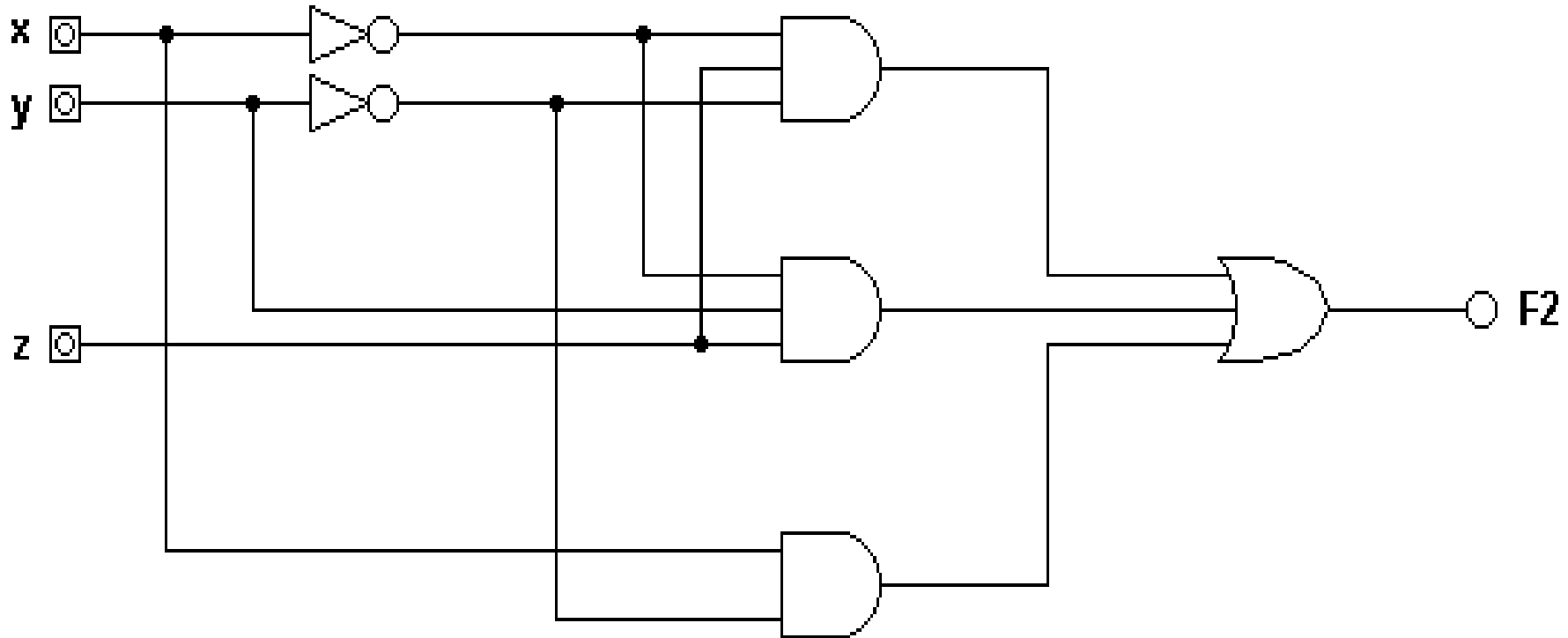

Minimization of the F_2


- The function can be minimized as follows:

$$X'y'z + x'yz + xy' =$$

$$= x'z \cdot (y' + y) + xy' \quad \text{postulate} \quad 4(a)$$


$$= x'z \cdot 1 + xy' \quad 5(a)$$

$$= x'z + xy' \quad 2(b)$$

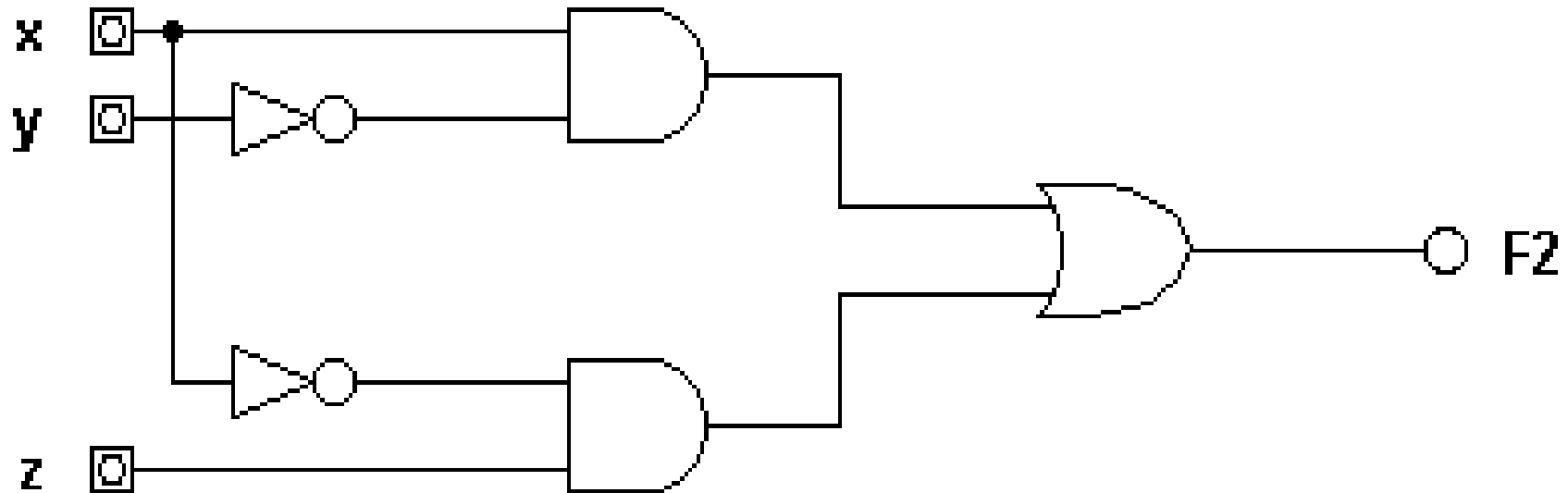


Implementations of Boolean Function F_2

- Non-minimized Function

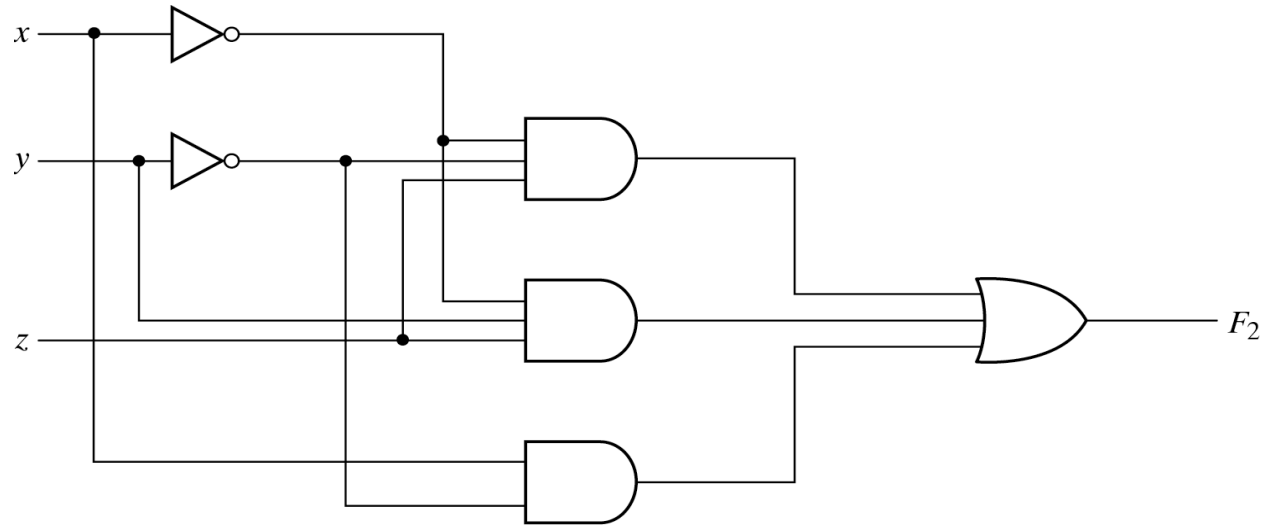

(a) $F_2 = x'y'z + x'yz + xy'$

- Minimized Function

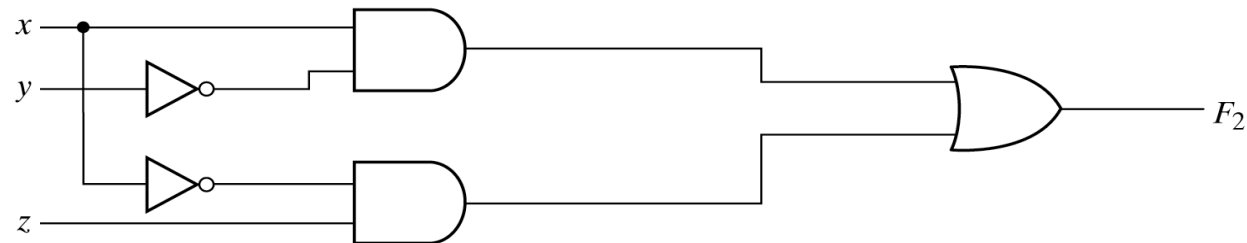

(b) $F_2 = xy' + x'z$

Fig. 2-2 Implementation of Boolean function F_2 with gates

Algebraic Manipulation

- By reducing the number of **terms**, the number of **literals** (single variable) or both in a Boolean function, it is possible to obtain a simpler circuit, as each term requires a gate and each variable within the term designates an input to the gate .
- For example consider the following function F_1
 $F_1 = x'y'z + x'yz + xy'$ which contains 3 terms and 8 literals
After simplification the minimized function is $F_2 = x'z + xy'$ and it contains 2 terms and 4 literals.
- The reduced function contains lesser terms and literals. It can now be implemented with fewer gates i.e optimized design.

Example Manipulations

- The following are some example manipulations:
 1. $x(x' + y) = xx' + xy = 0 + xy = xy$
 2. $x + x'y = (x + x')(x + y) = 1(x + y) = x + y$
 3. $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x$
 4. $xy + x'z + yz = xy + x'z + yz(x + x')$
$$= xy + x'z + xyz + x'yz$$
$$= xy(1 + z) + x'z(1 + y)$$
$$= xy + x'z$$
 5. $(x + y)(x' + z)(y + z) = (x + y)(x' + z)(y + z + x.x')$
$$= (x + y)(x' + z)(y + z + x)(y + z + x')$$
$$= (x + y)(x + y + z)(x' + z)(x' + z + y)$$
$$= (x + y)(x' + z)$$

Complement of a Function

- The complement of a function F is F' .
 - It is obtained by interchanging 0's for 1's and 1's for 0's in the value of F .
- The **complement** of a function may be derived algebraically through **DeMorgan's theorem**.
 - Theorem 5(a) (DeMorgan): $(x + y)' = (x' \cdot y')$
 - Theorem 5(b) (DeMorgan): $(x \cdot y)' = (x' + y')$
- Example:
 - $F_1 = x'yz' + x'y'z$
 $F_1' = (x'yz' + x'y'z)'$
 $= (x + y' + z)(x + y + z')$

Complement of a Function (Example)


- If $F_1 = A+B+C$
- Then $F_1' = (A+B+C)'$
 - $= (A+X)'$ let $B+C = X$
 - $= A'X'$ by DeMorgan's
 - $= A'(B+C)'$
 - $= A'(B'C')$ by DeMorgan's
 - $= A'B'C'$ associative
- The generalized expression for DeMorgan's law for a function with multiple terms is
 - $(A+B+C+D+....)' = A'.B'.C'.D'.....$
 - $(A.B.C.D.....)' = A'+B'+C'+D'+....$

Complement of a Function (More Examples)

- $F = x'yz' + x'y'z$
 $F' = (x'yz' + x'y'z)'$
 $F' = (x'yz')' (x'y'z)'$
 $= (x+y'+z) (x+y+z')$
- $F = [x(y'z' + yz)]$
 $F' = [x(y'z' + yz)]'$
 $F' = x' + (y'z' + yz)'$
 $= x' + (y'z')' \cdot (yz)'$
 $= x' + (y+z) (y'+z')$
- A simpler procedure
 - take the **dual** of the function (interchanging AND and OR operators and 1's and 0's) and **complement** each literal. {DeMorgan's Theorem}
 - $x'yz' + x'y'z$
The **dual** of function: $F_D = (x'+y+z') (x'+y'+z)$
Complement of each literal: $F' = (x+y'+z)(x+y+z')$

Representation Conversion

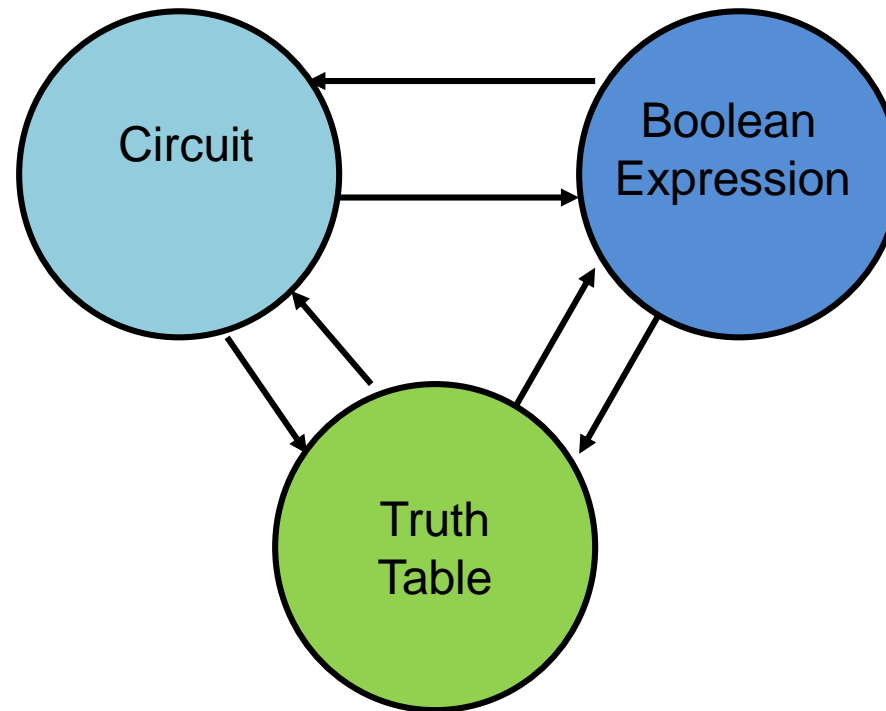- Need to transition between Boolean expression, truth table, and circuit (symbols).
- Converting between truth table and expression is easy.
- Converting between expression and circuit is easy.
- More difficult to convert to truth table.



Different Representations of a Boolean Function

- Standard Forms are sum-of-products and product-of-sums
 - Sum-of-Products (SOP) i.e $F(X,Y,Z)=X'+YZ$
 - Product-of-Sums (POS) i.e $F(X,Y,Z)=(X'+Y)Z$
- Canonical Forms are sum-of-minterms (SSOP) and product-of-maxterms (SPOS)
 - Standard Sum-of-Products (SSOP) i.e $F(X,Y,Z)=X'Y'Z+X'YZ'+XYZ$
 - Standard Product-of-Sums (SPOS) i.e $F(X,Y,Z)=(X'+Y'+Z')(X'+Y'+Z)(X+Y+Z)$
- Non-Standard or Mixed Forms are those neither in standard nor canonical forms
i.e $F(X,Y,Z)=X'(Y'Z+YZ')+YZ$

The End