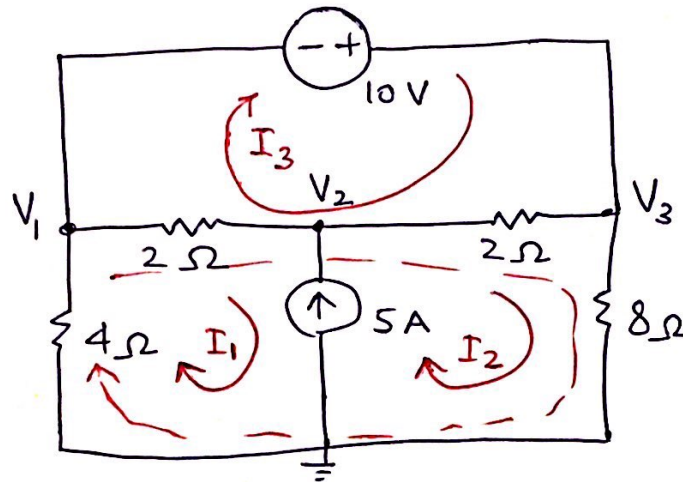


Prob: Mesh Analysis

Determine node voltages  $V_1$ ,  $V_2$  and  $V_3$  using mesh analysis.



Solution: Assign clockwise mesh currents to each mesh. Make a "Supermesh" by considering mesh '1' and '2' together. Draw a broken line to show "Supermesh".

— Apply KVL to "Supermesh" and remaining meshes.

$$4I_1 + 2(I_1 - I_3) + 2(I_2 - I_3) + 8I_2 = 0 \quad \text{--- (1)}$$

— Apply KVL to mesh "3";

$$2(I_3 - I_1) - 10 + 2(I_3 - I_2) = 0 \quad \text{--- (2)}$$

— The third required information is:

$$\text{Constraint} \Rightarrow I_2 - I_1 = 5 \quad \text{--- (3)}$$

— By solving (1), (2) and (3)

$$I_1 = -\frac{30}{12} \text{ A}, \quad I_2 = \frac{30}{12} \text{ A} \quad \text{and} \quad I_3 = \frac{30}{12} \text{ A}$$

$$\begin{aligned} \text{So } V_1 &= 10 \text{ volts} \\ V_2 &= 20 \text{ volts} \\ V_3 &= 20 \text{ volts} \end{aligned}$$

Note: No current flows thru  $2\Omega$  between  $V_2$  and  $V_3$ .