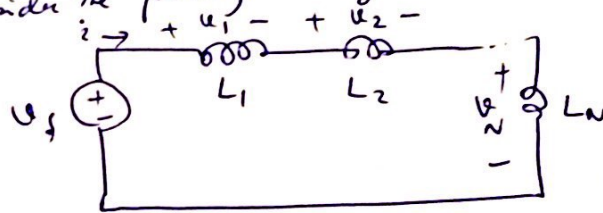


7.3 Inductance and Capacitance Combinations

(PP 235 8th Ed HKD)


Inductors in Series (PP 235)

Consider the following arrangement :-



The derived equivalent circuit (with v_s and $i(t)$ remaining same)

is :

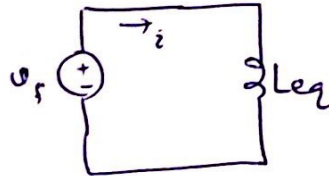

$$\text{Now } v_s = v_1 + v_2 + \dots + v_N$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + \dots + L_N) \frac{di}{dt}$$

For the equivalent circuit


$$v_s = L_{eq} \frac{di}{dt}$$

$$\text{Thus } L_{eq} = L_1 + L_2 + \dots + L_N$$


$$\text{or } L_{eq} = \sum_{n=1}^N L_n$$

Inductors in Parallel (PP236)

Consider

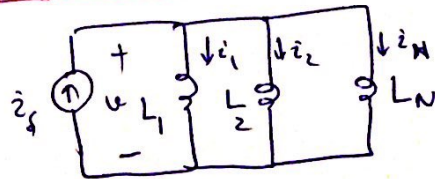

and equivalent ckt:

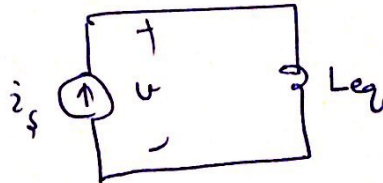

$$\text{Now } v = L_1 \frac{di_1}{dt} \quad \text{or} \quad i_1 = \frac{1}{L_1} \int v dt$$

$$\text{and } i_2 = \frac{1}{L_2} \int v dt \quad \text{and} \quad i_3 = \frac{1}{L_3} \int v dt$$

For the equivalent ckt:-

$$i_s = \frac{1}{L_{eq}} \int v dt$$

$$\text{So } i_s = i_1 + i_2 + \dots + i_N = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int v dt$$


$$\text{Hence } \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

For the special case of two inductors in parallel,


$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Capacitors in Series (PP 236)

Consider the following arrangement:

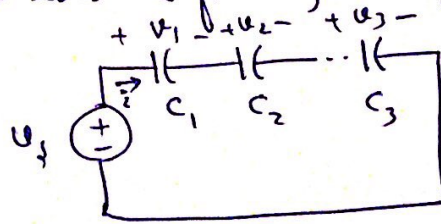

and equivalent circuit

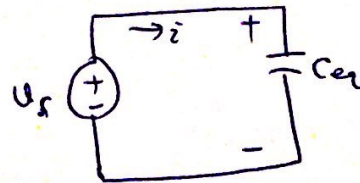

Because same charge appears on each plate

$$Q = C_1 V_1, \quad Q = C_2 V_2 \quad \text{and} \quad Q = C_3 V_3$$

$$\text{also} \quad Q = C_{eq} V_s$$

$$\text{Now} \quad V_s = V_1 + V_2 + V_3 = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\text{and} \quad V_s = \frac{Q}{C_{eq}}$$

$$\text{So} \quad \frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$


$$\text{or} \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

For the special case of two capacitors in parallel


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Capacitors in Parallel (pp 237)

Consider the following arrangement:-

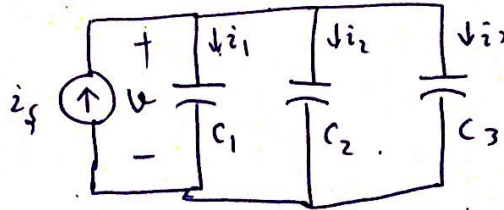

and the equivalent circuit

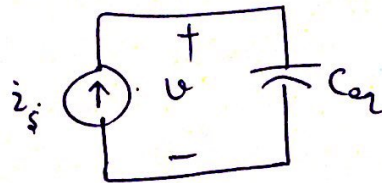

$$\text{Now } Q_1 = C_1 V \text{ and } Q_2 = C_2 V, Q_3 = C_3 V$$

$$\text{Also } Q_{eq} = C_{eq} V$$

$$\text{Now } i_s = i_1 + i_2 + i_3$$

$$\text{and } i = \frac{dQ}{dt}$$

$$\text{So } \frac{dQ_1}{dt} + \frac{dQ_2}{dt} + \frac{dQ_3}{dt} = \frac{dQ_{eq}}{dt}$$

$$\text{or } Q_1 + Q_2 + Q_3 = Q_{eq} \text{ ————— (important)}$$

$$\text{Hence } C_1 V + C_2 V + C_3 V = C_{eq} V$$

$$\text{Therefore } C_{eq} = C_1 + C_2 + C_3$$

$$\begin{aligned} \text{also } i_1 &= C_1 \frac{dV}{dt} \\ i_2 &= C_2 \frac{dV}{dt} \text{ etc etc} \end{aligned}$$