



Chapter6: Registers and Counters

Lecture2- An Introduction to Counters

Engr. Arshad Nazir, Asst Prof
Dept of Electrical Engineering
SEECS

Objectives

- Study Asynchronous (Ripple) and Synchronous Counters

Counter

- A special type of register that goes through a prescribed sequence of states upon the application of input pulses
 - Input pulses: May be clock pulses or originate from some external source
 - The sequence of states may follow
 - the binary number sequence (\Rightarrow Binary counter) or
 - any other sequence of states
- There are two main categories of counters
 - Ripple counters (Asynchronous Counters)

There is no common clock pulse (not synchronous) and the flip-flop output transition of one serves as a source for triggering other flip-flops
 - Synchronous counters


The CLK inputs of all flip-flops receive a common clock


Example: 4-bit Binary Ripple Counter

- A 4-bit Binary Ripple Up Counter follows the sequence 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1110, 1111, back to 0000, and repeat.
- Count pulse is applied only to A_0 generating the least significant bit of counting sequence. The output state transition of A_0 will be connected with C input of A_1 and trigger it, and so on.
- The flip-flops used in the design of 4-bit Binary Ripple Counters are self-complementing and toggle output state on negative edge of each count pulse.
- The timing diagram of the counter for counting sequence 0000 through 1000 is shown in the next slide.


A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

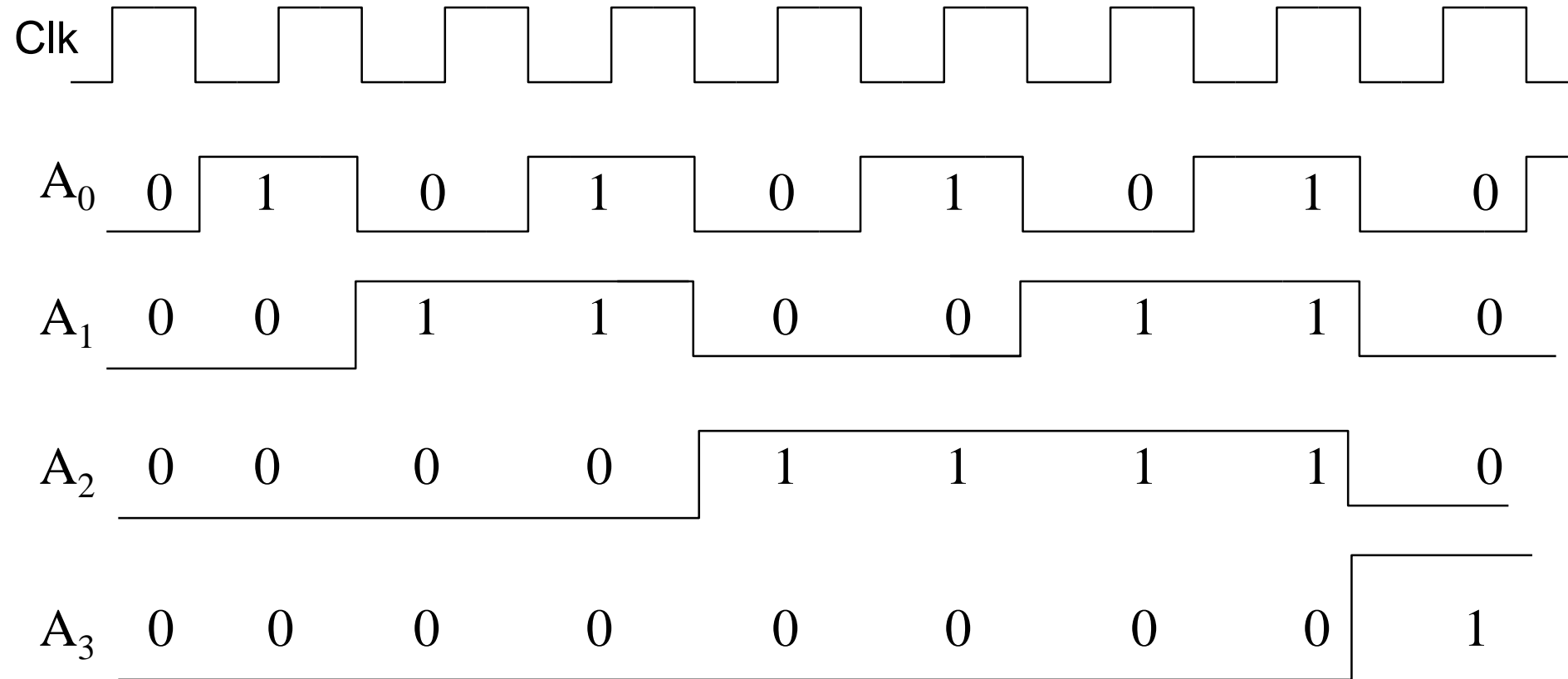Partial Timing of a 4-bit binary ripple counter



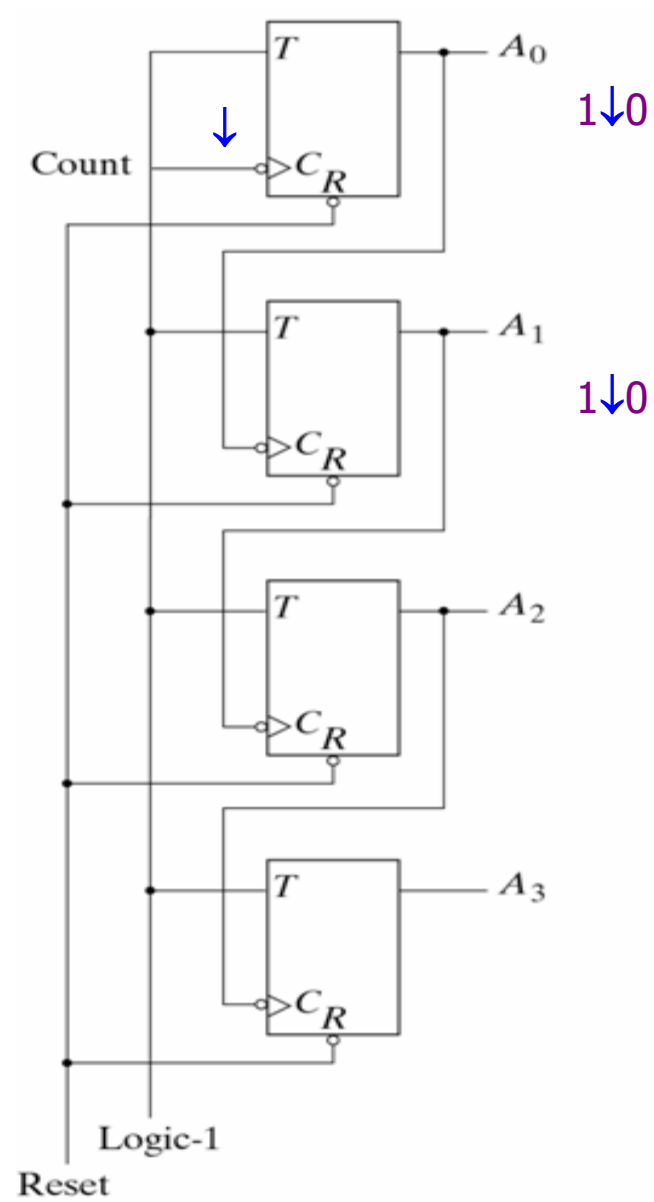


(a) With T flip-flops

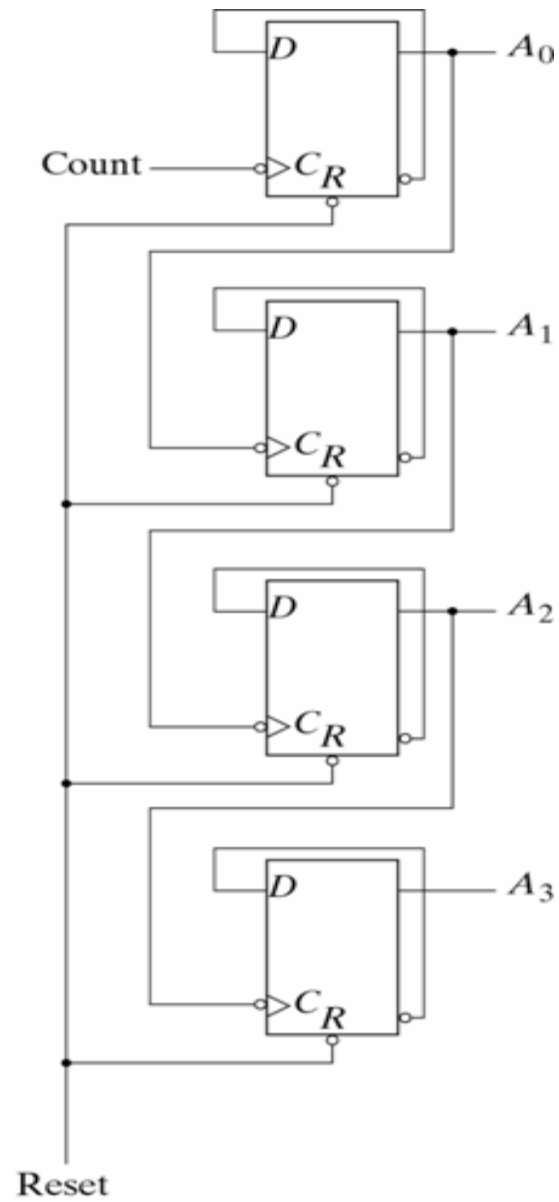

(b) With D flip-flops

Fig. 6-8 4-Bit Binary Ripple Counter


Example: BCD Ripple Counter

 

Copyright ©2013 Pearson Education, publishing as Prentice Hall

- A BCD Ripple Counter follows the sequence 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, back to 0000 and repeats.
- It can also be constructed using different types of flip-flops such that count pulse is applied to the flip-flop generating the least significant bit of counting sequence and output state transition of one triggers others.

Timing Diagram of BCD Ripple Counter

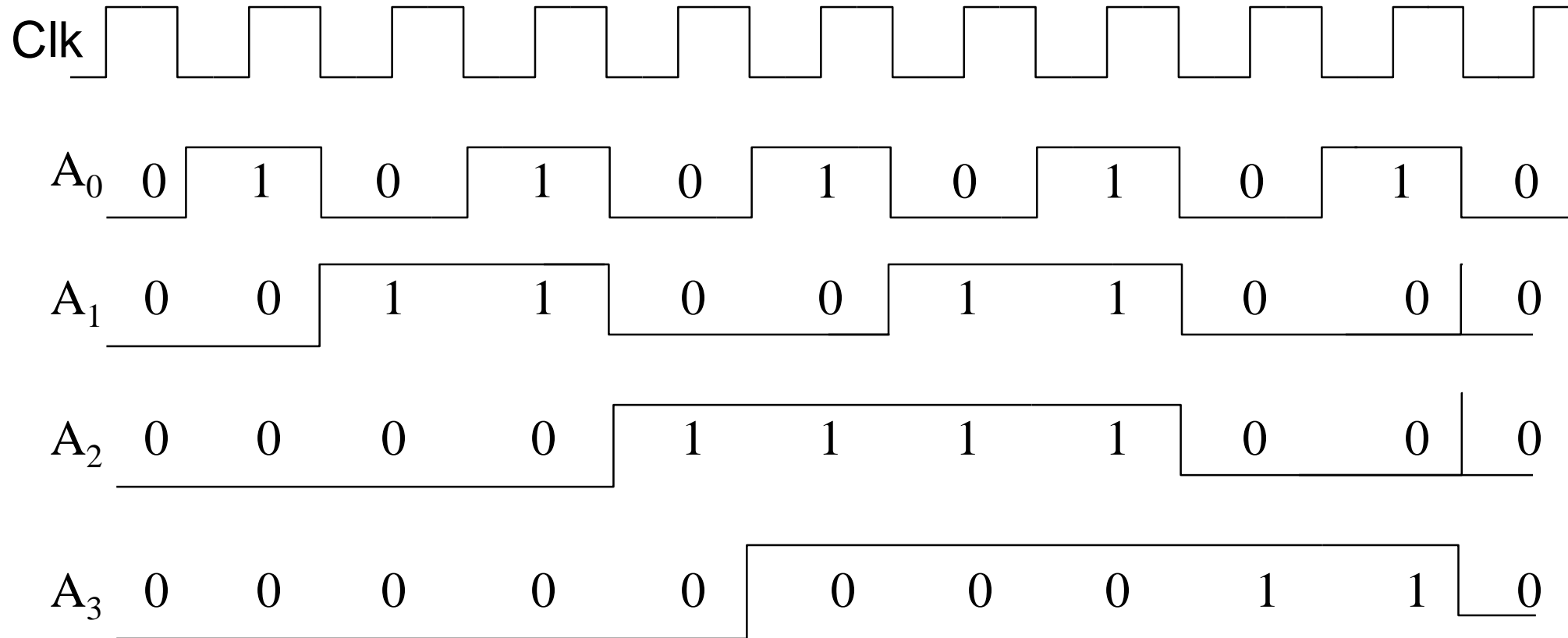

The BCD Ripple Counter Circuit (with JK FF)

Counting Sequence

0000

0001

0010

0011

0100

0101

0110

0111

1000

1001

1010 (0000)

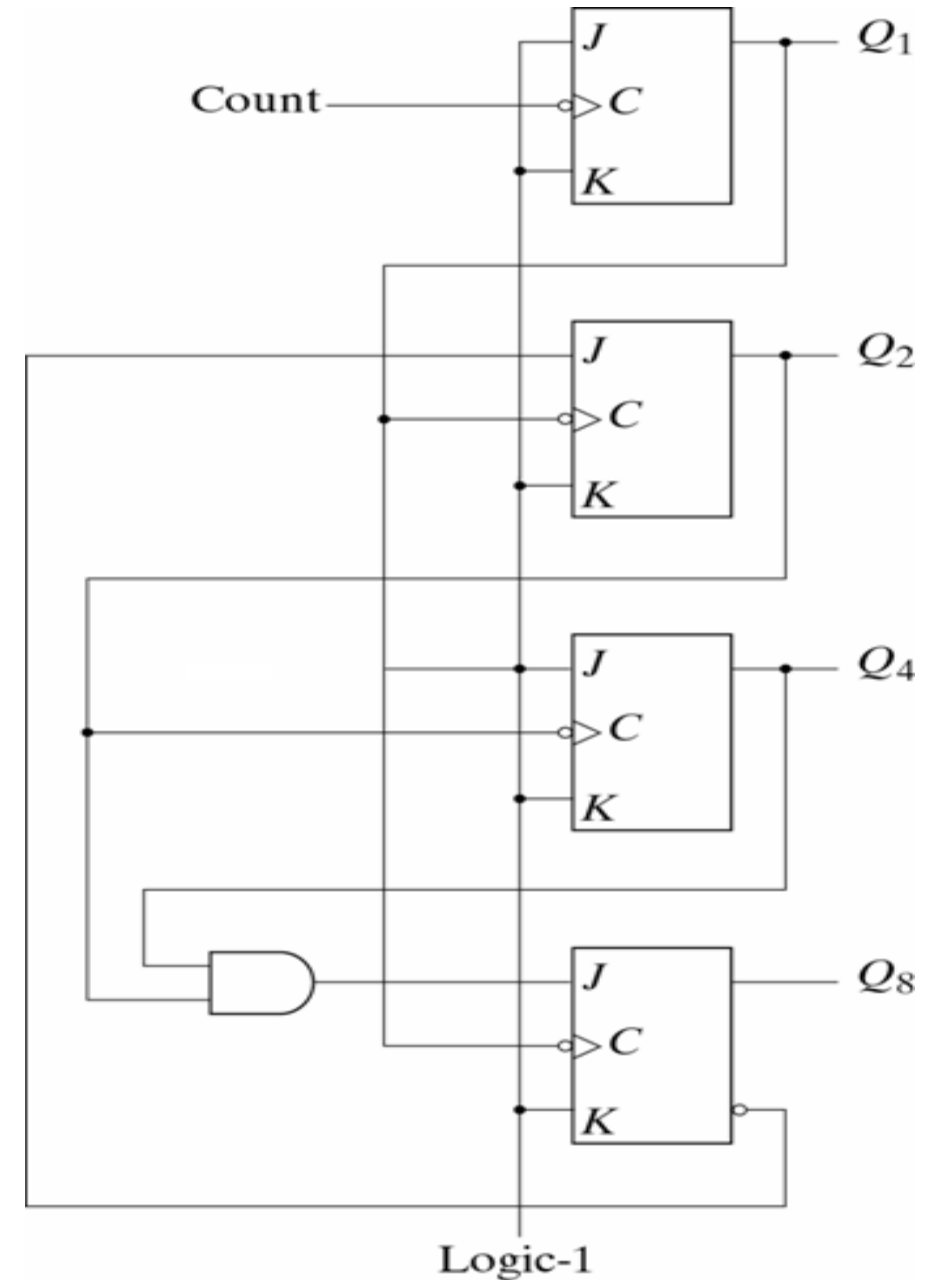


Fig. 6-10 BCD Ripple Counter

Cascading Counter Stages

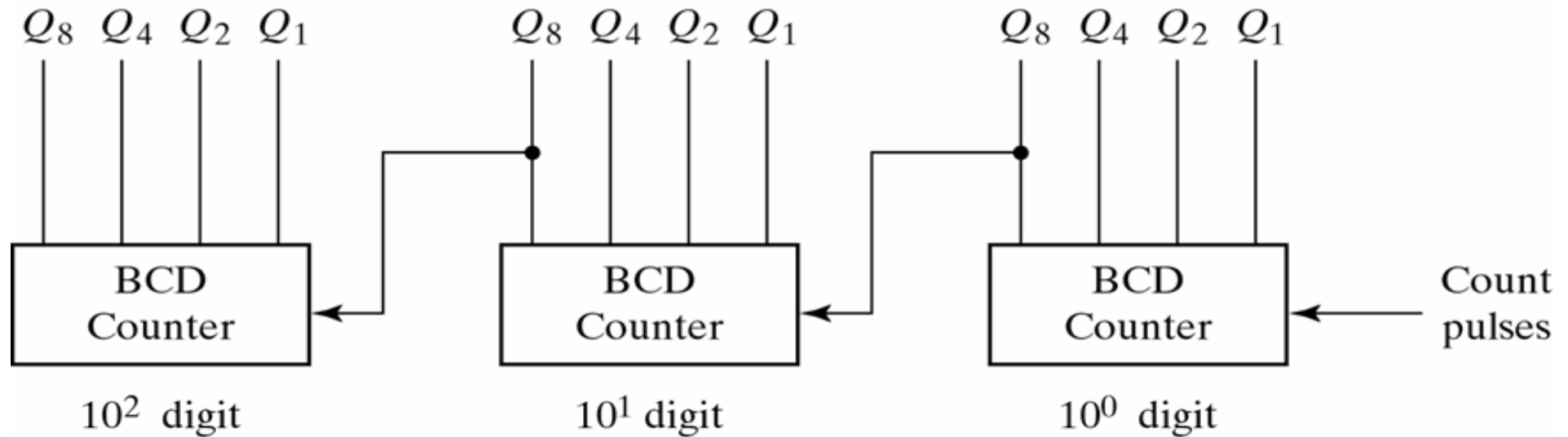


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

Synchronous Counters

- Synchronous counters are those in which common clock triggers all flip-flops simultaneously.
- In the design of synchronous counters, apply the same procedure of synchronous sequential circuits.
- Design of 4-bit Binary Up Synchronous Counter is much simpler and can be implemented after due scrutiny of counting sequence bits pattern.
- Flip-flops may be positive or negative-edge triggered.

$A_0 = 1$ will complement A_1 , $A_0 A_1 = 1$, $A_0 A_1 A_2 = 1$, and $A_0 A_1 A_2 A_3 = 1$ will reset all flip-flops to 0 synchronously.


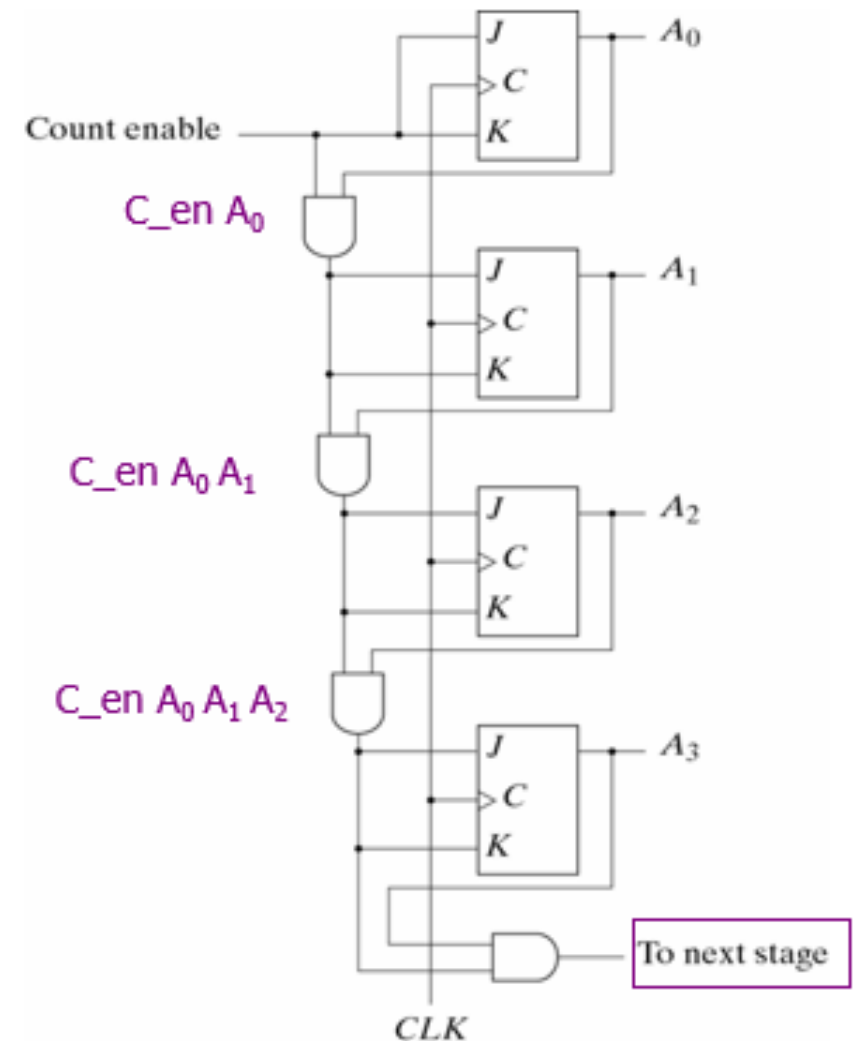


Fig. 6-12 4-Bit Synchronous Binary Counter

4-bit up/down binary counter

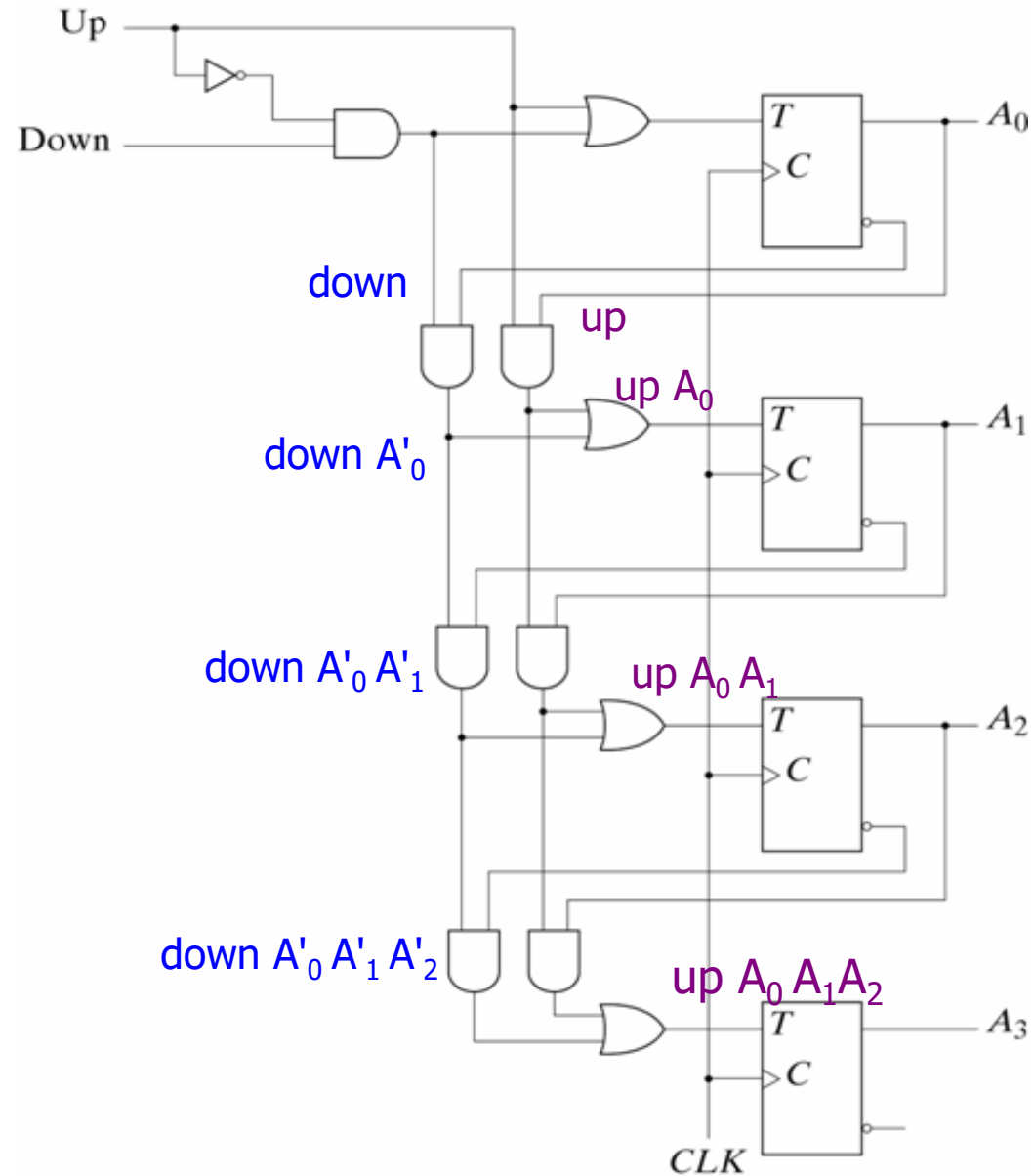

Fall 2021

Fig. 6-13 4-Bit Up-Down Binary Counter

BCD Counters

Table 6-5
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Using map method, we get

$$TQ_1 = 1; \quad TQ_2 = Q_8'Q_1; \quad TQ_4 = Q_2Q_1; \quad TQ_8 = Q_8Q_1 + Q_4Q_2Q_1$$

$$Y = Q_8Q_1$$

4-bit Binary Counter with Parallel Load

Table 6-6

Function Table for the Counter of Fig. 6-14

Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change


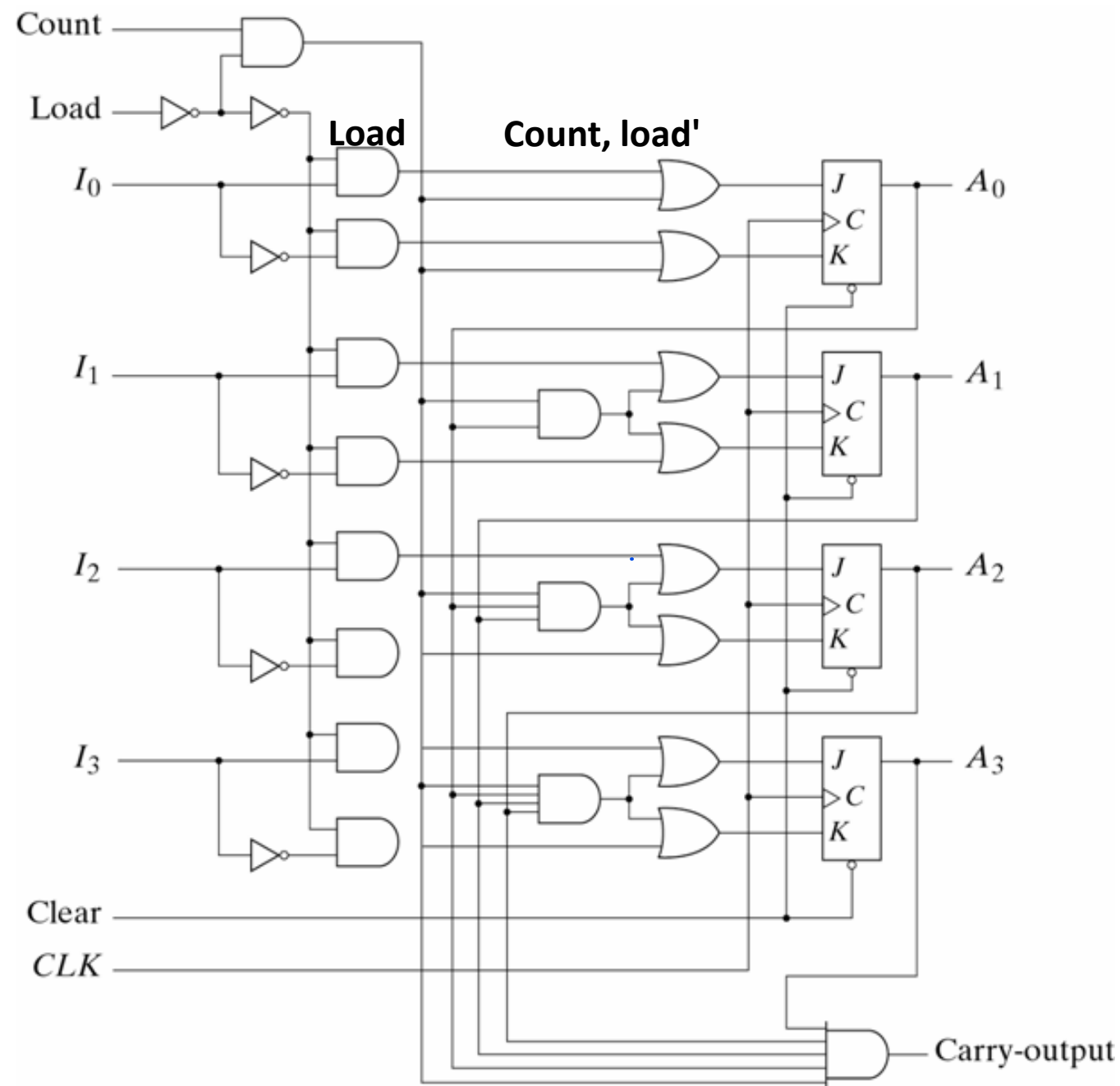



Fig. 6-14 4-Bit Binary Counter with Parallel Load

BCD Counter Design Examples

 - Generate any count sequence using this counter with parallel load i.e BCD counting sequence after states decoding



(a) Using the load input

 

(b) Using the clear input

Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

The End