



Assignment # 5

Electrical Network Analysis (EE-211)

Submitted to: Ahsan Azhar

Class: BEE 12 C

Due: 16/06/2021


By

Muhammad Umer

CMS: 345834

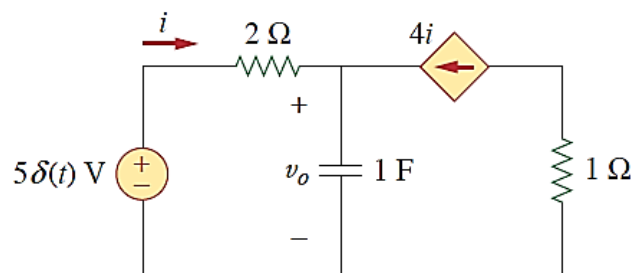Problem 16.16


The capacitor in the circuit of Fig. 16.39 is initially uncharged. Find $v_0(t)$ for $t > 0$.



Solution

The circuit in s-domain transforms to:
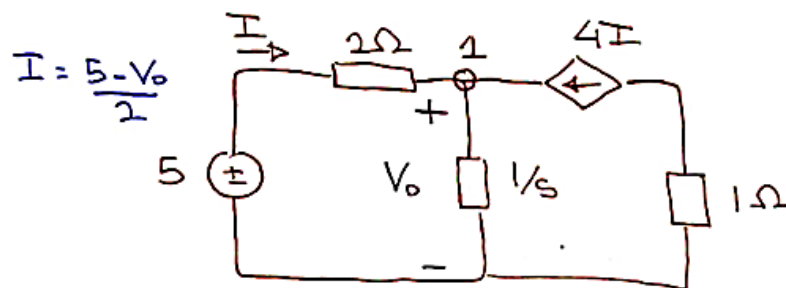
$$\begin{aligned} 5\delta(t) &\rightarrow 5 \\ i &\rightarrow I \\ 2\Omega &\rightarrow 2\Omega \\ 1F &\rightarrow \frac{1}{s} \\ 1\Omega &\rightarrow 1\Omega \end{aligned}$$



Applying Nodal Analysis at 1:

$$\Rightarrow I + 4I = V_o(s)$$

$$\Rightarrow 5I = sV_o$$

However, $I = \frac{5 - V_o}{2}$; Substituting

$$\Rightarrow 5\left(\frac{5 - V_o}{2}\right) = sV_o$$

$$\Rightarrow 5(5 - V_0) = 2s V_0$$

$$\Rightarrow 25 - 10V_0 = 2s V_0$$

$$\Rightarrow V_0(10 + 2s) = 25$$

$$\Rightarrow V_0 = \frac{25}{10 + 2s} = \frac{12.5}{s + 5/2}$$


$$\bullet V_0(t) = \mathcal{L}^{-1}(V_0(s))$$

$$V_0(t) = (12.5 e^{-2.5t}) u(t) \text{ V}$$

$$\therefore e^{-at} \leftrightarrow \frac{1}{s+a}$$

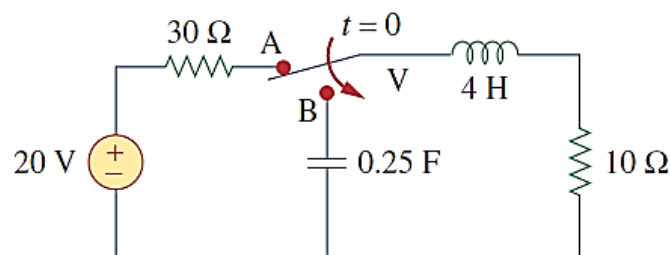
Problem 16.19

The switch in Fig. 16.42 moves from position A to position B at $t = 0$ (please note that the switch must connect to point B before it breaks the connection at A, a make before break switch). Find $v(t)$ for $t > 0$.



Solution

For $t < 0$

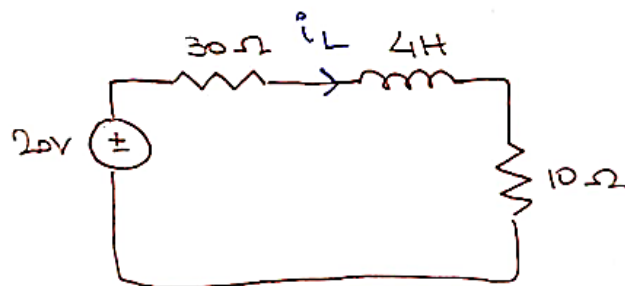

We can find $i_L(0)$ by shorting the inductor. Hence,


$$i_L(0) = \frac{20}{30 + 10} = \boxed{0.5 \text{ A}}$$

For $t > 0$

$$\frac{1}{4} F \rightarrow \frac{4}{s}$$

$$4 H \rightarrow 4s$$

$$L i_L(0) \rightarrow 2V$$

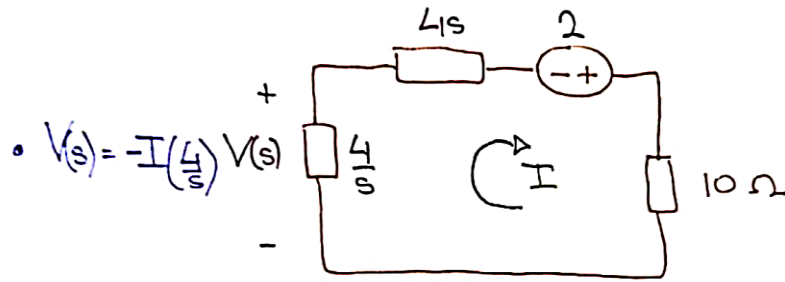

$$\Rightarrow \frac{4}{s} I + 4s I - 2 + 10 I = 0$$

$$\Rightarrow I \left(\frac{4}{s} + 4s + 10 \right) = 2$$

$$\Rightarrow I = \frac{2}{\frac{4}{s} + 4s + 10} \Rightarrow \frac{2s}{4 + 4s^2 + 10s}$$

• Using Ohm's Law for V required

$$V = -I \left(\frac{4}{s} \right)$$

$$= \frac{-2s}{4 + 4s^2 + 10s} \left(\frac{4}{s} \right) = \frac{-8}{4s^2 + 10s + 4}$$

$$V(s) = \frac{-2}{s^2 + 2.5s + 1}$$

$$\Rightarrow \frac{-2}{s^2 + 2.5s + 1} = \frac{A}{s+2} + \frac{B}{s+1/2} \quad \therefore \text{Poles}$$

For A :

$$\left. \frac{-2}{s+1/2} \right|_{s=-2} \Rightarrow A = 4/3$$

For B:

$$\left. \frac{-2}{s+2} \right|_{s=-1/2} \Rightarrow B = -4/3$$


$$\begin{aligned} \Rightarrow V(s) &= \frac{4}{3(s+2)} - \frac{4}{3(s+1/2)} \\ &= \frac{4}{3} \left(\frac{1}{s+2} - \frac{1}{s+1/2} \right) \end{aligned}$$

Taking \mathcal{L}^{-1} of $V(s)$

$$\Rightarrow \boxed{v(t) = \frac{4}{3} \left(e^{-2t} - e^{-0.5t} \right) u(t) \text{ V}}$$

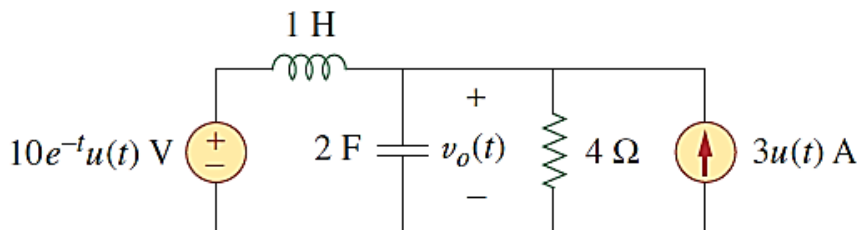Problem 16.35

Find $V_o(t)$ in the circuit of Fig. 16.58.



Solution


Converting this circuit into s-domain;

$$10e^{-t}u(t) \rightarrow \frac{10}{s+1}$$

$$1 \text{ H} \rightarrow s$$

$$2F \rightarrow \frac{1}{2s}$$

$$3u(t) \rightarrow \frac{3}{s}$$

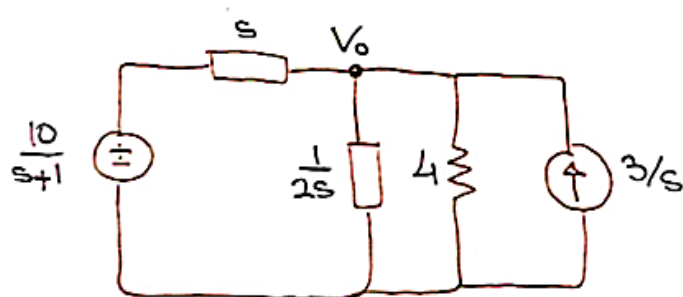

Applying KCL to V_0 ,

$$\Rightarrow \frac{V_0}{1/2s} + \frac{V_0}{4} + \frac{V_0 - 10/s+1}{s} = 3/s$$

Multiplying with s ,

$$\Rightarrow 2V_0s^2 + \frac{V_0s}{4} + V_0 = 3 + \frac{10}{s+1}$$

$$\Rightarrow V_0 \left(2s^2 + \frac{s}{4} + 1 \right) = 3 + \frac{10}{s+1}$$

$$\Rightarrow V_0 = \frac{\frac{3s+3+10}{s+1}}{\left(2s^2 + \frac{s}{4} + 1 \right)}$$

$$\Rightarrow V_0 = \frac{3s+13}{(s+1)(2s^2+s/4+1)} = \frac{1.5s+6.5}{(s+1)(s^2+s/8+1/2)}$$

Using Heaviside Expansion;

$$\Rightarrow \frac{1.5s + 6.5}{(s+1)(s^2 + s/8 + 1/2)} = \frac{A}{s+1} + \frac{B}{(s + \frac{1}{16} - \frac{\sqrt{127}}{16}j)} + \frac{B^*}{(s + \frac{1}{16} + \frac{\sqrt{127}}{16}j)}$$

• For A

$$\left. \frac{1.5s + 6.5}{s^2 + s/8 + 1/2} \right|_{s=-1} \Rightarrow A = \frac{40}{11}$$

• For B

$$\left. \frac{1.5s + 6.5}{(s+1)(s + \frac{1}{16} + \frac{\sqrt{127}}{16}j)} \right|_{s = -\frac{1}{16} + \frac{\sqrt{127}}{16}j}$$

$$\Rightarrow B = \frac{1.5(-1/16 + \sqrt{127}/16j) + 6.5}{(15/16 + \sqrt{127}/16j)(\frac{\sqrt{127}}{8}j)} = 3.93 \angle -117.55^\circ$$

Substituting in old equation;

$$\Rightarrow \frac{1.5s + 6.5}{(s+1)(s^2 + \frac{s}{4} + 1)} = \frac{40/11}{s+1} + \left[\frac{3.93 \angle -117.55^\circ}{s + \frac{1}{16} - \frac{\sqrt{127}}{16}j} + \frac{3.93 \angle 117.55^\circ}{s + \frac{1}{16} + \frac{\sqrt{127}}{16}j} \right]$$

Taking \mathcal{L}^{-1}

$$V_o(t) = \frac{40}{11} e^{-t} + \left[2R e^{\sigma t} (\cos(\omega t + \phi)) \right]$$

• Dotted Part :

$$R = 3.93, \quad \sigma = -1/16, \quad \omega = \frac{\sqrt{127}}{16}, \quad \phi = 117.55$$

$$V_o(t) = \frac{40}{11} e^{-t} + 7.86 e^{-t/16} \cos\left(\frac{\sqrt{127}}{16}t - 117.55\right) u(t) \text{ V}$$