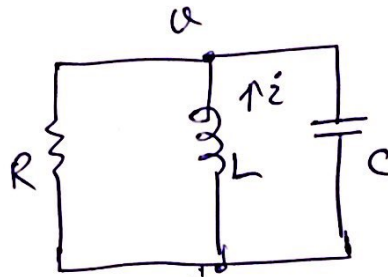


# Q.1 The Source-Free Parallel RLC Circuit

(PP 322 8th Ed HAD)

Consider:



— The direction of ' $i$ ' is arbitrary. And the initial conditions are

$$\left. \begin{aligned} i(0^+) &= I_0 \\ \text{and } u(0^+) &= V_0 \end{aligned} \right\} \text{HKS}$$

$$\left. \begin{aligned} \text{Sadiku} \\ i(0) &= I_0 \\ \text{initial inductor} \\ \text{current etc} \end{aligned} \right\}$$

— The single node equation can be written as:-

$$\frac{u}{R} + \frac{1}{L} \int_{t_0}^t u dt' - i(t_0) + C \frac{du}{dt} = 0$$

— This integro-differential equation can be differentiated to get a linear 2nd-order differential equation as:

$$C \frac{d^2 u}{dt^2} + \frac{1}{R} \frac{du}{dt} + \frac{1}{L} u = 0$$

— its solution  $u(t)$  is the desired natural response.

— Note: For series RLC:                     

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

## Solution of the Differential Equation (PP 322 8th Ed HKD)

The differential equation is

$$C \frac{d^2 u}{dt^2} + \frac{1}{R} \frac{du}{dt} + \frac{1}{L} u = 0$$

Let us assume the solution as

$$u = A e^{st}$$

where  $A$  and  $s$  may be complex numbers, if necessary.

$$\text{Then } \frac{du}{dt} = A s e^{st}$$

$$\text{and } \frac{d^2 u}{dt^2} = A s^2 e^{st}$$

— Substituting the assumed solution in the second-order differential equation, we get

$$C(A s^2 e^{st}) + \frac{1}{R}(A s e^{st}) + \frac{1}{L}(A e^{st}) = 0$$

$$\text{So } C s^2 + \frac{1}{R} s + \frac{1}{L} = 0 \quad \left\{ s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \right\}$$

because  $A e^{st} \neq 0$

— This equation is usually called the auxiliary equation or the characteristic equation.

— Since this is a quadratic equation, there are two solutions

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

\_\_\_\_\_ contd

—Contd (324)

So we have the general form of the natural response as

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

where  $A_1$  and  $A_2$  are two arbitrary constants which are to be selected to satisfy the two specified initial conditions.

\_\_\_\_\_ (12)

## Definition of Frequency Terms (PP 324 8th Ed HKD)

The general form of the natural response is

$$u(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Since the exponents  $s_1 t$  and  $s_2 t$  must be dimensionless,  $s_1$  and  $s_2$  must have the unit of some dimensionless quantity "per second".

— so from  $s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$

we see that the units of  $\frac{1}{2RC}$  and  $\frac{1}{\sqrt{LC}}$  must also be  $s^{-1}$ .

— units of this type are called frequencies.

— we define  $\omega_0$  (omega-zero)

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

and reserve the term resonant frequency for it.

— we also call  $\frac{1}{2RC}$  the neper frequency or the exponential damping coefficient  $\alpha$ , so  $\alpha = \frac{1}{2RC}$

— Note:  $\alpha$  is called exponential damping coefficient as it is a measure of how rapidly the natural response decays to its steady final value (usually zero).

————— contd



— contd (324)

Finally  $s_1$  and  $s_2$  are called complex frequencies.

So the natural response of the parallel RLC circuit is

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{where } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC}$$

$$(\alpha = \frac{R}{2L} \text{ for series})$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

and  $A_1$  and  $A_2$  must be found by applying the given initial conditions.

Note: The ratio of  $\alpha$  to  $\omega_0$  ( $\frac{\alpha}{\omega_0}$ ) is called the damping ratio by control system engineers and is designated by  $\zeta$  (Zeta).

Summary:

$\omega_0$  = resonant frequency  
(undamped natural frequency)

$\omega_d$  = natural resonant frequency  
(damped natural frequency)

$\alpha$  = exponential damping coefficient

$\frac{\alpha}{\omega_0}$  = damping ratio