



Name: Muhammad Umer


Total Marks: 10

Registration No. and Sections: 345834 BEE12C


Home Assignment No 4: Maximum Power Transfer Theorem

What value of load connected to this network shall receive maximum power?

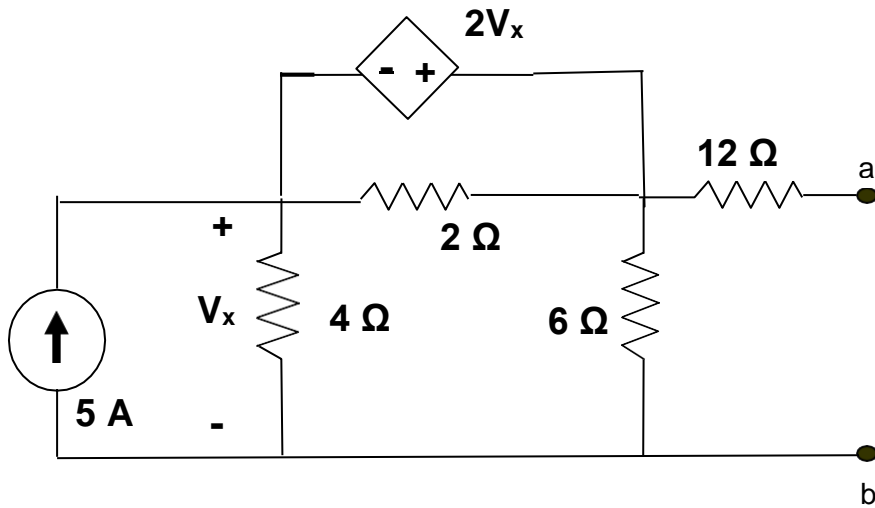(Note: Please show all steps including any rough work. Use only A4 size white paper. The title of uploaded file must be HA No 4 in pdf.)



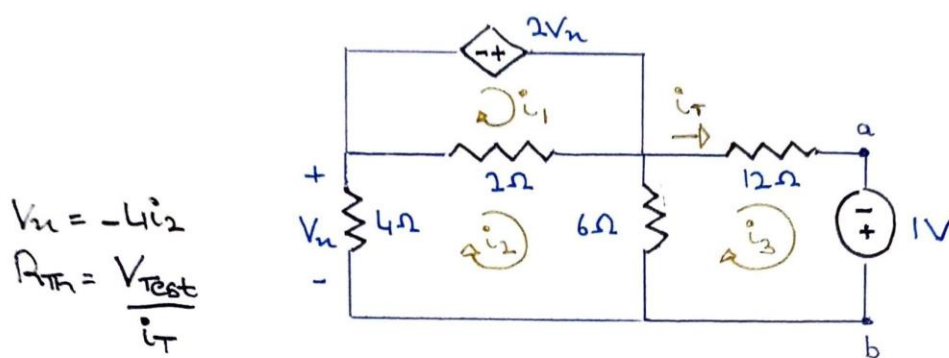Connecting a test source between a and b and eliminating any independent sources.



$$V_{th} = -4i_2$$
$$R_{Th} = \frac{V_{test}}{i_T}$$

Mesh 1:

$$-2V_{th} + 2(i_1 - i_2) = 0$$

$$-2(-4i_2) + 2(i_1 - i_2) = 0$$

$$8i_2 + 2i_1 - 2i_2 = 0$$

$$\underline{2i_1 + 6i_2 = 0}$$

Mesh 2:

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$

$$\underline{-2i_1 + 12i_2 - 6i_3 = 0}$$

Mesh 3:

$$12i_3 - 1 + 6(i_3 - i_2) = 0$$

$$\underline{-6i_2 + 18i_3 = 1}$$

$$\boxed{i_3 = 0.0625} \quad \therefore i_3 = I_T$$

$$\text{Now, } R_{Th} = \frac{V_T}{I_T}$$
$$= 1 / 0.0625$$

$$\underline{R_{Th} = 16 \Omega}$$

- The power is maximum when $R_L = R_{Th}$. Hence, the value of R_L is ;

$$\boxed{R_L = 16 \Omega}$$