

Question 1

- $\text{pf} = \cos \theta = 0.8$; $\theta = 36.86^\circ$ (Lagging)
- $X_s = 1.1 \Omega$; $R_A = 0.15 \Omega$
- $V_{L\text{rated}} = 2300 \text{ V}$; $V_{\phi\text{rated}} = 1328 \text{ V}$ " $V_L = \sqrt{3} V_\phi$

a) At no load , $I_F = ?$

From the open circuit curve ,

$$\gg V_t = 2300 \text{ V} \rightarrow \underline{I_F = 4.3 \text{ A}}$$

b) Internal generated Voltage

$$V_{\phi\text{rated}} = 1328 \text{ V} ; S = \sqrt{3} V_L I_A$$

$$I_A = \frac{1000 \text{ kW}}{\sqrt{3} 2300} = 251 \text{ A}$$

$$\gg E_A = V_\phi + R_A I_A + j X_s I_A$$

$$\begin{aligned} \gg E_A &= 1328 + (251 \angle -36.86^\circ)(0.15) + j(251 \angle -36.86^\circ)(1.1) \\ &= \underline{1537 \angle 7.4^\circ \text{ V}} \end{aligned}$$

c) Field current at rated conditions

$$E_A = 1537 \text{ corresponds to } V_{T,oc} = \sqrt{3} (1537)$$

$$\gg V_{T,oc} = 2662 \text{ V} \rightarrow \underline{I_F = 5.85 \text{ A}}$$

d) Power and Torque

$$\gg P_{out} = 3 V_\phi I_A \cos(\theta) = 800 \text{ kW}$$

$$\gg P_{in} = P_{out} + P_{cu} + P_{fsw} + P_{core}$$

$$\gg P_{cu} = 3 I_A^2 R_A = 28.35 \text{ kW}$$

$$\begin{aligned} P_{in} &= 800 \text{ k} + 28.35 \text{ k} + 24 \text{ k} + 18 \text{ k} \\ &= \underline{870.35 \text{ kW}} \end{aligned}$$

$$\gg \text{Torque } \tau_{app} = P_{in} / \omega_m$$

$$n_m = \frac{120 f}{P} = \frac{120 (60)}{2} = 3600 \text{ rev/min}$$

$$\begin{aligned} \omega_m &= 3600 \text{ rev/min} (1 \text{ min}/60 \text{ s}) (2\pi \text{ rad}/1 \text{ rev}) \\ &= 120 \pi \text{ rad/s} \end{aligned}$$

$$\tau_{app} = \frac{870.35 \text{ k}}{120 \pi} = \underline{2308 \text{ N}\cdot\text{m}}$$

Question 2

a) Torque angle δ

At rated conditions, $I_A = 251$ (from Q1)
with a pf of 1 (unity pf).

$$\begin{aligned} \gg E_A &= V_\phi + R_A I_A + j X_L I_A \\ &= 1328 + (0.15)(251 \angle 0^\circ) + j(1.1)(251 \angle 0^\circ) \\ &= 1393 \angle 11.4^\circ \end{aligned}$$

$$\gg \text{Torque angle } \underline{\delta = 11.4^\circ}$$

b) Stability Limit

- Stability is limited to $\delta = 90^\circ$

$$\text{Factor } E = \frac{90^\circ}{11.4^\circ} = 7.89$$

» Static stability limit is 7.89 times away from the computed torque angle δ .

Example 5.2

$$\Delta \text{ connected : } V_t = V_\phi ; I_L = \sqrt{3} I_\phi$$

- a) Speed n_m

$$n_m = \frac{120 f}{P} = \frac{120 (60)}{4} = \underline{1800 \text{ rev/min}}$$

- b) OC $\rightarrow I_A = 0$

$$V_t = V_\phi = E_A = 480 \text{ V}$$

$$\text{From OCC, } \underline{I_F = 4.5 \text{ A}}$$

- c) $I_L = 1200 \text{ A}$

$$\Delta \text{ connected ; } I_A = \frac{1200}{\sqrt{3}} = \underline{692.8 \text{ A}}$$

$$E_A = V_\phi + I_A R_A + j X_S I_A$$

$$= 480 + (692.8 \angle -36.87^\circ)(0.015) \\ + j(692.8 \angle -36.87^\circ)(0.1)$$

$$= 532 \angle 5.3^\circ \text{ V}$$

From OCC, $I_F = 5.7 \text{ A}$

d) $P_{out} = \sqrt{3} V_T I_L \cos \theta = 798 \text{ kW}$

$$\begin{aligned} P_{in} &= P_{out} + P_{cu} + P_{fsw} + P_{core} \\ &= 798 \text{ k} + 3 I_A^2 R_A + 30 \text{ k} + 40 \text{ k} \\ &= 889.6 \text{ kW} \end{aligned}$$

$$\text{Efficiency } \eta = \frac{P_{out}}{P_{in}} \times 100\% = \underline{89.75\%}$$

e) After load is disconnected, $I_A \rightarrow 0$ and since I_F remains unchanged, V_ϕ rises to match $E_A = 532 \text{ V}$.


f) With 0.8 pf leading;

$$\begin{aligned} E_A &= 480 + (692.8 \angle 36.87^\circ)(0.015) + j(692.8 \angle 36.87^\circ)(0.1) \\ &= \underline{451 \angle 7.1^\circ \text{ V}} \end{aligned}$$

Example 5.3

a) $n_m = \frac{120 f_e}{P} = \frac{120 (60)}{6} = 1000 \text{ rev/min}$

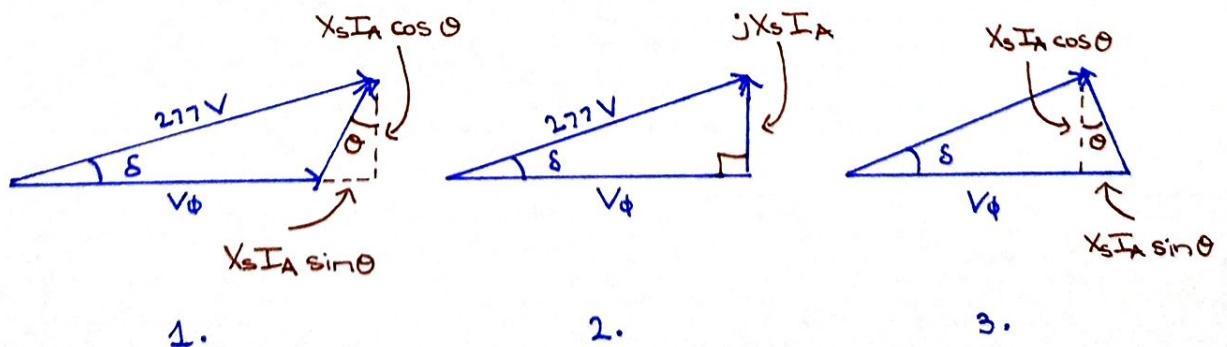b) Y-connected $\rightarrow E_A = 480 / \sqrt{3} = 277 \text{ V}$



$$1. \quad E_A = \sqrt{(V_\phi + X_s I_A \sin \theta)^2 + (X_s I_A \cos \theta)^2}$$

$$277 = \sqrt{(V_\phi + 36)^2 + 2304}$$

$$V_\phi = 236.8 \text{ V} \rightarrow V_t = \sqrt{3} \cdot 236.8 = \underline{410 \text{ V}}$$

$$2. \quad E_A = \sqrt{V_\phi^2 + (X_s I_A)^2}$$

$$277 = \sqrt{V_\phi^2 + 3600}$$

$$V_\phi = 270.4 \text{ V} \rightarrow V_t = \sqrt{3} \cdot 270.4 = \underline{468.4 \text{ V}}$$

$$3. \quad E_A = \sqrt{(V_\phi - X_s I_A \sin \theta)^2 + (X_s I_A \cos \theta)^2}$$

$$277 = \sqrt{(V_\phi - 36)^2 + 2304}$$

$$V_\phi = 308.8 \text{ V} \rightarrow V_t = \sqrt{3} \cdot 308.8 = \underline{535 \text{ V}}$$

$$c) \quad P_{out} = 3 V_\phi I_A \cos \theta = 34.1 \text{ kW}$$

$$P_{in} = P_{out} + P_{core} + P_{mech}$$

$$= 34.1 \text{ k} + 1 \text{ k} + 1.5 \text{ k}$$

$$= 36.6 \text{ kW}$$

$$\text{Efficiency } \eta = \frac{P_{out}}{P_{in}} \times 100\% = 93.2\%$$

$$d) \quad \text{Input Torque } \tau_{app} = \frac{P_{in}}{\omega_m} = \frac{36.6 \text{ k}}{125.7} = \underline{291.2 \text{ N.m}}$$

$$\text{Counter Torque } \tau_{ind} = \frac{P_{out}}{\omega_m} = \frac{34.1 \text{ k}}{125.7} = \underline{271.3 \text{ N.m}}$$

$$e) \quad VR = (V_{nl} - V_{fl}) / V_{fl} \times 100\%$$

$$1. \text{ Lagging } VR = (480 - 410) / 410 \times 100\% = 17.1\%$$

$$2. \text{ Unity } VR = (480 - 468) / 468 \times 100\% = 2.6\%$$

$$3. \text{ Leading } VR = (480 - 535) / 535 \times 100\% = -10.3\%$$

Problem 5.3

a) $I_F = 4.5 \text{ A} \rightarrow \text{From OCC, } V_t = 2385 \text{ V}$
 $E_A = V_\phi = 1377 \text{ V}$

$$\Delta\text{-Load} = 20 \angle 30^\circ \Omega$$

$$\gg \text{Equivalent to } Y = \frac{R^2}{3R} = \frac{1}{3} (20 \angle 30^\circ) = 6.67 \angle 30^\circ$$


$$I_A = \frac{E_A}{|R_A + jX_s + Z|} = \frac{1377}{|0.15 + j1.1 + 6.67 \angle 30^\circ|} \sim$$
$$= 186 \text{ A}$$

$$V_\phi = I_A Z = 1240 \text{ V}$$

$$V_t = \sqrt{3} V_\phi = \underline{2148 \text{ V}}$$

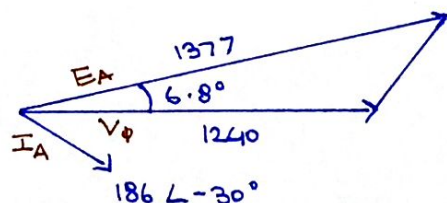b) $I_A = 186 \angle -30^\circ$

$$E_A = V_\phi + R_A I_A + jX_s I_A$$
$$= 1240 + (0.15)(186 \angle -30^\circ) + j(1.1)(186 \angle -30^\circ)$$
$$= \underline{1377 \angle 6.8^\circ \text{ V}}$$




c) $P_{out} = 3 V_\phi I_A \cos \theta = 599 \text{ kW}$

$$P_{in} = P_{out} + P_{cu} + P_{fsw} + P_{core}$$
$$= 599 \text{ kW} + 3 I_A^2 R_A + 24 \text{ kW} + 18 \text{ kW}$$
$$= 657 \text{ kW}$$

$$\text{Efficiency } \eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 \% = 91.1 \%$$

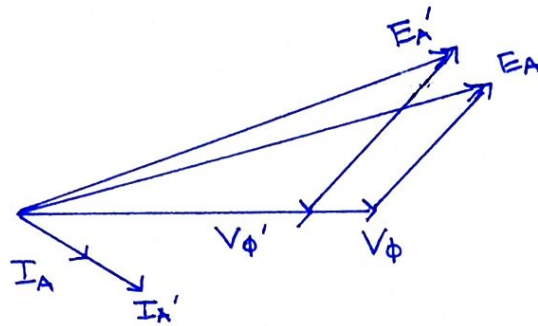d) Due to new load ; $V_{\phi}' < V_{\phi}$



Inference

$$\therefore |E_A'| = |E_A|$$

$$\therefore I_A' > I_A$$

$$\therefore V_{\phi}' < V_{\phi}$$

e) New impedance will be halved (in parallel)

$$Z = 3.33 \angle 30^\circ \Omega$$

$$I_A = \frac{E_A}{|R_A + jX_s + Z|} = 335 \text{ A}$$

$$V_{\phi} = I_A Z = 1117 \text{ V}$$

$$V_t = \sqrt{3} V_{\phi} = 1934 \text{ V}$$

f) To restore V_t to its original value, E_A must be increased (which can be done by increasing field current I_F)

Problem 5.4

a) As computed in "Question 1";

$$P_{\text{out}} = 800 \text{ kW} ; P_{\text{in}} = 870.4 \text{ kW}$$

$$\text{Efficiency } \eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 \% = 91.9 \%$$

b) As computed in "Question 1" ;

$$E_A = 1537 \angle 7.4^\circ$$

$$V_\phi = \frac{V_t}{\sqrt{3}} = 1328 \text{ V}$$

$$VR = \frac{1537 - 1328}{1328} \times 100\% = \underline{15.7\%}$$

c) Leading load $\rightarrow I_A = 251 \angle 36.87^\circ \text{ A}$

$$\begin{aligned} E_A &= V_\phi + R_A I_A + j X_s I_A \\ &= 1328 + (0.15)(251 \angle 36.87^\circ) + j(1.1)(251 \angle 36.87^\circ) \\ &= 1217 \angle 11.5^\circ \text{ V} \end{aligned}$$

$$VR = \frac{1217 - 1328}{1328} \times 100\% = \underline{-8.4\%}$$

d) Unity pf $\rightarrow I_A = 251 \angle 0^\circ \text{ A}$

$$\begin{aligned} E_A &= V_\phi + R_A I_A + j X_s I_A \\ &= 1328 + (0.15)(251 \angle 0^\circ) + j(1.1)(251 \angle 0^\circ) \\ &= 1393 \angle 11.4^\circ \text{ V} \end{aligned}$$

$$VR = \frac{1393 - 1328}{1328} \times 100\% = \underline{4.9\%}$$
