



NUST School of Electrical Engineering and Computer Science
(Department of Electrical Engineering)
EE 111

Name: Muhammed Umer


Total Marks : 10

Regn Number / Section: 345834 12-C

Home Assignment No 3 : Norton Equivalent Circuit (CLO 3)

Determine Norton equivalent across terminals a & b for the given circuit.

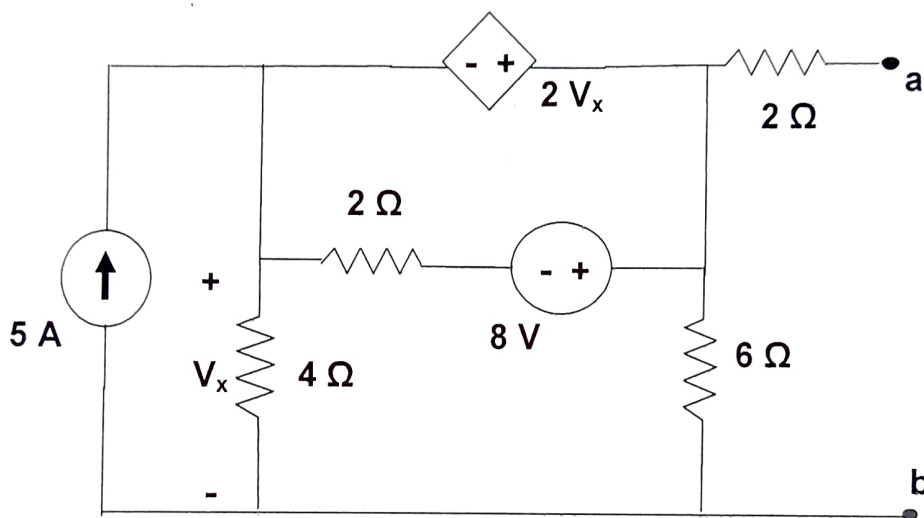
(Please upload it as one pdf file only with name HA No 3. Show all steps. For more space use only A4 size paper.)



- We find R_{Th} first by connecting a test source and eliminating independent source.

$$\therefore R_{Th} = \frac{V_{test}}{I_{test}}$$

$$\therefore V_n = -4i_2$$

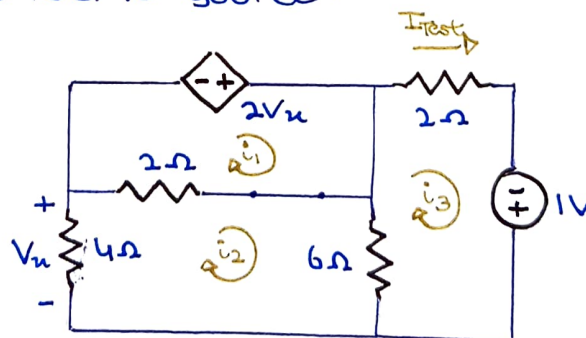

• Mesh 1: $-2V_n + 2(i_1 - i_2) = 0$
 $-2(-4i_2) + 2i_1 - 2i_2 = 0$
 $2i_1 + 6i_2 = 0$ ①

• Mesh 2:

$$2(i_2 - i_1) + 6(i_2 - i_3) + 4i_2 = 0$$
$$-2i_1 + 12i_2 - 6i_3 = 0$$
 ②


- Mesh 3: $2i_3 - 1 + 6(i_3 - i_2) = 0$
 $\underline{-6i_2 + 8i_3 = 1} \quad (3)$

Solving (1), (2) and (3)

$$i_3 = I_{\text{Test}} = \frac{1}{6} \text{ A}$$

$$\therefore R_{\text{Th}} = \frac{1}{I_{\text{Test}}} = \frac{1}{1/6} = 6 \Omega$$

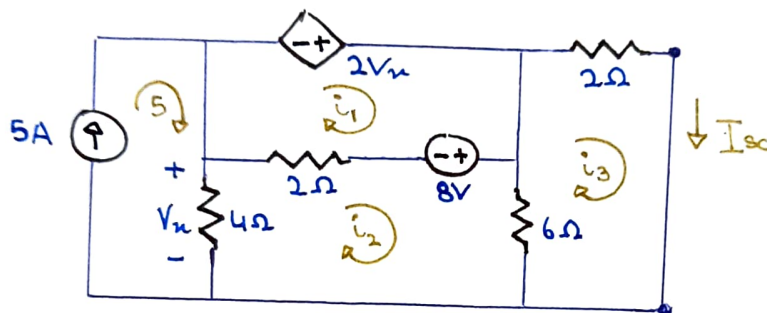- We find I_N or I_{sc} by connecting a wire between a & b.



$$\therefore I_{\text{sc}} = i_3$$

$$V_n = 4(5 - i_2)$$

- Mesh 1: $-2V_n + 8 + 2(i_1 - i_2) = 0$
 $-2[4(5 - i_2)] + 8 + 2(i_1 - i_2) = 0 \Rightarrow -4(5 - i_2) + 4 + i_1 - i_2 = 0$
 $\underline{i_1 + 3i_2 = 16} \quad (1)$

- Mesh 2: $4(i_2 - 5) + 2(i_2 - i_1) - 8 + 6(i_2 - i_3) = 0$
 $2(i_2 - 5) + i_2 - i_1 - 4 + 3(i_2 - i_3) = 0$
 $\underline{-i_1 + 6i_2 - 3i_3 = 14} \quad (2)$

- Mesh 3: $2i_3 + 6(i_3 - i_2) = 0 \Rightarrow -6i_2 + 8i_3 = 0$
 $\underline{-3i_2 + 4i_3 = 0} \quad (3)$

Solving (1), (2) and (3)

$$\therefore \underline{i_3 = I_{\text{sc}} = 3.33 \text{ A}}$$

- Norton Equivalent Circuit:

