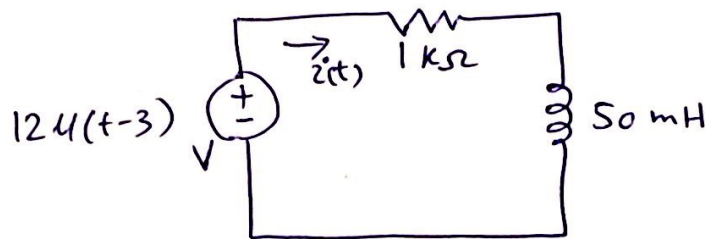


Example 8.7 Driven RL Circuits

(PP 288 8th Ed HKD) (PP 288)

Find $i(t)$ for $t = \infty$, 3^- , 3^+ and 100 μ s after
the source changes value. (Note: Source changes value at $t = 3^+$)



Note: The source changes value at $t = 3$; $t = 3^-$ indicates the instant just before the source changes value. Also $t = 3^+$ indicates the instant just after the source changes value.

Solution:

At $t = \infty$:

$$i(\infty) = \frac{12}{1 \times 10^3} = 12 \text{ mA}$$

At $t = 3^-$

$$i(3^-) = 0$$

At $t = 3^+$

$$i(3^+) = 0$$

We now determine

$$i(t);$$

as inductor current cannot change instantaneously; although resistor current can.

_____ contd

— contd (288)

The time constant $\tau = \frac{L_{eq}}{R_{eq}}$ (After all independent sources are eliminated)

$$= \frac{50 \times 10^{-3}}{1 \times 10^3} = 5 \times 10^{-6} \text{ s}$$

$$\text{or } \frac{1}{\tau} = 20,000$$

We know for a dc driven RL circuit:

$$i(t) = i(\infty) + \left[i(0^+) - i(\infty) \right] e^{-t/\tau}$$

$$i(t) = 12 + (0 - 12) e^{-20,000 t}$$

So at $t = 0.0001 \text{ s}$ (i.e. $100 \times 10^{-6} \text{ s}$)

Recalling $0.1 \rightarrow 10^{-1}$

0.01	10^{-2}
0.001	10^{-3}
0.0001	10^{-4}

$$\text{So } i(0.0001 \text{ s}) = 12 - 12 e^{-20,000 \times \frac{1}{10,000}}$$

$$= 12 - 12 e^{-2}$$

$$= 12 - 12 \times 0.135 \quad (e^{-2} = 0.135)$$

$$= 12 - 1.62 = 10.38 \text{ mA}$$

Note: If we replace t with $t-3$, then it will be $i(3.0001) = 10.38 \text{ mA}$