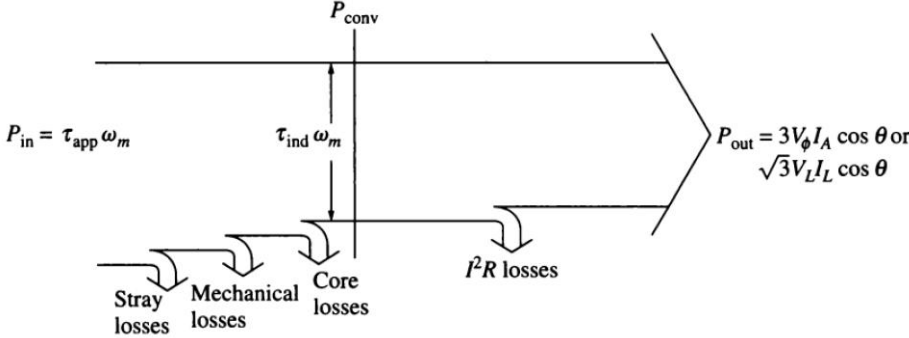


Magnetic Circuits & Linear DC Machine	Transformers
$\mathcal{F} = \phi \mathcal{R} \quad \mathcal{R} = \frac{l_c}{\mu A} \quad B = \mu H = \frac{\mu N i}{l_c}$	$\frac{V_P}{V_S} = a \quad \frac{I_P}{I_S} = \frac{1}{a}$
$e_{\text{ind}} = (\mathbf{v} \times \mathbf{B}) \cdot \mathbf{l} \quad \mathbf{F} = i(\mathbf{l} \times \mathbf{B})$	$\text{VR} = \frac{V_{S,\text{nl}} - V_{S,\text{fl}}}{V_{S,\text{fl}}} \times 100\% \quad \eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{loss}}} \times 100\%$
<p>As Generator: <math>e_{\text{ind}} = V_B + iR</math></p> <p>As Motor: <math>e_{\text{ind}} = V_B - iR</math></p>	<p><math>V_P = V_S' + I_S' (R_{\text{eq}} + jX_{\text{eq}})</math></p> <p><math>V_S' = aV_S \quad I_S' = \frac{I_S}{a}</math></p> <p><math>\text{VR} = \frac{V_P - aV_S}{aV_S} \times 100\%</math></p> <p>Referred to primary*</p>
	<p><math>V_P' = V_S + (R_{\text{EQ}} + jX_{\text{EQ}}) I_S</math></p> <p><math>V_P' = \frac{V_P}{a}</math></p> <p><math>\text{VR} = \frac{V_P/a - V_{S,\text{fl}}}{V_{S,\text{fl}}} \times 100\%</math></p> <p>No load voltage: referred to secondary*</p>

Autotransformers	Three-phase Transformers
$\frac{V_L}{V_H} = \frac{N_C}{N_{SE} + N_C} \quad \frac{I_L}{I_H} = \frac{N_{SE} + N_C}{N_C}$	$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{\sqrt{3}V_{\phi S}} = a \quad \text{Y-Y}$
$\frac{S_{IO}}{S_W} = \frac{N_{SE} + N_C}{N_{SE}}$	$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a \quad \Delta-\Delta$
When 'transforming' (hehe) a simple transformer to a step up/down autotransformer, use the rated power of the original transformer as $S_W$ , i.e., the power in the windings	$\frac{V_{LP}}{V_{LS}} = \sqrt{3}a \quad \text{Y}-\Delta$
The effective per-unit impedance of autotransformers is decreased by the power advantage factor, i.e., $\frac{S_{IO}}{S_W}$	$\frac{V_{LP}}{V_{LS}} = \frac{a}{\sqrt{3}} \quad \Delta-Y$
	$Z_{\text{base}} = \frac{3(V_{\phi,\text{base}})^2}{S_{\text{base}}} \quad I_{L,\text{base}} = \frac{S_{\text{base}}}{\sqrt{3}V_{L,\text{base}}}$


AC Machinery			
$\theta_{se} = \frac{P}{2} \theta_{sm}$	$f_{se} = \frac{P}{2} f_{sm}$	$\omega_{se} = \frac{P}{2} \omega_{sm}$	$f_{se} = \frac{n_{sm} P}{120}$
$i_{aa'}(t) = I_M \sin \omega t \quad \text{A}$	$\mathbf{B}_{aa'}(t) = B_M \sin \omega t \angle 0^\circ \quad \text{T}$	$i_{bb'}(t) = I_M \sin (\omega t - 120^\circ) \quad \text{A}$	$\mathbf{B}_{bb'}(t) = B_M \sin (\omega t - 120^\circ) \angle 120^\circ \quad \text{T}$
$i_{cc'}(t) = I_M \sin (\omega t - 240^\circ) \quad \text{A}$	$\mathbf{B}_{cc'}(t) = B_M \sin (\omega t - 240^\circ) \angle 240^\circ \quad \text{T}$		
To reverse direction of rotating magnetic field, swap any two of the three phases*			

$e_{\text{ind}} = \phi_{\text{max}} \omega \sin \omega t$	$E_{\text{max}} = N_C \phi \omega$	$E_A = \sqrt{2} \pi N_C \phi f$
$\tau_{\text{ind}} = k \mathbf{B}_R \times \mathbf{B}_S$	$\tau_{\text{ind}} = k B_R B_{\text{net}} \sin \delta$	
 <p style="text-align: right;">Generator power flow*</p>		
$\text{VR} = \frac{V_{\text{nl}} - V_{\text{fl}}}{V_{\text{fl}}} \times 100\%$	$\text{SR} = \frac{n_{\text{nl}} - n_{\text{fl}}}{n_{\text{fl}}} \times 100\%$	

Synchronous Generator		
$E_A = \sqrt{2} \pi N_C \phi f$	$E_A = K \phi \omega$	$K = \frac{N_c}{\sqrt{2}}$
$\mathbf{V}_\phi = \mathbf{E}_A - jX_S \mathbf{I}_A - R_A \mathbf{I}_A$	$P_{\text{conv}} = \frac{3V_\phi E_A}{X_S} \sin \delta$	
$P_{\text{max}} = \frac{3V_\phi E_A}{X_S}$	$\tau_{\text{ind}} = \frac{3V_\phi E_A}{\omega_m X_S} \sin \delta$	
Static stability limit		
$Z_S = \sqrt{R_A^2 + X_S^2} = \frac{E_A}{I_A} = \frac{V_{\phi,oc}}{I_A}$	$2R_A = \frac{V_{\text{DC}}}{I_{\text{DC}}}$	$\frac{2}{3} R_A = \frac{V_{\text{DC}}}{I_{\text{DC}}}$
	Y-Connected	$\Delta$ -Connected
Identifying synchronous generator's parameters*		
$P = s_p(f_{\text{nl}} - f_{\text{sys}})$	$Q = s_p(V_{T,\text{nl}} - V_{T,\text{fl}})$	
Adjusting governor set points adjusts $f$ , and hence control the real power supplied by the generator		
Adjusting field current adjusts $V_T$ , and hence controls the reactive power supplied by the generator		

Induction Motors		
$n_{\text{slip}} = n_{\text{sync}} - n_m$	$s = \frac{n_{\text{sync}} - n_m}{n_{\text{sync}}} (\times 100\%)$	$n_m = (1 - s)n_{\text{sync}}$
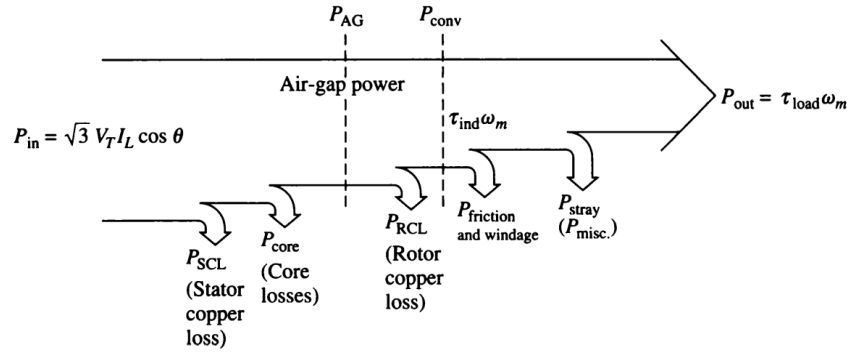
$$f_{re} = sf_{se} \quad f_{re} = \frac{P}{120} (n_{\text{sync}} - n_m)$$



$$\begin{aligned} P_{\text{RCL}} &= 3I_2^2 R_2 & P_{\text{SCL}} &= 3I_1^2 R_1 & P_{\text{conv}} &= 3I_2^2 R_2 \left( \frac{1-s}{s} \right) \\ P_{\text{core}} &= 3E_1^2 G_C & P_{\text{AG}} &= 3I_2^2 \frac{R_2}{s} \end{aligned}$$

$$P_{\text{RCL}} = s P_{\text{AG}} \quad P_{\text{conv}} = (1-s) P_{\text{AG}} \quad \tau_{\text{ind}} = \frac{P_{\text{conv}}}{\omega_m} = \frac{P_{\text{AG}}}{\omega_{\text{sync}}}$$

$$V_{\text{TH}} = V_\phi \frac{X_M}{\sqrt{R_1^2 + (X_1 + X_M)^2}} \quad V_{\text{TH}} \approx V_\phi \frac{X_M}{X_1 + X_M}$$

$$R_{\text{TH}} \approx R_1 \left( \frac{X_M}{X_1 + X_M} \right)^2 \quad X_{\text{TH}} \approx X_1$$

$$\tau_{\text{ind}} = \frac{3V_{\text{TH}}^2 R_2 / s}{\omega_{\text{sync}} [(R_{\text{TH}} + R_2/s)^2 + (X_{\text{TH}} + X_2)^2]} \quad s_{\text{max}} = \frac{R_2}{\sqrt{R_{\text{TH}}^2 + (X_{\text{TH}} + X_2)^2}}$$

$$\tau_{\text{max}} = \frac{3V_{\text{TH}}^2}{2\omega_{\text{sync}} [R_{\text{TH}} + \sqrt{R_{\text{TH}}^2 + (X_{\text{TH}} + X_2)^2}]}$$

Maximum torque occurs at a point ( $s_{\text{max}}$ ) independent of change in  $V_T$ \*

Maximum torque value is independent of change in rotor resistance  $R_2$ \*

**No-Load Test**

$$\begin{aligned} P_{\text{in}} &= 3I_1^2 R_1 + P_{\text{rot}} \\ P_{\text{rot}} &= P_{\text{core}} + P_{\text{F\&W}} + P_{\text{misc}} \\ |Z_{\text{eq}}| &= \frac{V_\phi}{I_{1,\text{nl}}} \approx X_1 + X_M \end{aligned}$$

$$\text{PF} = \cos \theta = \frac{P_{\text{in}}}{\sqrt{3} V_T I_L}$$

**DC Test**

$$\begin{aligned} 2R_A &= \frac{V_{\text{DC}}}{I_{\text{DC}}} \quad \text{Y-Connected} \\ \frac{2}{3} R_A &= \frac{V_{\text{DC}}}{I_{\text{DC}}} \quad \Delta\text{-Connected} \end{aligned}$$

**Locked-Rotor Test**

$$\begin{aligned} |Z_{\text{LR}}| &= \frac{V_\phi}{I_1} = \frac{V_T}{\sqrt{3} I_L} \\ Z_{\text{LR}} &= R_{\text{LR}} + jX'_{\text{LR}} \\ &= |Z_{\text{LR}}| \cos \theta + j|Z_{\text{LR}}| \sin \theta \\ R_{\text{LR}} &= R_1 + R_2 \\ X_{\text{LR}} &= \frac{f_{\text{rated}}}{f_{\text{test}}} X'_{\text{LR}} = X_1 + X_2 \end{aligned}$$

DC Test:  $R_A$  is  $R_1$ \*

Rotor Design	X <sub>1</sub> and X <sub>2</sub> as functions of X <sub>LR</sub>	
	X <sub>1</sub>	X <sub>2</sub>
Wound rotor	0.5 X <sub>LR</sub>	0.5 X <sub>LR</sub>
Design A	0.5 X <sub>LR</sub>	0.5 X <sub>LR</sub>
Design B	0.4 X <sub>LR</sub>	0.6 X <sub>LR</sub>
Design C	0.3 X <sub>LR</sub>	0.7 X <sub>LR</sub>
Design D	0.5 X <sub>LR</sub>	0.5 X <sub>LR</sub>

DC Machines			
$e_{\text{ind}} = \frac{2}{\pi} \phi \omega_m \qquad \tau_{\text{ind}} = \frac{2}{\pi} \phi i$		Armature loss: $P_A = I_A^2 R_A$ Field loss: $P_F = I_F^2 R_F$	
		$\frac{E_{A2}}{E_{A1}} = \frac{K' \phi n_{m2}}{K' \phi n_{m1}}$	
<b>Separately Excited and Shunt DC Motor</b> <div><div><math display="block">I_F = \frac{V_F}{R_F}</math><math display="block">V_T = E_A + I_A R_A</math><math display="block">I_L = I_A</math></div><div><math display="block">I_F = \frac{V_T}{R_F}</math><math display="block">V_T = E_A + I_A R_A</math><math display="block">I_L = I_A + I_F</math></div></div> $\omega_m = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{\text{ind}}$		<b>Series DC Motor</b> $I_A = I_S = I_L$ $V_T = E_A + I_A (R_A + R_S)$ $\omega_m = \frac{V_T}{\sqrt{Kc}} \frac{1}{\sqrt{\tau_{\text{ind}}}} - \frac{R_A + R_S}{Kc}$	
		<b>Compound DC Motor</b> $V_T = E_A + I_A (R_A + R_S)$ $I_A = I_L - I_F$ $I_F = \frac{V_T}{R_F}$ $I_F^* = I_F \pm \frac{N_{SE}}{N_F} I_A - \frac{\mathcal{F}_{AR}}{N_F}$	
See characteristic curves from book*			
<b>Separately Excited DC Generator</b> $I_L = I_A$ $V_T = E_A - I_A R_A$ $I_F = \frac{V_F}{R_F}$ $I_F^* = I_F - \frac{\mathcal{F}_{AR}}{N_F}$	<b>Shunt DC Generator</b> $I_A = I_F + I_L$ $V_T = E_A - I_A R_A$ $I_F = \frac{V_T}{R_F}$	<b>Series DC Generator</b> $I_A = I_S = I_L$ $V_T = E_A - I_A (R_A + R_S)$	<b>Compound DC Generator</b> $I_A = I_L + I_F$ $V_T = E_A - I_A (R_A + R_S)$ $I_F = \frac{V_T}{R_F}$ $\mathcal{F}_{\text{net}} = N_F I_F \pm N_{SE} I_A - \mathcal{F}_{AR}$
See characteristic curves from book*			

You made it this far! Good luck with your exams! ❤️

- Arctic Monkeys makes banger songs
- KitKat >> any chocolate
- Made by me! I should go sleep ...