

# EE-421: Digital System Design

## Verilog Operators Expressing Numbers in Verilog Hierarchical Design – Module Instantiation

Instructor: Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Verilog Operators


# Verilog Operators and Bit Lengths: For Reference

Category	Examples	Bit Length
Bitwise	$\sim A$ , $+A$ , $-A$ $A \& B$ , $A   B$ , $A \sim \wedge B$ , $A \wedge \sim B$	$L(A)$ $\text{MAX } (L(A), L(B))$
Logical	$!A$ , $A \&\& B$ , $A    B$	1 bit
Reduction	$\&A$ , $\sim\&A$ , $ A$ , $\sim A$ , $\wedge \sim A$ , $\sim \wedge A$	1 bit
Relational	$A == B$ , $A != B$ , $A > B$ , $A < B$ $A >= B$ , $A <= B$ $A === B$ , $A !== B$	1 bit
Arithmetic	$A + B$ , $A - B$ , $A * B$ , $A / B$ $A \% B$	$\text{MAX } (L(A), L(B))$
Shift	$A << B$ , $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B\{A\}\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX } (L(B), L(C))$

# Bitwise Operators in Behavioral Verilog

```
module gates(input  [3:0]  a, b,  
              output [3:0] y1, y2, y3, y4, y5);  
  
    /* Five different two-input logic  
       gates acting on 4 bit buses */  
  
    assign y1 = a & b;      // AND  
    assign y2 = a | b;      // OR  
    assign y3 = a ^ b;      // XOR  
    assign y4 = ~(a & b);   // NAND  
    assign y5 = ~(a | b);   // NOR  
  
endmodule
```


# Bitwise Operators: Schematic View

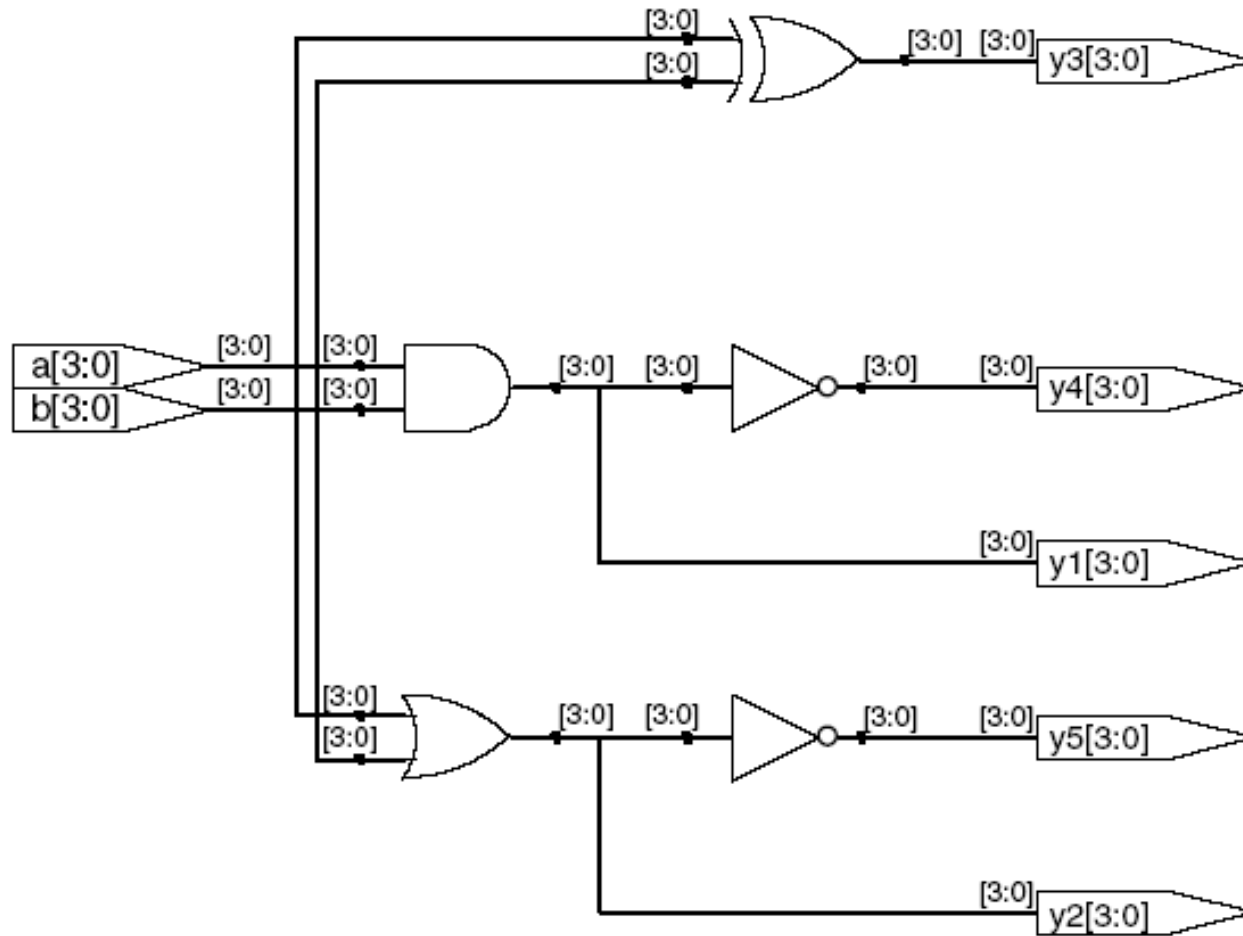

# Reduction Operators in Behavioral Verilog

```
module and8(input  [7:0] a,  
            output  y);  
  
    assign y = &a;  
  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //             a[3] & a[2] & a[1] & a[0];  
  
endmodule
```

# Reduction Operators: Schematic View

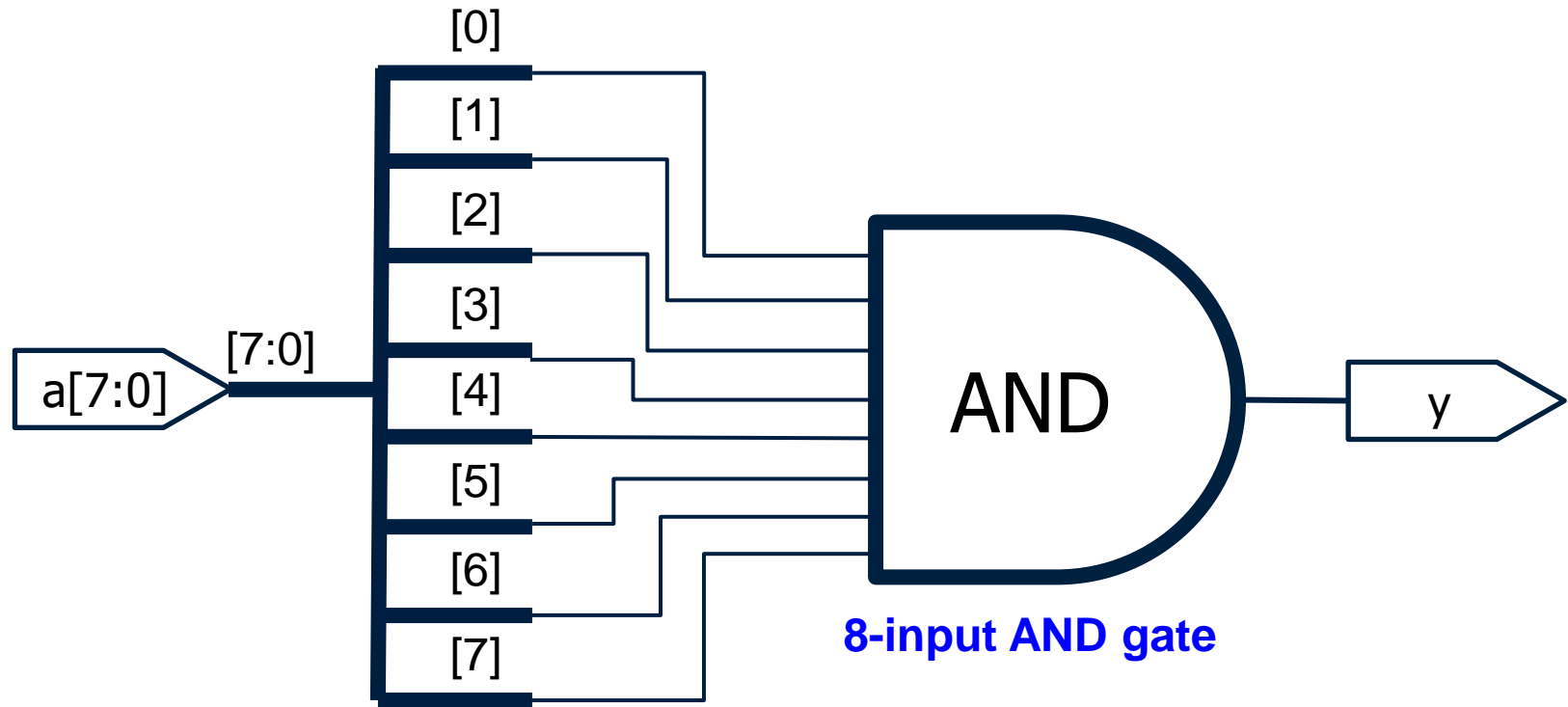


# Conditional Assignment in Behavioral Verilog

```
module mux2(input  [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

- ? : is also called a **ternary operator** as it operates on three inputs:
  - s
  - d1
  - d0



# Conditional Assignment: Schematic View

 

# More Complex Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
               : ( s[0] ? d1 : d0);

    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

# Even More Complex Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
               (s == 2'b10) ? d2 :
               (s == 2'b01) ? d1 :
               d0;

    // if      (s = "11" ) then y= d3
    // else if (s = "10" ) then y= d2
    // else if (s = "01" ) then y= d1
    // else                      y= d0

endmodule
```

# Verilog Operators and Bit Lengths: For Reference

Category	Examples	Bit Length
Bitwise	$\sim A$ , $+A$ , $-A$ $A \& B$ , $A   B$ , $A \sim \wedge B$ , $A \wedge \sim B$	$L(A)$ $\text{MAX } (L(A), L(B))$
Logical	$!A$ , $A \&\& B$ , $A    B$	1 bit
Reduction	$\&A$ , $\sim\&A$ , $ A$ , $\sim  A$ , $\wedge \sim A$ , $\sim \wedge A$	1 bit
Relational	$A == B$ , $A != B$ , $A > B$ , $A < B$ $A >= B$ , $A <= B$ $A === B$ , $A !== B$	1 bit
Arithmetic	$A + B$ , $A - B$ , $A * B$ , $A / B$ $A \% B$	$\text{MAX } (L(A), L(B))$
Shift	$A << B$ , $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B\{A\}\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX } (L(B), L(C))$

# Precedence of Operations in Verilog

**Highest**

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

**Lowest**

# Expressing Numbers in Verilog

# How to Express Numbers ?

N'Bxx

8'b0000\_0001

- (N) Number of bits
  - Expresses how many bits will be used to store the value
- (B) Base
  - Can be b (binary), h (hexadecimal), d (decimal), o (octal)
- (xx) Number
  - The value expressed in base
  - Can also have X (invalid) and Z (floating), as values
  - Underscore \_ can be used to improve readability

# Number Representation in Verilog

Verilog	Stored Number	Verilog	Stored Number
4' b1001	1001	4' d5	0101
8' b1001	0000 1001	12' hFA3	1111 1010 0011
8' b0000_1001	0000 1001	8' o12	00 001 010
8' bxX0X1zZ1	XX0X 1ZZ1	4' h7	0111
'b01	0000 .. 0001	12' h0	0000 0000 0000


**32 bits**  
**(default)**


 
# Reminder: Floating Signals (Z)

- **Floating signal:** Signal that is not driven by any circuit
  - Open circuit, floating wire
- Also known as: **high impedance, hi-Z, tri-stated** signals


```
module tristate_buffer(input  [3:0] a,  
                      input    en,  
                      output [3:0] y);  
  
    assign y = en ? a : 4'bz;  
  
endmodule
```



# Recall: Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire

Tristate  
Buffer

 


$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1

**Figure 2.40** Tristate buffer

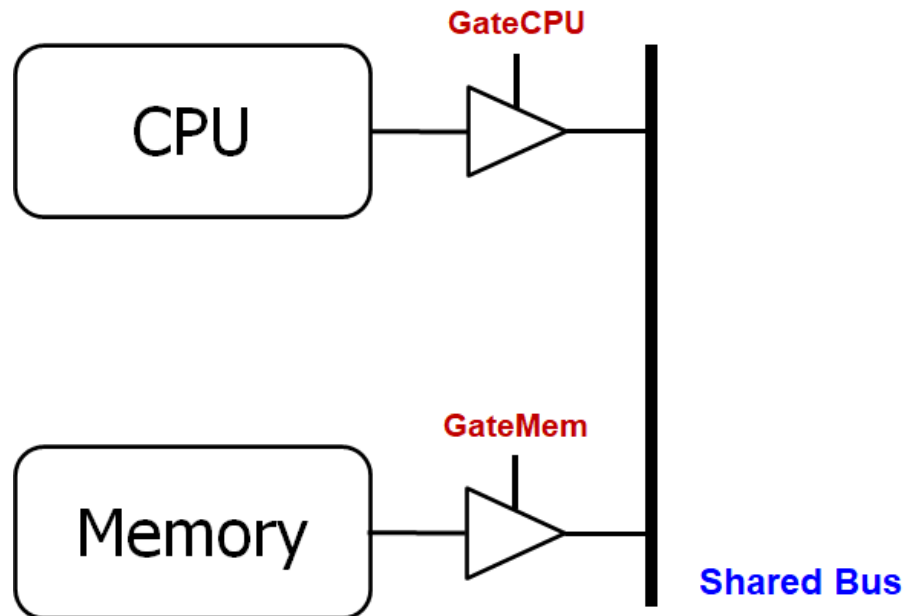
# Recall: Example Use of Tri-State Buffers

- Imagine a wire connecting the CPU and memory
  - At any time only the CPU or the memory can place a value on the wire, both not both
  - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time



# Module Instantiation

# Instantiating a Module

 


**Schematic of module "top" that is built from two instances of module "small"**

# Instantiating a Module

- Module Definitions in Verilog**

```
module top(A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small(A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

# Instantiating a Module

- Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


# Instantiating a Module

- The first instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// instantiate small once  
small i_first ( .A(A),  
                .B(SEL),  
                .Y(n1) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```



# Instantiating a Module


- The second instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
  // instantiate small second time  
  small i_second ( .A(n1),  
                   .B(C),  
                   .Y(Y) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```


```
  // description of small
```

```
endmodule
```
 
# Instantiating a Module

- **Short form of module instantiation**

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i_second ( .B(C),  
                  .Y(Y),  
                  .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

**Short form is not good practice  
as it reduces code maintainability**

# Module Parametrization

# Writing More Reusable Verilog Code

- We have a module that can compare two 4-bit numbers
- What if in the overall design we need to compare:
  - **5**-bit numbers?
  - **6**-bit numbers?
  - ...
  - **N**-bit numbers?
  - Writing code for each case looks tedious
- What could be a better way?

# Parameterized Modules

In Verilog, we can define **module parameters**

```
module mux2
  #(parameter width = 8) // name and default value
  (input  [width-1:0] d0, d1,
   input                               s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

We can set the parameters to different values  
when instantiating the module

# Instantiating Parameterized Modules

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input          s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

```
// If the parameter is not given, the default (8) is assumed
mux2 i_mux (d0, d1, s, out);

// The same module with 12-bit bus width:
mux2 #(12) i_mux_b (d0, d1, s, out);

// A more verbose version:
mux2 #(.width(12)) i_mux_b (.d0(d0), .d1(d1),
                           .s(s), .out(out));
```