



NATIONAL UNIVERSITY OF SCIENCES & TECHNOLOGY

Electric Network Analysis (EE-211)

**Assignment # 3**

**Submitted to:** Ahsan Azhar

**Submitted by:** Muhammad Umer

**Class:** BEE-12C


**Semester:** 2<sup>nd</sup>

**Dated:** 5/4/2021

**CMS ID:** 345834

# Assignment # 3

12.11)

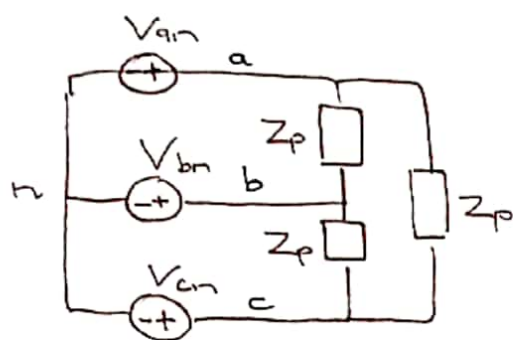


$$V_{an} = 240 \angle 0^\circ \text{ V}$$

$$Z_p = 2 - j3 \, \Omega$$

It is a  $\gamma - \Delta$  connection;  
Converting  $Z_p$  to a  $\gamma$  load

$$Z_Y = \frac{Z_\Delta}{3} = \frac{2 - j3}{3} = \frac{2}{3} - j$$

Single Phase Equivalent

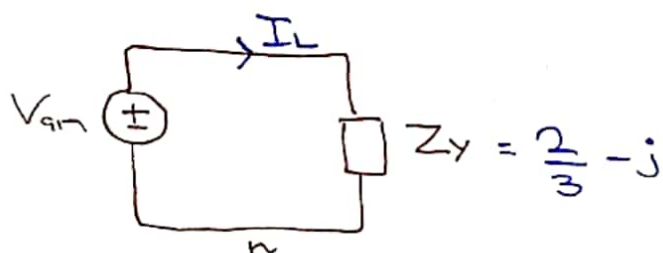

$$I_L = \frac{V_{an}}{|Z_Y|} = \frac{240}{1.201} = \boxed{199.83 \text{ A}}$$


$$V_L = V_p (\sqrt{3}) = \boxed{415.69 \text{ V}}$$

12.25)


$$V_{ab} = 440 \angle 10^\circ \text{ V}$$

$$V_{bc} = 440 \angle -110^\circ \text{ V}$$
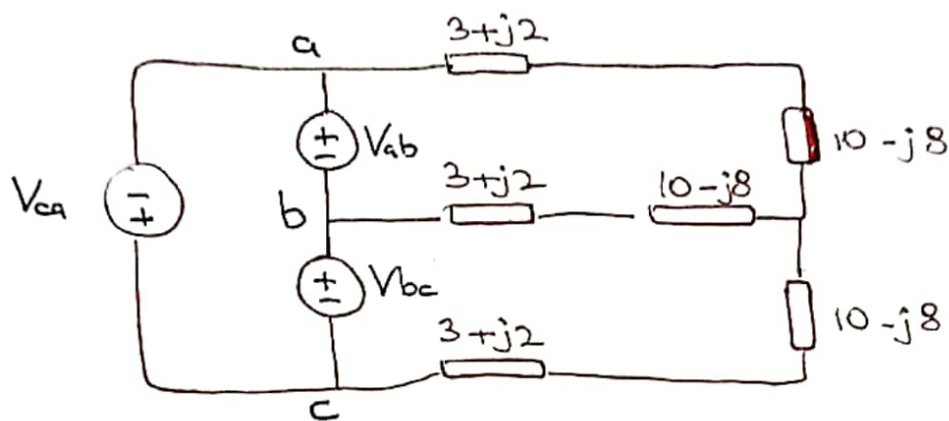
$$V_{ca} = 440 \angle 130^\circ \text{ V}$$



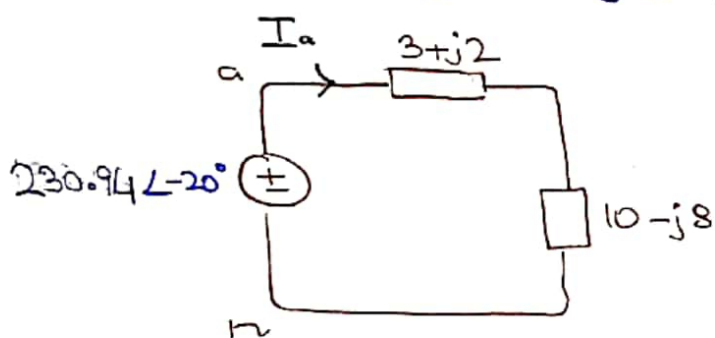Converting  $\Delta$  source to  $Y$  equivalent;  
And considering single phase equivalent



$$I_a = \frac{230.94 \angle -20^\circ}{13 - j6} = 17.742 \angle 4.77^\circ \text{ A}$$

Then,

$$I_b = 17.742 \angle -115.23^\circ \text{ A}$$

$$I_c = 17.742 \angle 124.77^\circ \text{ A}$$

12.36)

a) Complex Power

$$|S| = 10^6 \text{ VA}$$

$$\phi = \cos^{-1}(0.75) = 41.41^\circ$$

$$\begin{aligned}
 S &= |S| \angle \phi \\
 &= 10^6 \angle 41.4^\circ \\
 \text{or } &750111 + 661311.8j
 \end{aligned}$$

b) Power Loss

$$\begin{aligned}
 S &= 3 V_{rms} I_{rms}^* \\
 I_{rms} &= I_p, \quad V_{rms} = V_p \\
 I_p^* &= \frac{S}{3V_p} = \frac{750111 + 661311.8j}{3 \times 4200} \\
 I_p &= 59.53 - j52.48 \text{ A}
 \end{aligned}$$

$$P_{loss} = |I_p|^2 R_L = (79.36)^2 (4) = 25.19 \text{ kW}$$

c) Voltage at Sending End

$$\begin{aligned}
 V_s &= V_p + I_p (4 + j) \\
 &= 4200 + (59.53 - j52.48)(4 + j) \\
 &= 4493 \angle -1.91^\circ
 \end{aligned}$$

12.41)

$$P = 5 \text{ kW}$$

$$\text{pf} = 0.8 \text{ (lag)}$$


$$S = P/\text{pf} = 5\text{k}/0.8 = 6250 \text{ VA}$$

$$\text{And, } S = \sqrt{3} V_L I_L$$

$$\sqrt{3} V_L I_L = 6250$$

$$\begin{aligned} I_L &= \frac{6250}{\sqrt{3} (400)} \\ &= \boxed{9.021 \text{ A}} \end{aligned}$$

13.11)

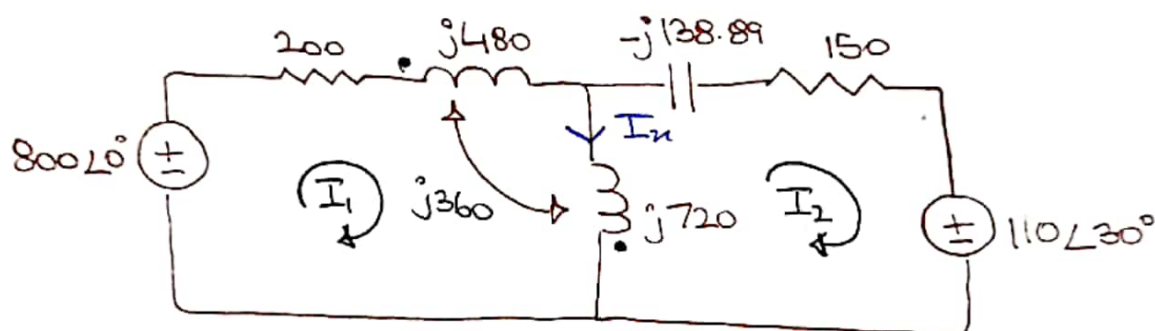

1 →

$$\begin{aligned} -800 + 200 I_1 + I_1 (j480) + I_1 (j720) - I_2 (j720) \\ + I_2 (j360) = 0 \end{aligned}$$

$$\bullet (1200j + 200) I_1 - (360j) I_2 = 800$$

2 →

$$\begin{aligned} 110 \angle 30 + (j720) I_2 - (j720) I_1 + I_2 (-j138.9) \\ + 150 I_2 + (j360) I_1 = 0 \end{aligned}$$

$$\bullet (-360j) I_1 + (150 + j581.1) I_2 = -95.26 - 55j$$


Solving gets us;

$$I_1 = 0.73 \angle -76.68$$


$$I_2 = 0.29 \angle -54.51$$

$$I_n = I_1 - I_2 = \boxed{0.474 \cos(600t - 90.02) \text{ A}}$$

13.24)

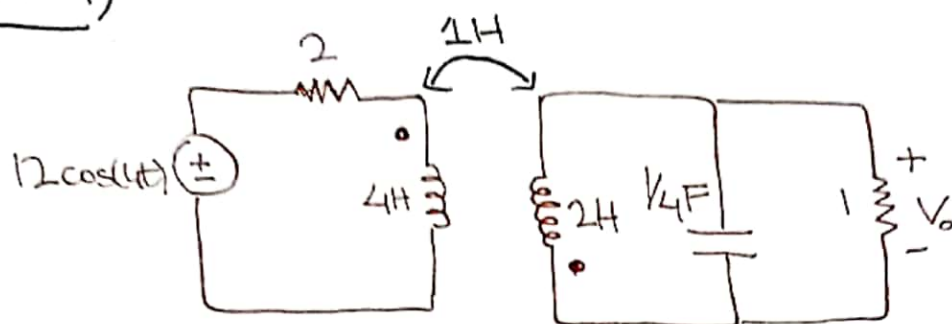

In complex system,

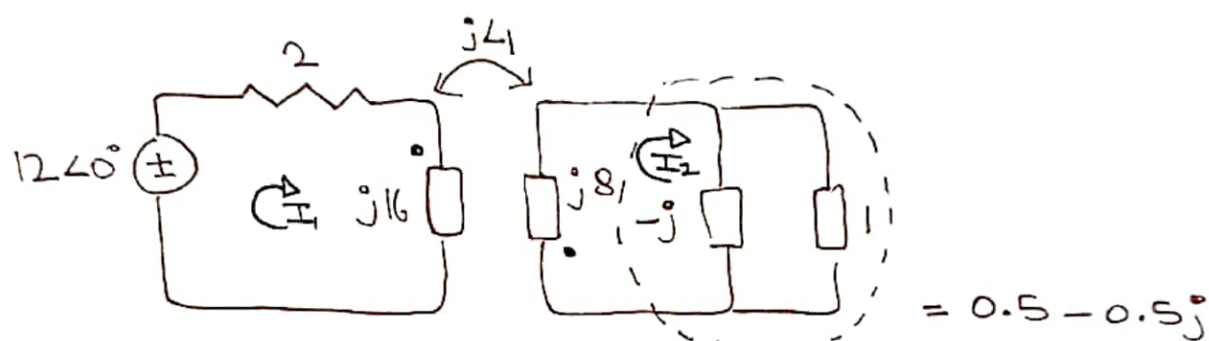

a)  $k = M / \sqrt{L_1 L_2} = 1 / \sqrt{4 \times 2} = \boxed{0.3535}$

$\xrightarrow{1} -12 + 2I_1 + j16(I_1) + j4(I_2) = 0$

•  $(2 + j16)I_1 + (j4)I_2 = 12$

$\xrightarrow{2} (0.5 - 0.5j)I_2 + j8(I_2) + j4(I_1) = 0$

•  $(j4)I_1 + (0.5 + 7.5j)I_2 = 0$

$I_1 = 0.85 \angle -81.23^\circ$

$I_2 = 0.45 \angle 102.59^\circ$

b)  $V_o = I_2 (0.5 - 0.5j)$   
 $= \underline{321.7 \cos(4t + 57.59^\circ) V}$

$$c) \dot{i}_1 = 0.855 \cos(4t - 81.21^\circ)$$

$$\dot{i}_2 = 0.45 \cos(4t + 102.59^\circ)$$

$$\text{At } t = 2s$$

$$\dot{i}_1 = 0.812 \text{ A}$$

$$\dot{i}_2 = -0.420 \text{ A}$$


$$\bullet W = \frac{1}{2} L_1 \dot{i}_1^2 + \frac{1}{2} L_2 \dot{i}_2^2 + M \dot{i}_1 \dot{i}_2$$

$$= (0.5)(4)(0.812)^2 + (0.5)(2)(-0.420)^2 + (1)(0.812)(-0.420)$$

$$W = 1.154 \text{ J}$$

$$13.49) \quad \omega = 2$$
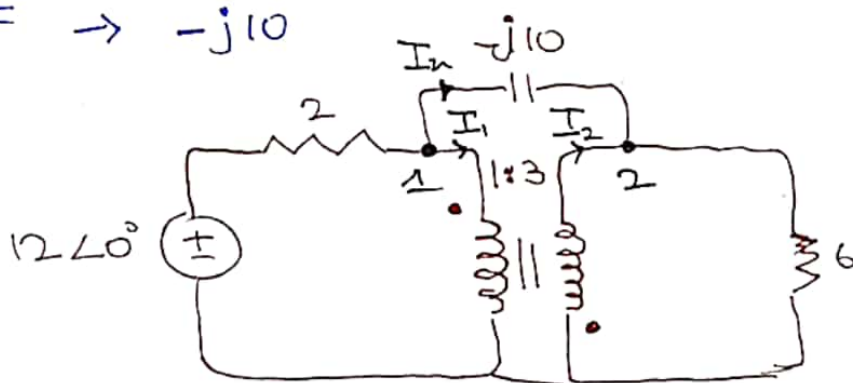
$$\frac{1}{20} \text{ F} \rightarrow -j10$$



$$\xrightarrow{1} \frac{V_1 - 12}{2} + \frac{V_1 - V_2}{-j10} + I_1 = 0$$

$$\xrightarrow{2} \frac{V_2 - V_1}{-j10} + \frac{V_2}{6} = I_2$$

From terminals of transformer,



$$V_2 = -3V_1$$

$$I_2 = -\frac{1}{3}I_1$$


By substituting into 1 and 2;

$$V_1 = 1.829 - j1.463 \text{ V}$$

$$I_n = \frac{V_1 - V_2}{-j10} = \frac{4V_1}{-j10} = \boxed{0.937 \angle 51.34^\circ}$$


$$I_n \Rightarrow i_n(t) = \boxed{937 \cos(2t + 51.34^\circ) \text{ mA}}$$

13.62)

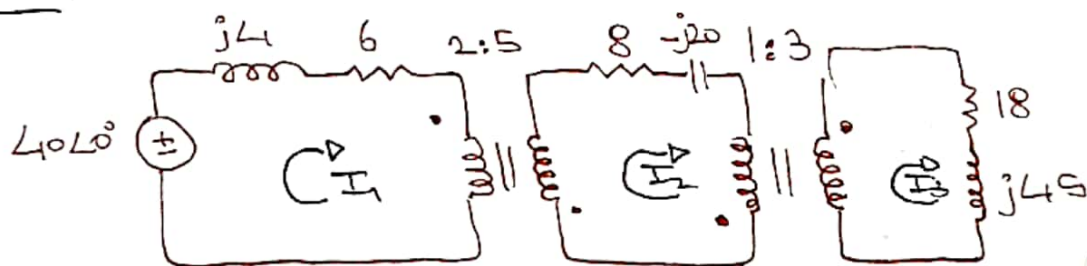


$$Z_L' = 8 - j20 + \frac{18 + j45}{3^2}$$

$$Z_L' = 10 - j15$$

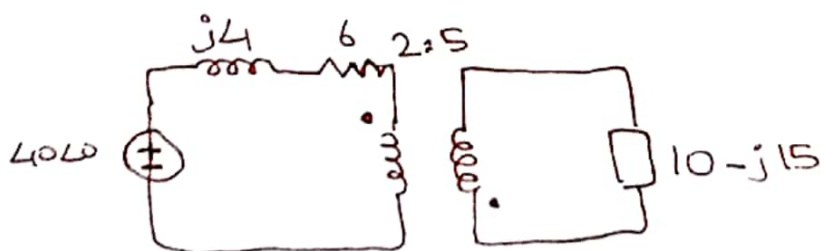
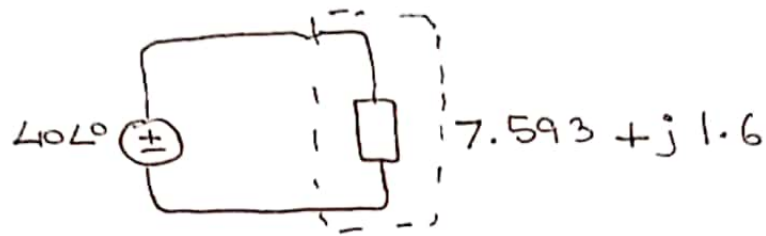
$$Z_{in} = 6 + j4 + \frac{10 - j15}{(5/2)^2} = 7.76 \angle 11.88^\circ$$





$$S = V_s I_1^* = (40) \left( \frac{40}{7.593 + j1.6} \right)^*$$

$$\boxed{S = 206.19 \angle 11.9^\circ \text{ VA}}$$

b) Average Power of  $18 \Omega$

$$\Rightarrow I_2 = -\frac{I_1}{n}$$

$$\Rightarrow I_3 = -\frac{I_2}{n'} = \frac{I_1}{n'n}$$

$$= \frac{5.154 \angle -11.9^\circ}{\left(\frac{5}{2}\right)(3)}$$

$$I_3 = 0.6867 \angle -11.89^\circ \text{ A}$$

$$P_{18\Omega} = |I_3|^2 (R)$$

$$= (0.6867)^2 (18)$$

$$= \boxed{8.4188 \text{ W}}$$