



National University of Sciences & Technology (NUST)
School of Electrical Engineering and Computer Science (SEECs)
Department of Electrical Engineering

Faculty Member: _____

Dated: _____

Semester: _____

Section: _____

EE313: ELECTRONIC CIRCUIT DESIGN

Lab10: Differential pair

(Mismatches and Offset Null adjustment)

S.no	Name	Reg. no.	Total/25
1			
2			
3			
4			



Objective

The input offset voltage of operational amplifiers (op amps) arises from unavoidable mismatches in the differential input stage of the op-amp circuit caused by mismatched transistor pairs, collector currents, current-gain betas (β), collector or emitter resistors, etc. This experiment deals with voltage offset due to collector resistance mismatch.

Materials

The items listed in table 1 will be needed. For this lab, assume all NPN transistors are identical 2N2222 BJTs.

CAUTION: Please DO NOT leave the circuit on for long periods since there is a risk of heating up of transistors.

Components	Quantity
Transistors:	2N2222 NPN x2
Resistors:	10k x 1 ,5.6k x 2, 1k variable resistor

Introduction

Consider the simplified input-stage circuit of the operational amplifier in Figure 1. The input offset voltage of the op amp results from mismatches in collector/emitter resistors and the transistor pair of the differential input. Each of these mismatches is examined separately below.

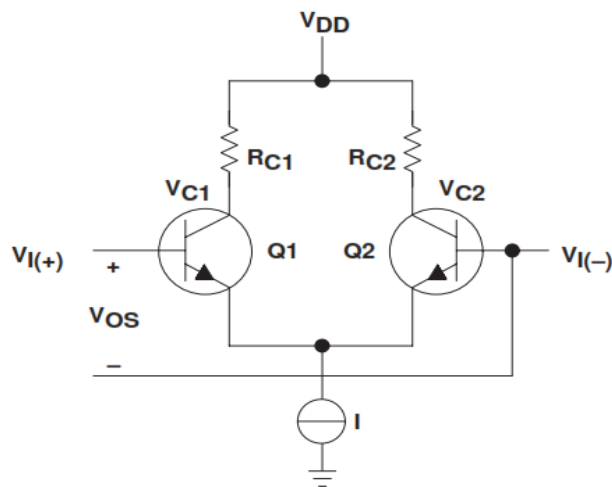


Figure 1. The Simplified Differential Input Circuit



Effect of Collector-Resistor (R_c) Mismatch on V_{os}

When the transistors Q_1 and Q_2 in Figure 1 are perfectly matched, the current, I , is divided equally between them.

$$\text{Let } R_c = \frac{R_{c1} + R_{c2}}{2} \text{ and } \Delta R_c = R_{c1} - R_{c2}$$

$$\text{Then, } R_{c1} = R_c + \frac{\Delta R_c}{2} \text{ and } R_{c2} = R_c - \frac{\Delta R_c}{2}$$

Thus, the output voltage, V_o , is [1a]:

$$\begin{aligned} V_o = V_{c2} - V_{c1} &= \left(V_{DD} - \frac{\alpha I}{2} R_{c2} \right) - \left(V_{DD} - \frac{\alpha I}{2} R_{c1} \right) = \left[V_{DD} - \frac{\alpha I}{2} \left(R_c - \frac{\Delta R_c}{2} \right) \right] \\ &- \left[V_{DD} - \left(\frac{\alpha I}{2} \right) \left(R_c + \frac{\Delta R_c}{2} \right) \right] = \Delta R_c \frac{\alpha I}{2} \end{aligned}$$

$$\text{The input offset voltage is } V_{os} = \frac{V_o}{A_d} = \frac{V_o}{g_m R_c} = \frac{\alpha \left(\Delta R_c \right) \left(\frac{I}{2} \right)}{\frac{\alpha I}{2} R_c} = V_T \frac{\Delta R_c}{R_c} = \frac{kT}{q} \frac{\Delta R_c}{R_c} \quad (1)$$

where

$$\alpha = \frac{\beta}{\beta + 1}; \text{ differential gain : } A_d = g_m R_c; g_m = \frac{I_c}{V_T} \text{ and } V_T = \frac{kT}{q} \text{ is the thermal voltage.}$$

Here k is Boltzmann's constant and q is the charge on the electron

Procedure

PART 1- CALCULATION

a) Consider the circuit shown in Figure 2 using 2N2222 transistors for the NPN BJTs.

Use $R_3 = 10 \text{ k } \Omega$, $R_1 = R_2 = 5.6 \text{ k } \Omega$, $V_{CC} = 9 \text{ V}$ and $V_{EE} = -9 \text{ V}$

b) Calculate the DC bias currents I_{C1} and I_{C2} and Voltages V_{C1} and V_{C2} .



I_{C1} : _____, I_{C2} : _____

V_{C1} : _____ V_{C2} : _____

c) Hence calculate the differential gain A_d for the give circuit.

A_d = _____

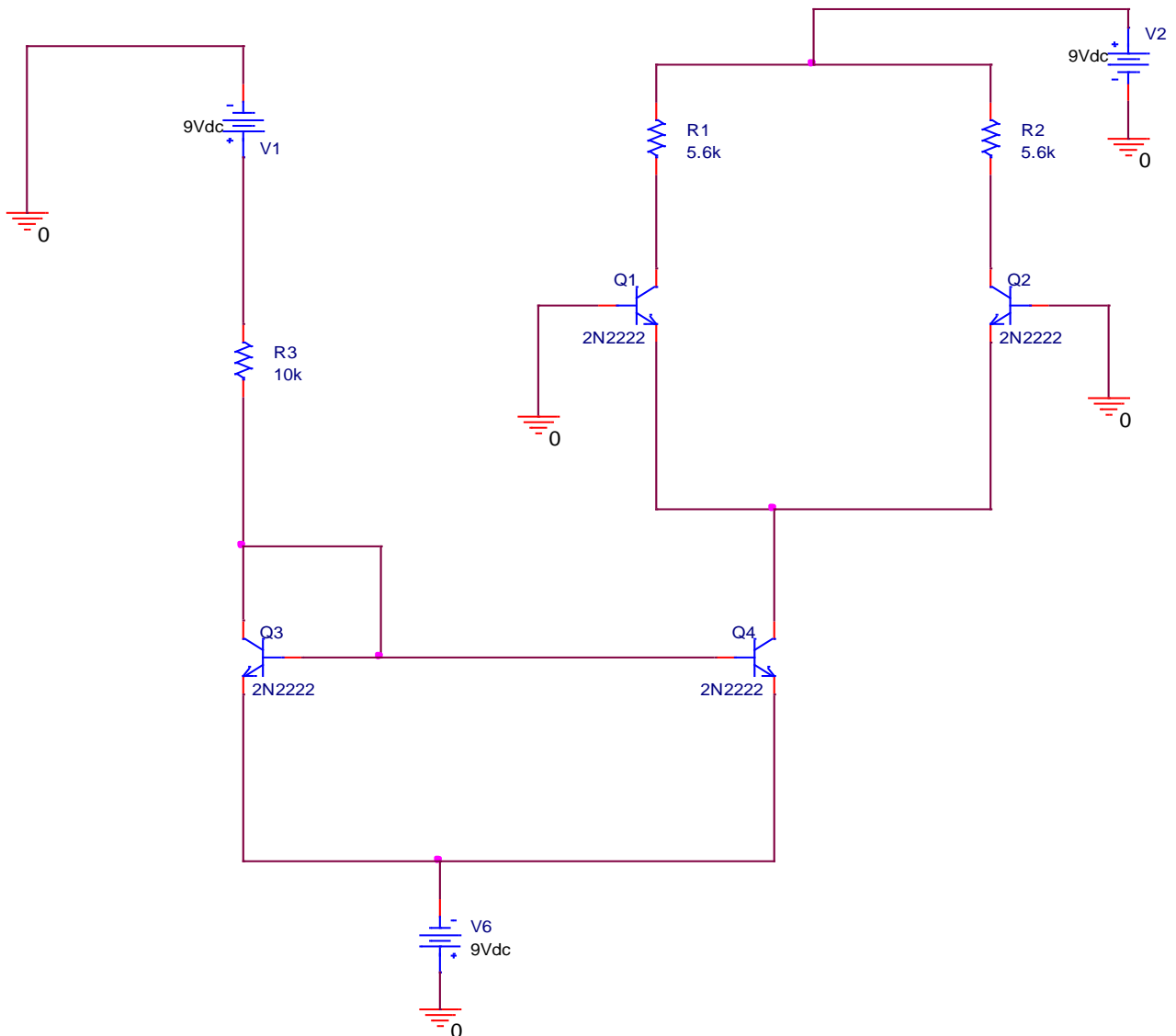


Figure 2. Differential Amplifier



d) Use a multimeter to measure the exact resistance of the 5.6k Ohms resistances. (Note: We shall use the higher resistance as R1 as shown in figure1.)

R1 (measured):_____ R2 (measured):_____

e) Using the values measured above calculate the mismatch.

$$\frac{\Delta R_c}{R_c} = \underline{\hspace{2cm}}$$

f) Using the measured values of resistance calculate the new collector voltages and hence the difference between the collector voltages

V_{C1}:_____ V_{C2}:_____

V_{C2}- V_{C1}:_____

d) Calculate the offset voltage using the formula given in introduction section.

V_{OS}=_____

PART 2- IMPLEMENTATION

a) On breadboard construct the circuit shown in Figure 2 using 2N2222 transistors for the NPN BJTs.

Use R3 = 10 k Ω , R1 = R2 = 5.6 k Ω , VCC = 9 V and VEE= - 9V

Note: Use the higher value resistance of the two 5.6kohm resistances as R1

b) Measure the DC bias currents I_{C1} and I_{C2} and Voltages V_{C1} and V_{C2}.

I_{C1}:_____, I_{C2}:_____



V_{C1} :_____ V_{C2} :_____ $V_{C2} - V_{C1}$:_____

c) Hence using the measured current, calculate the differential gain A_d for the give circuit.

A_d =_____

d) Using the measured values for $V_{C2} - V_{C1}$ and A_d , Determine the offset voltage V_{OS} . Does it compare with the values calculated for PART 1?

V_{OS} =_____

e) Now add a variable resistor as shown in figure 3. Make sure that the resistance is equal on both sides.

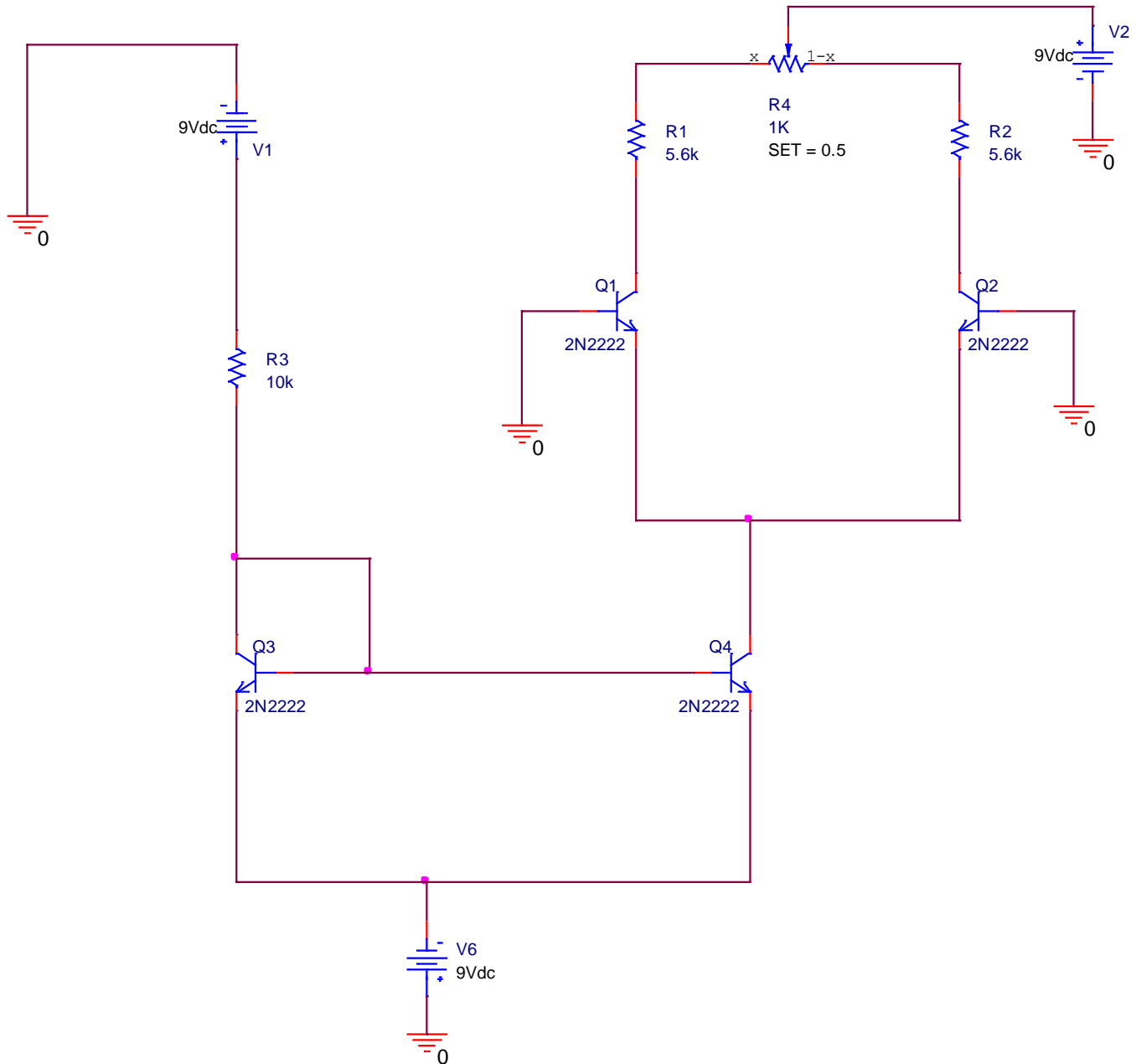


Figure 3. Differential Amplifier with potentiometer.

f) Adjust the potentiometer so that $V_{C2} - V_{C1}$ becomes 0. Measure the resistances labeled x and $1-x$ on figure3.

X: _____

1-X: _____



PART 3- SIMULATION

- a) Simulate in PSpice the circuit shown in Figure 3 using 2N2222 transistors for the NPN BJTs. Use potentiometer(POT) from the breakout library in PSPICE

Use $R_3 = 10 \text{ k } \Omega$, $R_1 = R_2 = 5.6 \text{ k } \Omega$, $V_{CC} = 9 \text{ V}$ and $V_{EE} = -9 \text{ V}$

Note: Use the measured values for R_1 and R_2 and the higher value resistance of the two as R_1

- b) Use bias point analysis for DC bias currents I_{C1} and I_{C2} and Voltages V_{C1} and V_{C2} . When potentiometer is set at 0.5.

I_{C1} : _____, I_{C2} : _____

V_{C1} : _____ V_{C2} : _____ $V_{C2} - V_{C1}$: _____

- c) Use the same values for X and 1-X measured for PART 2 and calculate the set point of potentiometer. Write down the

Note: Set: 0 means 1-x: 1kohms and set: 1 means $x=1 \text{ k ohms}$ for the potentiometer

V_{C1} : _____ V_{C2} : _____ $V_{C2} - V_{C1}$: _____