


# EE-421: Digital Systems Design

## Expressing Sequential Circuits

Instructor: Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Quick Review: Sequential Circuits


# Combinational + Memory = Sequential

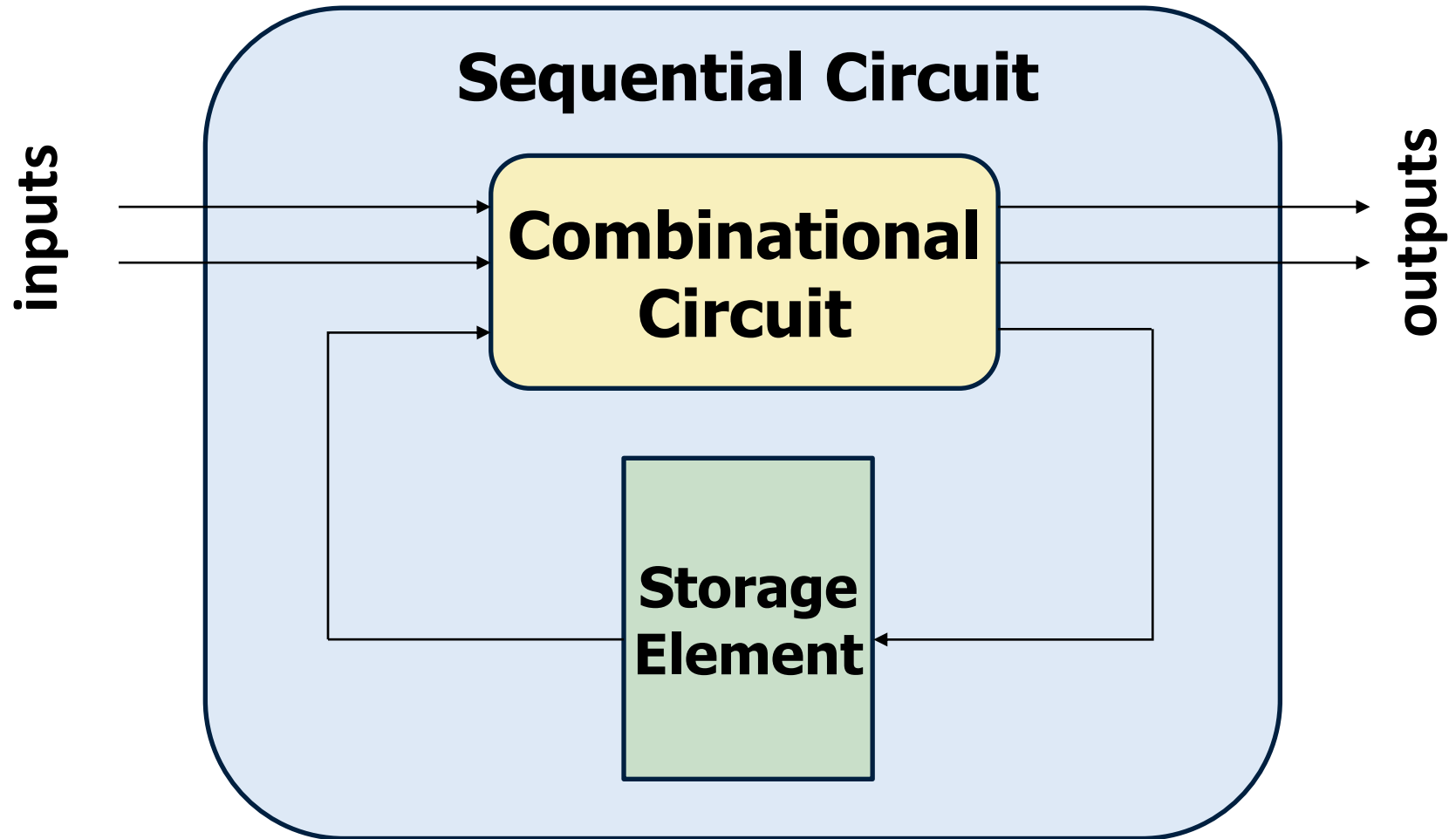

# Review: Sequential Logic


- In a **combinational** circuit, the values of the outputs are determined solely by the **present values** of its inputs.
- A **sequential** circuit has states, which in conjunction with the present values of inputs determine its behavior:
  - Such circuits include **storage elements** that store the values of logic signals
  - The contents of the storage elements are said to represent the **state of the circuit**

# Review: Gated D Latch

 


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 


(c) Graphical symbol

 


(d) Timing diagram


# Review: Master Slave D-flip flop

 

(a) Circuit

 


(c) Graphical symbol

 


(b) Timing diagram
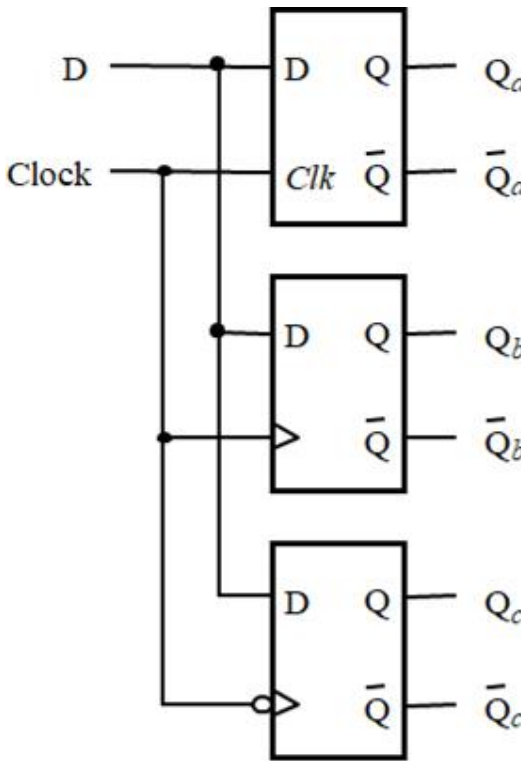
# Level-Sensitive vs Edge-Triggered Storage Elements



(a) Circuit

 

(b) Timing diagram

A flip-flop is a storage element that can have its output state changed **only on the edge of the controlling clock signal**

# Discussion: Level-Sensitive vs Edge-Triggered Storage Elements

- Ref to fig in the previous slide:
- The D input changes its values more than once during each half of the clock cycle.
- Observe that:
  - the gated D latch follows the D input as long as the clock is high.
  - The positive-edge-triggered flip-flop responds only to the value of D when the clock changes from 0 to 1
  - The negative-edge-triggered flip-flop responds only to the value of D when the clock changes from 1 to 0.



# Expressing Sequential Circuits in Verilog-HDL

# Sequential Logic in Verilog

- Define blocks that have memory:
  - *Flip-Flops, Latches, Finite State Machines*
- Sequential Logic state transition is triggered by a “CLOCK” signal:
  - Latches are sensitive to level of the signal
  - Flip-flops are sensitive to the transitioning of signal
- Combinational constructs are **not** sufficient:
  - We need **new constructs**:
    - **always\_ff**
    - **posedge/negedge**

# Recall: The “always” Block

```
always @ (sensitivity list)  
    statement;
```

Whenever the event in the **sensitivity list** occurs,  
the statement is **executed**

# Describing a Positive-Edge D-Flip Flop

```
module flop(input clk,  
            input [3:0] d,  
            output [3:0] q);  
  
    always_ff @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- **posedge** defines a rising edge (transition from 0 to 1).
- Statement executed when the **clk signal rises (posedge of clk)**
- Once the clk signal rises: the value of **d** is copied to **q**

# Describing a Positive-Edge D-Flip Flop

```
module flop(input logic clk,  
            input logic d,  
            output logic q);  
  
    always_ff @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- **Also note:**

- assign statement is **not** used within an always block
- <= describes a **non-blocking** assignment
- clk is the only input that can cause an event on the output
  - Therefore **clk is the only signal in the sensitivity list**
- Special sensitivity list @(posedge Clock):
  - This event expression tells the Verilog compiler that any reg variable assigned a value in the **always construct is the output of a D flip-flop**


# Describing a Positive-Edge D-Flip Flop

```
module flop(input logic clk,  
            input logic d,  
            output logic q);  
  
    always_ff @ (posedge clk)  
        q <= d;           // pronounced “q gets d”  
  
endmodule
```

- Assigned variables need to be declared as **reg**
- The name **reg** does not necessarily mean that the value is a register (It could be, but it does not have to be)
  - We have seen examples before while doing combinational ccts!!!
 
# Recommended Reading

- Digital System Design with Verilog HDL, 3/e, b **S**Stephen Brown and **Z**vonko Vranesic. [**S&Z**]
  - S&Z,
    - Chapter-5



# THANK YOU

