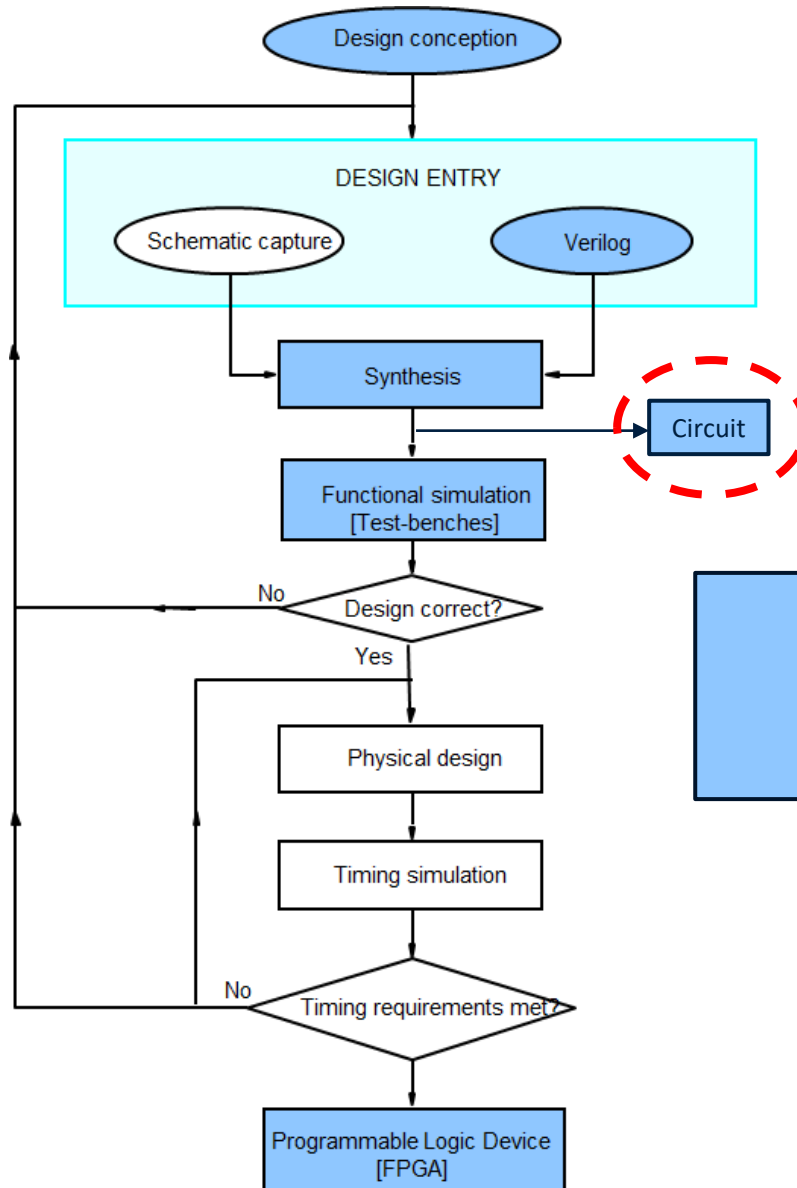


EE-421: Digital System Design

Circuit Timing

Instructor: Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Where are we Heading?



More specifically, we'll focus on the following circuit attributes:

- Circuit Timing
- Metastability


Flip-Flop Timing Constraints

Flip-flop Timing Constraints

- Flip-Flop Timing Constraints:
 - Clock-to-Q Delay
 - Setup Time
 - Hold Time

Setup Time

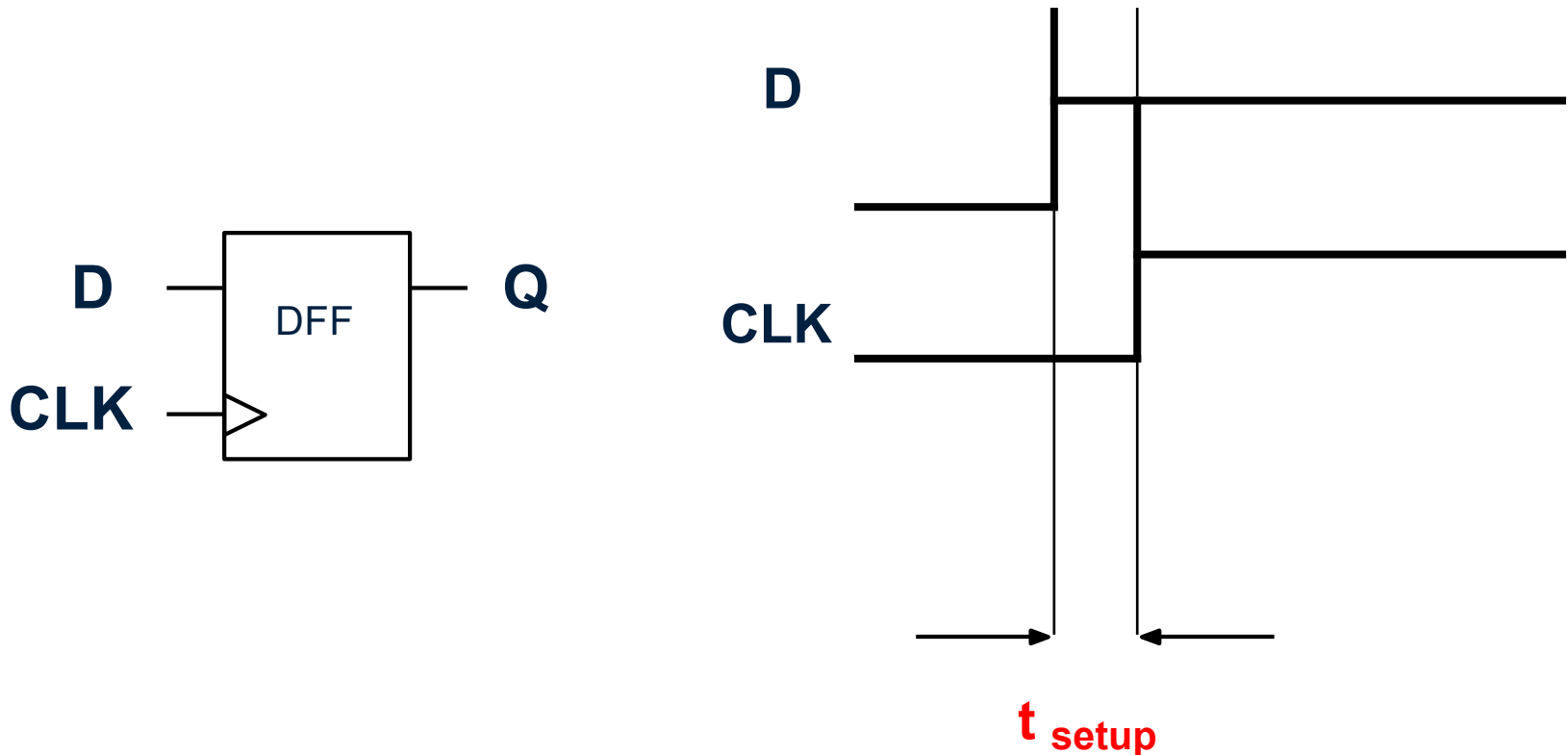
- Input to flip-flop cannot change for a certain amount of time **PRIOR** to clock rising-edge.



Time for input to propagate “into” the flip-flop before clock arrives

Hold Time

 
- Input to flip-flop cannot change for a certain amount of time **AFTER** clock rising-edge.



Time for flip-flop to fully read input before the value is “taken away”

Clock-to-Q Delay

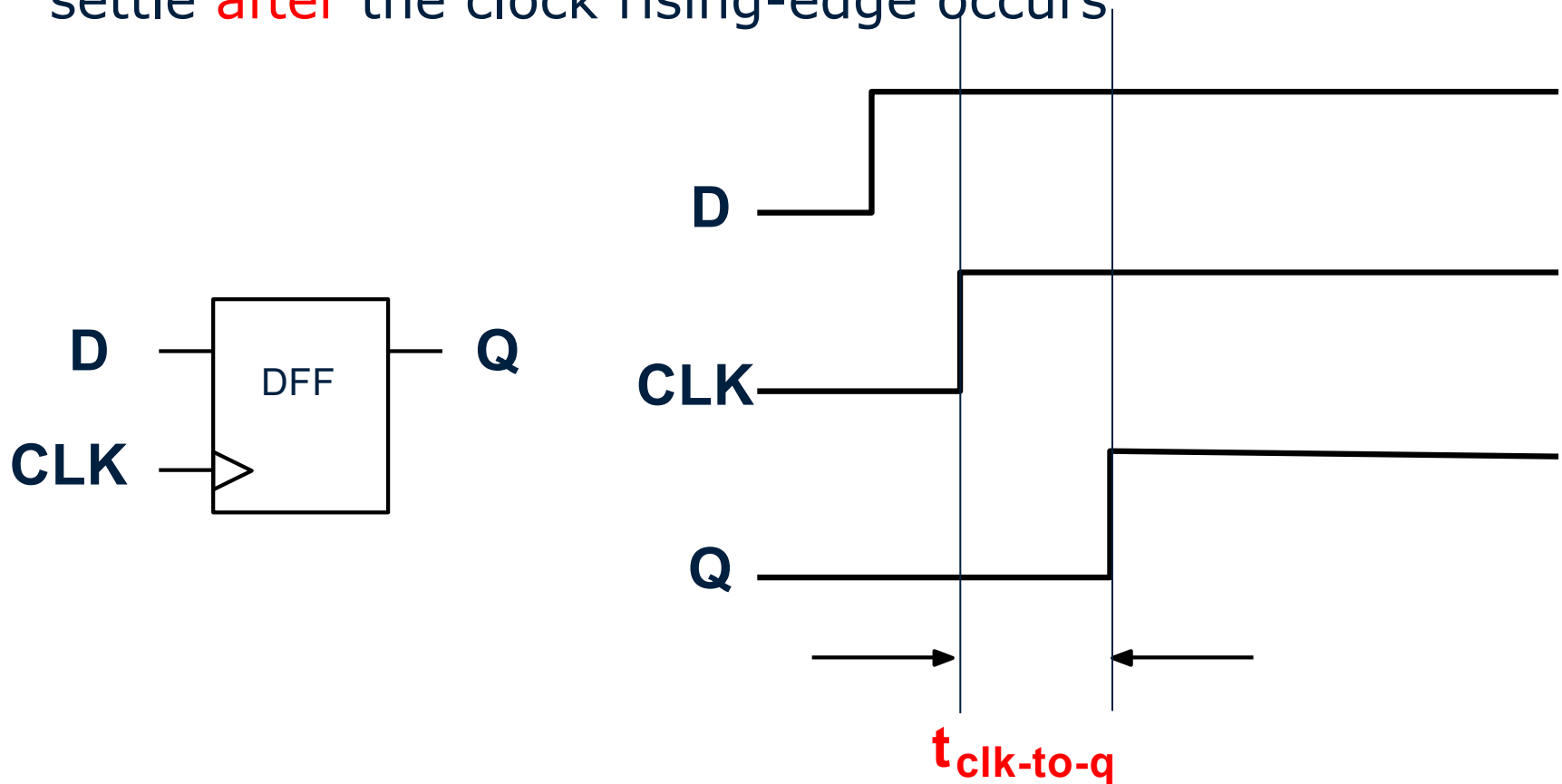- The time that it takes for the **output** of a Flip-Flop to settle **after** the clock rising-edge occurs



Note: the delay may not be exactly the same for the cases when Q changes from 1 to 0 or 0 to 1. Therefore, clk-to-q delay is often given as a max and a min value.

Summary of Flip-Flop Timing

