



# **NATIONAL UNIVERSITY OF SCIENCES & TECHNOLOGY**

## **Electrical Network Analysis (EE-211)**

### **Assignment # 2**

**Submitted to:** Ahsan Azhar

**Submitted by:** Muhammad Umer

**Class:** BEE-12C

**Semester:** 2<sup>nd</sup>


**Dated:** 01/04/2021

**CMS ID:** 345834


# Assignment 2

11.12


$Z_{TH}, Z_L$   
Max Power

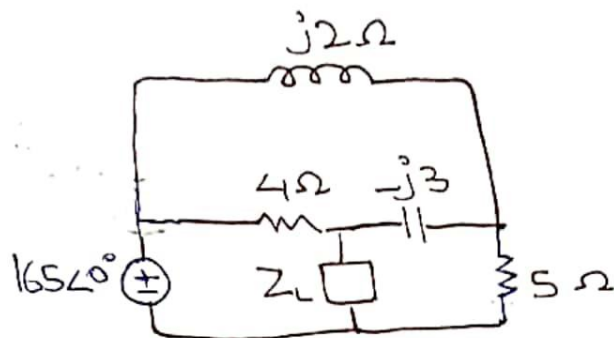

For  $Z_{TH}$

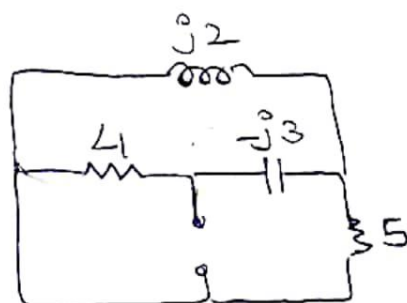


5 and  $j2$  are parallel

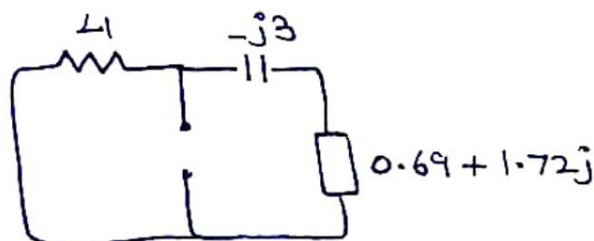

$$Z_{TH} = \frac{(0.69 + 1.72j - 3j) \times 4}{(0.69 + 1.72j - 3j) + 4} = \boxed{0.8241 - j0.866 \Omega}$$

$$Z_L = Z_{TH}^* = \boxed{0.8241 + j0.866 \Omega}$$

For  $V_{TH}$

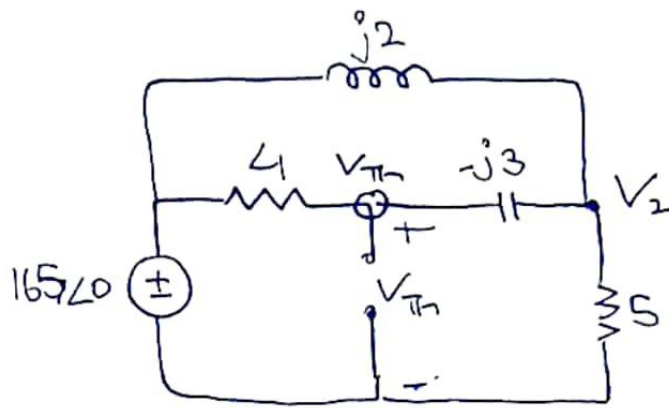

Applying KCL,

$$\circ \frac{V_{TH} - 165}{4} + \frac{V_{TH} - V_2}{-j3} = 0$$

$$(0.25 + 0.333j)V_{TH} + (-0.333j)V_2 = 41.25$$

$$\circ \frac{V_2}{5} + \frac{V_2 - V_{TH}}{-3j} + \frac{V_2 - 165}{2j} = 0$$

$$(-0.333j)V_{TH} + (0.2 - 0.1667j)V_2 = -82.5j$$

Upon solving, we get:

$$V_{TH} = 167.44 \angle -17.32^\circ$$

$$V_2 = 129.26 \angle -20.63^\circ$$

Max Power is:  $\frac{|V_{TH}|^2}{8R_{TH}} \Rightarrow \frac{(167.44)^2}{8(0.824)}$

$$P_{avg} \Rightarrow 4227.56 \text{ W}$$

11.26



$$\begin{aligned} V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\ &= \sqrt{\frac{1}{4} \int_0^2 (10)^2 dt + \int_2^4 (20)^2 dt} \\ &= \frac{1}{2} \sqrt{100t \Big|_0^2 + 400t \Big|_2^4} \\ &= \frac{1}{2} \sqrt{200 + 1600 - 800} \end{aligned}$$

$$V_{\text{rms}} = 15.811 \text{ V}$$

11.42

$$V_{\text{rms}} = 110 \text{ V}, f = 60 \text{ Hz}, |S| = 120 \text{ VA}, \text{pf} = 0.707 \text{ lag}$$

$$\text{a) } \cos^{-1}(0.707) = 45^\circ = \phi_v - \phi_i$$

$$\vec{S} = |S| \angle \phi_v - \phi_i = \boxed{120 \angle 45^\circ}$$

$$\text{b) } |I_{\text{rms}}| = |S| / |V_{\text{rms}}| = 120 / 110 = \boxed{1.091 \text{ A}}$$

$$\text{c) } S = I_{\text{rms}}^2 Z \Rightarrow Z = \frac{120 \angle 45^\circ}{(1.091)^2} = \boxed{71.277 + j 71.277}$$

$$\text{d) } Z = R + j\omega L = 71.277 + j 71.277$$


$$R = 71.277 \Omega$$

$$\omega L = 71.277$$

$$2\pi f L = 71.277$$

$$L = \frac{71.277}{2\pi(60)} = \boxed{0.189 \text{ H}}$$

11.61

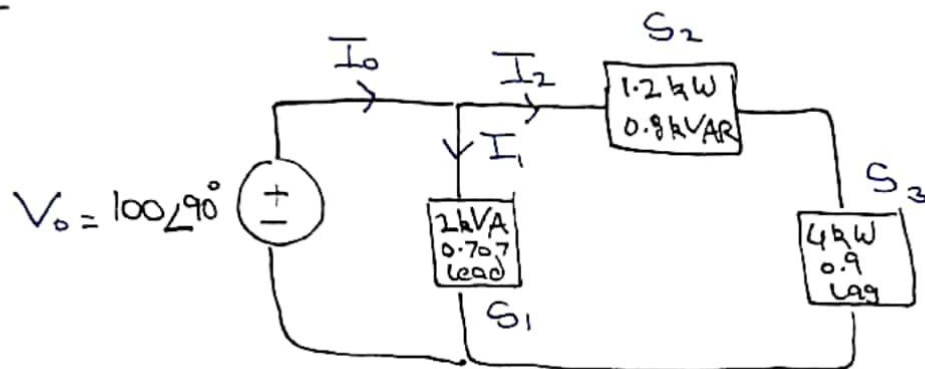


$S_1$ :

$$|S| = 2 \text{ kVA} ; \theta = \cos^{-1}(0.707)$$

$$\theta = 45^\circ$$

$$P = \cos(45^\circ) \times S = 0.707 \times 2 \text{ k}$$
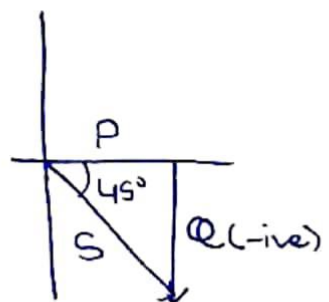
$$\underline{P_{avg} = 1414.213 \text{ W}}$$



$$Q = -\tan(45^\circ) \cdot (1414.213)$$

$$= -1414.2 \text{ VAR}$$

$$S = P + jQ$$

$$\underline{S_1 = 1414.2 - j1414.2 \text{ VA} \rightarrow 1.414 - j1.414 \text{ kVA}}$$

$$S_2:$$

$$P_{avg} = 1.2 \text{ kW}$$

$$Q = 0.8 \text{ kVAR}$$

$$\begin{aligned} S_2 &= P + jQ \\ &= \underline{1.2 + j0.8 \text{ kVA}} \end{aligned}$$


$$S_3:$$

$$P_{avg} = 4 \text{ kW}$$

$$\cos^{-1}(0.9) = \theta \Rightarrow \theta = 25.84^\circ$$

$$\tan(25.84) = Q/P$$
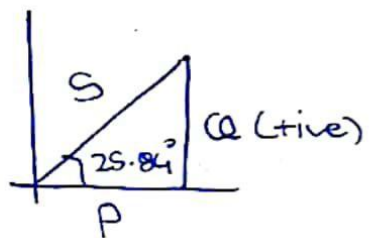
$$\begin{aligned} Q &= 0.484 \cdot 4 \times 10^3 \\ &= \underline{1937.28 \text{ VAR}} \end{aligned}$$



$$\begin{aligned} S_3 &= P + jQ \\ &= \underline{4 + j1.937 \text{ kVA}} \end{aligned}$$

For  $I_o$ :

$$\begin{aligned} I_o^* &= I_1^* + I_2^* \\ &= \frac{S_1}{V_o} + \left( \frac{S_2 + S_3}{V_o} \right) \end{aligned}$$

$$I_o^* = (11.37 - 52j) + (-14.14 - j14.14)$$


$$I_o^* = -2.77 - 66.14j$$

$$\underline{I_o = -2.77 + 66.14j = 66.19 \angle 92.4}$$

For  $S_o$ :

$$\begin{aligned} S_o &= V_{rms} \underline{I}_o^* \\ &= (100 \angle 90)(-2.77 - 66.14j) \\ &= \underline{6.61 \angle -2.4^\circ \text{ kVA}} \end{aligned}$$

11.69

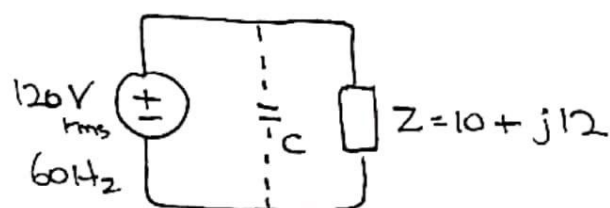


a)  $Z = R + jX$

$$Z = 10 + j12$$

$$\tan(\theta) = 12/10$$

$$\theta = 50.19^\circ$$

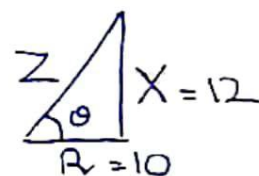


$$\text{PF} = \cos(\theta) = 0.6401$$

b) Current leads in Capacitive circuit.

$$S = \frac{V_{rms}^2}{Z^*} = \frac{120^2}{10 - j12}$$

$$S_1 = 590 + 708.1j$$

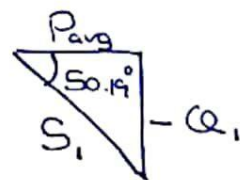

$$\underline{P = \text{Re}(S) = 590 \text{ W}}$$

$$\underline{Q = \text{Im}(S) = 708.1 \text{ VAR}}$$

$$S_2 = S_{\text{New}}$$



c)

For unity pf,

$$\cos(\theta) = 1$$

$$\theta = 0$$


From triangle,

$$-Q_2 = \tan(\theta) P_{avg} \Rightarrow (0) P_{avg}$$

$$Q_2 = 0$$

$$\begin{aligned} S_2 &= P_{avg} + jQ_2 \\ &= 590 + 0 \end{aligned}$$

$$\boxed{S_2 = 590 \text{ VA}}$$

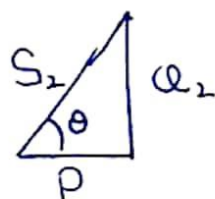

$$S_2 = S_1 + S_c$$

$$590 = 590 + j708.1 + (0 + jQ_c)$$

$$jQ_c = -j708.1$$

$$Q_c = -708.1 \text{ VAR}$$

$$\frac{V_{rms}^2}{-X_c} = -708.1$$

$$-\omega C V_{rms}^2 = -708.1$$

$$C = \frac{708.1}{\omega V_{rms}^2} = \frac{708.1}{2\pi(60)(120)^2}$$

$$\boxed{C = 130.41 \mu F}$$