



Chapter2: Boolean Algebra and Logic Gates

Lecture5- Positive and Negative Logic

Engr. Arshad Nazir, Asst Prof
Dept of Electrical Engineering
SEECs

Objectives

- Study Positive and Negative Logic
- Integrated Circuits
- Digital Logic Families

Positive and Negative Logic

- Binary signals in a circuit can have one of two values.
 - One signal represents logic-1 and the other logic-0.
- A circuit input or output will hold either a high or low signal.
 - Choosing the high level, H , to represent logic-1 is called a positive logic system.
 - Choosing the low level, L , to represent logic-1 is called a negative logic system


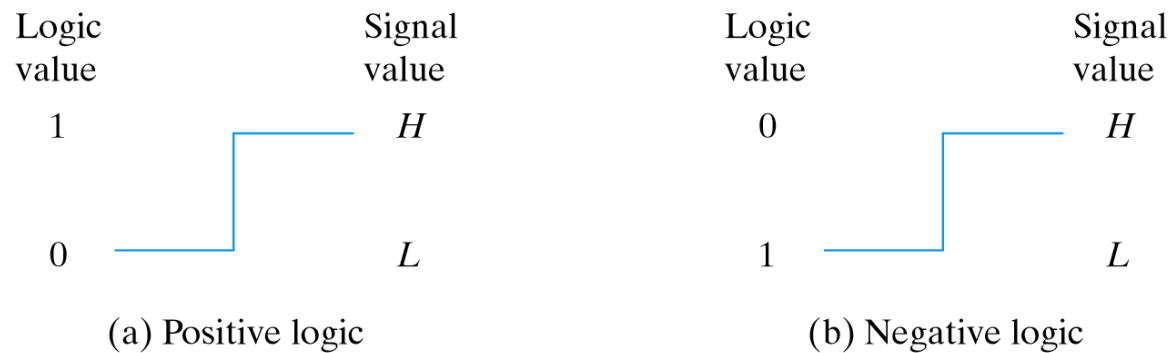


Fig. 2-9 signal assignment and logic polarity

Positive and Negative Logic gates

| x | y | F |
|-----|-----|-----|
| L | L | L |
| L | H | L |
| H | L | L |
| H | H | H |


(a) Truth table with H and L

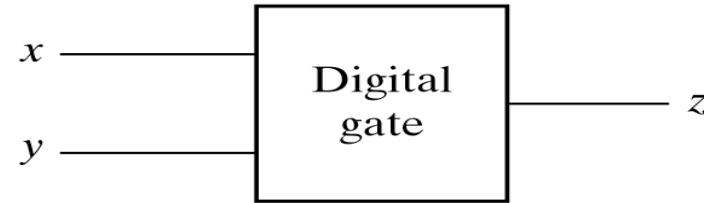

(b) Gate block diagram

| x | y | z |
|-----|-----|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

(c) Truth table for positive logic

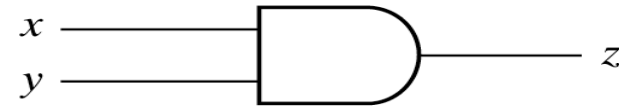

(d) Positive logic AND gate

| x | y | z |
|-----|-----|-----|
| 1 | 1 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 0 | 0 | 0 |

(e) Truth table for negative logic



(f) Negative logic OR gate

Fig. 2-10 Demonstration of positive and negative logic

Integrated Circuits

- An **integrated circuit (IC)** is a silicon semiconductor crystal, called a chip, containing the electronic components for constructing digital gates.
 - Gates are interconnected within the chip to form the required circuit
 - The IC is housed inside a ceramic or plastic container with connections welded to external pins
 - There can be 14 to several thousand pins on a chip
 - Each IC has a numeric designation printed on the surface for identification. The number can be looked up in catalogs (paper and electronic) that contain descriptions and information about the IC

Levels of Integration

- ICs are categorized by the number of gates that they contain in them:
 - **Small-scale integration (SSI)** devices contain several (usually **less than 10**) independent gates in a single package. Early 60's
 - **Medium-scale integration (MSI)** devices include **10 to 1000** gates in a single package, used to perform elementary digital operations. Late 60's
 - **Large-scale integration (LSI)** devices contain **thousands** of gates in a single package, used in processors, memory chips, and programmable logic devices. Mid 70's
 - **Very Large-scale integration (VLSI)** devices contain **hundreds of thousands** of gates in a single package, used in large memory arrays and complex microcomputer chips. 80's
 - **Ultra Large-scale integration (ULSI)** devices contain **millions** of gates in a single package. 90's and 00's
 - **Giga-scale integration (GSI)** devices contain **hundreds of millions** of gates in a single package.
 - **Tera-scale integration (TSI)** devices contain **millions of millions** of gates in a single package.

Digital Logic Families

- ICs are also classified by the specific circuit technology (digital logic family) that they belong to:
 - Transistor-transistor logic (TTL) is a standard.
 - Emitter-coupled logic (ECL) is used in high-speed operation.
 - Metal-oxide semiconductor (MOS) is used for high component density.
 - Complementary metal-oxide semiconductor (CMOS) is used in low power consumption.
 - Diode-Transistor Logic (DTL) being obsolete not used these days.
 - Resistor-Transistor Logic (RTL) not used these days.

Logic Family Characteristics

- Digital logic families are usually compared by the following characteristics:
 - **Fan-out** specifies the number of standard loads that the output of a gate can drive without impairing its normal operation or it specifies the amount of current that an output needs to drive many input pins on other gates.
 - **Fan-in** is the number of inputs available in a gate.
 - **Power dissipation** is the power consumed by the gate.
 - **Propagation delay** is the average delay time for the signal to propagate from input to output.
 - **Noise margin** is the maximum external noise voltage added to an input signal that does not cause an undesirable change in the circuit output.
 - **Reliability** is the long-term success factor of the IC.

Integrated Circuits Design

- Why is it better to have more gates on a single chip?
 - Easier to build systems
 - Less power consumption
 - Higher clock frequencies
- What are the drawbacks of large circuits?
 - Complex to design
 - Chips have design constraints
 - Need tools to help develop integrated circuits
- Need tools to help develop integrated circuits
 - Computer Aided Design (CAD) tools
 - Automate tedious steps of design process
 - Hardware description language (HDL) describe circuits

The End