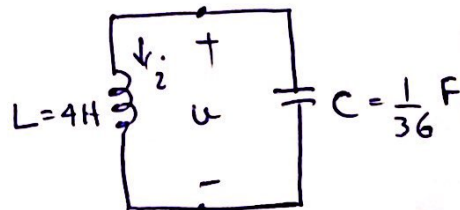


9.7 The Lossless LC Circuit ($\alpha < \omega_0$)

(PP 357 7th Ed HKD)

— When the value of the resistance in a parallel RLC circuit becomes infinite, or zero in a series RLC circuit, it results in a simple LC loop in which an oscillatory response can be maintained for ever.

— Consider



$$i(0) = -\frac{1}{6} \text{ A}$$

$$\text{and } u(0) = 0 \text{ V}$$

— Now $\alpha = \frac{1}{2RC}$ parallel — R infinite $\alpha \Rightarrow 0$

or $\alpha = \frac{R}{2L}$ Series — R zero $\alpha \Rightarrow 0$

— However, $\omega_0 = \frac{1}{\sqrt{LC}}$ for both (resonant frequency)

— So in lossless circuit $\alpha = 0$ (undamped response)

$$\text{and } \omega_0 = \frac{1}{\sqrt{4 \times \frac{1}{36}}} = \sqrt{9} \text{ (undamped natural frequency)}$$

— The ^{damped} natural resonant frequency
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{9 - 0} = 3 \text{ rad/s}$ could
(damped natural frequency)

— contd (357)

— In the absence of exponential damping;

$$v = (A \cos 3t + B \sin 3t) e^{-\alpha t} \quad \alpha = 1$$

$$\text{Since } v(0) = 0$$

$$0 = A \times 1 + B \times 0$$

$$A = 0$$

$$\text{So } v = B \sin 3t$$

$$\text{Now } \frac{dv}{dt} = 3B \cos 3t \Big|_{t=0} = 3B$$

$$\text{Also } \frac{dv}{dt} \Big|_{t=0} = -\frac{1}{C} \dot{i}(0^+) \quad \left(\begin{array}{l} \text{The -ve sign because } \dot{i}(0^+) \text{ enters} \\ \text{-ve terminal of } v \text{ of capacitor} \end{array} \right)$$

In our case due passive sign convention


$$\frac{dv}{dt} \Big|_{t=0} = -\frac{-1/6}{1/36} = 6 \quad \text{because } \dot{i}(0^+) = -1/6$$

$$\text{So } 3B = 6$$

$$B = 2$$

Hence

$$v(t) = 2 \sin 3t \text{ V}$$

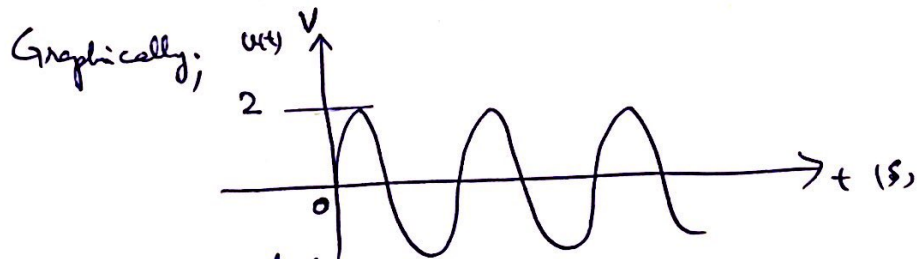

$$\text{If we are interested in current } i \text{ it is } = -C \frac{dv}{dt} = -\frac{1}{6} \cos 3t \text{ A}$$

— contd

— contd (357)

Alternately we can start with

$$i(t) = A \cos 3t + B \sin 3t$$

$$i(0) = -\frac{1}{6}$$

$$-\frac{1}{6} = A + B \times 0$$

$$\text{So } A = -\frac{1}{6} \quad \text{————— (1)}$$

And $\left. \frac{di}{dt} \right|_{t=0} = -3A \sin 3t + 3B \cos 3t$

$$\left. \frac{di}{dt} \right|_{t=0} = 3B$$

$$\text{Now } V_L = L \frac{di}{dt}$$

$$\frac{V_L(0^+)}{L} = \left. \frac{di}{dt} \right|_{t=0^+}$$

$$\left\{ \begin{array}{l} \text{because } V_L(0^+) = V_C(0^+) \\ \text{in parallel} \end{array} \right\}$$

$$\frac{0}{L} = \left. \frac{di}{dt} \right|_{t=0^+}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = 0$$

$$\text{So } 3B = 0$$

$$B = 0$$

$$\text{Hence } i(t) = -\frac{1}{6} \cos 3t \quad A$$

as before.