

9.3 Critical Damping $\alpha = \omega_0$

(PP 334 8th Ed HND)

When $\alpha = \omega_0$, the roots are real and equal.


Consider $L = 7\text{H}$

$$C = \frac{1}{42}\text{F}$$

$$\text{and } R = \frac{7\sqrt{6}}{2} \quad (\text{Earlier } R = 6\Omega)$$

$$v(0) = 0$$

$$\text{and } i(0) = 10\text{A}$$

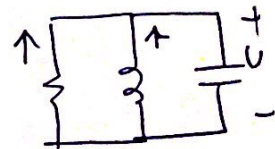

$$\text{Now } \alpha = \frac{1}{2RC} = \sqrt{6}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{6}$$

$$\text{Hence } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_{1,2} = -\sqrt{6} s^{-1}$$

Returning to original differential

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\text{or } \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\left(\text{Now } \frac{1}{RC} = 2\alpha \right)$$

$$\text{and } \alpha^2 = \omega_0^2 = \frac{1}{LC}$$

$$\text{Thus } \frac{d^2 v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v = 0$$

This v has a standard solution:-

$$v = e^{-\alpha t} (A_1 t + A_2)$$

_____ contd

— contd (335)

So we get

$$u(t) = A_1 t e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t}$$

Given $u(0) = 0$

$$0 = A_1 \times 0 \times 1 + A_2$$

So $A_2 = 0$

— Hence

$$u(t) = A_1 t e^{-\sqrt{6}t} + 0$$

or $u(t) = A_1 t e^{-\sqrt{6}t}$

— For 2nd constant

$$\frac{du}{dt} = A_1 t e^{-\sqrt{6}t} (-\sqrt{6}) + A_1 e^{-\sqrt{6}t}$$

or $\frac{du}{dt} = A_1 e^{-\sqrt{6}t} - \sqrt{6} A_1 t e^{-\sqrt{6}t}$

— but $\left. \frac{du}{dt} \right|_{t=0} = \frac{i_c(0)}{C} = \frac{i_R(0)}{C} + \frac{i(0)}{C} = \frac{10}{\frac{1}{42}} = 420$

Thus $A_1 = 420$

— Hence

$$u(t) = 420 t e^{-2.45t}, \quad V$$



* Critical Damping: Proof

Proceeding from: $\frac{d^2u}{dt^2} + 2\alpha \frac{du}{dt} + \alpha^2 u = 0$

or $\frac{d}{dt} \left(\frac{du}{dt} + \alpha u \right) + \alpha \left(\frac{du}{dt} + \alpha u \right) = 0$

Let $\frac{du}{dt} + \alpha u = f$ ——— (A)

— Then $\frac{df}{dt} + \alpha f = 0$

— This is a 1st order $=n$ so

$f = A_1 e^{-\alpha t}$ is the solution

— So we get from (A)

$$\frac{du}{dt} + \alpha u = A_1 e^{-\alpha t}$$

— or $e^{\alpha t} \frac{du}{dt} + e^{\alpha t} (\alpha u) = A_1$

— This can be written as

$$\frac{d}{dt} (e^{\alpha t} u) = A_1$$

— Integrating both sides

$$e^{\alpha t} u = A_1 t + A_2$$

or $u = e^{-\alpha t} (A_1 t + A_2), \quad u$

Graphical Representation of the Critically Damped Response

(PP 336 8th Ed H2D)

With the values of R , L and C such that $\alpha = \omega_0$, we have arrived at the end result :-

$$v(t) = 420t e^{-2.45t} \text{ V}$$

— This result confirms that the specified initial value is zero as $v(0) = 0$; $i_L(0) = 10 \text{ A}$.

— It is not obvious that the response also approaches zero as t becomes infinitely large; which it should for the given source-free circuit.

— However, using L'Hospital's rule

$$\lim_{t \rightarrow \infty} v(t) = 420 \lim_{t \rightarrow \infty} \frac{t}{e^{2.45t}}$$

$$= 420 \lim_{t \rightarrow \infty} \frac{1}{2.45 e^{2.45t}} = 0$$

— To determine the time t_m at which maximum value occurs, we differentiate wrt time and put the result equal to zero.

$$\frac{dv}{dt} = 420 \left\{ t_m \times -2.45 e^{-2.45t_m} + e^{-2.45t_m} \times 1 \right\} = 0$$

$$-2.45t_m = -1$$

$$t_m = 0.408 \text{ s}$$

(overdamped had 0.358)

— Putting this value in $v(t)$, we get

$$v_m = 63.1 \text{ V}$$

(overdamped had 49V)

_____ contd

(Optional)

— Contd (334)



— The settling time at which 1% of max value is reached is $\frac{V_m}{100} = \frac{63.1}{100} = 420 t_s e^{-2.45 t_s}$

— By trial and error;

$$t_s = 3.12 \text{ s}$$

(5.15 s overdamped)

Graphically:

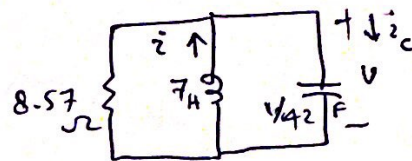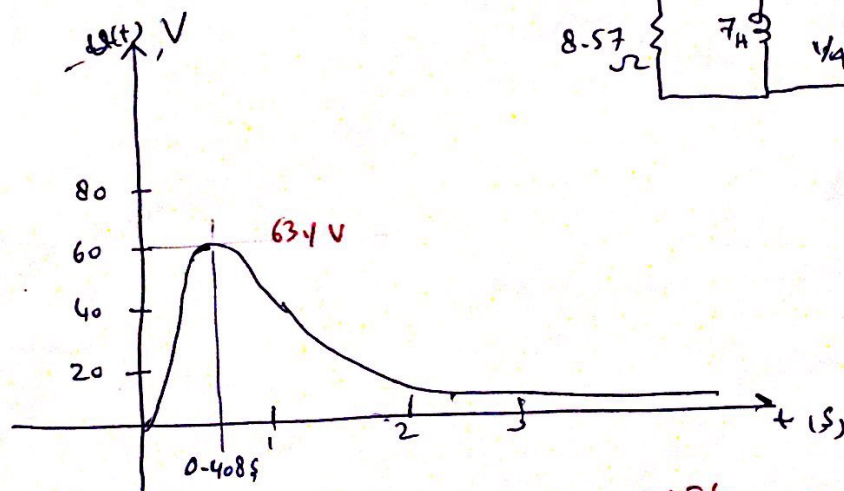

(Plot of $u(t) = 420 t e^{-2.45 t} \text{ V}$)
