



Department of Electrical Engineering and
Computer Science

Faculty Member: Dr. Rehan Ahmed

Dated: 15/02/2023

Semester: 6th

Section: BEE 12C

EE-421: Digital System Design

Lab 2: Introduction to Altera DE-10 Board

Learn to connect simple I/O devices to an FPGA chip

Group Members

Name	Reg. No	PLO4-CLO3		PLO5 - CLO4	PLO8 - CLO5	PLO9 - CLO6
		Viva / Quiz / Lab Performance	Analysis of data in Lab Report	Modern Tool Usage	Ethics and Safety	Individual and Teamwork
		5 Marks	5 Marks	5 Marks	5 Marks	5 Marks
Danial Ahmad	331388					
Muhammad Umer	345834					
Tariq Umar	334943					



1 Table of Contents

2	Switches, Lights, and Multiplexers.....	3
2.1	Objectives.....	3
2.2	Introduction	3
2.3	Software.....	3
3	Lab Procedure	4
3.1	Part I	4
3.2	Part II.....	6
3.3	Part III.....	10
4	Conclusion.....	14



2 Switches, Lights, and Multiplexers

2.1 Objectives

The purpose of this exercise is to learn how to connect simple input and output devices to an FPGA chip and implement a circuit that uses these devices. We will use the switches on the DE-series boards as inputs to the circuit. We will use light emitting diodes (LEDs) and 7-segment displays as output devices.

2.2 Introduction

The field of digital design has been revolutionized by the advent of Field-Programmable Gate Arrays (FPGAs), which allow designers to create complex digital circuits using programmable logic. In this lab exercise, we will be using Intel's Quartus Prime software to design and implement a circuit that utilizes switches, lights, and multiplexers. The objective of this exercise is to gain hands-on experience in designing and implementing digital circuits using FPGAs, and to understand how switches, lights, and multiplexers can be used in a digital circuit. By the end of this lab, we will have a deeper understanding of the basic components of digital circuits and how they can be used to create complex systems. Additionally, we will have gained valuable experience in using Intel's Quartus Prime software, which is a leading platform for digital design.

2.3 Software

Quartus Prime is a comprehensive design software developed by Intel Corporation for designing digital circuits using Field-Programmable Gate Arrays (FPGAs). It is a leading software platform in the field of digital design, offering a range of advanced tools and features that enable users to easily create, debug, and verify complex digital circuits. With Quartus Prime, users can benefit from a streamlined design flow that facilitates the creation of digital circuits from concept to implementation. It provides an intuitive graphical user interface that allows users to easily design, test, and debug their circuits. Additionally, Quartus Prime supports a variety of popular programming languages, making it a versatile platform for digital designers of all levels.



3 Lab Procedure

3.1 Part I

The objective of this part is to display a character on a 7-segment display. The specific character displayed depends on a two-bit input. Figure 1 shows a 7-segment decoder module that has the two-bit input c_1c_0 . This decoder produces seven outputs that are used to display a character on a 7-segment display. Table 1 lists the characters that should be displayed for each valuation of c_1c_0 for your DE-series board. Note that in some cases the ‘blank’ character is selected for code 11.

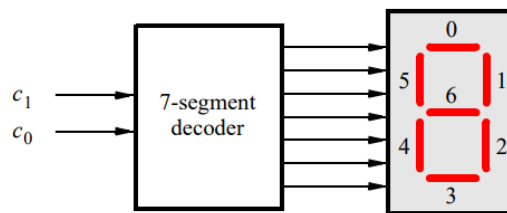


Figure 1: A 7-segment decoder.

c_1c_0	DE10-Lite	DE0-CV	DE1-SoC	DE2-115
00	d	d	d	d
01	E	E	E	E
10	1	0	1	2
11	0			

Table 1: Character codes for the DE-series boards.

1. Create a new Quartus project for your circuit.
2. Create a Verilog module for the 7-segment decoder. Connect the c_1c_0 inputs to switches SW1–0 and connect the outputs of the decoder to the HEX0 display on your DE-series board. The segments in this display are called HEX00, HEX01, . . . , HEX06, corresponding to Figure 1. You should declare the 7-bit port 1 **output [6:0] HEX0**; in your Verilog code so that the names of these outputs match the corresponding names in your board’s user manual and pin assignment file.
3. After making the required pin assignments, compile the project.
4. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit by toggling the SW1–0 switches and observing the 7-segment display.


```
module standard (
    input  [9:0] SW,
    output [6:0] HEX0
);

    task_1 dut (
        .c1 (SW[1]),
        .c0 (SW[0]),
        .hex(HEX0)
    );


endmodule
```




```
module task_1 (  
    input c1,  
    c0,  
    output [6:0] hex  
);  
  
    assign hex[0] = (~c1 & ~c0) | (c1 & ~c0);  
    assign hex[1] = (~c1 & c0);  
    assign hex[2] = (~c1 & c0);  
    assign hex[3] = (c1 & ~c0);  
    assign hex[4] = (c1 & ~c0);  
    assign hex[5] = (~c1 & ~c0) | (c1 & ~c0);  
    assign hex[6] = (c1 & ~c0) | (c1 & c0);  
  
endmodule
```

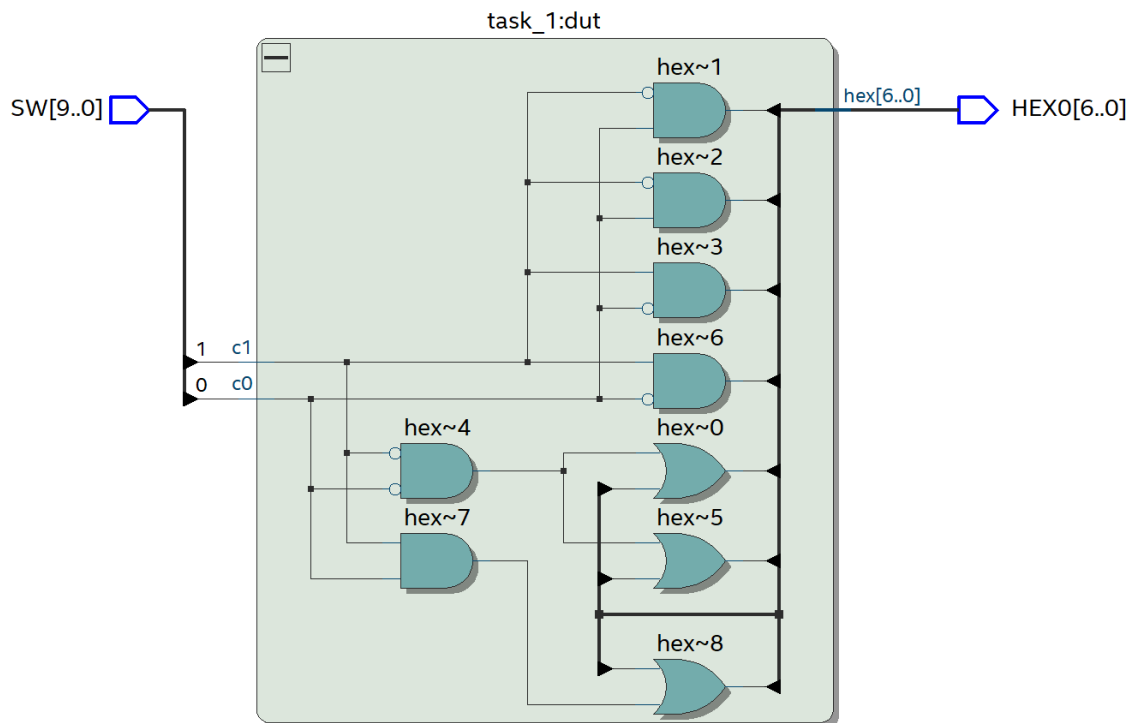

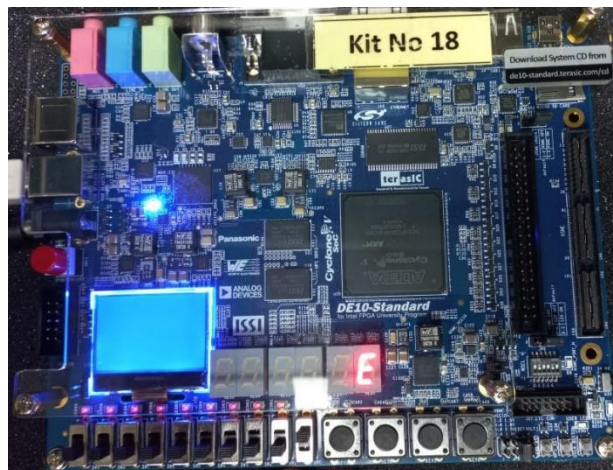Following are sample hardware demonstrations of Part I on the DE-10 board:



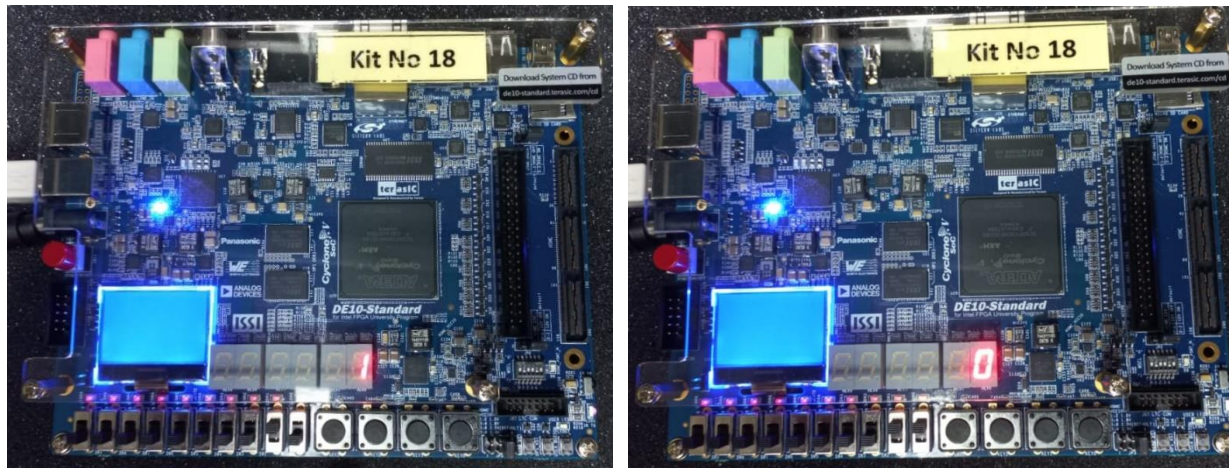

3.2 Part II

Consider the circuit shown in Figure 2. It uses a two-bit wide 4-to-1 multiplexer to enable the selection of four characters that are displayed on a 7-segment display. Using the 7-segment decoder from Part IV this circuit can display the characters d, E, 0, 1, 2, or 'blank' depending on your DE-series board. The character codes are set according to Table 1 by using the switches SW7–0, and a specific character is selected for display by setting the switches SW9–8.

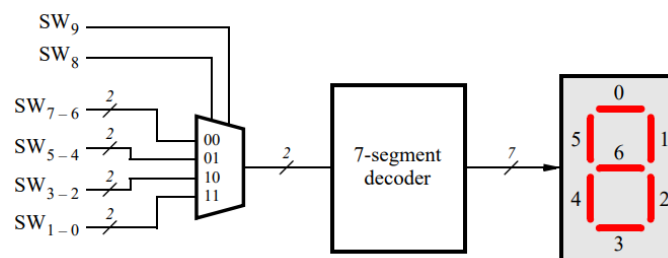


Figure 2: A circuit that can select and display one of four characters.

SW ₉₋₈	Characters
00	d E 1 0
01	E 1 0 d
10	1 0 d E
11	0 d E 1

Table 2: Rotating the word dE10 on four displays.

1. Create a new Quartus project for your circuit.
2. Include your Verilog module in the Quartus project. Connect the switches SW9–8 to the select inputs of each of the four instances of the two-bit wide 4-to-1 multiplexers. Also connect SW7–0 to each instance of the multiplexers as required to produce the patterns of characters shown in Table 1. Connect the SW switches to the red lights LEDR and connect the outputs of the four multiplexers to the 7-segment displays HEX3, HEX2, HEX1, and HEX0.
3. Include the required pin assignments for your DE-series board for all switches, LEDs, and 7-segment displays. Compile the project.



4. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit by setting the proper character codes on the switches SW7–0 and then toggling SW9–8 to observe the rotation of the characters.

```
module part5 (SW, LEDR, HEX0);  
    input [9:0] SW;                // slide switches  
    output [9:0] LEDR;             // red lights  
    output [0:6] HEX0;             // 7-seg display  
  
    wire [1:0] M0;  
  
    mux_2bit_4to1 U0 (SW[9:8], SW[7:6], SW[5:4], SW[3:2], SW[1:0], M0);  
    char_7seg H0 (M0, HEX0);  
  
    // implements a 2-bit wide 4-to-1 multiplexer  
    module mux_2bit_3to1 (S, U, V, W, X, M);  
        input [1:0] S, U, V, W, X;  
        output [1:0] M;  
        ... code not shown  
    endmodule  
  
    // implements a 7-segment decoder for d, E, 1 and 0  
    module char_7seg (C, Display);  
        input [1:0] C;             // input code  
        output [0:6] Display;      // output 7-seg code  
        ... code not shown  
    endmodule  
  
endmodule
```

Figure 3: Verilog code for the circuit in Figure 2.

```
module standard (  
    input  [9:0] SW,  
    output [6:0] HEX0,  
    output [6:0] HEX1,  
    output [6:0] HEX2,  
    output [6:0] HEX3  
);  
  
    wire [27:0] HEX;  
  
    task_2 dut (  
        .switch(SW),  
        .hex(HEX)  
    );  
  
    assign HEX0 = HEX[6:0], HEX1 = HEX[13:7], HEX2 = HEX[20:14], HEX3 = HEX[27:21];  
endmodule  
  
module task_2 (  
    input  [ 9:0] switch,  
    output [27:0] hex  
);
```



```
);

wire [1:0] s1, s2, s3, s4;

assign s1 = switch[9:8], s2 = switch[9:8] + 1, s3 = switch[9:8] + 2, s4 = switch[9:8] + 3;

wire [7:0] s;
wire [7:0] m;

wire [1:0] u = switch[1:0], v = switch[3:2], w = switch[5:4], x = switch[7:6];

assign s = {s1, s2, s3, s4};

genvar i;
generate
    for (i = 1; i < 8; i = i + 2) begin : mux
        mux_2b_4to1 muxstage (
            .s(s[i:i-1]),
            .u(u),
            .v(v),
            .w(w),
            .x(x),
            .m(m[i:i-1])
        );
    end
endgenerate

generate
    for (i = 1; i < 8; i = i + 2) begin : seg_decoder
        task_1 decoderstage (
            .c1 (m[i]),
            .c0 (m[i-1]),
            .hex(hex[7*((i+1)/2)-1:7*((i-1)/2)])
        );
    end
endgenerate

endmodule


module mux_2b_4to1 (
    input [1:0] s,
    input [1:0] u,
    input [1:0] v,
    input [1:0] w,
    input [1:0] x,

    output reg [1:0] m
);

always @(*) begin
    case (s)
        2'b00: begin
            m[0] = u[0];
            m[1] = u[1];
        end
        2'b01: begin
            m[0] = v[0];
            m[1] = v[1];
        end
        2'b10: begin
```




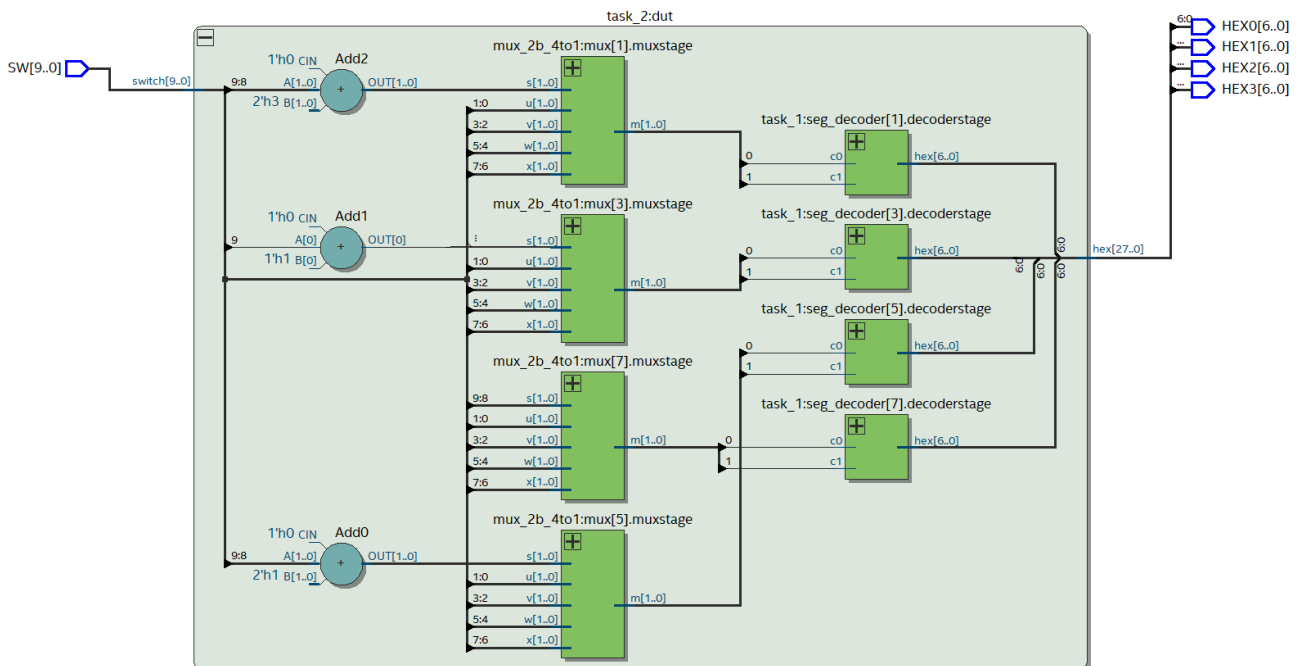
```
m[0] = w[0];  
m[1] = w[1];  
end  
2'b11: begin  
    m[0] = x[0];  
    m[1] = x[1];  
end  
endcase  
end  
endmodule
```







To test the functional relationship between the switches and the 7-segment displays, we implement the following testbench:
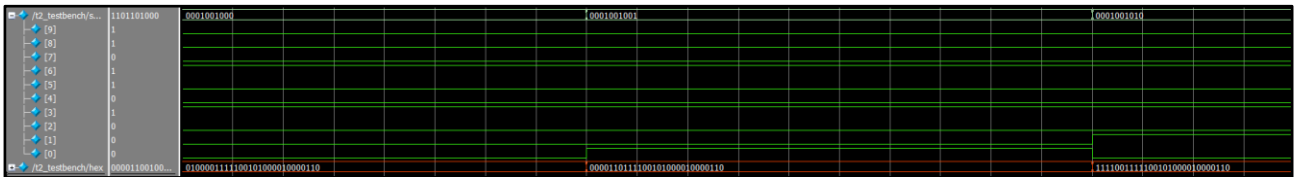
```
module t2_testbench ();  
  
    reg [ 9:0 ] switch;  
    wire [27:0] hex;  
  
    task_2 dut (  
        .switch(switch),  
        .hex(hex)  
    );  
    integer i;  
  
    initial begin  
        for (i = 0; i < 2 ** 10; i = i + 1) begin  
            {switch} = i;  
            #10;  
        end  
    end  
endmodule
```



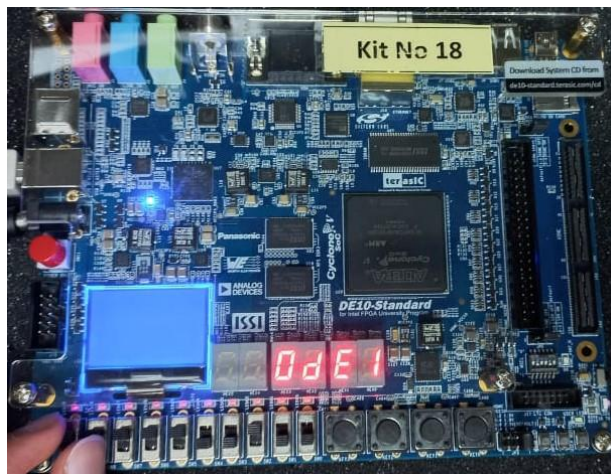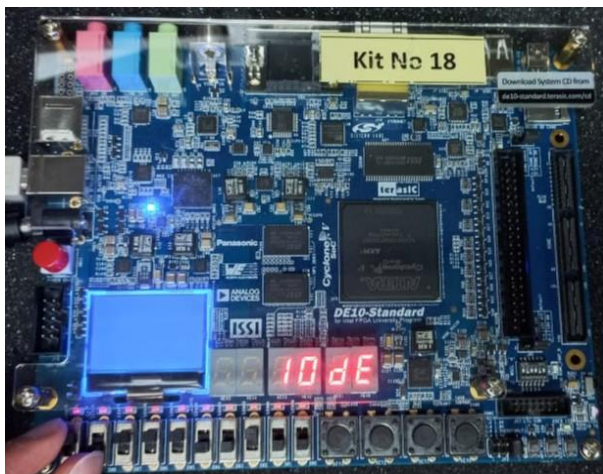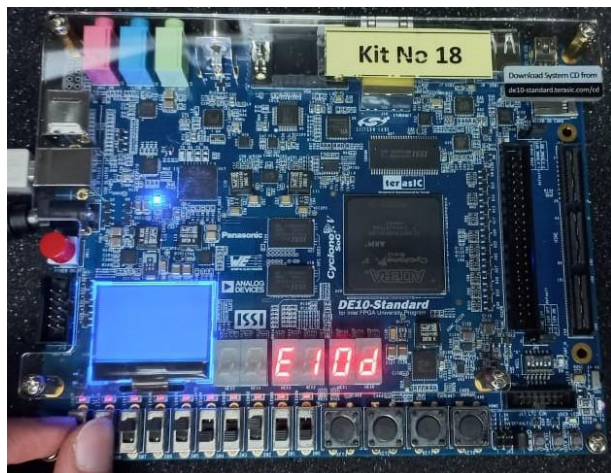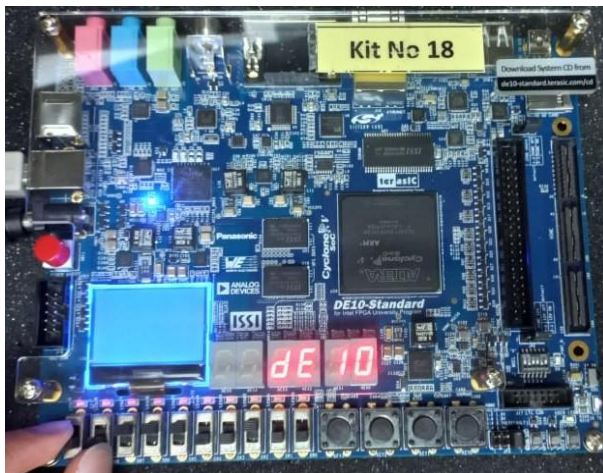Following are sample hardware demonstrations of Part II on the DE-10 board:



3.3 Part III

Extend your design from Part V so that it uses all 7-segment displays on your DE-series board. Your circuit needs to display a three- or four-letter word, corresponding to Table 2, using 'blank' characters for unused displays. Implement rotation of this word from right-to-left as indicated in Table 3 and Table 4. To do this, you will need to connect 6-to-1 multiplexers to each of six 7-segment display decoders for the DE10-Lite, DE0-CV and DE1-SoC. Note that for the DE10-Lite you will need to use 3-bit codes for your characters, because five characters are needed when including the 'blank' character (your 7-segment decoder will have to use 3-bit codes, and you will need to use 3-bit wide 6-to-1 multiplexers).



SW ₉₋₇	Character pattern
000	d E 1 0
001	d E 1 0
010	d E 1 0
011	E 1 0 d
100	1 0 d E
101	0 d E 1

Table 3: Rotating the word dE10 on six displays.

SW ₉₋₇	Character pattern
000	d E 2
001	d E 2
010	d E 2
011	d E 2
100	d E 2
101	d E 2
110	E 2 d
111	2 d E

Table 4: Rotating the word dE2 on eight displays.

1. Create a new Quartus project for your circuit.
2. Include your Verilog module in the Quartus project. Connect the switches SW9–7 to the select inputs of each instance of the multiplexers in your circuit. Connect the outputs of your multiplexers to the 7-segment displays HEX5, . . . , HEX0 of the DE10- Lite, DE0-CV and DE1-SoC or HEX7, . . . , HEX0 for the DE2-115.
3. Include the required pin assignments for your DE-series board for all switches, LEDs, and 7-segment displays. Compile the project.
4. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit by toggling SW9–7 to observe the rotation of the characters.

```

module standard (
    input  [9:0] SW,
    output [6:0] HEX0,
    output [6:0] HEX1,
    output [6:0] HEX2,
    output [6:0] HEX3,
    output [6:0] HEX4,
    output [6:0] HEX5
);

wire [41:0] HEX;

task_3 dut (
    .switch(SW),
    .hex(HEX)
);

assign HEX0 = HEX[6:0],
       HEX1 = HEX[13:7],
       HEX2 = HEX[20:14],
       HEX3 = HEX[27:21],
       HEX4 = HEX[34:28],
       HEX5 = HEX[41:35];

endmodule

module task_3 (
    input  [ 9:0] switch,
    output [41:0] hex
);

wire [17:0] m;
wire [17:0] s;
wire [2:0] s1, s2, s3, s4, s5, s6;

```



```
assign s1 = switch[9:7] + 5,
       s2 = switch[9:7] + 4,
       s3 = switch[9:7],
       s4 = switch[9:7] + 1,
       s5 = switch[9:7] + 2,
       s6 = switch[9:7] + 3;

wire [2:0] u = 3'b011, v = 3'b010, w = 3'b001, x = 3'b000, y = 3'b111, z = 3'b111;

assign s = {s1, s2, s3, s4, s5, s6};

genvar i;
generate
    for (i = 2; i < 18; i = i + 3) begin : mux
        mux_3b_6to1 muxstage (
            .s(s[i:i-2]),
            .u(u), .v(v),
            .w(w), .x(x),
            .y(y), .z(z),
            .m(m[i:i-2])
        );
    end
endgenerate

generate
    for (i = 2; i < 18; i = i + 3) begin : seg_decoder
        t3_decoder decoderstage (
            .c2 (m[i]),
            .c1 (m[i-1]),
            .c0 (m[i-2]),
            .hex(hex[7*((i+1)/3)-1:7*((i-1)/3)])
        );
    end
endgenerate

endmodule

module mux_3b_6to1 (
    input [2:0] s,
    input [2:0] u,
    input [2:0] v,
    input [2:0] w,
    input [2:0] x,
    input [2:0] y,
    input [2:0] z,

    output reg [2:0] m
);


always @(*) begin
    case (s)
        3'b000: m = u;
        3'b001: m = v;
        3'b010: m = w;
        3'b011: m = x;
        3'b100: m = y;
        3'b101: m = z;
        default: m = 3'b111;
    endcase
end
```



```
endmodule

module t3_decoder (
    input c2,
    c1,
    c0,
    output reg [6:0] hex
);
    wire [2:0] c = {c2, c1, c0};

    always @(*) begin
        if (c == 3'b111) hex = 7'b1111111;
        else hex[0] = (~c1 & ~c0) | (c1 & ~c0);
        hex[1] = (~c1 & c0);
        hex[2] = (~c1 & c0);
        hex[3] = (c1 & ~c0);
        hex[4] = (c1 & ~c0);
        hex[5] = (~c1 & ~c0) | (c1 & ~c0);
        hex[6] = (c1 & ~c0) | (c1 & c0);
    end
endmodule
```

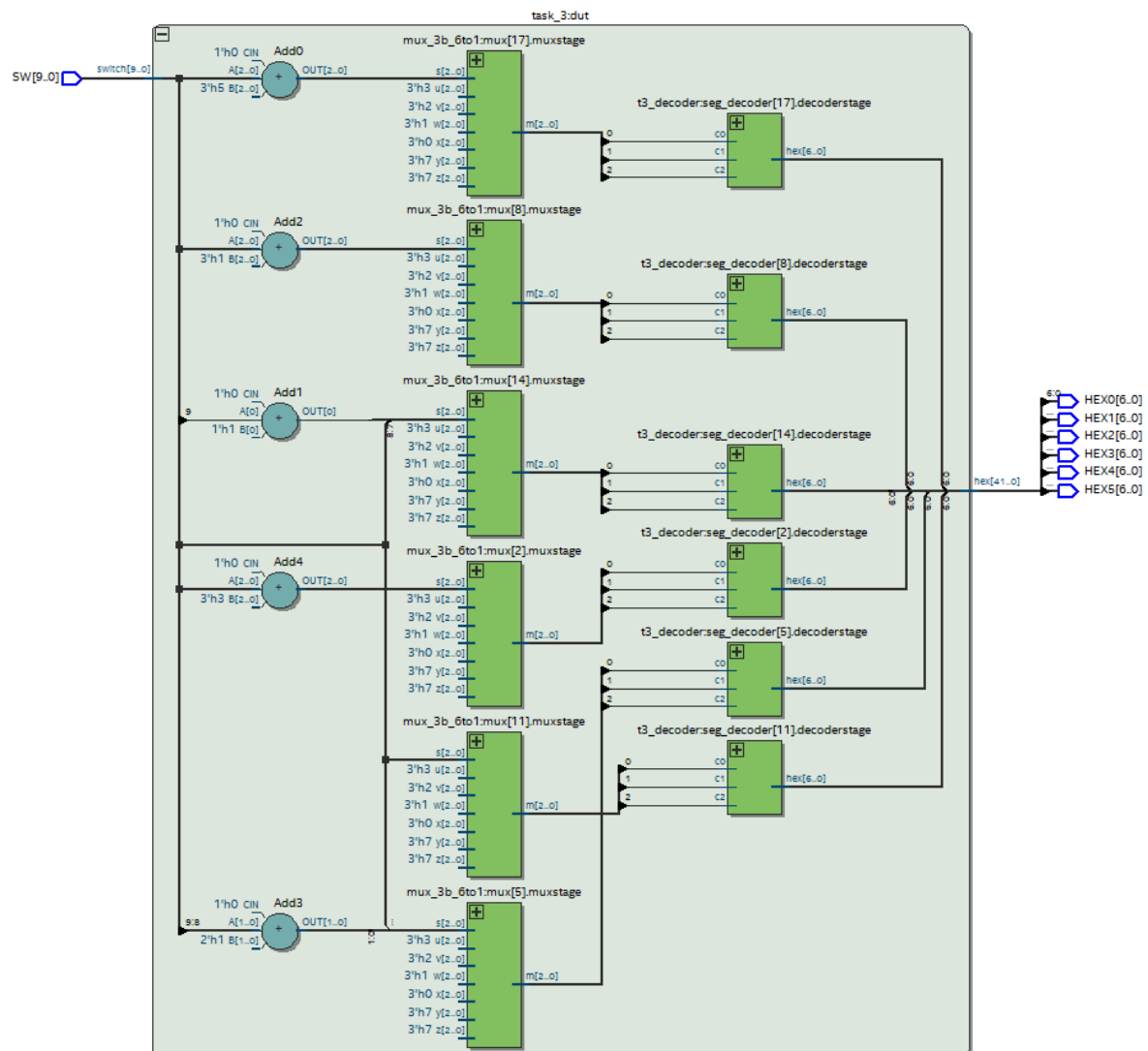




To test the functional relationship between the switches and the 7-segment displays, we implement the following testbench:

```
module t3_testbench ();

    reg [ 9:0] switch;
    wire [41:0] hex;

    task_3 dut (
        .switch(switch),
        .hex(hex)
    );
    integer i;

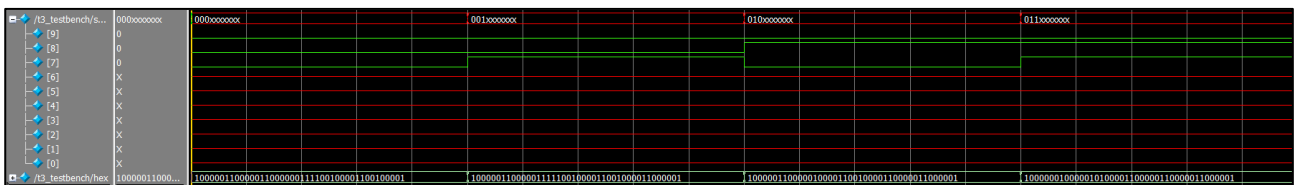    initial begin
        for (i = 0; i < 2 ** 3; i = i + 1) begin
            {switch[9:7]} = i;
            #10;
        end
    end
endmodule
```



4 Conclusion

In conclusion, this lab exercise provided an opportunity to gain hands-on experience in designing and implementing digital circuits using Field-Programmable Gate Arrays (FPGAs) and Intel's Quartus Prime software. Through the integration of switches, lights, and multiplexers, we were able to understand how these basic components can be used to create complex digital circuits. The exercise also allowed us to explore the design flow of Quartus Prime, from creating the circuit design to programming the FPGA.