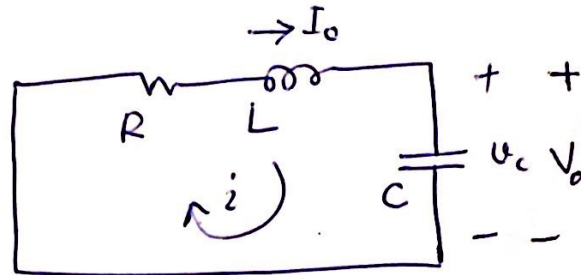


9.5 The Source-Free Series RLC Circuit

(PP346 8th Ed HAD)

The Series RLC circuit is :-



— The fundamental integro-differential equation is:-

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{t_0}^t i dt + V_c(t_0) = 0$$

— Differentiating wrt time:-

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0$$

— Rearranging:

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

(Recall for parallel RLC circuit

$$C \frac{d^2v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0)$$

— The overdamped response is:-

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\alpha > \omega_0)$$

————— contd

— contd (346)

$$\text{where } s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\text{and } \alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

— The form of the critically damped response is:

$$i(t) = e^{-\alpha t} (A_1 t + A_2) \quad (\alpha = \omega_0)$$

— And the underdamped response may be written

$$\text{as: } i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \quad (\alpha < \omega_0)$$

$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$\omega_d = \underline{\text{damped}}$ natural frequency.

$\omega_0 = \text{resonant frequency}$
also called undamped natural frequency.