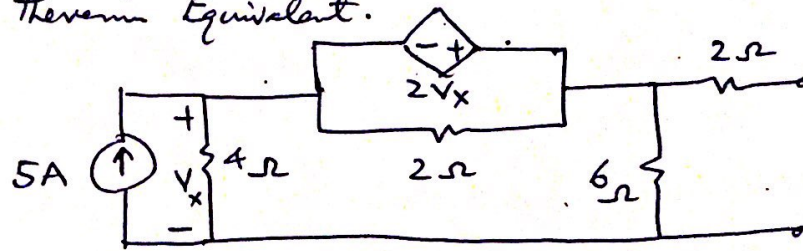
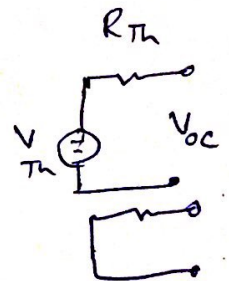
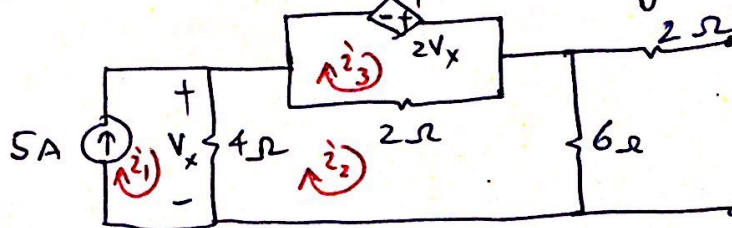


Example 4.9 Thevenin Equivalent(PP 142 5th Ed Sadiku)

Find Thevenin Equivalent.

Solution: We determine V_{Th} by mesh analysis— By inspection $i_1 = 5 \text{ A}$ — KVL mesh 2 $4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$ putting $i_1 = 5$ and simplifying

$$4(i_2 - 5) + 2(i_2 - i_3) + 6i_2 = 0$$

becomes

$$12i_2 - 2i_3 = 20 \quad \text{--- (A)}$$

— Now KVL mesh 3

$$-2V_x + 2(i_3 - i_2) = 0$$

$$\text{By inspection } V_x = 4(i_1 - i_2)$$

$$\text{So we get } -8i_1 + 8i_2 + 2i_3 - 2i_2 = 0 \quad (i_1 = 5)$$

$$\text{becomes } 6i_2 + 2i_3 = 40 \quad \text{--- (B)}$$

— could

— contd (142)


Solving (A) and (B)

$$\dot{i}_2 = \frac{60}{18} \text{ A}$$

$$\text{and } V_{Th} = 6\dot{i}_2 = 6 \times \frac{60}{18} = 20 \text{ V}$$

— To determine R_{Th} , the independent current source is made zero and either a test voltage source or a test current source is applied across terminals where R_{Th} is to be determined.

— The circuit becomes

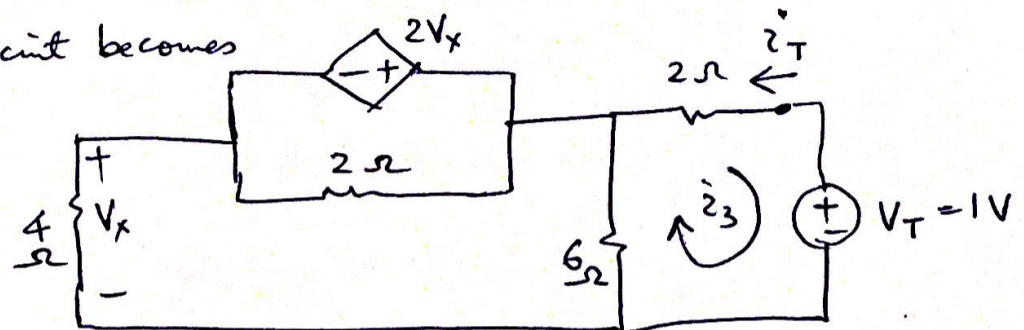


— Again using mesh analysis: (not done here)

$$\dot{i}_3 = -\frac{1}{6} \text{ A}$$


$$\text{So } \dot{i}_T = \frac{1}{6} \text{ A}$$

$$\text{and } R_{Th} = \frac{V_T}{\dot{i}_T} = 6 \Omega$$

— Thevenin equivalent circuit is:

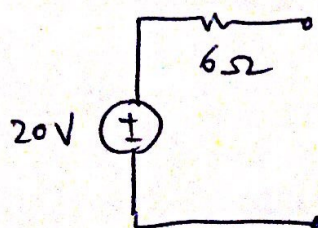

Contd (Using I_{sc} method)

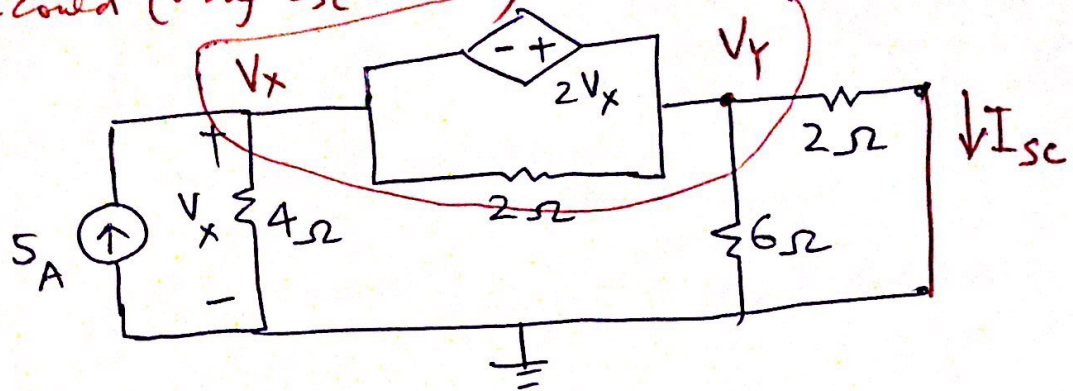

Using nodal analysis:

Applying KCL to supernode $V_x - V_y$:

$$\frac{V_x}{4} - 5 + \frac{V_y}{2} + \frac{V_y}{6} = 0 \quad \times 12$$

$$3V_x - 60 + 6V_y + 2V_y = 0$$

$$3V_x + 8V_y = 60 \quad \text{--- (A)}$$

Constraint equation

$$V_x - V_y = -2V_x$$

$$3V_x = V_y$$

$$V_x = \frac{V_y}{3} \quad \text{--- (B)}$$

So (A) becomes

$$3 \times \frac{V_y}{3} + 8V_y = 60$$

$$9V_y = 60 \quad \text{or} \quad V_y = \frac{60}{9}$$

$$\text{So } I_{sc} = \frac{60}{9} \times \frac{1}{2} = \frac{60}{18}$$

We already have $V_{oc} = 20$

$$\text{So } R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{20}{\frac{60}{18}} = 6$$

$$R_{Th} = 6 \Omega$$