



**Department of Electrical Engineering and
Computer Science**

Faculty Member: Dr. Rehan Ahmed

Dated: 3/05/2023

Semester: 6th

Section: BEE 12C

EE-421: Digital System Design

Lab 11: Adders, Subtractors, and Multipliers

Group Members

Name	Reg. No	PLO4-CLO3		PLO5 - CLO4	PLO8 - CLO5	PLO9 - CLO6
		Viva / Quiz / Lab Performance	Analysis of data in Lab Report	Modern Tool Usage	Ethics and Safety	Individual and Teamwork
		5 Marks	5 Marks	5 Marks	5 Marks	5 Marks
Danial Ahmad	331388					
Muhammad Umer	345834					
Tariq Umar	334943					



1 Table of Contents

2	Adders, Subtractors, and Multipliers	3
2.1	Objectives.....	3
2.2	Introduction	3
2.3	Software.....	3
3	Lab Procedure	4
3.1	Part I	4
3.2	Part II.....	8
3.3	Part III.....	10
4	Conclusion.....	12



2 Adders, Subtractors, and Multipliers

2.1 Objectives

The purpose of this exercise is to examine arithmetic circuits that add, subtract, and multiply numbers. Each circuit will be described in Verilog and implemented on an Intel FPGA DE10-Lite, DE0-CV, DE1-SoC, or DE2-115 board.

2.2 Introduction

The purpose of this exercise is to examine arithmetic circuits that add, subtract, and multiply numbers. Each circuit will be described in Verilog and implemented on an Intel FPGA DE10-Standard. Arithmetic circuits are the building blocks of many digital systems. They are used to perform basic operations on numbers, such as addition, subtraction, multiplication, and division. Arithmetic circuits can be implemented in a variety of ways, including using logic gates, flip-flops, and registers. In this exercise, we will implement three different arithmetic circuits on an Intel FPGA DE10-Standard. The first circuit will be an arithmetic adder, which is a simple and straightforward way to add two numbers. The second circuit will be the same as circuit one, albeit with the ability to subtract the numbers as well. The third circuit will be a multiplier, which is used to multiply two numbers together.

2.3 Software


Quartus Prime is a comprehensive design software developed by Intel Corporation for designing digital circuits using Field-Programmable Gate Arrays (FPGAs). It is a leading software platform in the field of digital design, offering a range of advanced tools and features that enable users to easily create, debug, and verify complex digital circuits. With Quartus Prime, users can benefit from a streamlined design flow that facilitates the creation of digital circuits from concept to implementation. It provides an intuitive graphical user interface that allows users to easily design, test, and debug their circuits. Additionally, Quartus Prime supports a variety of popular programming languages, making it a versatile platform for digital designers of all levels.



3 Lab Procedure

3.1 Part I

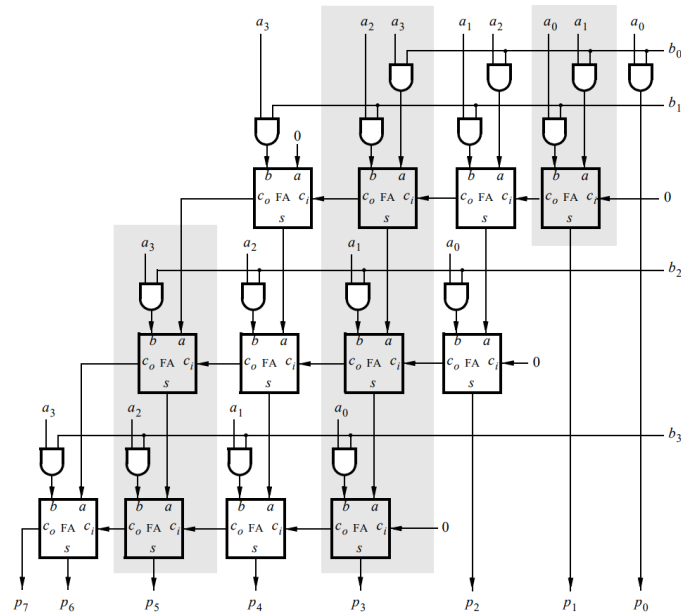1. Create a new Quartus project.
2. Generate the required Verilog file. Use switches SW7–4 to represent the number A and switches SW3–0 to represent B. The hexadecimal values of A and B are to be displayed on the 7-segment displays HEX2 and HEX0, respectively. The result $P = A \times B$ is to be displayed on HEX5 – 4.



```
module task_3 (  
    input  [3:0] KEY,  
    input  [9:0] SW,  
    output [9:0] LEDR,  
    output [6:0] HEX0,  
    output [6:0] HEX1,  
    output [6:0] HEX2,  
    output [6:0] HEX3,  
    output [6:0] HEX4,  
    output [6:0] HEX5  
);  
  
    wire reset = KEY[2];  
    wire clk = KEY[1];  
    wire s = ~KEY[0];  
    wire [3:0] DataA = SW[7:4];  
    wire [3:0] DataB = SW[3:0];  
    wire [7:0] P;  
    reg [7:0] DataP;  
    wire [7:0] A, sum;  
    wire z;  
    reg done;  
    reg [1:0] p_state, n_state;  
    wire [7:0] B;  
    reg enA, enB, enP, selP;
```



```
integer k;

parameter S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;

always @(*) begin
    case (p_state)
        S1:
            if (s == 0) n_state = S1;
            else n_state = S2;
        S2:
            if (z == 0) n_state = S2;
            else n_state = S3;
        S3:
            if (s == 1) n_state = S3;
            else n_state = S1;
        default: n_state = 2'bxx;
    endcase
end

always @(posedge clk, negedge reset) begin
    if (reset == 0) p_state <= n_state;
    else p_state <= n_state;
end

always @(*) begin
    enA = 0;
    enB = 0;
    enP = 0;
    done = 0;
    selP = 0;
    case (p_state)
        S1: enP = 1;
        S2: begin
            enA = 1;
            enB = 1;
            selP = 1;
            if (B[0]) enP = 1;
            else enP = 0;
        end
        S3: done = 1;
    endcase
end

shiftrne ShiftB (
    DataB,
    LB,
    enB,
    1'b0,
    clk,
    B
);
defparam ShiftB.n = 4;

shiftrlne ShiftA (
    {{4{1'b0}}, DataA},
    LA,
    enA,
```



```
        1'b0,
        clk,
        A
    );
    defparam ShiftA.n = 8;

    assign z    = (B == 0);
    assign sum = A + P;

    always @(selP, sum) for (k = 0; k < 2 * 4; k = k + 1)
        DataP[k] = selP ? sum[k] : 1'b0;
    regne RegP (
        DataP,
        clk,
        Resetn,
        enP,
        P
    );
    defparam RegP.n = 8;

    decoder digit0 (
        .in (DataA),
        .HEX(HEX0)
    );
    decoder digit2 (
        .in (DataB),
        .HEX(HEX2)
    );
    decoder digit4 (
        .in (DataP[7:4]),
        .HEX(HEX4)
    );
    decoder digit5 (
        .in (DataP[7:4]),
        .HEX(HEX5)
    );
endmodule

module shiftrne (
    input [n-1:0] in,
    output [n-1:0] out,
    input en,
    input rst,
    input clk,
    output reg [n-1:0] LB
);
    parameter n = 4;
    integer i;

    always @(posedge clk, negedge rst) begin
        if (rst == 0) LB <= 0;
        else if (en == 1) begin
            LB[0] <= in[0];
            for (i = 1; i < n; i = i + 1) LB[i] <= in[i-1];
        end
    end
end
```



```
    assign out = LB;

endmodule

module shiftLine (
    input [n-1:0] in,
    output [n-1:0] out,
    input en,
    input rst,
    input clk,
    output reg [n-1:0] LA
);
    parameter n = 8;
    integer i;

    always @(posedge clk, negedge rst) begin
        if (rst == 0) LA <= 0;
        else if (en == 1) begin
            LA[n-1] <= in[n-1];
            for (i = 0; i < n - 1; i = i + 1) LA[i] <= in[i+1];
        end
    end


    assign out = LA;

endmodule

module regne (
    input [n-1:0] in,
    input clk,
    input rst,
    input en,
    output reg [n-1:0] out
);
    parameter n = 8;

    always @(posedge clk, negedge rst) begin
        if (rst == 0) out <= 0;
        else if (en == 1) out <= in;
    end

endmodule
```

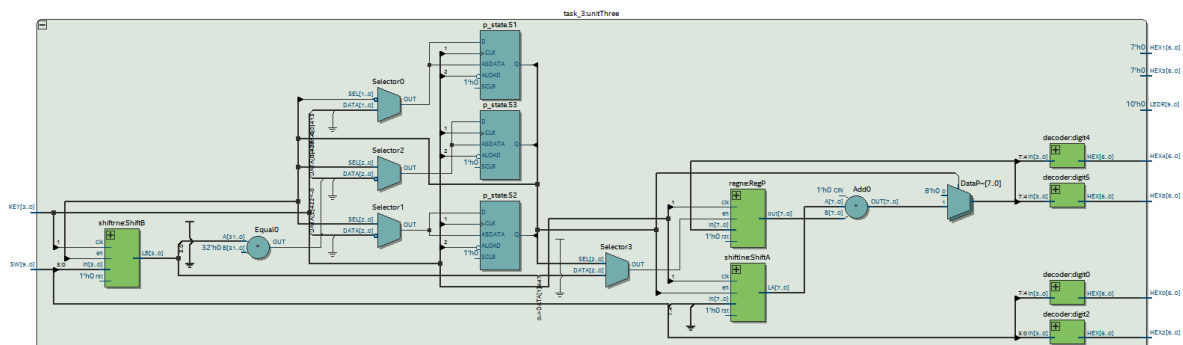



3.2 Part II

1. Create a new Quartus project and write the required Verilog file.
2. Use switches SW7–0 to provide the data inputs to the circuit. Use SW9 as the enable signal EA for register A, and use SW8 as the enable for register B. When SW9 = 1 display the contents of register A on the red lights LEDR and display the contents of register B on these lights when SW8 = 1. Use KEY0 as a synchronous reset input and use KEY1 as a manual clock signal. Show the product $P = A \times B$ as a hexadecimal number on the 7-segment displays HEX3-0.
3. Make the necessary pin assignments needed to implement the circuit on your DE-series board and compile the circuit.
4. Test the functionality of your design by inputting various data values and observing the generated products.

```
module task_2 (  
    input  [3:0] KEY,  
    input  [9:0] SW,  
    output [9:0] LEDR,  
    output [6:0] HEX0,  
    output [6:0] HEX1,  
    output [6:0] HEX2,  
    output [6:0] HEX3  
);  
  
    wire clk = KEY[1];  
    wire rst = KEY[0];  
    wire enA = SW[9];  
    wire enB = SW[8];  
    reg [7:0] A;  
    reg [7:0] B;  
    reg [15:0] P;  
    reg [15:0] P_reg;  
    wire [7:0] shifted_A[0:7];  
    reg [15:0] p_prod[0:7];  
    integer i;  
  
    // Register inputs  
    always @(posedge clk, negedge rst) begin  
        if (~rst) begin  
            A <= 8'd0;  
        end else if (enA) begin  
            A <= SW[7:0];  
        end  
    end  
    always @(posedge clk, negedge rst) begin  
        if (~rst) begin  
            B <= 8'd0;  
        end else if (enB) begin  
            B <= SW[7:0];  
        end  
    end  
  
    // Shift A left by row index  
    assign shifted_A[0] = A << 0;
```




```
assign shifted_A[1] = A << 1;
assign shifted_A[2] = A << 2;
assign shifted_A[3] = A << 3;
assign shifted_A[4] = A << 4;
assign shifted_A[5] = A << 5;
assign shifted_A[6] = A << 6;
assign shifted_A[7] = A << 7;


// Calculate partial product for each row
always @(posedge clk, negedge rst) begin
    if (~rst) begin
        for (i = 0; i < 8; i = i + 1) begin
            p_prod[i] <= 16'd0;
        end
    end else begin
        for (i = 0; i < 8; i = i + 1) begin
            p_prod[i] <= shifted_A[i] * B;
        end
    end
end

// Add partial products to get final product
always @(posedge clk, negedge rst) begin
    if (~rst) begin
        P <= 16'd0;
    end else begin
        P <= p_prod[0] + p_prod[1] + p_prod[2] + p_prod[3] +
            p_prod[4] + p_prod[5] + p_prod[6] + p_prod[7];
    end
end

// Register output
always @(posedge clk, negedge rst) begin
    if (~rst) begin
        P_reg <= 16'd0;
    end else begin
        P_reg <= P;
    end
end

decoder digit0 (.in (P[3:0]), .HEX(HEX0));
decoder digit1 (.in (P[7:4]), .HEX(HEX1));
decoder digit2 (.in (P[11:8]), .HEX(HEX2));
decoder digit3 (
    .in (P[15:12]),
    .HEX(HEX3)
);

endmodule
```

 



3.3 Part III

In this part you are to implement an 8 x 8 multiplier circuit by using the adder-tree approach. Inputs A and B, as well as the output P should be registered as in Part II.

```
module task_3 (
    input [3:0] KEY,
    input [9:0] SW,
    output [9:0] LEDR,
    output [6:0] HEX0,
    output [6:0] HEX1,
    output [6:0] HEX2,
    output [6:0] HEX3
);

    wire clk = KEY[1];
    wire rst = KEY[0];
    wire enA = SW[9];
    wire enB = SW[8];
    reg [7:0] A;
    reg [7:0] B;
    reg [15:0] P;
    reg [15:0] P_reg;

    // calculate partial products using for loops
    integer i, j;
    reg [7:0] p[8][8];
    always @(*) begin
        for (i = 0; i < 8; i = i + 1) begin
            for (j = 0; j < 8; j = j + 1) begin
                p[i][j] = A[i] & B[j] ? 1 << (i + j) : 0;
            end
        end
    end

    // sum partial products to get result
    always @(posedge clk, posedge rst) begin
        if (rst) begin
            A <= 0;
            B <= 0;
            P <= 0;
            P_reg <= 0;
        end else begin
            // update inputs based on enable signals
            if (enA) A <= SW[7:0];
            if (enB) B <= SW[7:0];

            // sum partial products
            for (i = 0; i < 15; i = i + 1) begin
                reg [7:0] s;
                s = 0;
                for (j = 0; j < 8; j = j + 1) begin
                    if (i - j >= 0 && i - j < 8) begin
                        s = s + p[j][i-j];
                    end
                end
            end
        end
    end
```




```

        P[i] = s[0];
        if (i < 15) begin
            P[i+1] = s[1:0];
        end
    end
    P_reg <= P; // store the result for display
end
end

decoder digit0 (
    .in (P[3:0]),
    .HEX(HEX0)
);
decoder digit1 (
    .in (P[7:4]),
    .HEX(HEX1)
);
decoder digit2 (
    .in (P[11:8]),
    .HEX(HEX2)
);
decoder digit3 (
    .in (P[15:12]),
    .HEX(HEX3)
);
endmodule

```

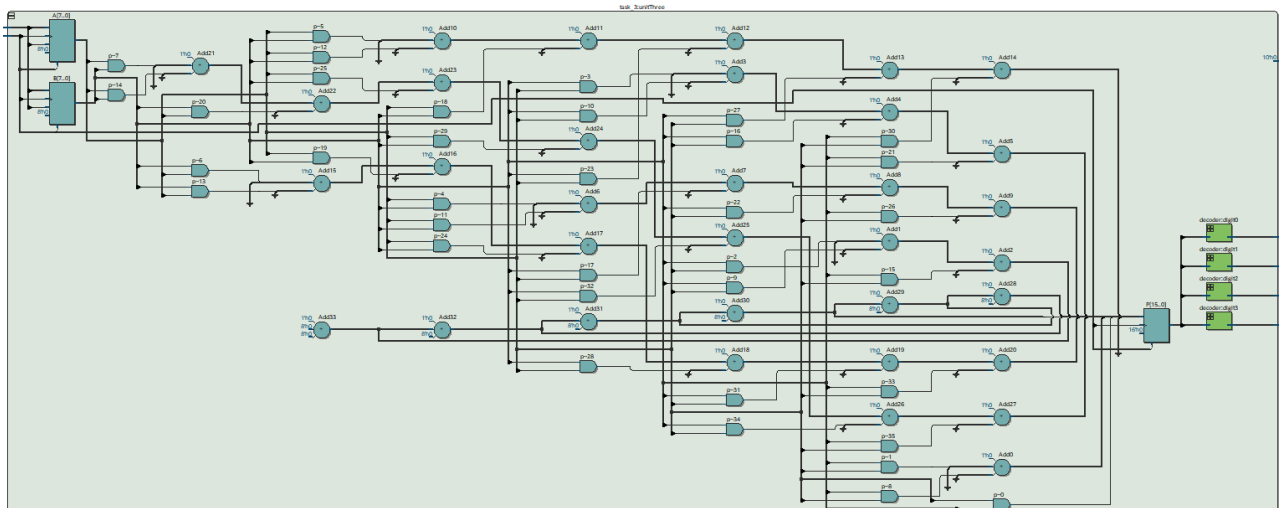



4 Conclusion

In this exercise, we have examined arithmetic circuits that add, subtract, and multiply numbers. We have described each circuit in Verilog and implemented it on an Intel FPGA DE10-Standard. We have also tested the circuits by using them to perform a variety of arithmetic operations. The results of this exercise have shown that arithmetic circuits can be implemented efficiently on an FPGA. We have also learned that there are a variety of different ways to implement arithmetic circuits, each with its own advantages and disadvantages. This exercise has provided us with a good understanding of the basic principles of arithmetic circuits.