

EE-421: Digital System Design


Synchronous vs Asynchronous Reset

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Asynchronous and Synchronous Reset


- **Reset** signals are used to **initialize** the hardware to a known state
 - Usually activated **at system start** (on power up)
- **Asynchronous Reset**
 - The reset signal is sampled **independent** of the clock
 - **Reset gets the highest priority**
 - Sensitive to **glitches**, may have **metastability** issues
 - Will be discussed later in the course

Timing diagram

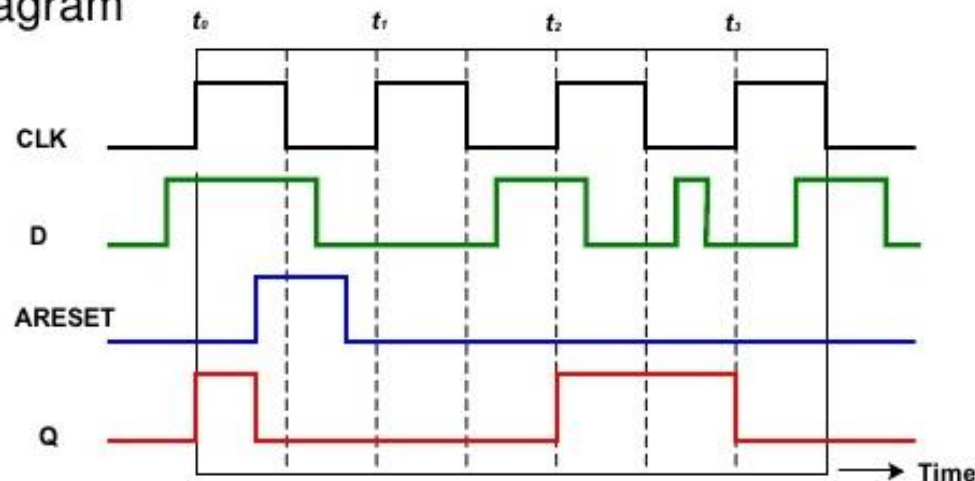

Asynchronous and Synchronous Reset

 - **Reset** signals are used to **initialize** the hardware to a known state
 - Usually activated **at system start** (on power up)
- **Synchronous Reset**
 - The reset signal is sampled **with respect to the clock**
 - The reset **should be active long enough** to get sampled at the clock edge
 - Results in **completely synchronous circuit**



D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0;    // when reset
        else            q <= d;    // when clk
    end
endmodule
```

- In this example: two events can trigger the process:
 - A **rising edge** on clk
 - A **falling edge** on reset

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0;    // when reset
        else            q <= d;    // when clk
    end
endmodule
```

- For longer statements, a **begin-end** pair can be used
 - To improve readability
 - In this example, it was not necessary, but it is a good idea

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0; // when reset
        else            q <= d;  // when clk
    end
endmodule
```

- First **reset** is checked: if **reset** is 0, **q** is set to 0.
 - This is an **asynchronous** reset as the reset can happen **independently** of the clock (on the negative edge of reset signal)
- If there is no reset, then regular assignment takes effect

D Flip-Flop with **Synchronous** Reset

```
module flop_sr (input          clk,
                 input          reset,
                 input    [3:0] d,
                 output reg [3:0] q);

  always @ (posedge clk)
  begin
    if (reset == '0') q <= 0;    // when reset
    else              q <= d;    // when clk
  end
endmodule
```

- The process is sensitive to only clock
 - Reset ***happens only*** when the ***clock rises***. This is a **synchronous** reset

D Flip-Flop with Enable and Reset


```
module flop_en_ar (input          clk,
                  input          reset,
                  input          en,
                  input [3:0] d,
                  output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0;    // when reset
    else if (en)       q <= d;    // when en AND clk
  end
endmodule
```

- A flip-flop with **enable** and **reset**
 - Note that the **en** signal is **not** in the *sensitivity list*
- **q** gets **d** only when **clk** is rising **and** **en** is 1

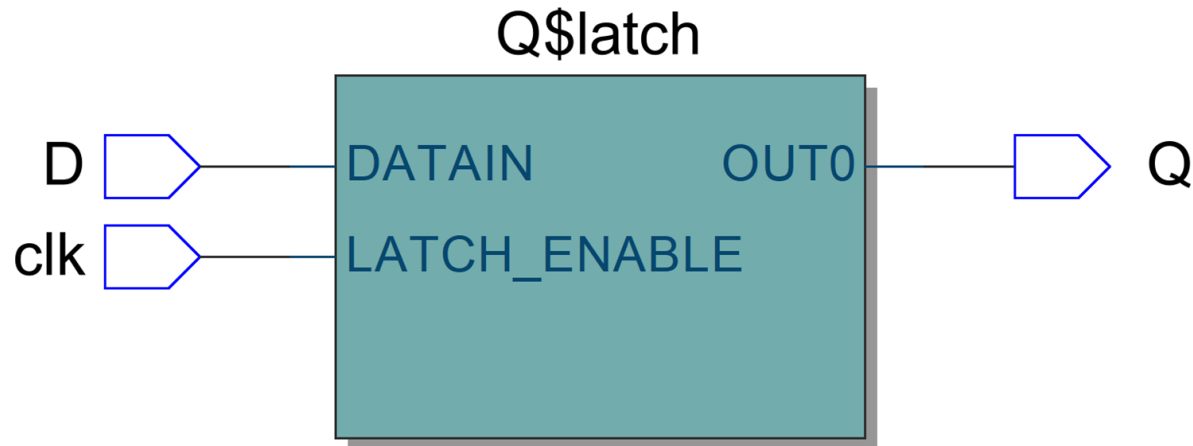Example: D Latch

```
module latch (input          clk,  
              input          [3:0] d,  
              output reg [3:0] q);  
  
  always @ (clk, d)  
    if (clk) q <= d;      // latch is transparent when  
                          // clock is 1  
  
endmodule
```




Summary: Sequential Statements So Far

- Sequential statements are within an `always` block
- The sequential block is triggered with a change in the `sensitivity list`
- Signals assigned within an **`always`** must be declared as `reg`
- We use `<=` for (non-blocking) assignments and do not use `assign` within the `always` block.

Recommended Reading

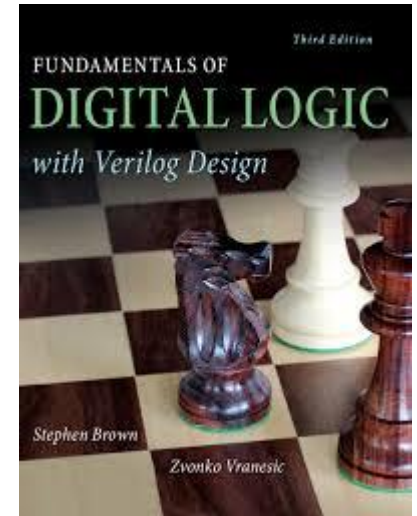- Digital System Design with Verilog HDL, 3/e, b **Stephen Brown** and **Zvonko Vranesic**. [**S&Z**]
 - S&Z,
 - Chapter-5 for review
 - 5.1, 5.3, 5.8
 - 5.13.1 for Verilog



THANK YOU

