

✓ (Conceptual)
(Yes)


Voltage Divider Series

Prob 9.61 The Complete Response of the RLC Circuit

(Like 9.56 8*)

(PP 367 7* Ex HKD)

Find $u_c(t)$ for $t > 0$.

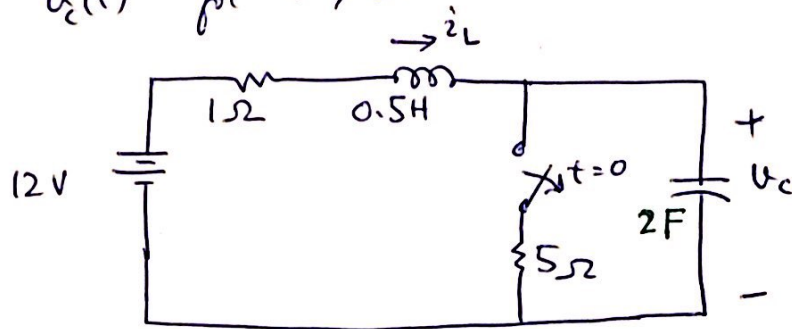

Solution:

For a series RLC circuit:- (Turning off the independent source)

$$\alpha = \frac{R}{2L} = \frac{1}{1} = 1$$

$$\text{and } \omega_0^2 = \frac{1}{LC} = 1 \quad \text{so } \omega_0 = 1$$

$\alpha = \omega_0$ so critically damped.

$$\text{Now } V_{\text{eff}} = 12 \text{ V}$$

$$\text{and } u_c(0^-) = \left(\frac{5}{5+1} \right) \times 12 = 10 \text{ V} = u_c(0^+)$$

$$\text{also } i_L(0^-) = \frac{12}{6} = 2 \text{ A} = i_L(0^+)$$

$$\text{We know } f_n(t) = e^{-\alpha t} (A_1 t + A_2)$$

$$f_f(t) = 12$$

$$\text{So } u_c(t) = 12 + e^{-\alpha t} (A_1 t + A_2)$$

$$u_c(0) = 12 + e^{-1 \times 0} (A_1 \times 0 + A_2) = 10$$

$$\text{Therefore } A_2 = -2$$

$$\text{Hence } u_c(t) = 12 + e^{-t} (A_1 t - 2)$$

_____ contd

(Conceptual)
(Yes)

— contd (367)

$$\text{Now } i_c = C \frac{dv_c}{dt}$$

$$\left. \frac{dv_c(t^+)}{dt} \right|_{t=0^+} = \frac{1}{C} i_c(t^+) = \frac{1}{2} i_c(t^+)$$

$$\text{As } i_L(t^-) = i_L(t^+) = 2 = i_c(t^+)$$

$$\text{So } \frac{1}{2} i_c(t^+) = \frac{1}{2} \times 2 = 1$$

$$\begin{aligned} \text{— And } \frac{dv_c}{dt} &= e^{-t} \times A_1 + A_1 t - e^{-t} - 2(-)e^{-t} \\ &= A_1 e^{-t} - A_1 t e^{-t} + 2e^{-t} \end{aligned}$$

$$\left. \frac{dv_c(t)}{dt} \right|_{t=0} = A_1 + 2$$

$$\text{Finally } A_1 + 2 = 1$$

$$A_1 = -1$$

$$\text{Therefore } v_c(t) = 12 + e^{-t}(-1t - 2)$$

$$\text{or } v_c(t) = 12 - e^{-t}(t+2), \quad \forall \quad t > 0$$

(Note: i_c can be calculated if required)

or i_L

$$\text{which } i = C \frac{dv_c}{dt}$$

Notice no steady-state (forced)
current due to presence of
capacitor.