

# EE-421: Digital Systems Design

Metastability - When A Good Flip-Flop goes Bad:

From BiStables to Metastable States

*"Causes and Cure"*


Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Learning Objectives

- Understand what metastability is, and how it can cause system failure
- Understand why metastability happens at the first place
- Be able to design a circuit to reduce the probability that metastability causes system failure
- To be able to calculate the mean time between failure due to metastability

What happens if we violate a flip-flop's setup and/or hold time requirements?
 
# Violating Flip-Flop Setup/Hold Times (1)




## Possible Outcomes: Q may...

- get the correct value
- get the wrong value (0 or 1)
- become **metastable** - get a value between 0 and 1
  - *Remember, in reality, we are working with voltages which can take on a continuous range of values*

 
# Violating Flip-Flop Setup/Hold Times (2)

- **Metastable** - a value between 0 and 1




# Violating Flip-Flop Setup/Hold Times (3)

- Metastability

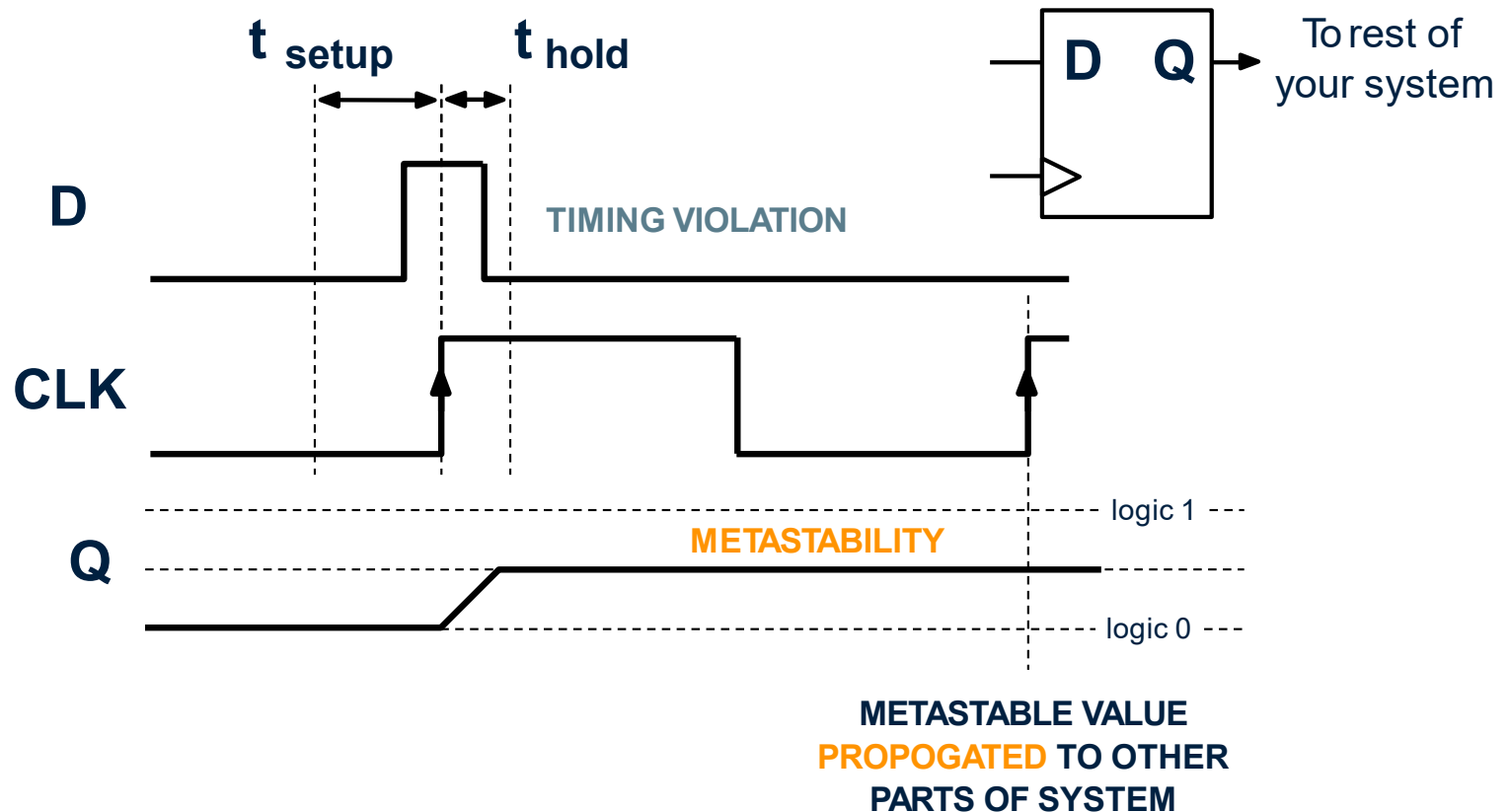


**MAY CAUSE SYSTEM-WIDE FAILURE**

# Example of Metastable Signals

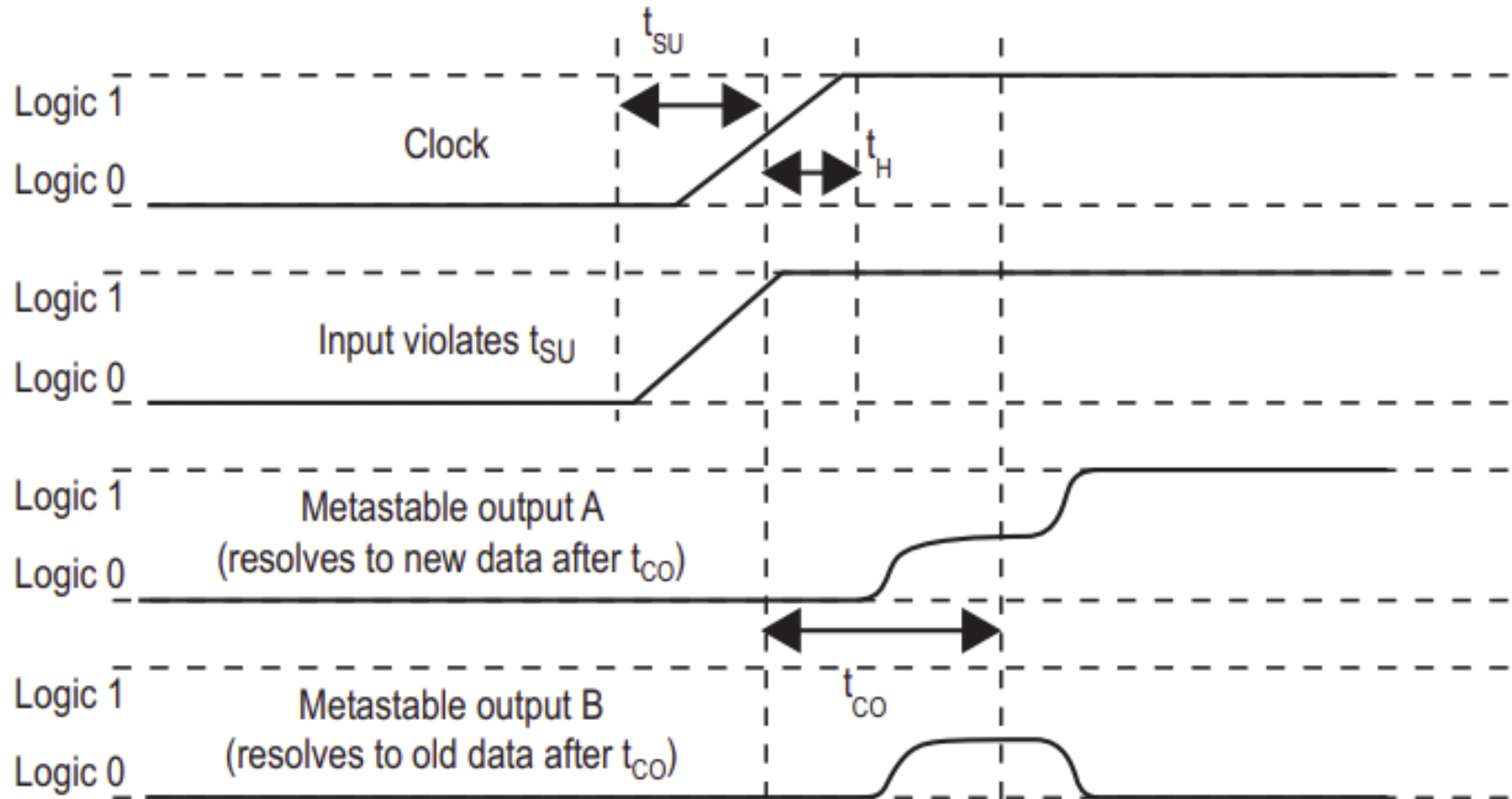


# Real Metastable Example

 

Picture taken from W. J. Dally, Lecture notes for EE108A, Lecture 13: Metastability and Synchronization Failure (ow When Good Flip-Flops go Bad) 11/9/2005.




# Real Metastable Example

 

Picture taken from W. J. Dally, Lecture notes for EE108A, Lecture 13: Metastability and Synchronization Failure (ow When Good Flip-Flops go Bad) 11/9/2005.

# Let's Understand Metastable State through a Mechanical Analogy

# Mechanical Analogy

 


Imagine dropping a ball on a hill

- perfectly smooth and symmetrical hill
- no forces except gravity

Depending on where you drop the ball, it will settle in one of two states

- either on the left side or the right side

# Mechanical Analogy

 


The closer you drop the ball near either side, the faster it settles

- Shorter distance
- Steeper slope

# Mechanical Analogy


## Two Stable States

 

**Once ball reaches either state,  
it will stay there forever**
 
# Mechanical Analogy

There is a **THIRD** state: “**Metastable State**”!




Imagine the ball is dropped perfectly in the middle

The slope at the exact middle is flat

There are no other forces besides gravity

**In theory, ball will stay there forever**


# Mechanical Analogy

 

**In practice, ball will eventually settle to a stable state**

- Gust of wind
- Non-perfect hill
  - Not perfectly symmetrical
  - Slope not perfectly flat in the middle

# Mechanical Analogy

 

**Into which state will it settle?**


**How long before it settles?**

**Not predictable!**



OK, Got it! But how does this apply  
to flip-flops?

# A Theoretical Storage Element

 


## Two Stable States

- $A=0, B=1$
- $A=1, B=0$

This element isn't very practical (no way to change state)

But **ALL** state-holding digital circuits\* are based off of using positive-feedback loops


 
# Preview – Possible Topology for a D-Latch



When CLK is 1, Q' follows D (but inverted)

When CLK is 0, D is disconnected, feedback loop is connected to reinforce “stored” value, Q' does not change with D

# Inverter Voltage Transfer Curve (VTC)

  

Say that in our technology:



Logic 1 is 1.8V

Logic 0 is 0V

**IDEAL Behaviour:**

$$V_{out} = \begin{cases} 1.8 V, & V_{in} < 0.9 V \\ 0 V, & V_{in} \geq 0.9 V \end{cases}$$

# Inverter Voltage Transfer Curve (VTC)

  

Say that in our technology:

Logic 1 is 1.8V


Logic 0 is 0V

**REALISTIC Behaviour**

$$V_{out} = f(V_{in})$$


# Storage Element – Scenario 1

Say we externally drive A to **0 V**

 

 
1. B gets driven to 1.8 V by the top inverter
2. A then gets driven to 0 V by the bottom inverter (reinforced)
3. which then causes B to be driven to 1.8 V (reinforced)
4. ...

Positive feedback **INSTANTLY** reinforces Internal value.



# Storage Element – Scenario 2


Say we externally drive A to **1.8 V**

 

 1. B gets driven to 0 V by the top inverter
2. A then gets driven to 1.8 V by the bottom inverter (reinforced)  
which then causes B to be driven to 0 V (reinforced)


...

Positive feedback **INSTANTLY** reinforces Internal value.




# Storage Element – Scenario 3

Say we externally drive A to **1.35 V**

 

 1. B gets driven to 0.2 V by the top inverter
2. A then gets driven to 1.75 V by the bottom inverter
3. which then causes B to be driven to 0.01 V
4. ...


Positive feedback **VERY QUICKLY** settles Internal value.






# Storage Element – Scenario 4

Say we externally drive A to **1V**

 

 
1. B gets driven to 0.75 V by the top inverter
2. A then gets driven to 1.5 V by the bottom inverter
3. which then causes B to be driven to 0.2 V
4. ...

Positive feedback **TAKING LONGER** now to settle internal value.




# Storage Element – Scenario 5

Say we externally drive A to **0.9 V**

 


 1. B gets driven to 0.9 V by the top inverter
2. A then gets driven to 0.9 V by the bottom inverter
3. which then causes B to be driven to 0.9 V
4. ...



**STUCK IN METASTABLE STATE!**

# Storage Element – Metastable State

 


In reality, there are sources of noise:

- Thermal, crosstalk, quantum transistor effects
- Noise is like the “gust of wind” from mechanical example

**NOISE will push the circuit out of metastability**


- But we won't know how long this will take
- Nor will we know which of the two stable states it will assume

# D Flip-Flop: Master-Slave Topology

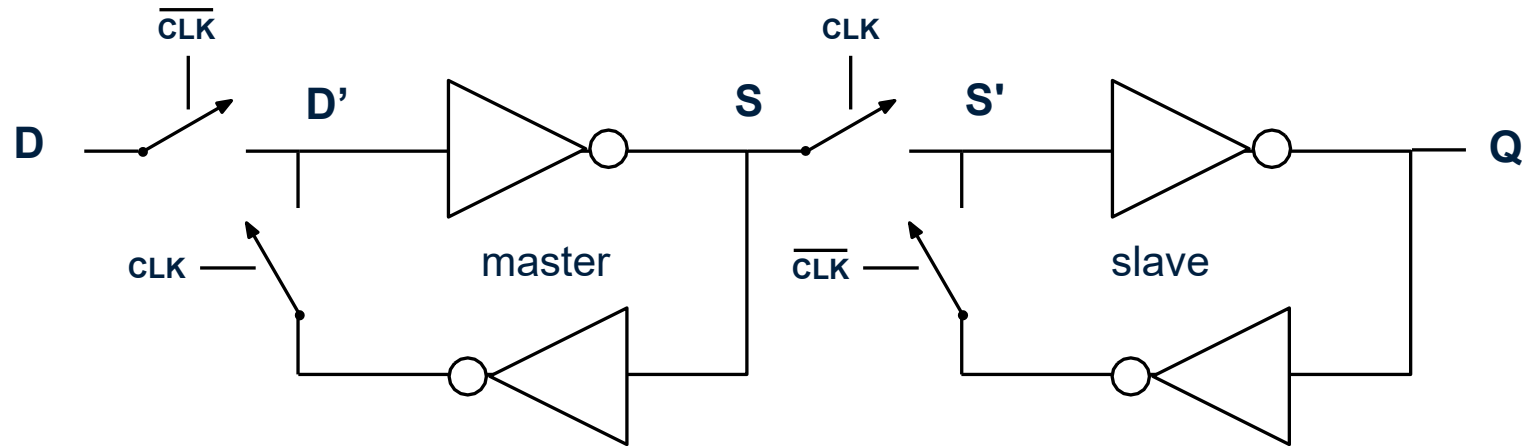

**Built using two D-Latches**

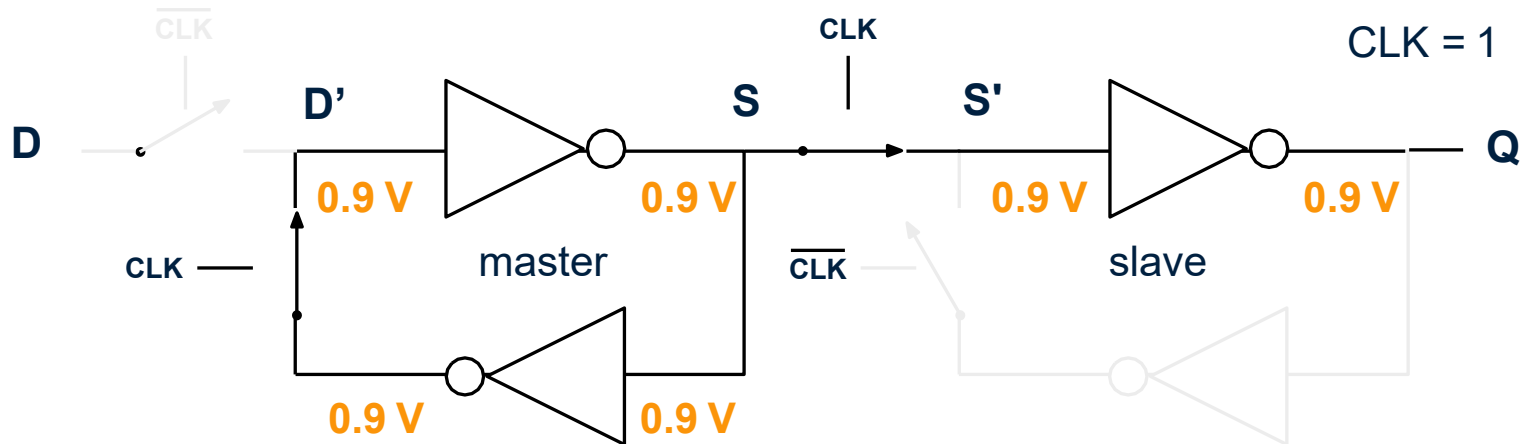
# Violating Setup or Hold Time Requirements in a D-Flop (1)



## Risks putting 0.9V onto S or D'

- We know that the master feedback loop could be stuck in metastable state for unknown amount of time
- Will also put slave into metastable state
- Q would then be metastable

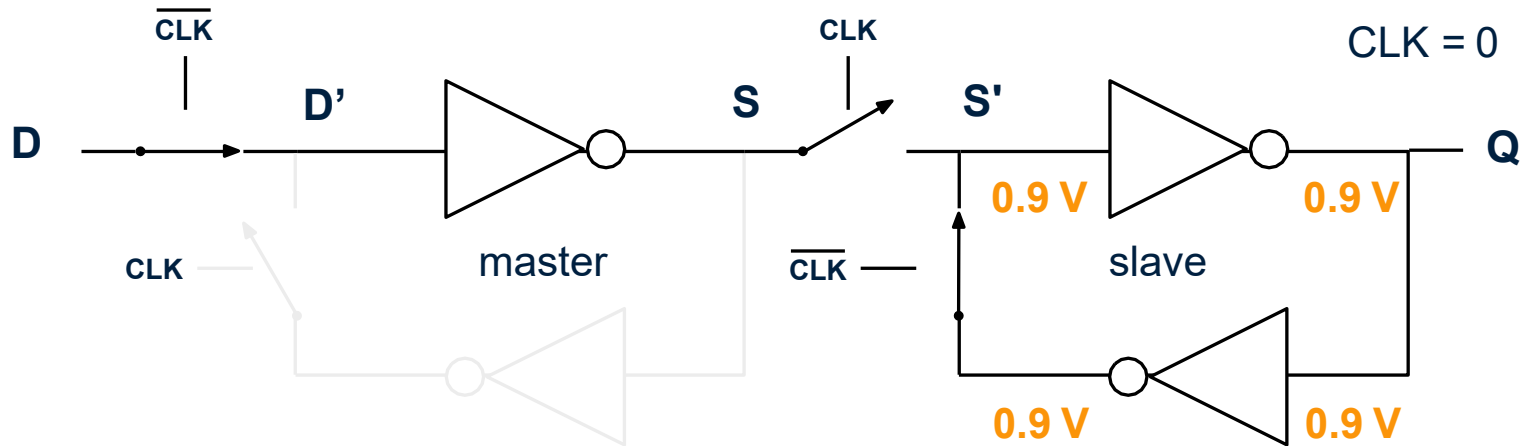
# Violating Setup or Hold Time Requirements in a D-Flop (2)



## After falling edge

- Slave feedback gets stuck in metastable state
- Q still metastable
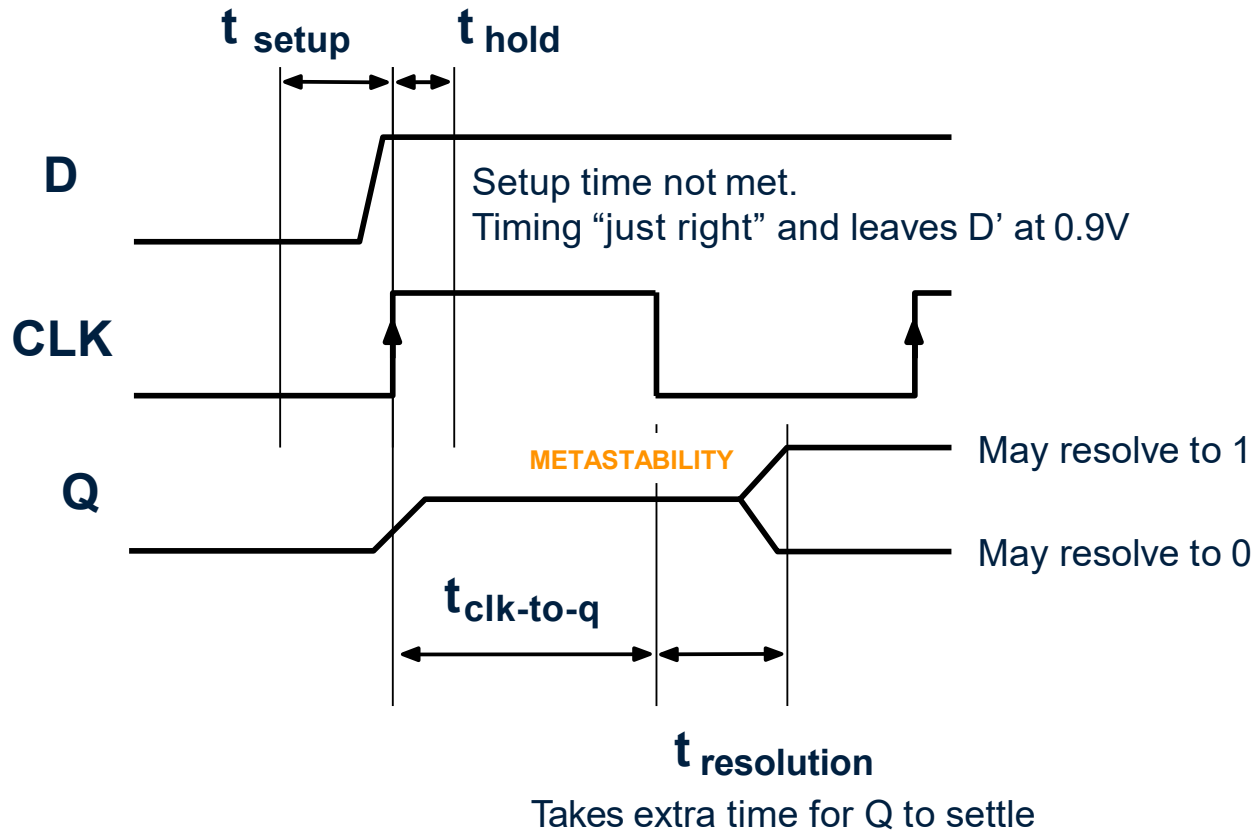
# Metastability: Violating Setup or Hold Time




Resolution time is **UNBOUNDED**

# Path Slack




# Path Slack

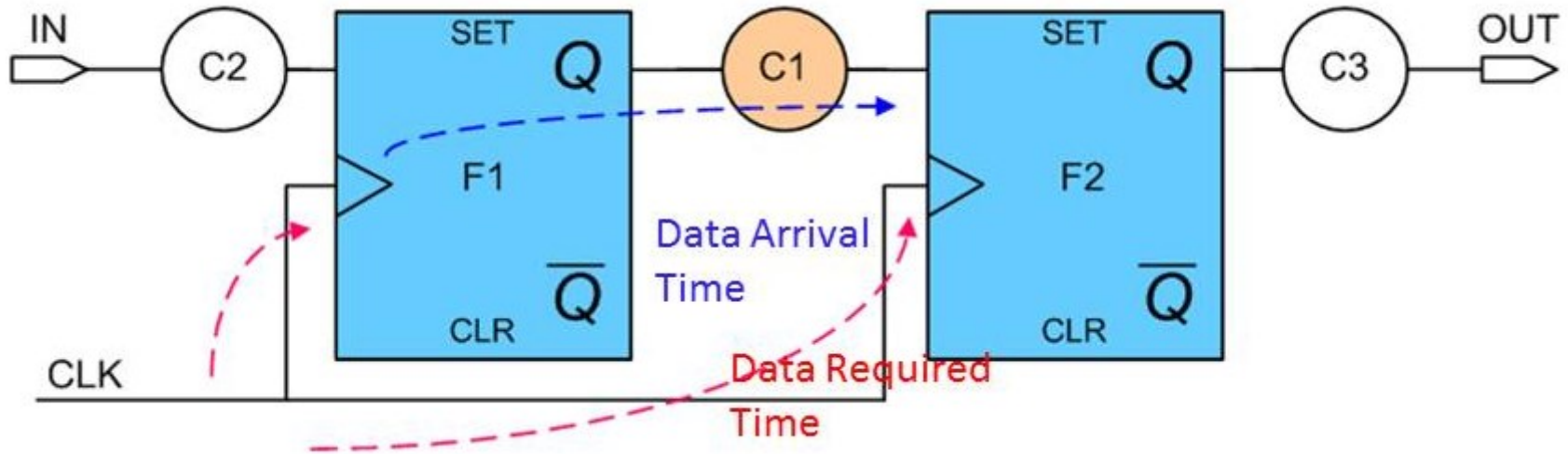

- Slack is defined as difference between actual or achieved time and the desired time for a timing path:
  - A +ve slack means design is working at the specified frequency and it has some more margins as well.
  - Zero slack specifies design is exactly working at the specified frequency and there is no margin available.
  - ve slack implies that design doesn't achieve the constrained frequency and timing. Timing Violation!

**If  $t_{\text{resolution}}$  is GREATER  
than the amount of path slack,  
then system failure!**

# Why System Failure?

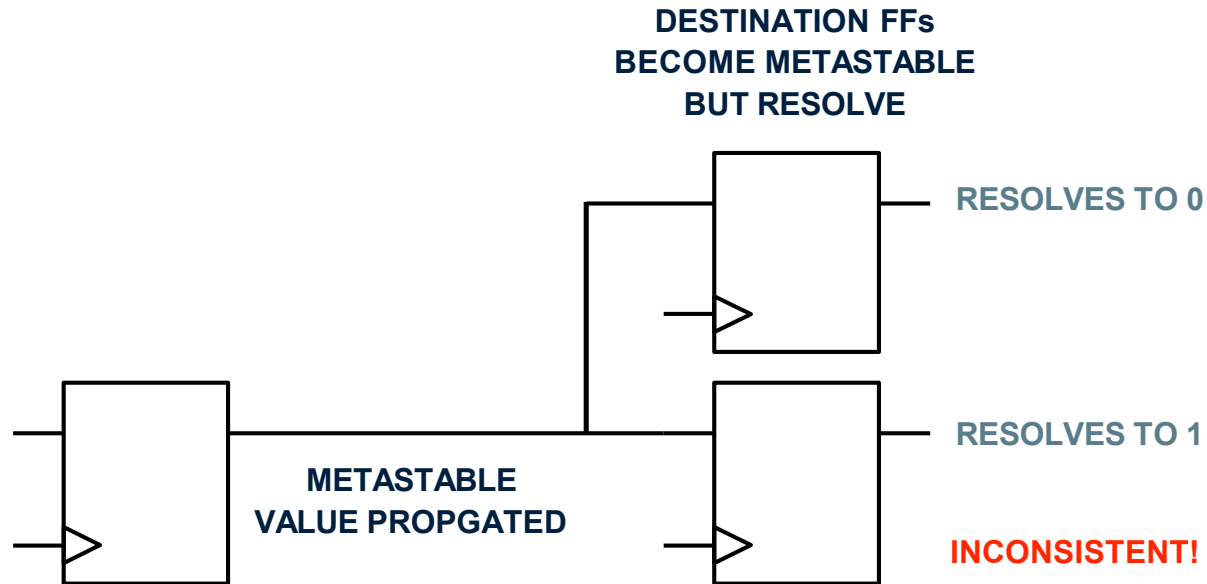

If metastable value is propagated, FFs at next stage will become metastable and may...


- further propagate metastable value
- or resolve inconsistently
  - different destinations FFs see different values for the same signal

**Bottom Line:**

**Don't change flip-flop input too close to clock edge**


# Dealing with Metastability ...

# Synchronizer Register Chain

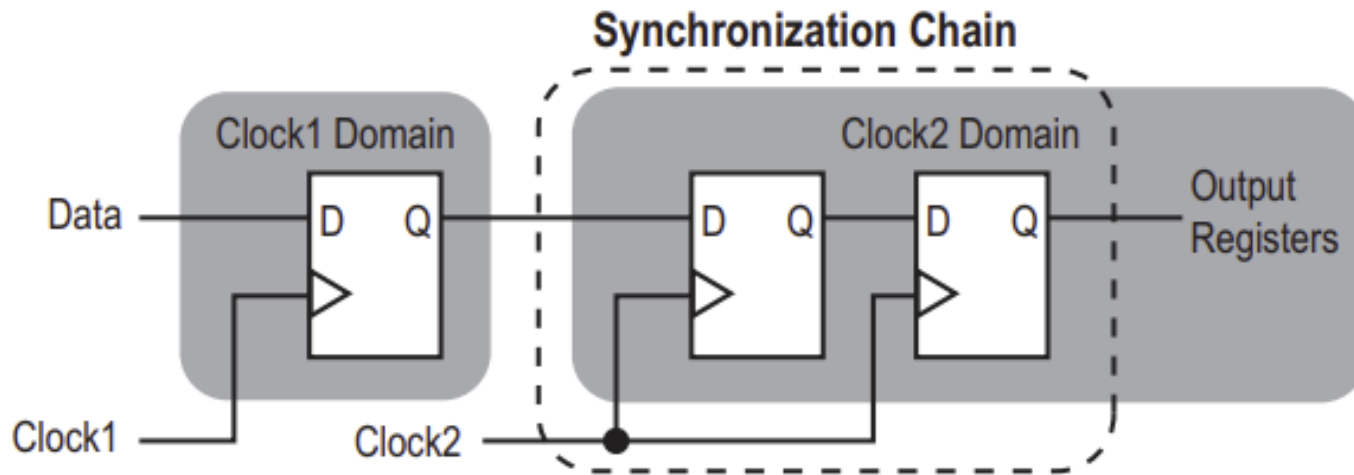

- **Synchronizer Circuit**
  - Two flip-flops instead of one i.e two-bit shift register
  - If output of the first flop goes metastable, it has an **entire clock-cycle** to resolve itself and appear correctly at the second flop
- This is a VERY common technique – add synchronizers to all async interfaces

# Asynchronous Signals

 

## The whole point of synchronization:

Within our circuit, make sure both setup and hold requirements are always met for all paths

→ We can eliminate metastability inside of our circuit


But we often need to interface with **asynchronous** signals

# Asynchronous Signals

Asynchronous just mean that it doesn't adhere to the clock signal
 
## For Example: Real World Signals

- Real world signals, like buttons, don't change aligned to your clock
- Non-zero chance of input changing too close to clock edge






# Asynchronous Signals

## Another Example: Systems With Multiple Clocks

- Many systems have more than one clock
- Flip-flops still only listen to one clock
- Logic/FFs on the same clock belong to the same **clock-domain**

Signals sometime need to cross clock-domain boundaries

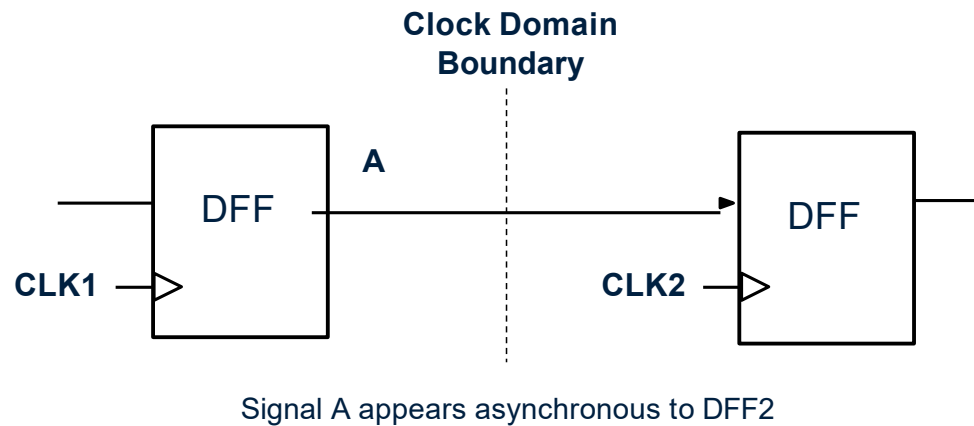If the clocks are unsynchronized (not multiples of each other), then the signal crossing the clock-domain appears asynchronous



# Mean-Time Between Failure (MTBF)

# Mean-time Between Failure (MTBF)

Metric to estimate the average time between two failure-causing instances of metastability on a given signal transfer

$$MTBF = \frac{e^{t_{slack}/C_0}}{C_1 \cdot f_{CLK} \cdot f_{DATA}}$$

- $f_{CLK}$  – Clock frequency
- $f_{DATA}$  – Toggling frequency of the FF input
- $t_{slack}$  – Amount of slack available on the path for metastability resolution
- $C_o, C_I$  – Constants dependent on operating conditions and process tech

# Mean-time Between Failure

Metric to estimate the average time between two failure-causing instances of metastability on a given signal transfer

$$MTBF(t_{slack}) = \frac{e^{t_{slack}/C_0}}{C_1 \cdot f_{CLK} \cdot f_{DATA}}$$


**Higher MTBF means more robust design**

- maybe hundreds or thousands of years

**Required MTBF depends on application**

- Life-critical medical equipment would need higher MTBF than consumer video game system
 
# MTBF Example Calculation - Synchronizer



$$MTBF = \frac{e^{t_{slack}/C_0}}{C_1 \cdot f_{CLK} \cdot f_{DATA}} = 20.1 \text{ days}$$

Quartus calculates all this for you!

# THANK YOU

