



**NATIONAL UNIVERSITY OF SCIENCES & TECHNOLOGY**

**Electric Network Analysis (EE-211)**

**Assignment # 4**

**Submitted to:** Ahsan Azhar

**Submitted by:** Muhammad Umer

**Class:** BEE-12C

**Semester:** 2<sup>nd</sup>

**Dated:** 27/05/2021

**CMS ID:** 345834

### Question 14.14

Draw the Bode plots for

$$H(\omega) = \frac{250(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

Solution

$$\Rightarrow \frac{250(j\omega + 1)}{j\omega[(j\omega)^2 + 10j\omega + 25]}$$


$$\Rightarrow \frac{250(j\omega + 1)}{j\omega 25[(j\omega/5)^2 + 10j\omega/25 + 25/25]}$$


$$\Rightarrow \frac{10(j\omega + 1)}{j\omega[(j\omega/5)^2 + 10j\omega/25 + 25/25]}$$

$$\underline{H_{dB}} = 20 \log_{10}(10) + 20 \log_{10}(1 + j\omega) - 20 \log_{10}(j\omega) - 20 \log_{10}(1 + 2/5 j\omega + (j\omega/5)^2)$$

$$\underline{\phi} = 0^\circ + \tan^{-1}(\omega) - 90^\circ - \tan^{-1}\left(\frac{2/5 \omega}{1 - \omega^2/25}\right)$$

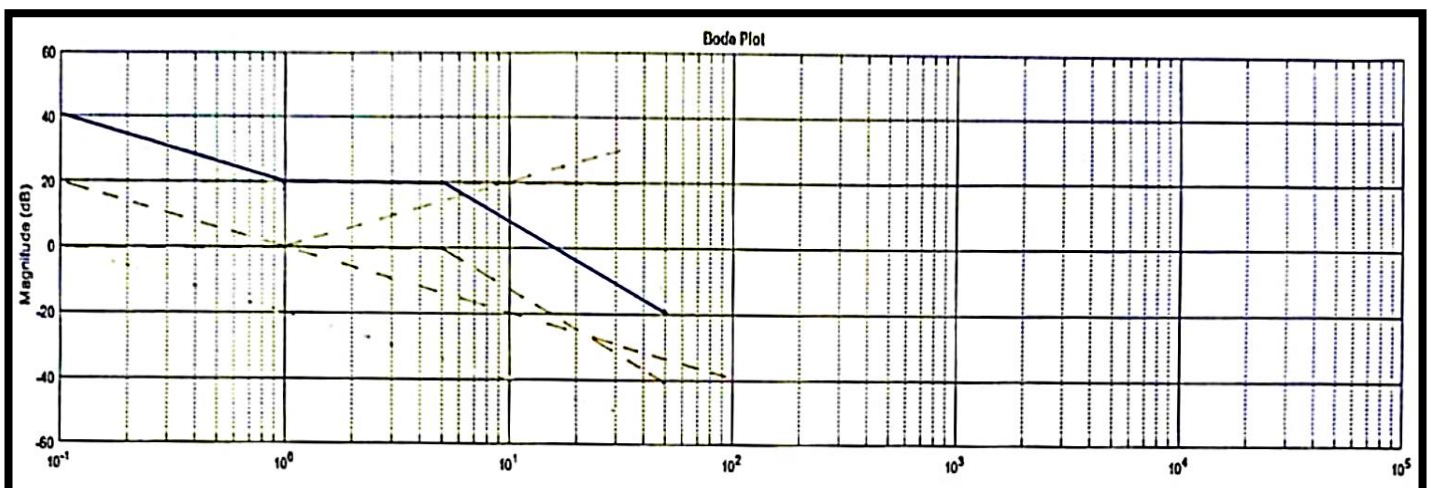Compiling and utilizing this onto a semi-logarithmic plot:



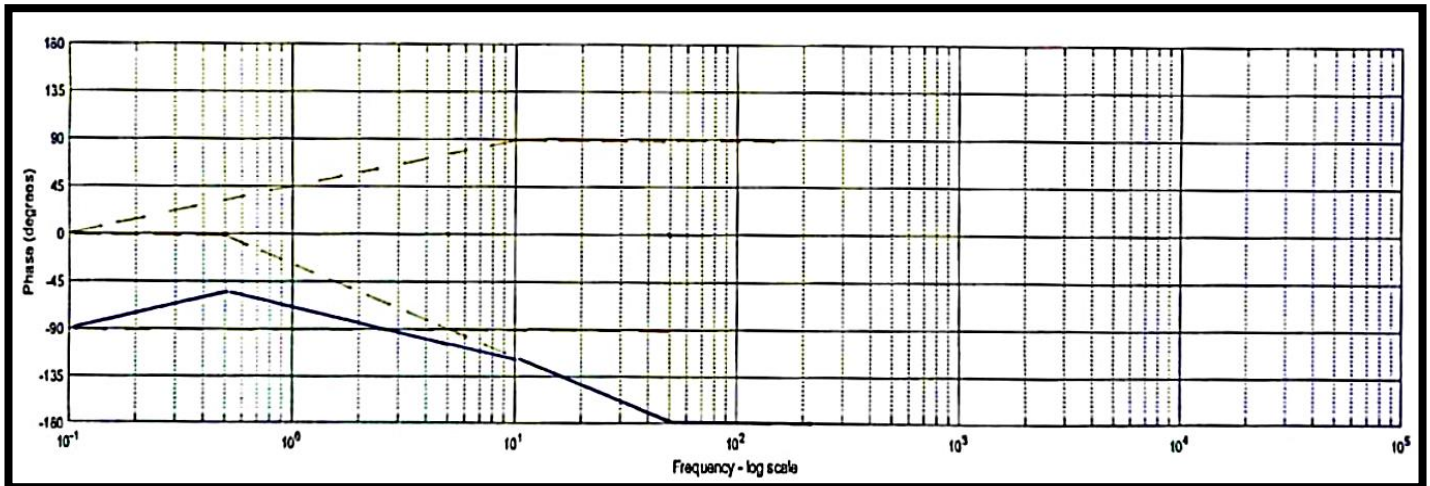

### Question 14.17

Sketch the Bode plots for

$$G(s) = \frac{s}{(s + 2)^2(s + 1)}, \quad s = j\omega$$



**Solution**

$$\begin{aligned} \Rightarrow G(\omega) &= \frac{j\omega}{(j\omega + 2)^2(j\omega + 1)} \\ &= \frac{j\omega}{4(1 + j\omega/2)^2(1 + j\omega)} \\ &= \frac{(1/4)j\omega}{(1 + j\omega/2)^2(1 + j\omega)} \end{aligned}$$

$$\begin{aligned} G_{dB} &= -20 \log_{10}(4) + 20 \log_{10}(j\omega) \\ &\quad - 40 \log_{10}(1 + j\omega/2) - 20 \log_{10}(1 + j\omega) \end{aligned}$$


$$\phi = 0^\circ + 90^\circ - 2 \tan^{-1}(\omega/2) - \tan^{-1}(\omega)$$

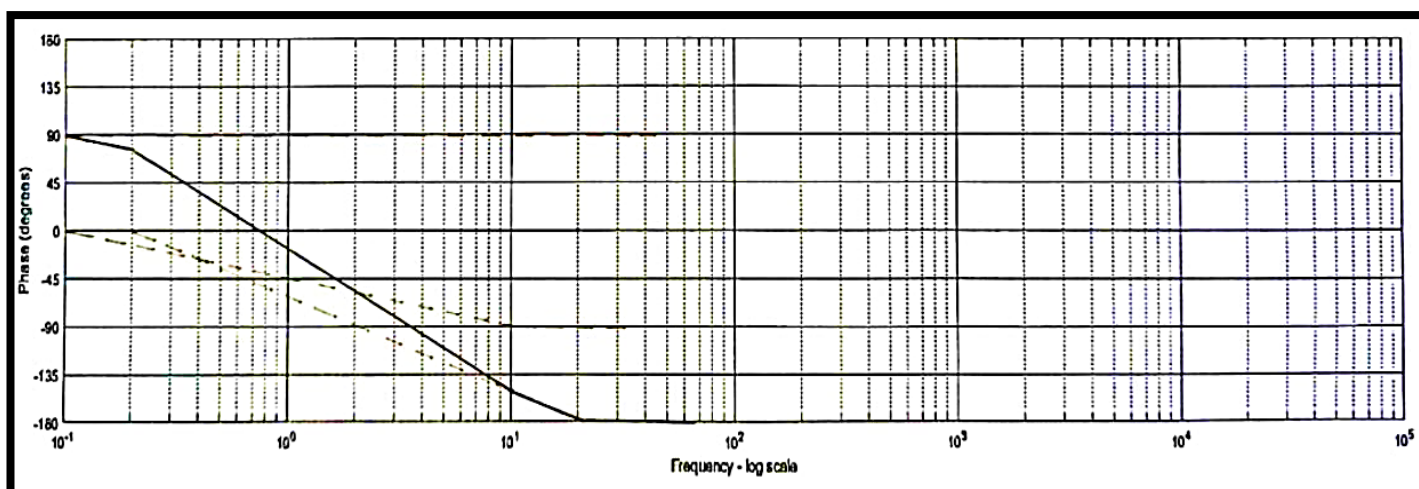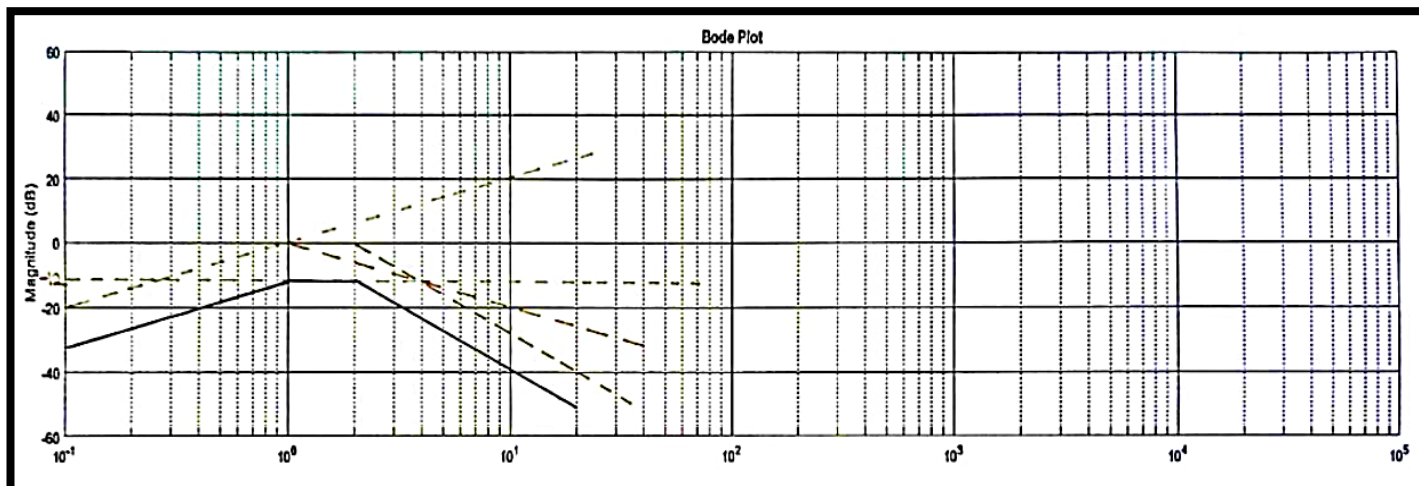Compiling and utilizing this onto a semi-logarithmic plot


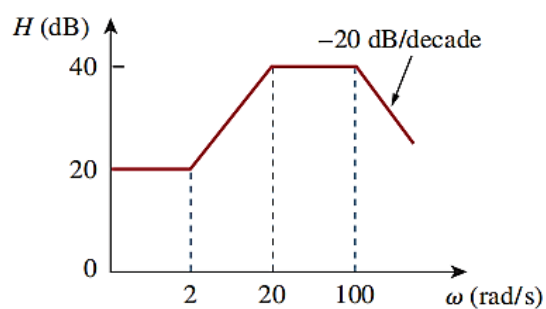
## Question 14.22

Find the transfer function with the Bode magnitude plot shown:



Solution

$$20 = 20 \log_{10}(K)$$

$$K = 10$$

Zero of  $+20 \text{ dB/sec}$  at  $\omega = 2$ ;

$$1 + j\omega/2$$

Pole of  $-20 \text{ dB/sec}$  at  $\omega = 20$ ;

$$1/(1 + j\omega/20)$$

Pole of  $-20 \text{ dB/sec}$  at  $\omega = 100$ ;

$$1/(1 + j\omega/100)$$

Thus,

$$H(\omega) = \frac{10(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)}$$

### Question 14.28

Design a series  $RLC$  circuit with  $\omega_0 = 1000 \text{ rad/s}$ . Find the circuit's  $Q$ . Let  $R = 10 \text{ Ohms}$ .

#### Solution

Given  $R = 10 \Omega$ ,  $B = 20 \text{ rad/s}$ ,  $\omega_0 = 1000 \text{ rad/s}$

Using,

$$B = \frac{R}{L} \Rightarrow L = \frac{R}{B} = \frac{10}{20} = 0.5 \text{ H}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega^2 = \frac{1}{LC}$$

$$\Rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(1000)^2 (0.5)} = 2 \mu\text{F}$$

$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$

Hence, the components of RLC circuit are:

- $R = 10$ ,  $L = 0.5 \text{ H}$ ,  $C = 2 \mu\text{F}$   
with Quality Factor = 50

### Question 14.40

A parallel resonance circuit has a resistance of  $R = 2 \text{ k Ohms}$  and half-power frequencies of 86 kHz and 90 kHz. Determine:

- (a) the capacitance
- (b) the inductance
- (c) the resonant frequency
- (d) the bandwidth
- (e) the quality factors

### Solution

$$B = \omega_2 - \omega_1 = (90 \text{ k} - 86 \text{ k}) 2\pi = \boxed{8\pi \text{ k rad/s}}^d$$

$$\omega_0 = \frac{1}{2} (\omega_2 + \omega_1) = \frac{1}{2} (176 \text{ k}) 2\pi = \boxed{176\pi \text{ k rad/s}}^c$$

$$B = \frac{\omega^2 L}{R} \Rightarrow L = \frac{BR}{\omega^2} = \frac{(8\pi \text{ k})(2 \text{ k})}{(176\pi \text{ k})^2} = \boxed{164.45 \mu\text{H}}^b$$

$$C = \frac{1}{\omega^2 L} = \frac{1}{(176\pi \text{ k})^2 (164.45 \mu)} = \boxed{19.89 \times 10^{-9} \text{ F}}^a$$

$$Q = \frac{\omega_0}{B} = \frac{176\pi \cancel{\text{k}}}{8\pi \cancel{\text{k}}} = \boxed{22}^e$$

---