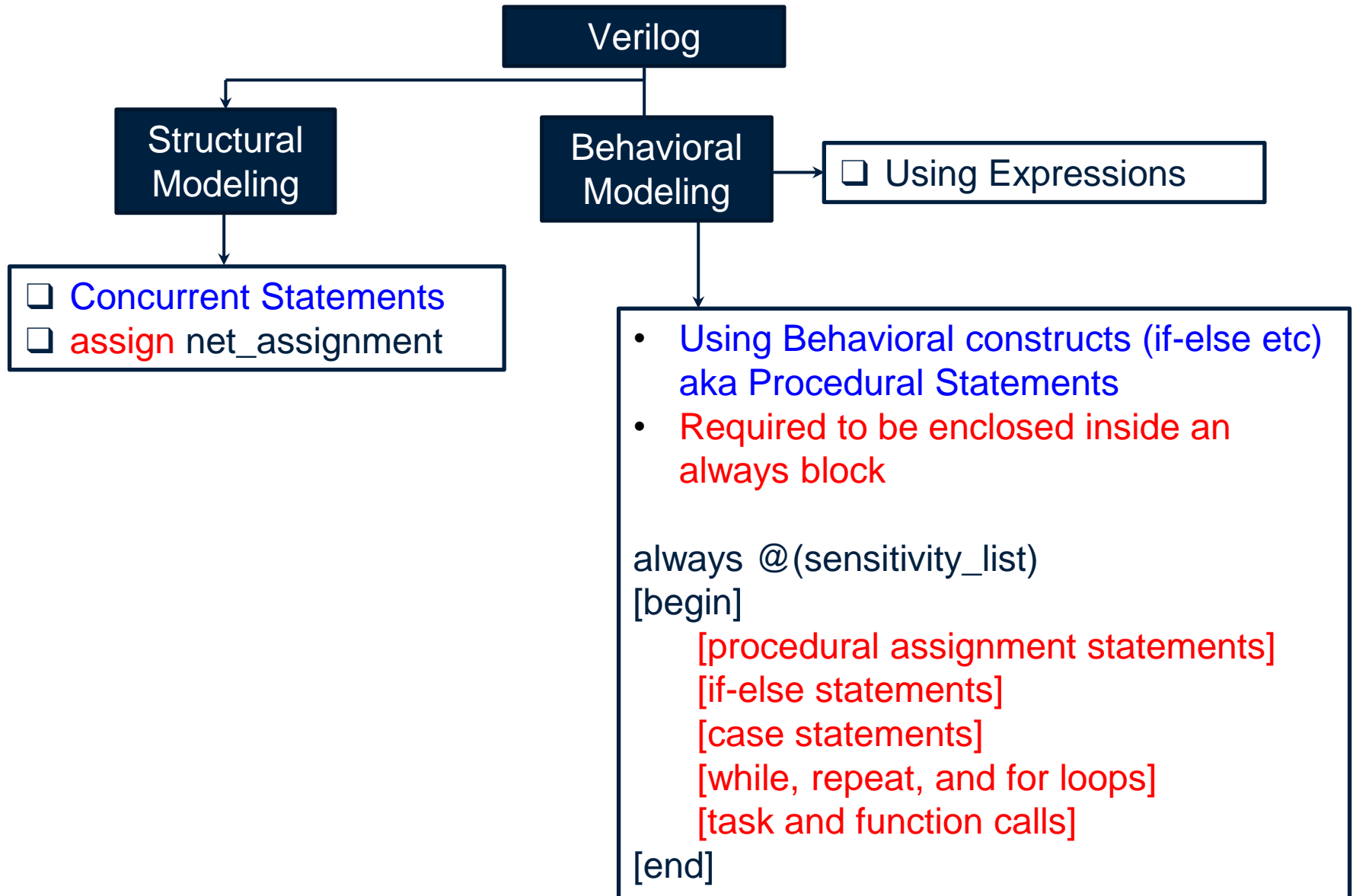


EE-421: Digital System Design

Combinational Circuit Building Blocks Using CAD Tools - Adder


Instructor: Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Recap: What have we seen so far . . .



Design of Arithmetic Circuits – Full Adder


Review: Half-Adder

 


(a) The four possible cases

		Carry	Sum
x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

(c) Circuit

 

(d) Graphical symbol

Review: Full-Adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 


(c) Circuit

Review: Full-Adder using Half-Adders

 

(a) Block diagram

 


(b) Detailed diagram

Full-Adder using Gate-Level Primitives

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;
```


```
  xor (s, x, y, Cin);  
  and (z1, x, y);  
  and (z2, x, Cin);  
  and (z3, y, Cin);  
  or (Cout, z1, z2, z3);
```

```
endmodule
```

 

Full-Adder using Continuous Assignment

```
module fulladd (Cin, x, y, s, Cout);  
    input Cin, x, y;  
    output s, Cout;  
  
    assign s = x ^ y ^ Cin;  
    assign Cout = (x & y) | (x & Cin) | (y & Cin);  
  
endmodule
```

 

Full-Adder at Behavioral

```
module fulladd (Cin, x, y, s, Cout);  
    input Cin, x, y;  
    output reg s, Cout;  
  
    always @(x, y, Cin)  
        {Cout, s} = x + y + Cin;  
  
endmodule
```

Design of Arithmetic Circuits – Multi-bit Adder

Four-bit Adder – Using Hierarchical Design Approach

```
module adder4 (carryin, x3, x2, x1, x0, y3, y2, y1, y0, s3, s2, s1, s0, carryout);  
    input carryin, x3, x2, x1, x0, y3, y2, y1, y0;  
    output s3, s2, s1, s0, carryout;
```

```
    fulladd stage0 (carryin, x0, y0, s0, c1);  
    fulladd stage1 (c1, x1, y1, s1, c2);  
    fulladd stage2 (c2, x2, y2, s2, c3);  
    fulladd stage3 (c3, x3, y3, s3, carryout);
```

```
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
    input Cin, x, y;  
    output s, Cout;  
  
    assign s = x ^ y ^ Cin,  
    assign Cout = (x & y) | (x & Cin) | (y & Cin);
```

```
endmodule
```

Code Improvement using Vectors

```
module adder4 (carryin, X, Y, S, carryout);  
    input carryin;  
    input [3:0] X, Y;  
    output [3:0] S;  
    output carryout;  
    wire [3:1] C;  
  
    fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);  
    fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);  
    fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);  
    fulladd stage3 (C[3], X[3], Y[3], S[3], carryout);  
  
endmodule
```

Code Improvement using Parametrization

```
module addern (carryin, X, Y, S, carryout);  
  parameter n=32;  
  input carryin;  
  input [n-1:0] X, Y;  
  output reg [n-1:0] S;  
  output reg carryout;  
  reg [n:0] C;  
  integer k;  
  
  always @(X, Y, carryin)  
  begin  
    C[0] = carryin;  
    for (k = 0; k < n; k = k+1)  
    begin  
      S[k] = X[k] ^ Y[k] ^ C[k];  
      C[k+1] = (X[k] & Y[k]) | (X[k] & C[k]) | (Y[k] & C[k]);  
    end  
    carryout = C[n];  
  end  
  
endmodule
```

Alternate Style using CASE

```
module fulladd (Cin, x, p_state, s, Cout);  
  input Cin, x, p_state;  
  output reg s, Cout;  
  
  always @(Cin, x, p_state)  
  begin  
    case ( {Cin, x, p_state} )  
      3'b000: {Cout, s} = 'b00;  
      3'b001: {Cout, s} = 'b01;  
      3'b010: {Cout, s} = 'b01;  
      3'b011: {Cout, s} = 'b10;  
      3'b100: {Cout, s} = 'b01;  
      3'b101: {Cout, s} = 'b10;  
      3'b110: {Cout, s} = 'b10;  
      3'b111: {Cout, s} = 'b11;  
    endcase  
  end  
  
endmodule
```


Code Improvement using Generate

```
module addern (carryin, X, Y, S, carryout);  
  parameter n = 32;  
  input carryin;  
  input [n-1:0] X, Y;  
  output [n-1:0] S;  
  output carryout;  
  wire [n:0] C;  
  
  genvar i;  
  assign C[0] = carryin;  
  assign carryout = C[n];  
  generate  
    for (i = 0; i <= n-1; i = i+1)  
      begin:addbit  
        fulladd stage (C[i], X[i], Y[i], S[i], C[i+1]);  
      end  
  endgenerate  
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  assign s = x ^ y ^ Cin,  
          Cout = (x & y) | (x & Cin) | (y & Cin);  
endmodule
```

Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **Stephen Brown** and **Zvonko Vranesic**. [**S&Z**]
 - S&Z,
 - Chapter-3 for review
 - 3.5 for Verilog



THANK YOU

