



NATIONAL UNIVERSITY OF SCIENCES & TECHNOLOGY

Electric Network Analysis (EE-211)

Assignment # 1

Submitted to: Ahsan Azhar

Submitted by: Muhammad Umer

Class: BEE-12C

Semester: 2nd

Dated: 19/03/2021

CMS ID: 345834

Assignment 1

9.2 $i_s = 15 \cos(25\pi t + 25^\circ) \text{ A}$

a) What is the amplitude of the current?

Since, $i(t) = i_m \cos(\omega t + \phi) \text{ A}$

Amplitude $i_m = 15 \text{ A}$

b) What is the angular frequency?

$\omega = 25\pi = 78.53 \text{ rad/s}$

c) Find the frequency of the current?

As $\omega = 2\pi f$

$f = \frac{\omega}{2\pi} = \frac{25\pi}{2\pi} = 12.5 \text{ Hz}$

d) Calculate i_s at $t = 2 \text{ ms}$.

$i_s = 15 \cos(25\pi(2 \times 10^{-3}) + 25^\circ)$

$i_s = 15 \cos(\pi/20 + 25^\circ \times \frac{\pi}{180^\circ})$

$i_s = 15 \cos(0.59341)$

$i_s = 12.435 \text{ A}$

9.5 $V_1 = 45 \sin(\omega t + 30^\circ) \text{ V}$

$V_2 = 50 \cos(\omega t - 30^\circ) \text{ V}$

$V_1 = 45 \sin(\omega t + 30^\circ) = 45 \cos(\omega t + 30^\circ - 90^\circ)$

$V_1 = 45 \cos(\omega t - 60^\circ) \text{ V}$


$\phi_{V_1} - \phi_{V_2} = -60^\circ - (-30^\circ) = -30^\circ$

The phase difference is of $\boxed{-30^\circ}$

The phase angle is $\boxed{30^\circ}$.

V_1 lags V_2 .


9.42

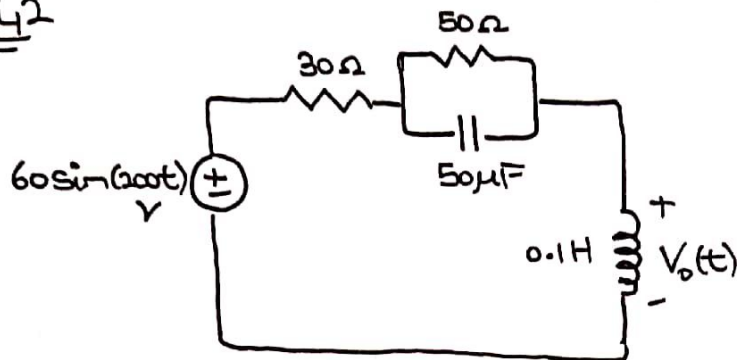

Source in terms of cosine,

$$V_s = 60 \sin(200t) = 60 \cos(200t - 90^\circ)$$

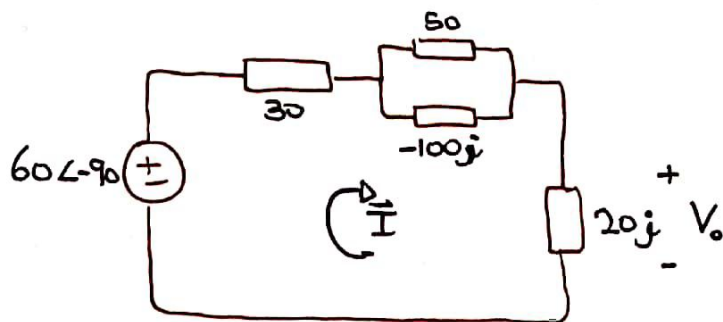In Phasor, $V_s = 60 \angle -90^\circ \text{ V}$




$$\vec{I} = \frac{\vec{V}}{\vec{Z}} = \frac{60 \angle -90^\circ}{(30 + (\frac{1}{50} + \frac{1}{-100j})^{-1} + 20j)} = -\frac{6}{7} j$$


$$V_o = \vec{I} (20j) = 17.14 \angle 0^\circ$$

$$\boxed{V_o(t) = 17.14 \cos(200t) \text{ V}}$$

9.52 $V_o = 8 \angle 30^\circ \text{ V}$

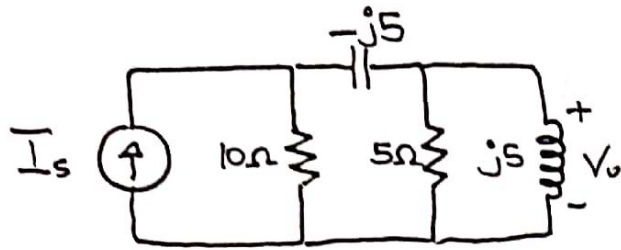

Combining parallel elements

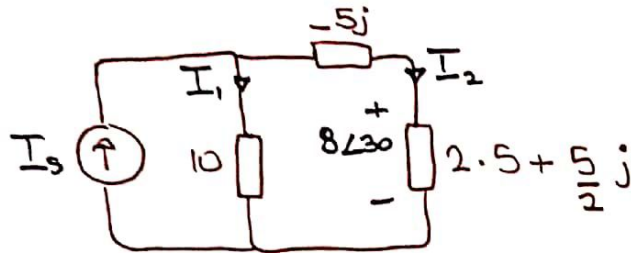

$$I_2 = \frac{V_o}{Z} = \frac{8 \angle 30^\circ}{2.5 + 2.5j} = 2.26 \angle -15^\circ$$


By CDR,

$$I_2 = I_s \left(\frac{10}{12.5 - 2.5j} \right)$$


$$2.26 \angle -15^\circ = I_s \left(\frac{10}{12.5 - 2.5j} \right)$$

$$I_s = 2.26 \angle -15^\circ \cdot \left(\frac{12.5 - 2.5j}{10} \right)$$

$I_s = 2.88 \angle -26.31^\circ$

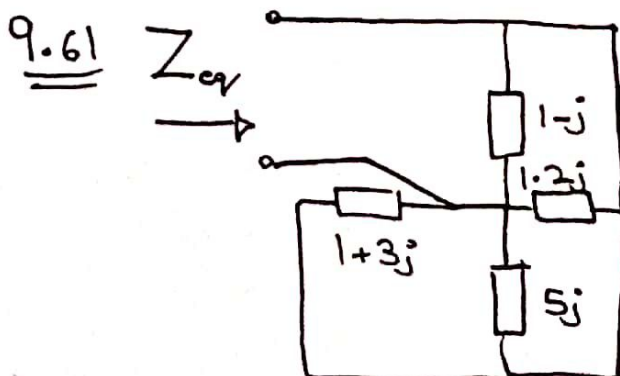

This can be redrawn as

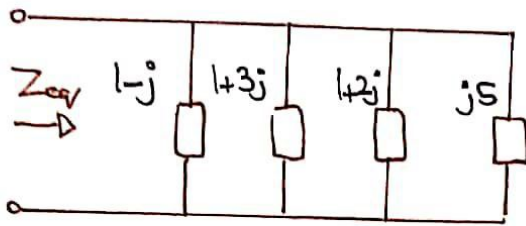

Hence, all are in parallel.

$$\begin{aligned} Z_{eq} &= \left(\frac{1}{1-j} + \frac{1}{1+j3} + \frac{1}{1+j2} + \frac{1}{j5} \right)^{-1} \\ &= \left(\frac{4}{5} - \frac{2}{5}j \right)^{-1} \\ &= 1 + j\frac{1}{2} \end{aligned}$$

$$\boxed{Z_{eq} = 1 + j0.5}$$