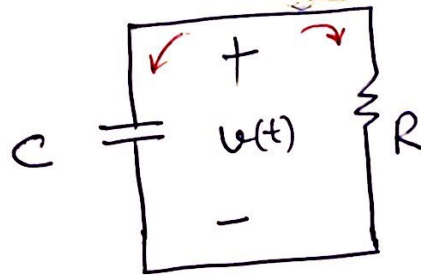


8.3 The Source-Free RC Circuit (PP 272 8th Ed HKD)

Consider the following circuit:-



Given $u(0) = V_0$

(Fig 8.15 A parallel RC circuit)

— Applying KCL (Sum of all currents leaving upper node is zero)

$$\text{So } C \frac{du}{dt} + \frac{u}{R} = 0$$

$$\text{or } \frac{du}{dt} + \frac{1}{RC} u = 0 \quad \text{--- (1)}$$

— Assume, the solution is:-

$$u(t) = A e^{s_1 t}$$

Taking derivative $\frac{du(t)}{dt} = A s_1 e^{s_1 t}$

— Putting in equation (1), it becomes

$$A s_1 e^{s_1 t} + \frac{1}{RC} A e^{s_1 t} = 0$$

————— contd

— contd (273)

$$\text{or } s_1 + \frac{1}{RC} = 0$$

$$\text{and } s_1 = -\frac{1}{RC}$$

— Now $u(t) = A e^{s_1 t}$

$$\text{so } u(0) = A = V_0$$

Hence the solution is:-

$$u(t) = V_0 e^{-\frac{1}{RC}t} \quad \text{Volts.}$$

Notice at $t=0$

$$u(0) = V_0$$

at $t = \infty$

$$u(t) \approx 0$$

— The time constant is found by noting the time at which the response has dropped to 37% of its initial value.

$$\text{so } \frac{\tau}{RC} = 1 \quad \text{because } e^{-1} = 0.36$$

$$\text{or } \tau = RC$$


— Recall that for an RL circuit,

$$\tau = \frac{L}{R}$$

————— contd

— contd (274)

The response curve can be sketched as:-

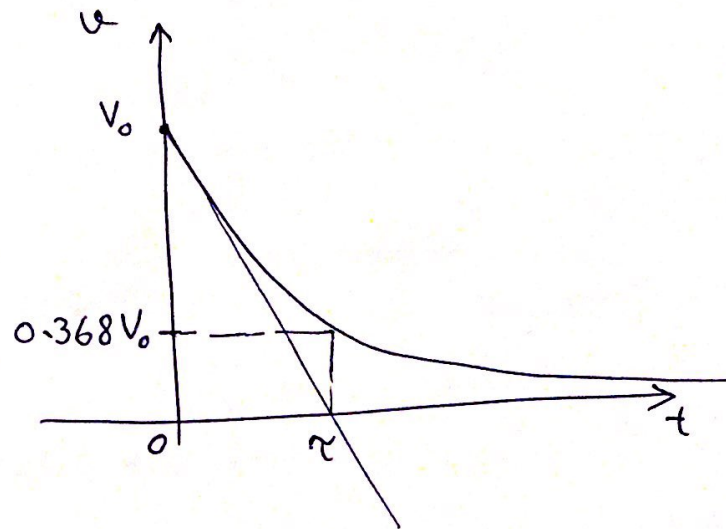

Slope:-

$$V(t) = V_0 e^{-\frac{t}{RC}}, \text{ volts}$$

$$\left. \frac{d \left(\frac{V(t)}{V_0} \right)}{dt} \right|_{t=0} = -\frac{1}{RC}$$

Now slope is equal to


$$m = \frac{y_2 - y_1}{x_2 - x_1}$$

$$m = \frac{0 - 1}{\tau - 0} = -\frac{1}{RC}$$

$$\tau = RC$$

The Source-Free RC circuit: Another approach (PP 220 6th Ed)

Consider the circuit:-

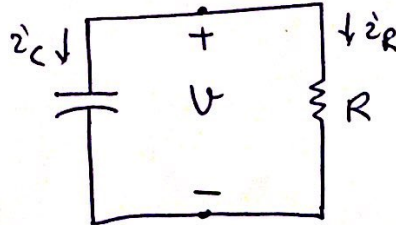

Assume at $t=0$, the initial voltage is:-

$$v(0) = V_0 \text{ volts}$$

— Applying KCL at top node:-

$$i_R + i_C = 0$$

$$\text{or } \frac{v}{R} + C \frac{dv}{dt} = 0 \quad \text{— (currents out of node)}$$

$$\text{So } \frac{dv}{v} = -\frac{1}{RC} dt$$

$$\text{Integrating; } \ln v = -\frac{t}{RC} + \ln A \quad (\ln A \text{ is constant of integration})$$

$$\text{or } \ln v - \ln A = -\frac{t}{RC}$$

$$\ln \frac{v}{A} = -\frac{t}{RC}$$

Anti-log

$$\frac{v(t)}{A} = e^{-\frac{t}{RC}}$$

$$\text{or } v(t) = A e^{-\frac{1}{RC}t}$$

$$\text{As } v(0) = A = V_0$$

$$\text{Therefore } v(t) = V_0 e^{-\frac{1}{RC}t}$$

— Exponentially decaying value of initial voltage. expre.

Note: If we choose i as the variable then

$$\frac{1}{C} \int_0^t i dt - v_0(t=0) + R i = 0$$

$$\text{or } \frac{1}{C} \times i + R \frac{di}{dt} = 0$$

$$\frac{v}{R} = i$$


$$\text{So } \frac{v}{RC} + \frac{dv}{dt} = 0$$

— M₃

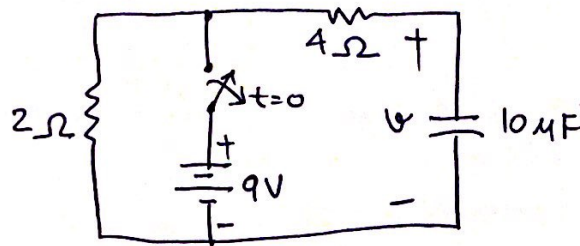Example 8.3 The Source-Free RC Circuit

(10 274 8th Ed HKD)

Find the voltage labeled ' v ' at $t = 200 \text{ ns}$.




Solution: To determine ' v ' we need to draw and

analyze: — one circuit corresponding to before the switch is thrown and

— another circuit corresponding to after the switch is thrown.

— The purpose of analyzing the circuit for $t \leq 0$ is to obtain initial capacitor voltage.

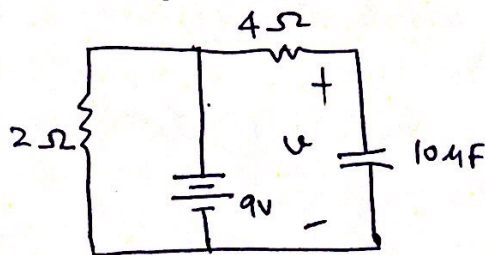— The circuit for $t \leq 0$ is: {Note $t \leq 0$ }




— we assume the transients died long time ago, so we have a purely DC circuit.

— By inspection $v(0) = 9 \text{ V}$

_____ contd

— contd (274)

— Now the circuit for $t \geq 0$ is:

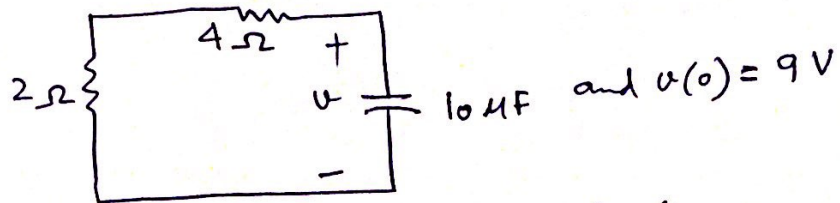

— We recognize that the time constant:

$$\tau = R_{eq}C = (2+4)(10 \times 10^{-6})$$

$$\tau = 60 \times 10^{-6} \text{ s}$$

— We also know that for the source-free circuit, the response is of the form

$$v(t) = V_0 e^{-t/\tau}$$

$$\text{where } V_0 = v(0) = 9 \text{ V}$$

$$\text{So } v(t) = 9 e^{-\frac{t}{60 \times 10^{-6}}} \text{ V}$$

$$\text{— At } t = 200 \mu\text{s} \quad v(200 \mu\text{s}) = 9 e^{-\frac{200 \times 10^{-6}}{60 \times 10^{-6}}} \text{ V}$$

$$\text{or } v(200 \mu\text{s}) = 9 e^{-\frac{10}{3}} \text{ V}$$

$$= 9 \times 0.03567$$

$$= 321.1 \text{ mV}$$