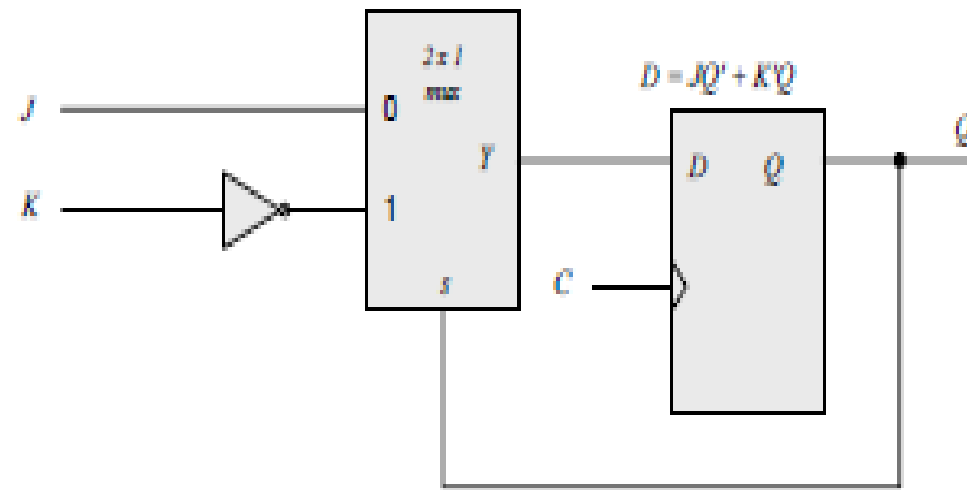


Chapter5-Synchronous Sequential Logic

Lecture8- Problem Solving Session

5-2: Construct a JK flip-flop using a D flip-flop, a two-to-one line multiplexer, and an inverter

Solution:




5-4: A PN flip-flop has four operations, clear to 0, no change, complement, and set to 1, when inputs P and N are 00, 01, 10, and 11 respectively.

- a) Tabulate the characteristic table
- b) Derive the characteristic equation
- c) Tabulate the excitation table
- d) Show how the PN flip-flop can be converted to a D flip-flop

Solution:

(a)	P	N	$Q(t+1)$
	0	0	0
	0	1	$\underline{Q(t)}$
	1	0	$\underline{Q'(t)}$
	1	1	1

(b)	P	N	$Q(t)$	$Q(t+1)$
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	1
	1	0	0	1
	1	0	1	0
	1	1	0	1
	1	1	1	1

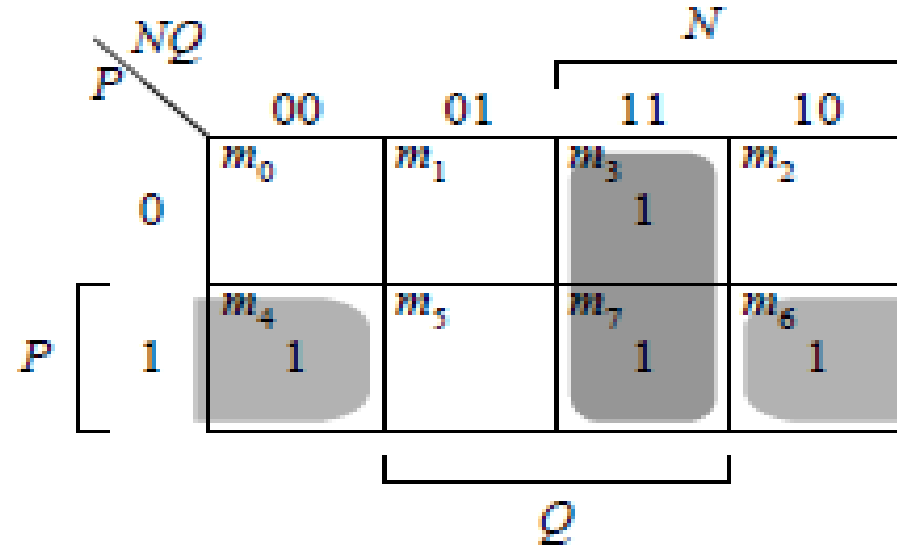

$$Q(t+1) = PQ' + NQ$$

(c)

$Q(t)$	$Q(t+1)$	P	N
0	0	0	x
0	1	1	x
1	0	x	0
1	1	x	1

(d) Connect P and N together.

5-8: Derive the state table and the state diagram of the sequential circuit shown in Fig5-8. Explain the function that the circuit performs.

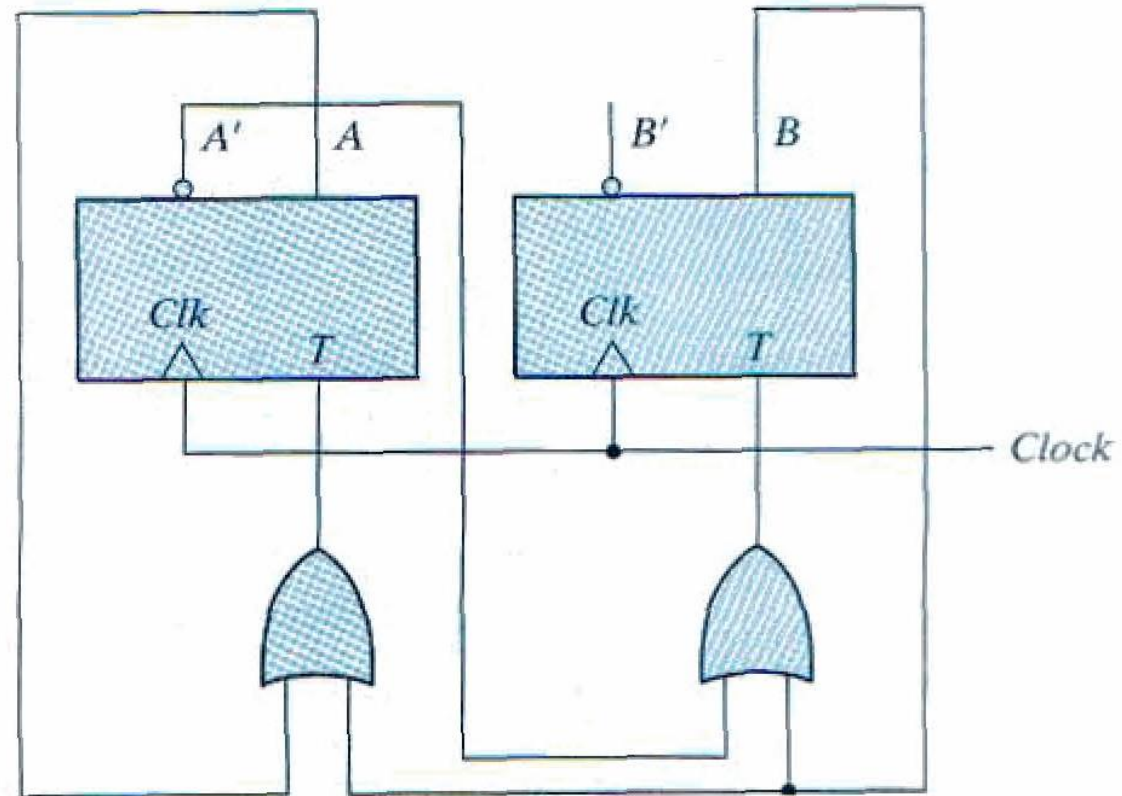


FIGURE P5.8

Solution:


A counter with a repeated sequence of 00, 01, 10.

<i>Present state</i>		<i>Next state</i>		<i>FF Inputs</i>	
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>T_A</i>	<i>T_B</i>
0	0	0	0	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

$$T_A = A + B$$

$$T_B = A' + B$$

Repeated sequence:

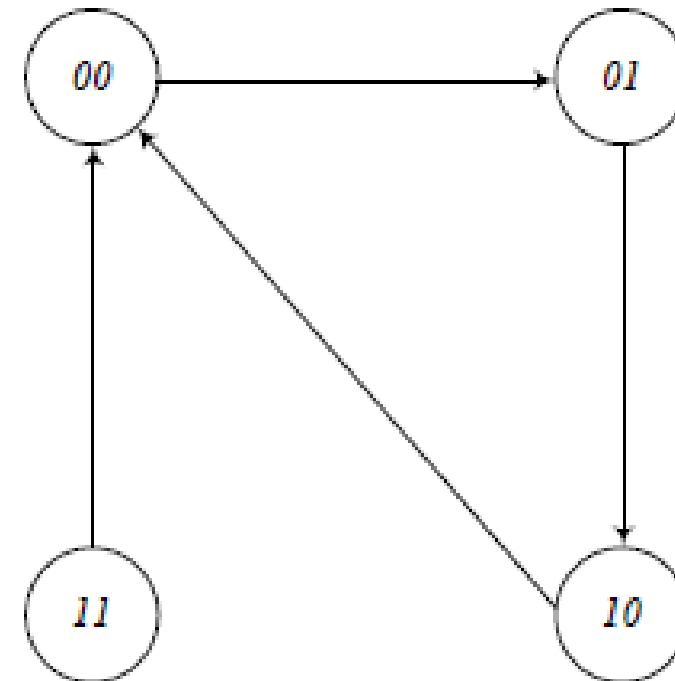

Problem5-10: A sequential circuit has two JK flip-flops, two inputs x and y, and one output z. The flip-flop input equations and circuit output equations are

$$J_A = Bx + B'x'$$

$$K_A = B'xy'$$

$$J_B = A'x$$

$$K_B = A + xy'$$

$$Z = Ax'y' + Bx'y'$$

Solution:

(b)

<i>Present state</i>		<i>Inputs</i>		<i>Next state</i>		<i>Output</i>	<i>FF Outputs</i>			
<i>A</i>	<i>B</i>	<i>x</i>	<i>y</i>	<i>A</i>	<i>B</i>	<i>z</i>	<i>J_A</i>	<i>K_A</i>	<i>J_A</i>	<i>J_B</i>
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	1	0	1	0
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1
1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	1	1	0	0	1

(c) State Equations of A and B

$$A(t+1) = J_A A' + K_A' A$$

$$= (Bx + B'y')A' + (B'xy')'A$$

$$= A'Bx + A'B'y' + AB + Ax' + Ay$$

$$= Bx + A'B'y' + AB + Ax' + Ay$$

$$= Bx + A'B'y' + Ax' + Ay$$

$$B(t+1) = J_B B' + K_B' B$$

$$= A'xB' + (A+xy')'B$$

$$= A'B'x + A'Bx' + A'By$$

Problem 5-12: Reduce the number of states in the following state table, and tabulate the reduced state table.


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

Solution:


Present state	Next state		Output	
	0	1	0	1
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>a</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>d</i>	0	1

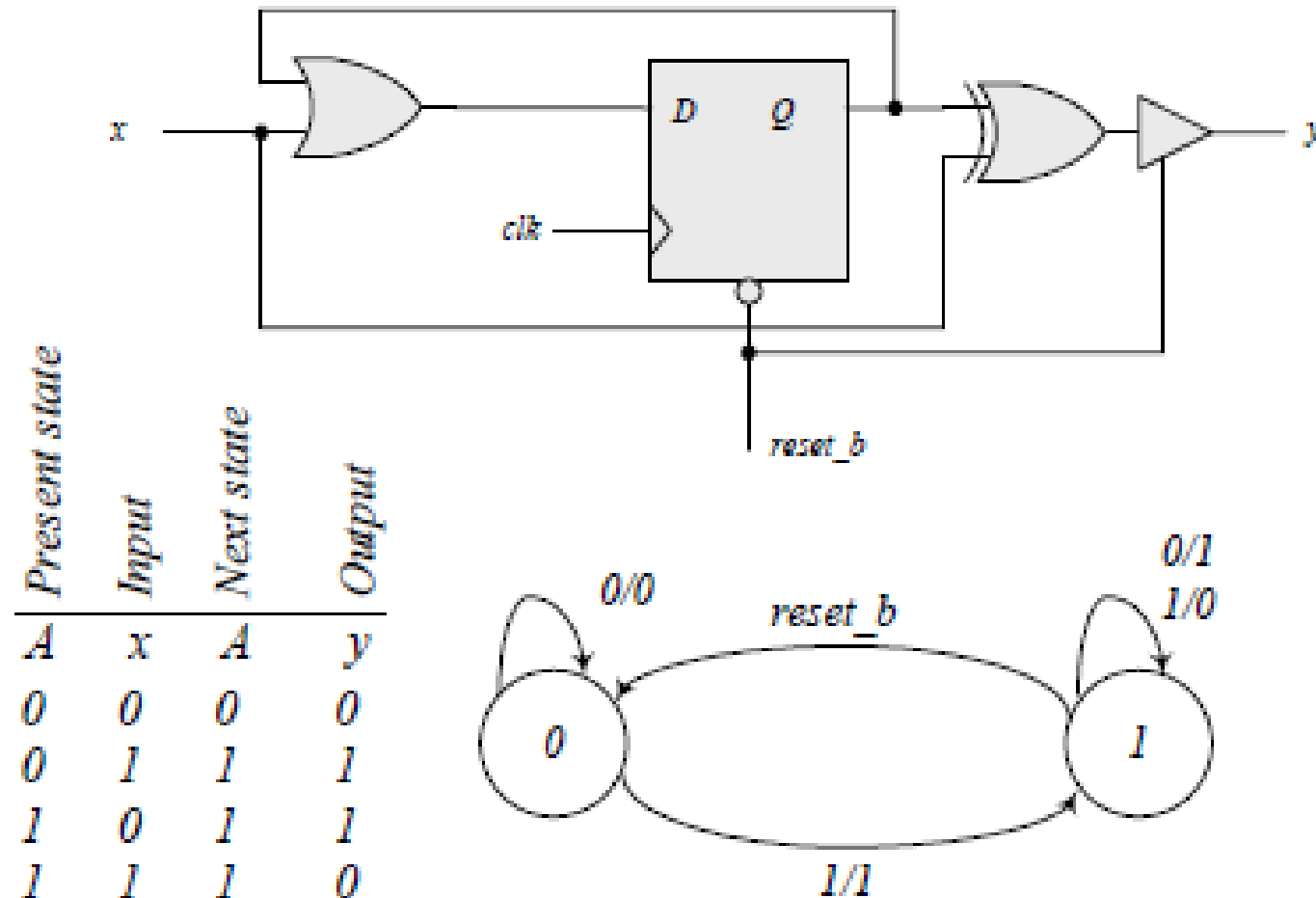Problem 5-17:


Design a one-input, one-output serial 2's complementer. The circuit accepts a string of bits from the input and generates the 2's complement at the output. The circuit can be reset asynchronously to start and end the operation.



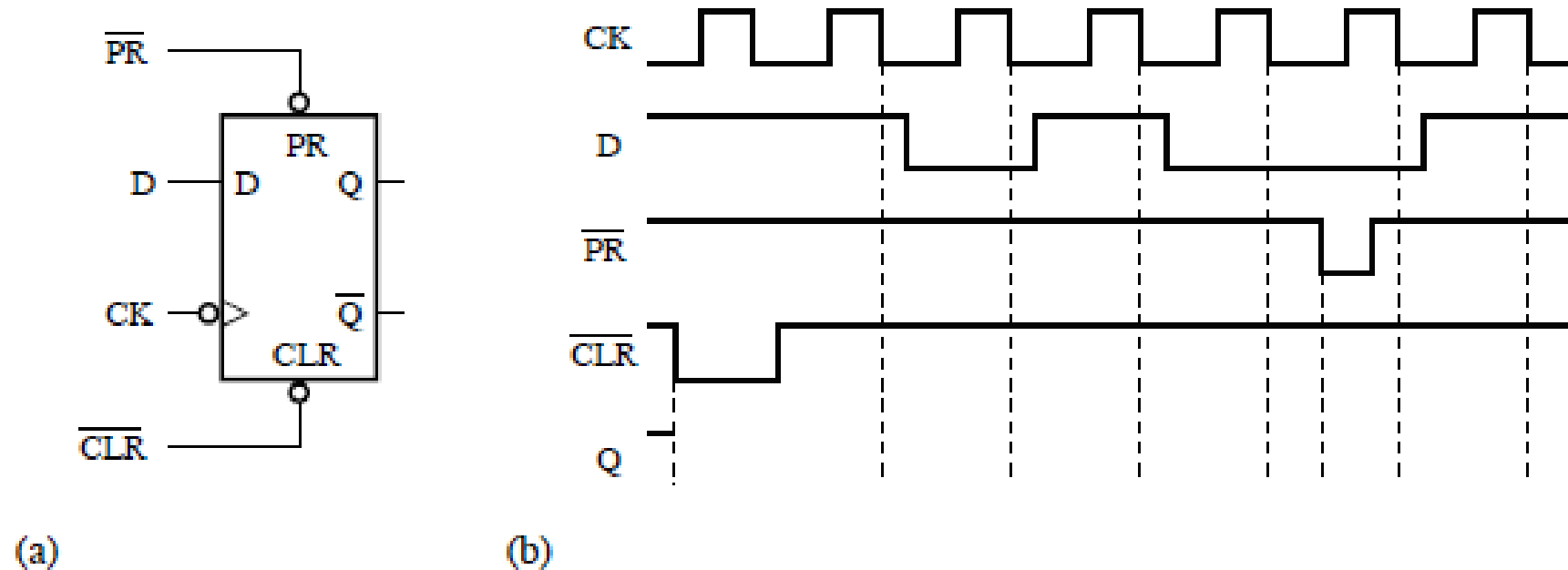
Problem: The logic circuit for a D flip-flop with asynchronous inputs is represented in the following Figure (a). Complete the timing diagram in Figure (b).



Solution:

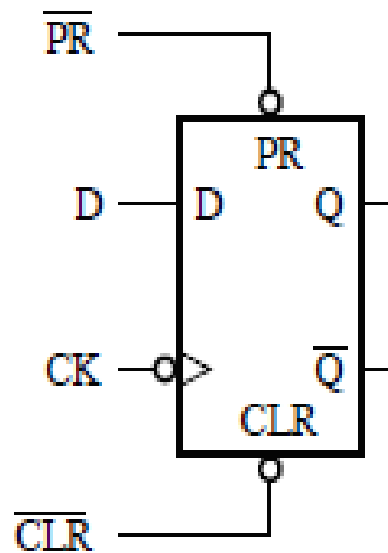

(a)

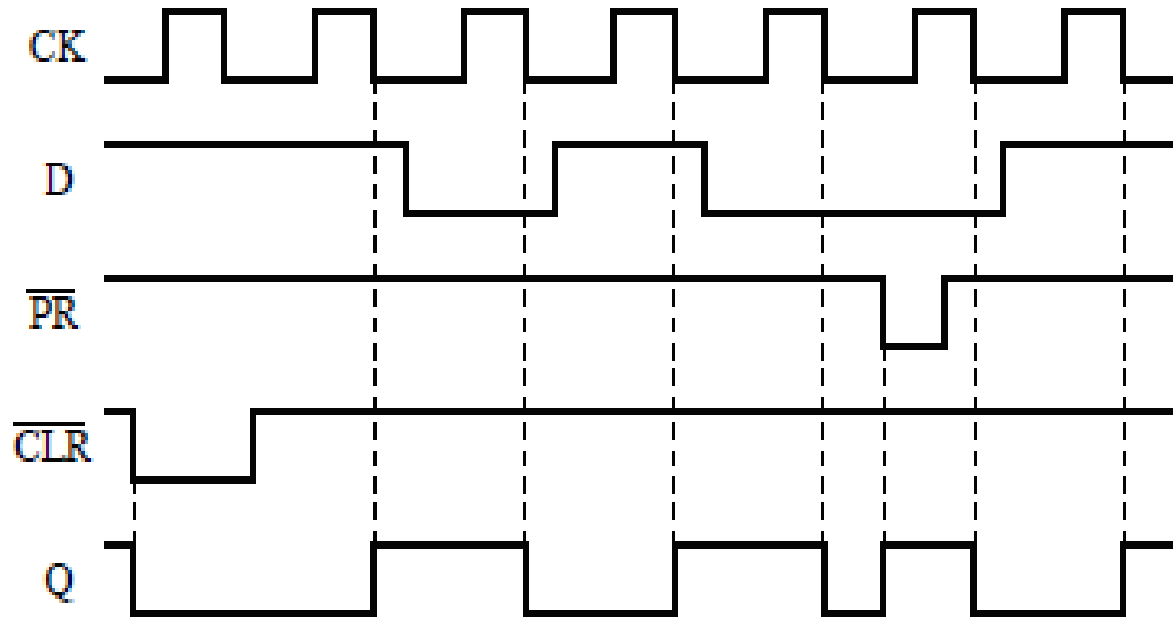

(b)

The End