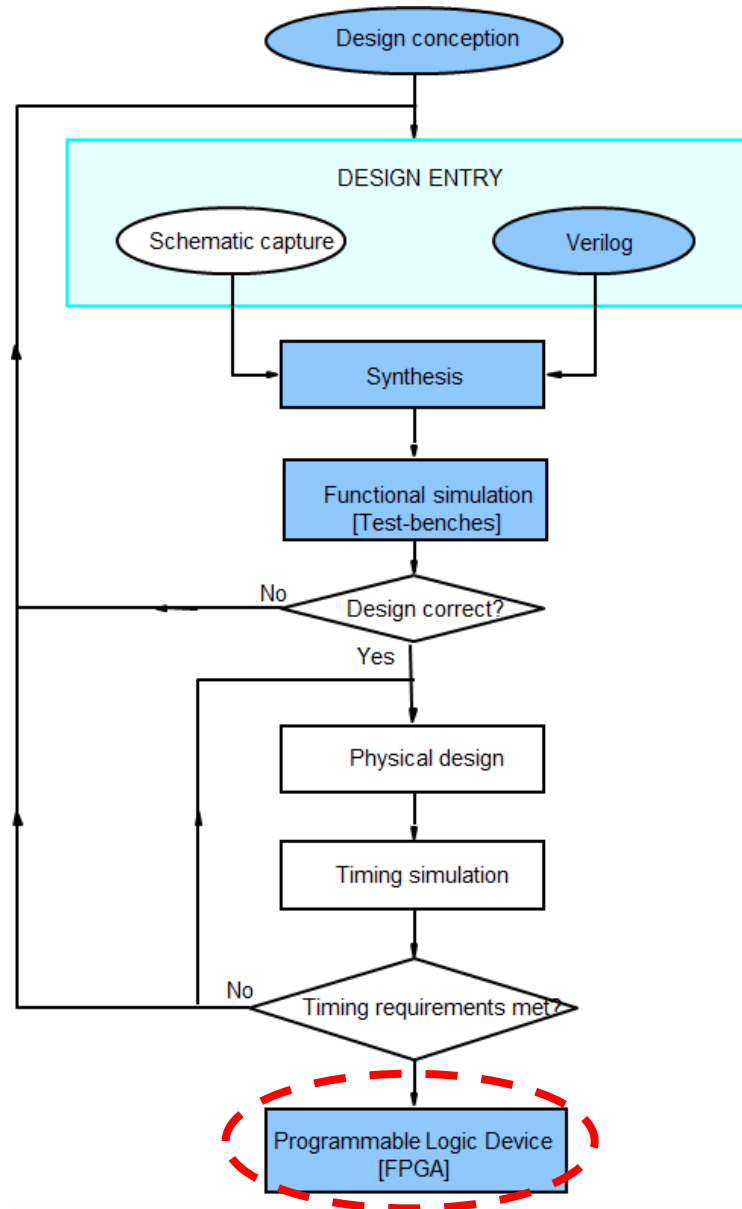


EE-421: Digital System Design



Programmable Logic Devices

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]


Where are we Heading?



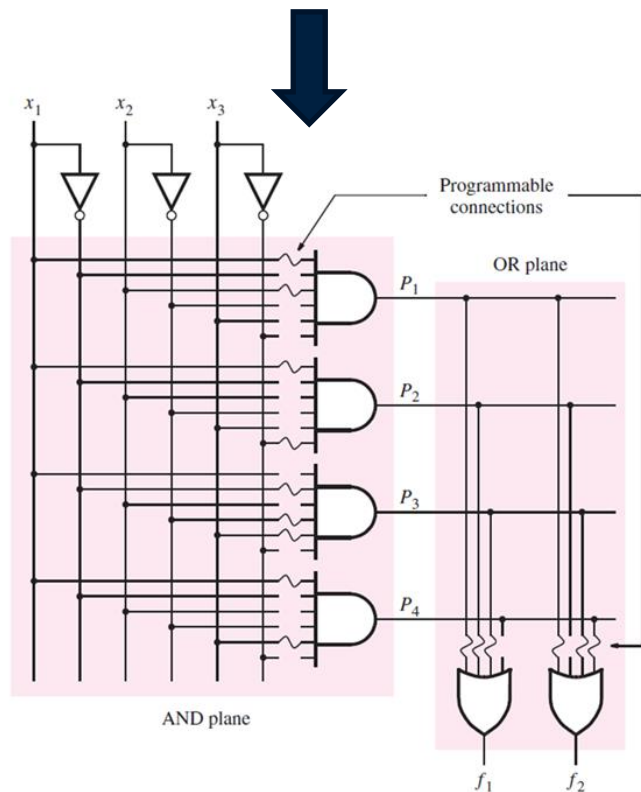 Programmable Logic Devices (computing platforms):



How did we get here?

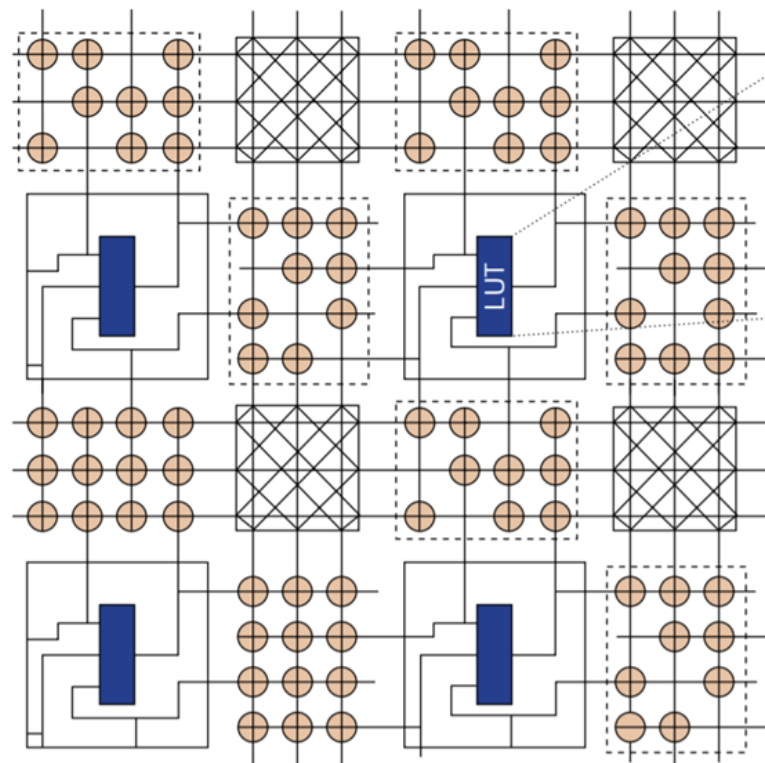


Review: SOP and POS

Type of Circuits

- *Digital Systems* consist of two basic types of circuits:
 - **Combinational Logic (CL)**
 - Output is a function of the inputs only, not the history of its execution
 - e.g. circuits to add A, B (ALUs)
 - **Sequential Logic (SL)**
 - Circuits that “remember” or store information
 - a.k.a. “State Elements”
 - e.g. memory and registers (Registers)

Converting Combinational Logic

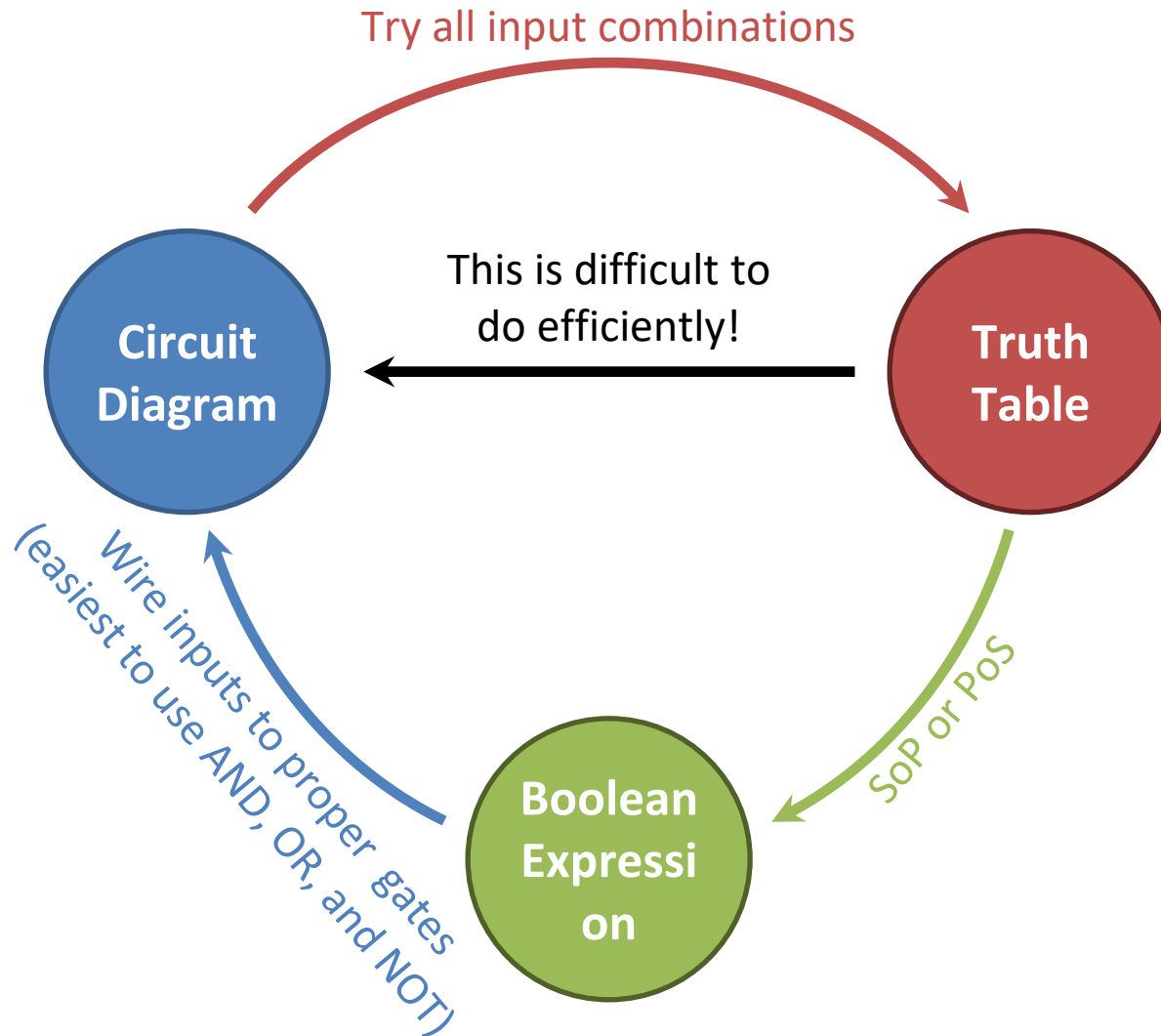

Representations of Combinational Logic

- ✓ Text Description
- ✓ Circuit Diagram
 - Transistors and wires
 - Logic Gates
- ✓ Truth Table
- ✓ Boolean Expression
- ✓ *All are equivalent*

Three Variable Minterms and Maxterms

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \overline{x}_1 \overline{x}_2 \overline{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \overline{x}_1 \overline{x}_2 x_3$	$M_1 = x_1 + x_2 + \overline{x}_3$
2	0	1	0	$m_2 = \overline{x}_1 x_2 \overline{x}_3$	$M_2 = x_1 + \overline{x}_2 + x_3$
3	0	1	1	$m_3 = \overline{x}_1 x_2 x_3$	$M_3 = x_1 + \overline{x}_2 + \overline{x}_3$
4	1	0	0	$m_4 = x_1 \overline{x}_2 \overline{x}_3$	$M_4 = \overline{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \overline{x}_2 x_3$	$M_5 = \overline{x}_1 + x_2 + \overline{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \overline{x}_3$	$M_6 = \overline{x}_1 + \overline{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \overline{x}_1 + \overline{x}_2 + \overline{x}_3$


Activity: A Three-Variable Function

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

- What is the function f ?
- Draw the logic circuit

Activity Answer


- $f = x_1'x_2' + x_1'x_2 + x_1x_2$

 


- How would you implement the above circuit in HW?

Standard Chips

Review: Standard Chips

 


(a) Dual-inline package

 

(b) Structure of 7404 chip


Review: Standard Chips

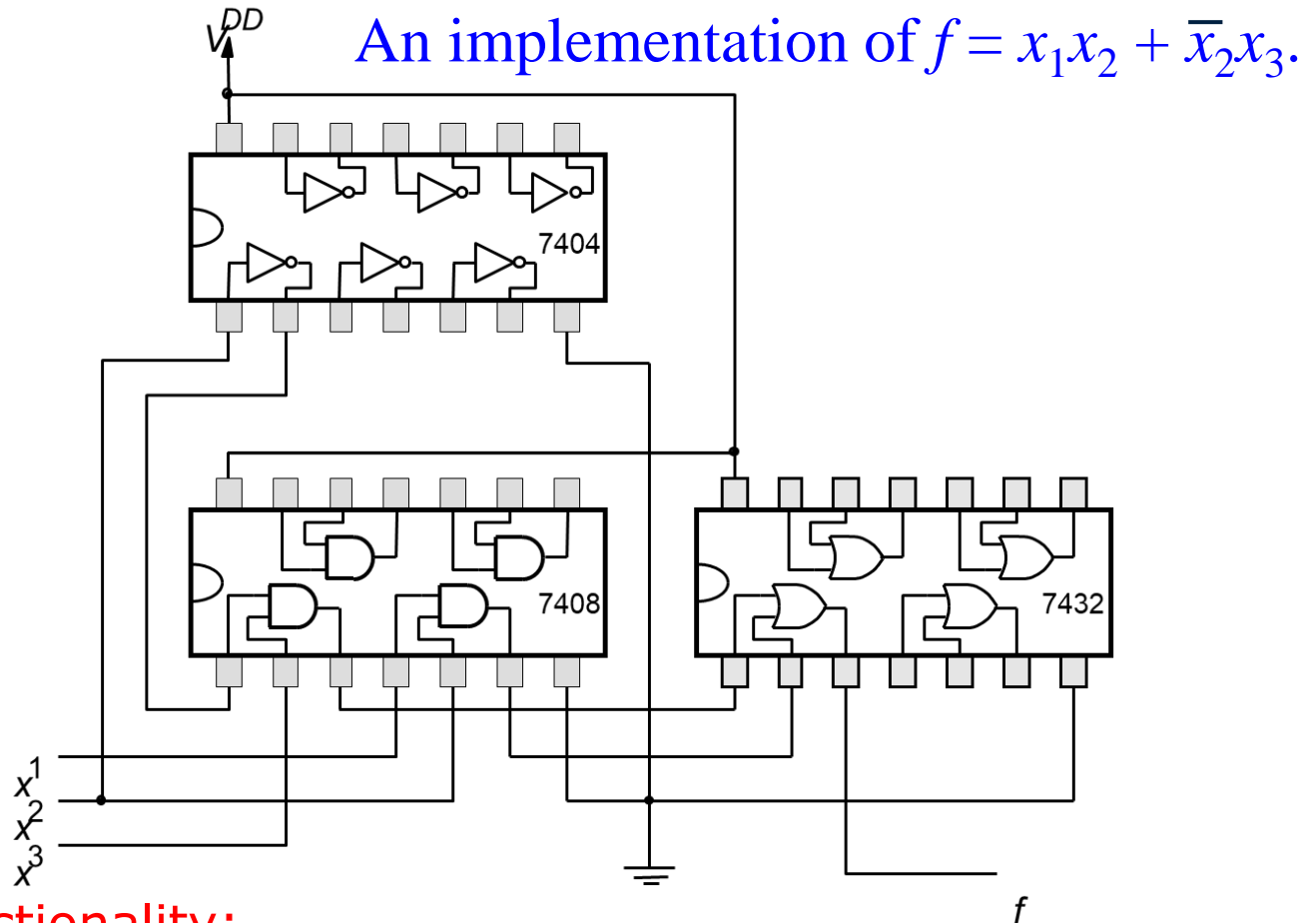

- Limitations:
 - Fixed functionality:
 - Cannot be tailored to suit a particular design situation
 - Each chip contains only a few logic gates:
 - Inefficient for building large circuits

Programmable Logic Devices: PLA, PAL, CPLD and FPGA


Programmable Logic Devices (PLD)

 


- PLD as a black box: (introduced in 1970s)
 - Inside: *Logic gates and Programmable Switches*
 - customizable in different ways -> *programmable switches* that allow the internal circuitry in the chip to be configured in many different ways.
 - The switches are programmed by the end user, rather than when the chip is manufactured !!

Programmable Logic Array (PLA)

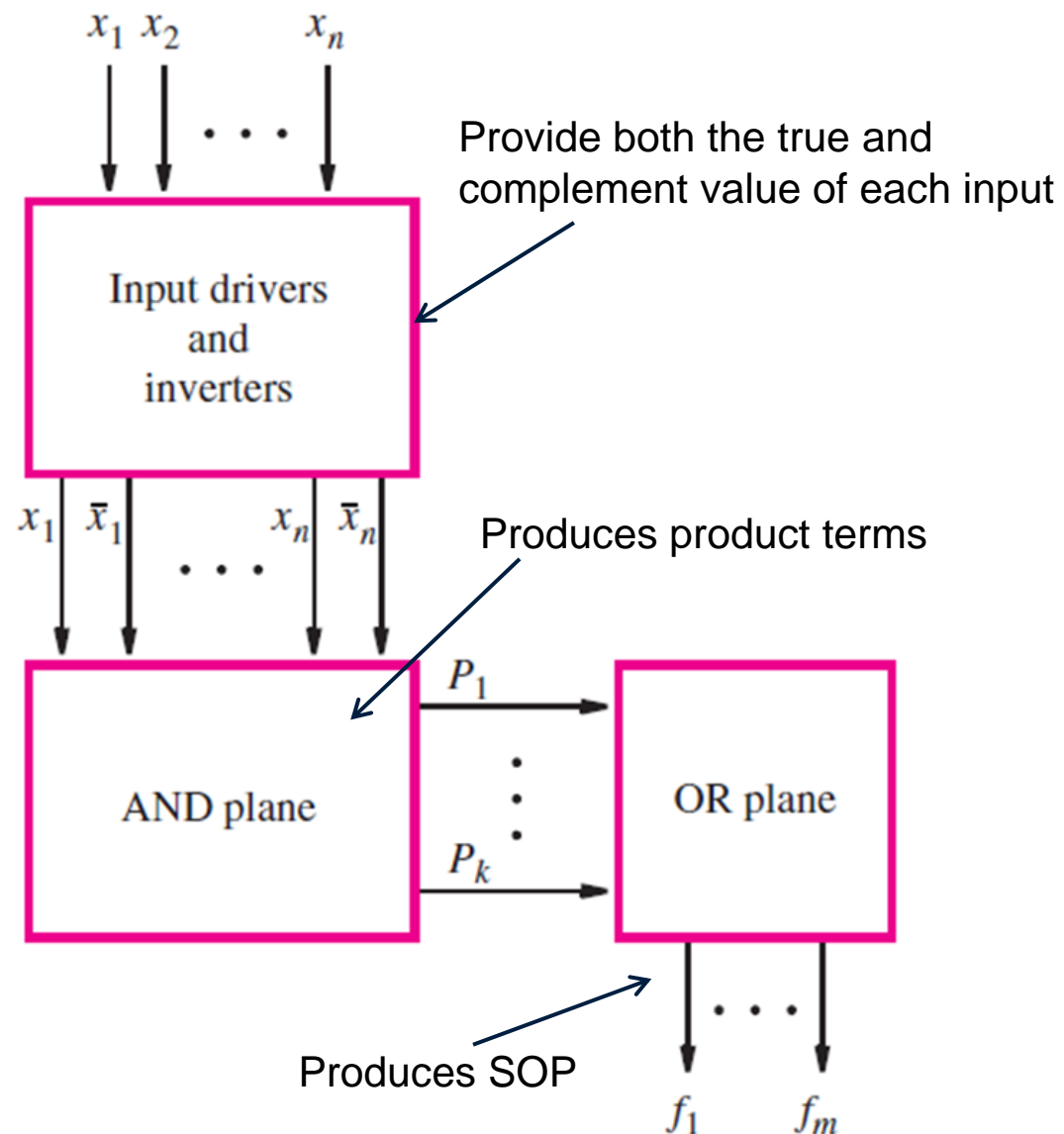- Based on the idea:
 - Logic function can be realized in SOP form*




Inside PLA

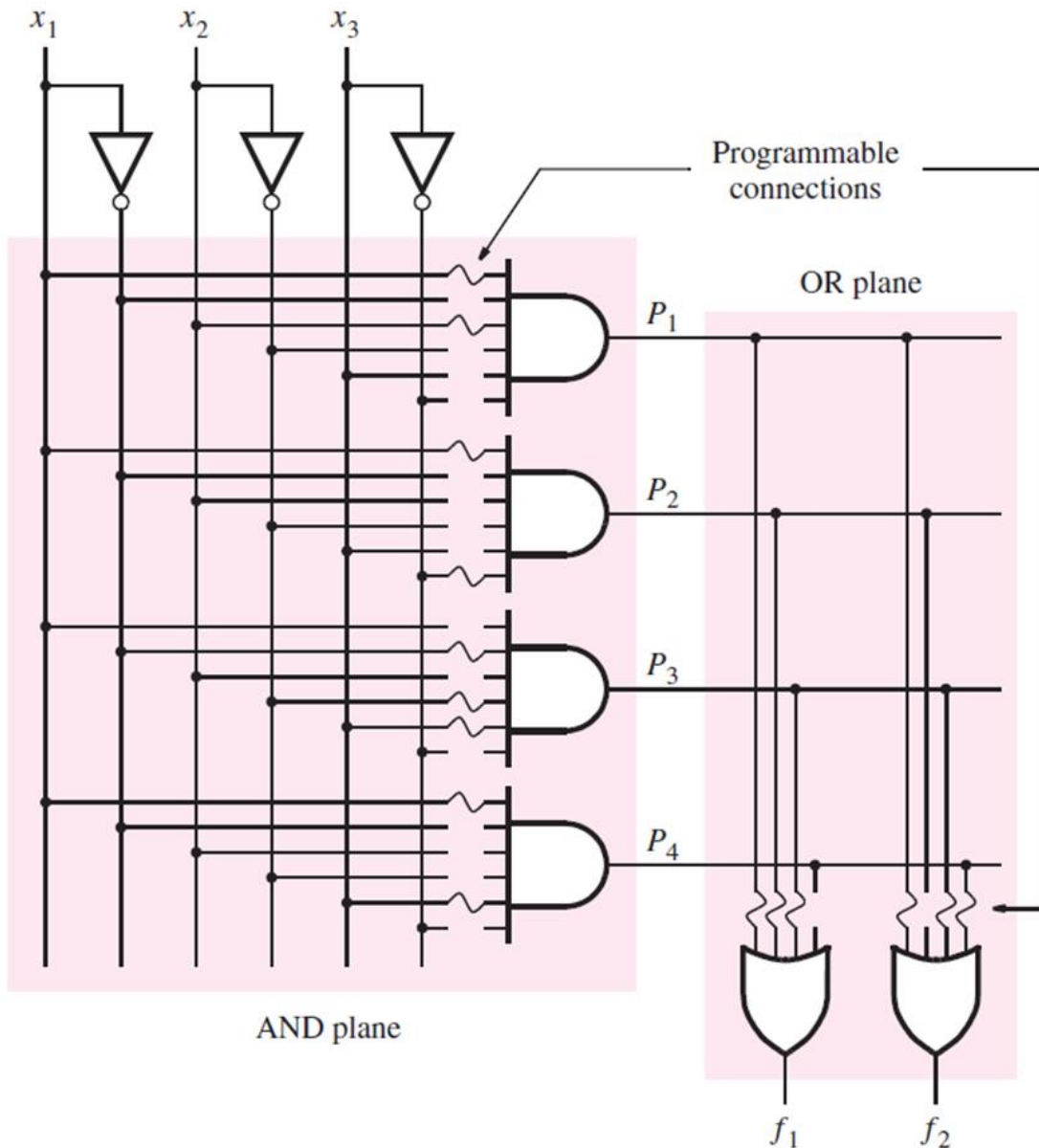


- Programming AND and OR planes differently could implement various functions.
 - Constraints:
 - size of AND/OR planes
- What is f_1 and f_2 ?
- $f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$.
- $f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$

Customary Schematic of PLA

 


- Programming AND and OR planes differently could implement various functions.
 - Constraints:
 - size of AND/OR planes
- Typical commercially available PLAs:
 - 16-inputs
 - 32 product terms
 - 8 outputs

Limitations of PLA

 

- Historically, the programmable switches presented two difficulties for manufacturers of these devices:
 - they were hard to fabricate correctly, and
 - they reduced the speed performance of circuits implemented in the PLAs.
- Both programmable planes occupy larger area

Programmable Array Logic (PAL)

 

- AND plane: Programmable
- OR plane: **Fixed**
- Less flexible than PLA but improved speed-performance
- What is f_1 and f_2 ?


$$f_1 = x_1x_2\bar{x}_3 + \bar{x}_1x_2x_3$$

$$f_2 = \bar{x}_1\bar{x}_2 + x_1x_2x_3$$

Programming of PLAs and PALs

- Commercial PAL and PLA chips contain a few thousand programmable switches:
 - not feasible for a user to specify manually
- CAD systems are employed for this purpose:
 - Generate a file, known as *Programming File/Fuse Map*
 - specifies the state of each programmable switch

Programming of PLAs and PALs

 


A Plastic Lead PLCC package with socket.

Programmable Logic Devices [CPLD]

Why CPLD?


- PLAs and PALs are useful for implementing a wide variety of small digital circuits:
 - Each device can be used to implement circuits that do not require more than:
 - the number of inputs,
 - product terms, and
 - outputs that are provided in the particular chip.
- These chips are limited to fairly modest sizes:
 - typically supporting a combined number of inputs plus outputs of not more than 32!

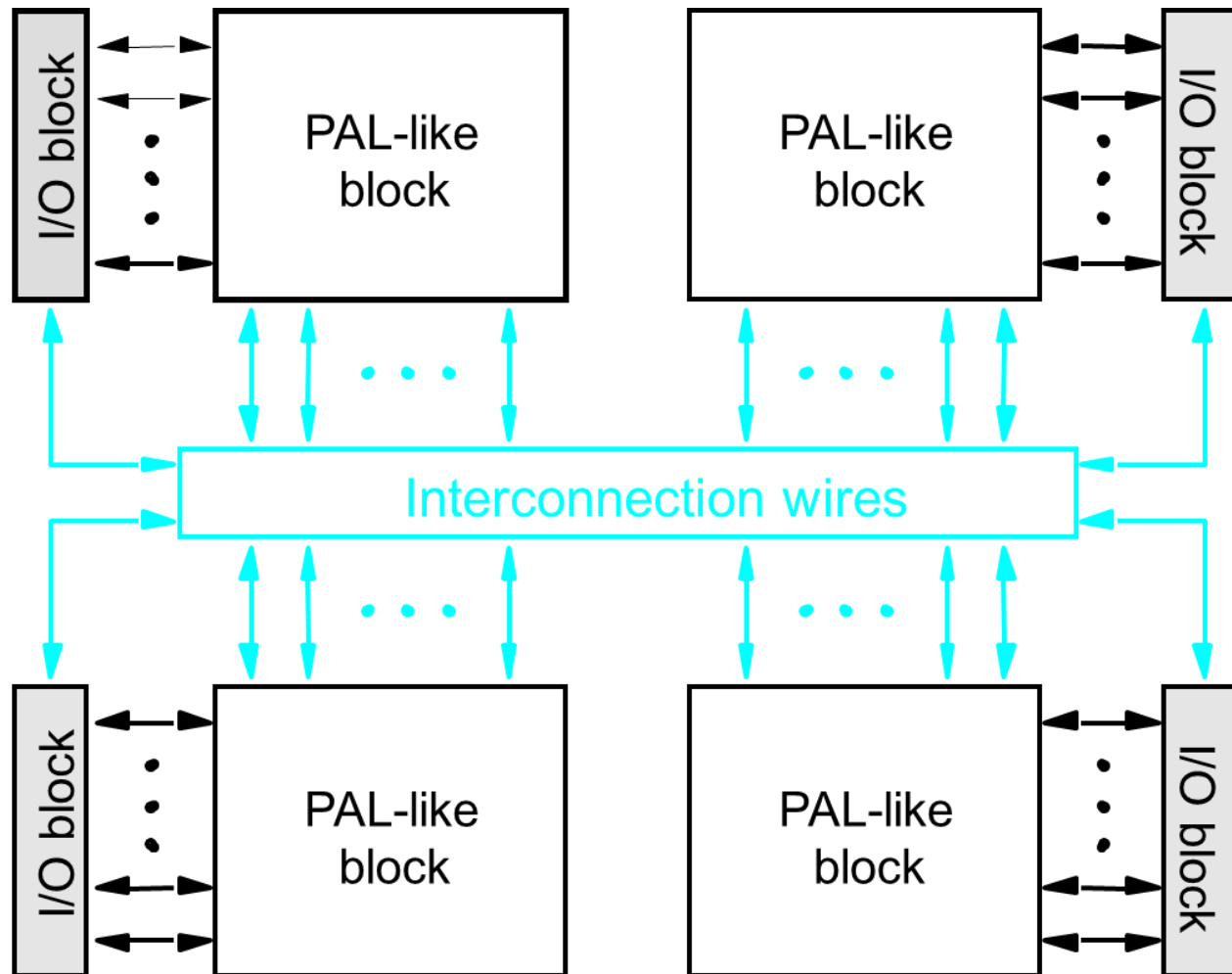Complex Programmable Logic Devices (CPLDs) - Structure




- Commercial CPLDs range in size from only 2 PAL-like blocks to more than 100 PAL-like blocks


CPLD – Inside PAL-like Block

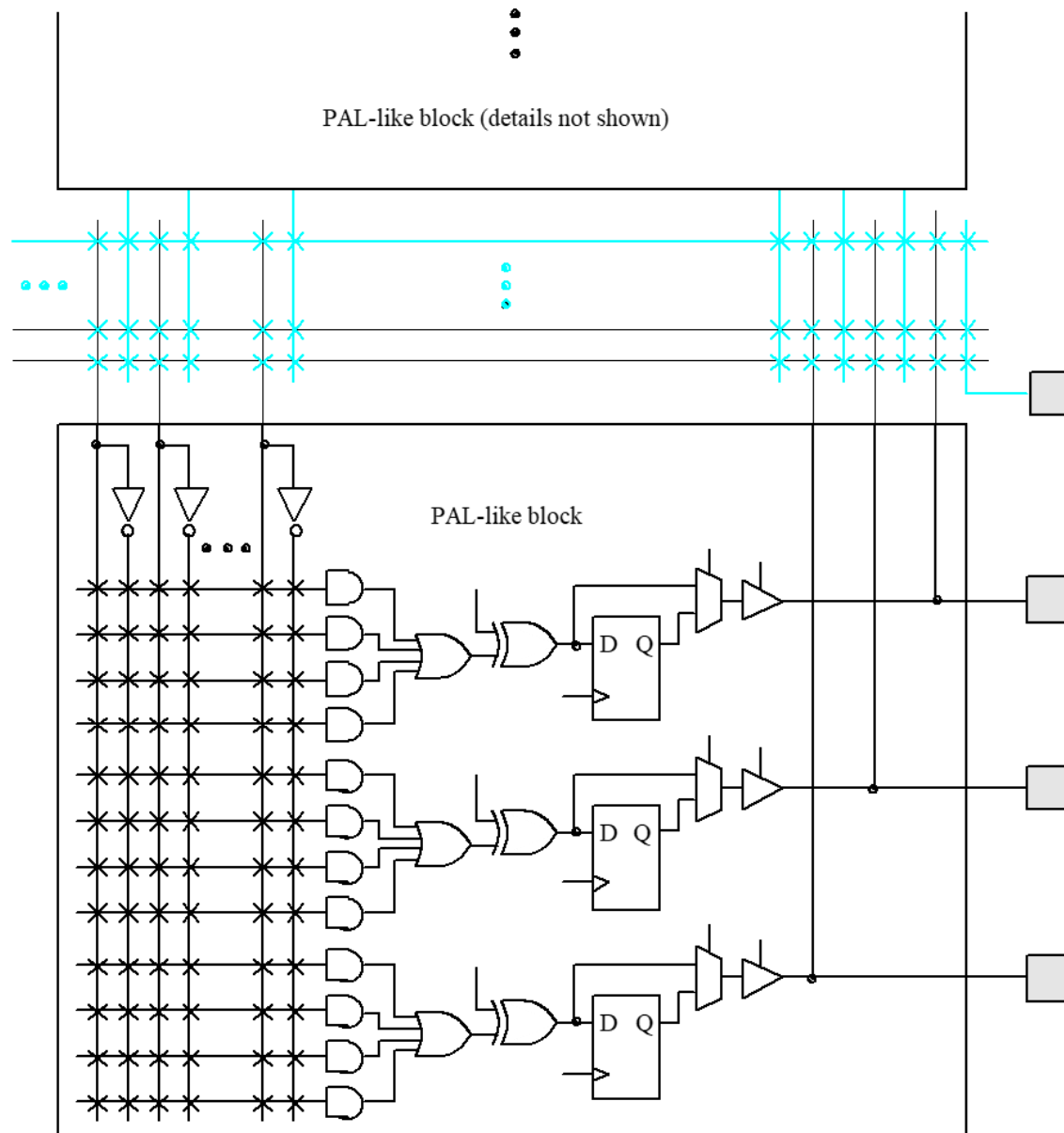

CPLD Programming

 

 (a) CPLD in a Quad Flat Pack (QFP) package




(b) JTAG programming

- Quad Flat Package (QFP) pins are much thinner than those on a PLCC:
 - programmed through In-System Programming (ISP) technique
 - Circuitry for ISP is Standardized by IEEE and is called JTAG port
 - (JTAG = Joint Test Access Group)

Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **Stephen Brown** and **Zvonko Vranesic**. [**S&Z**]
 - S&Z,
 - Appendix-B
 - B.5 to B.8



THANK YOU

