

EE-421: Digital System Design

Doing MATHS on an FPGA

Arithmetic Circuits: Serial Multiplier
(aka Shift-and-Add Multiplier)

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

FPGA Implementation of a Combinational Multiplier

- In Verilog:

$$\mathbf{P} = \mathbf{A} * \mathbf{B};$$

(make sure **P** has twice the number of bits of **A** and **B**)

- Synthesis tool will create a combinational multiplier if DSP Block inference is turned off.

F_{\max} of a Combinational Multiplier

- Measured on our Cyclone FPGA:

Multiplier Width (in bits)	F_{\max} (MHz)
8 x 8	464
16 x 16	396
32 x 32	104
64 x 64	66

Serial (Multi-cycle) Multiplier

Multi Cycle Multiplier

How do you multiply by hand?

$$\begin{array}{r} 1101 \quad A \\ \times 1011 \quad B \\ \hline 1101 \\ 11010 \\ 000000 \\ + 1101000 \\ \hline 10001111 \quad P \end{array}$$

One Possible Algorithm

	1101	A
×	1011	B
<hr/>		
	1101	
	11010	
	000000	
+	1101000	
<hr/>		
	10001111	P

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Note: This is NOT Verilog

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

				1	1	0	1
--	--	--	--	---	---	---	---

A

1	0	1	1
---	---	---	---

B

0

P_{old}

							0
--	--	--	--	--	--	--	---

P

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

				1	1	0	1
--	--	--	--	---	---	---	---

A

1	0	1	1
---	---	---	---

B

0

P_{old}

							0
--	--	--	--	--	--	--	---


P

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```


Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

 


```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

 


```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

 


```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

 

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Example

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

		1	1	0	1	0	0	A
+					1	1	0	P_{old}
<hr/>								
		1	0	0	1	1	1	P

0	0	1	0	B
---	---	---	---	----------

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Continue until B is ZERO

Final Result

$$13 \times 11 = 143$$

$$1101 \times 1011 = 10001111$$

1	1	0	1	0	0	0	0
---	---	---	---	---	---	---	---

A

0	0	0	0
---	---	---	---

B

0

P_{old}

1	0	0	0	1	1	1	1
---	---	---	---	---	---	---	---

P


```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

Alternate Algorithm Representation

```
P = 0
while B != 0:
    if B(0) == 1:
        P = P + A
    A = A << 1
    B = B >> 1
```

```
 $P = 0$  ;
for  $i = 0$  to  $n - 1$  do
    if  $b_i = 1$  then
         $P = P + A$  ;
    end if;
    Left-shift  $A$  ;
end for;
```


Top – Level Schematic

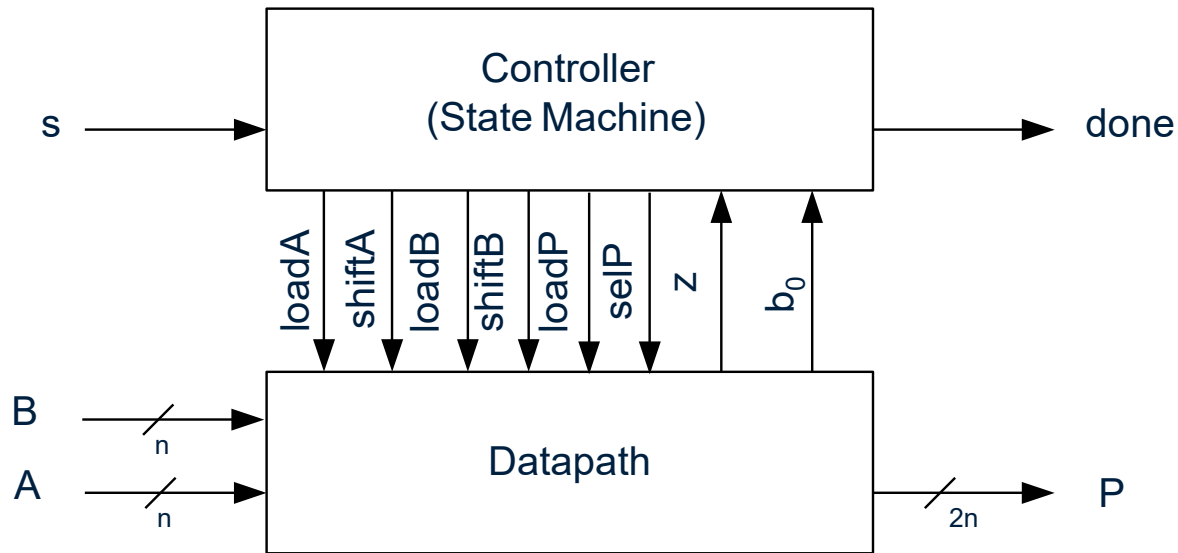


When **s** goes high, **n**-bit values are available on **A** and **B**.

The machine then multiplies, and when it is finished, asserts **done** and puts the result on **P**.

It then waits for **s** to go low.


Datapath

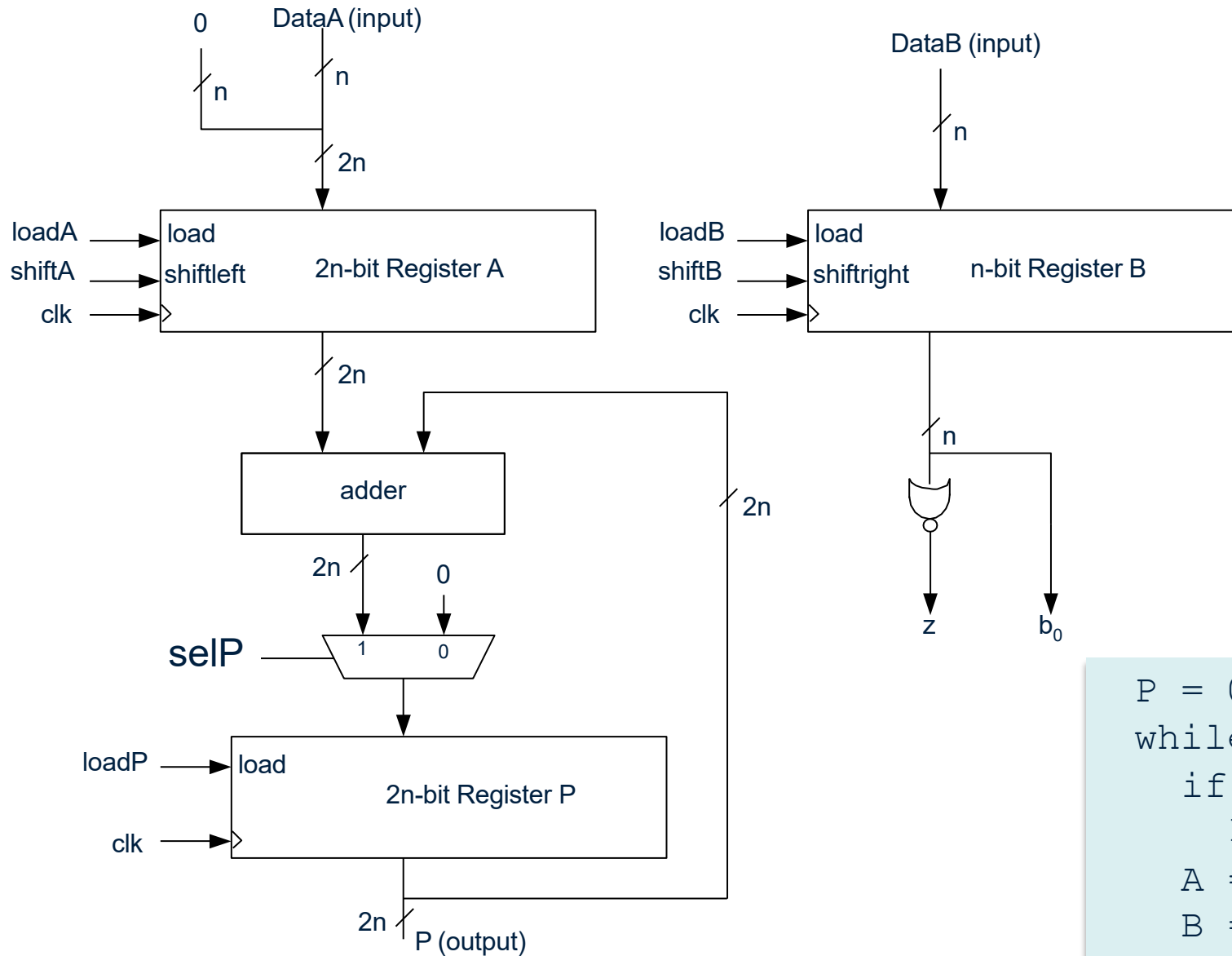



```

P = 0
while B != 0
    if B(0) == 1
        P = P + A
    A = A << 1
    B = B >> 1
    
```


Controlpath

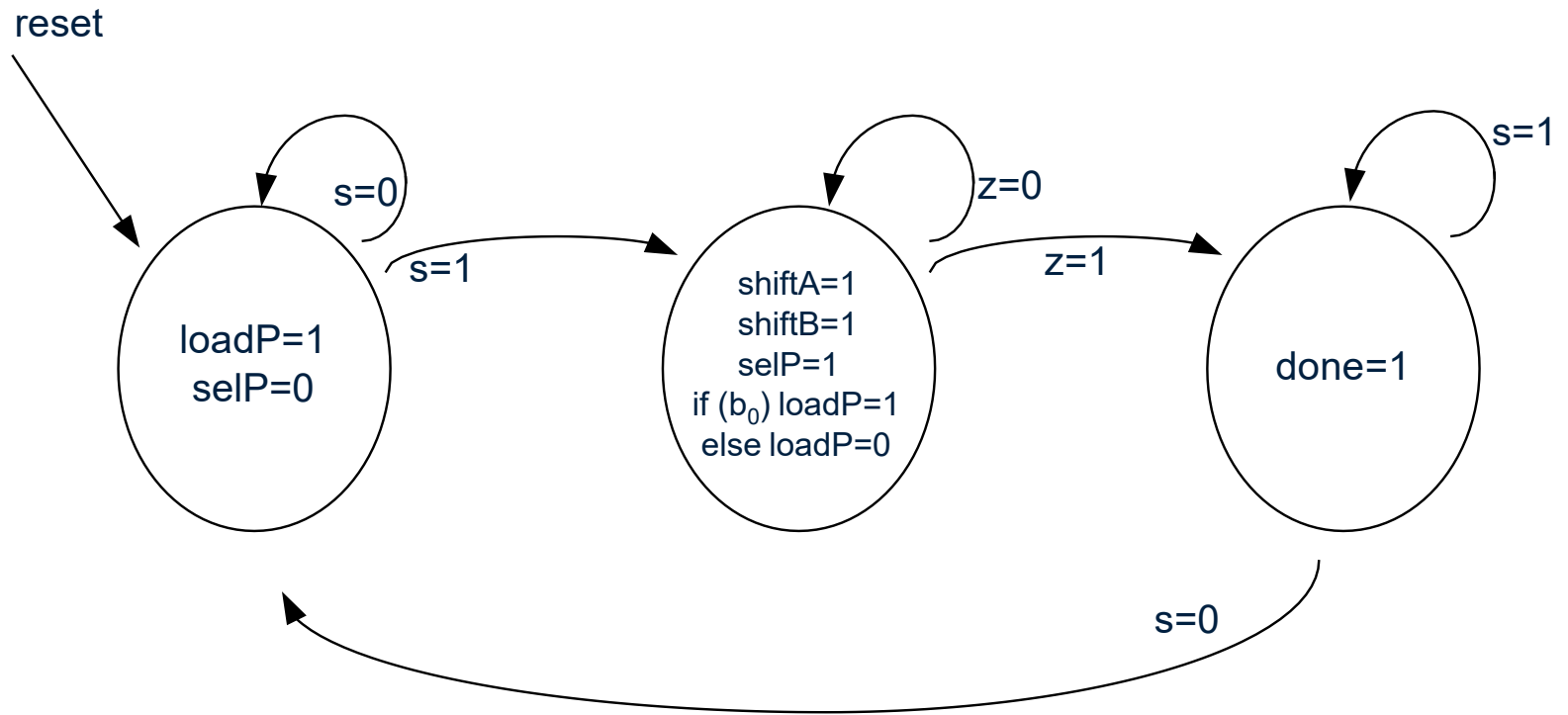

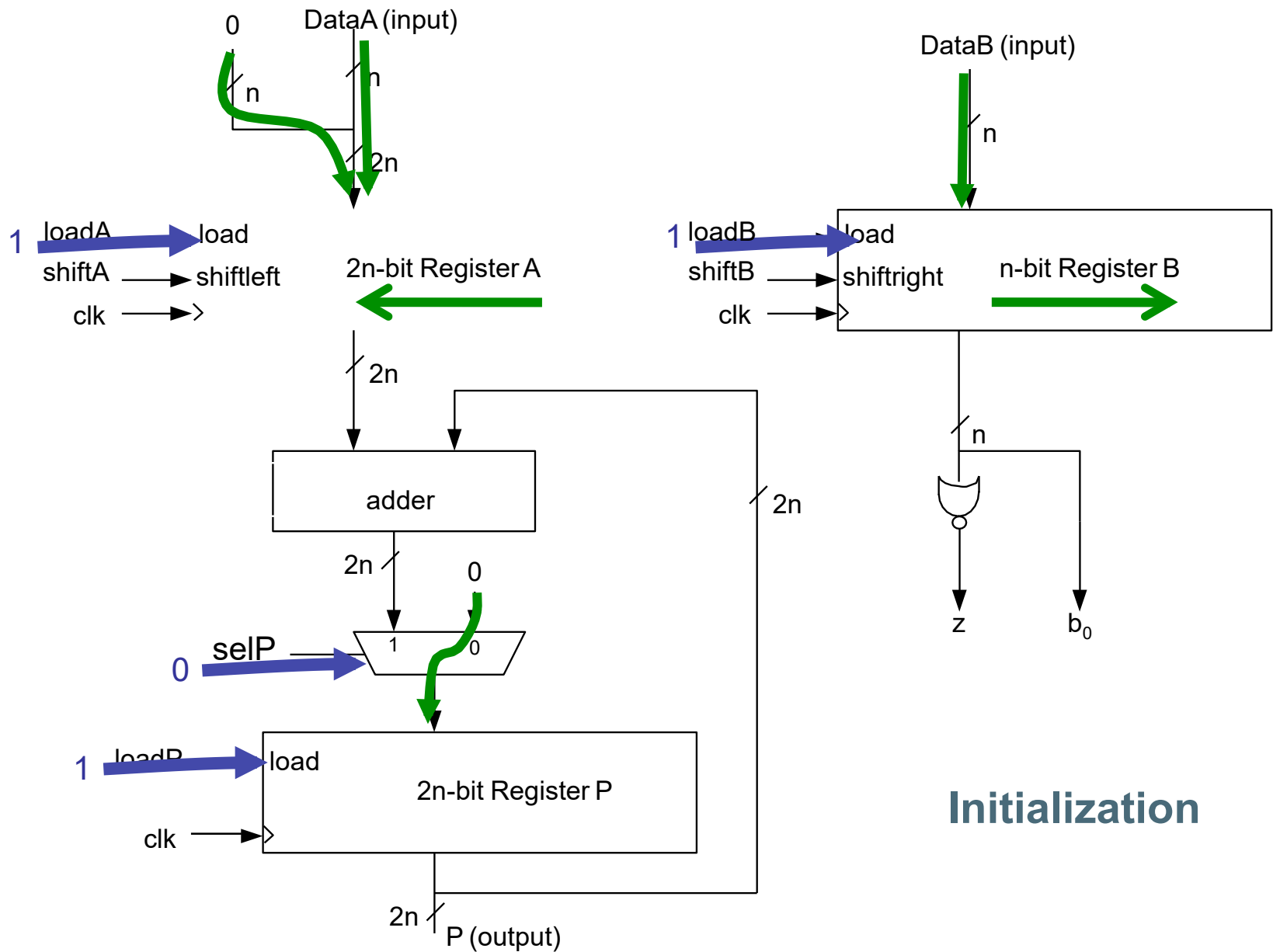

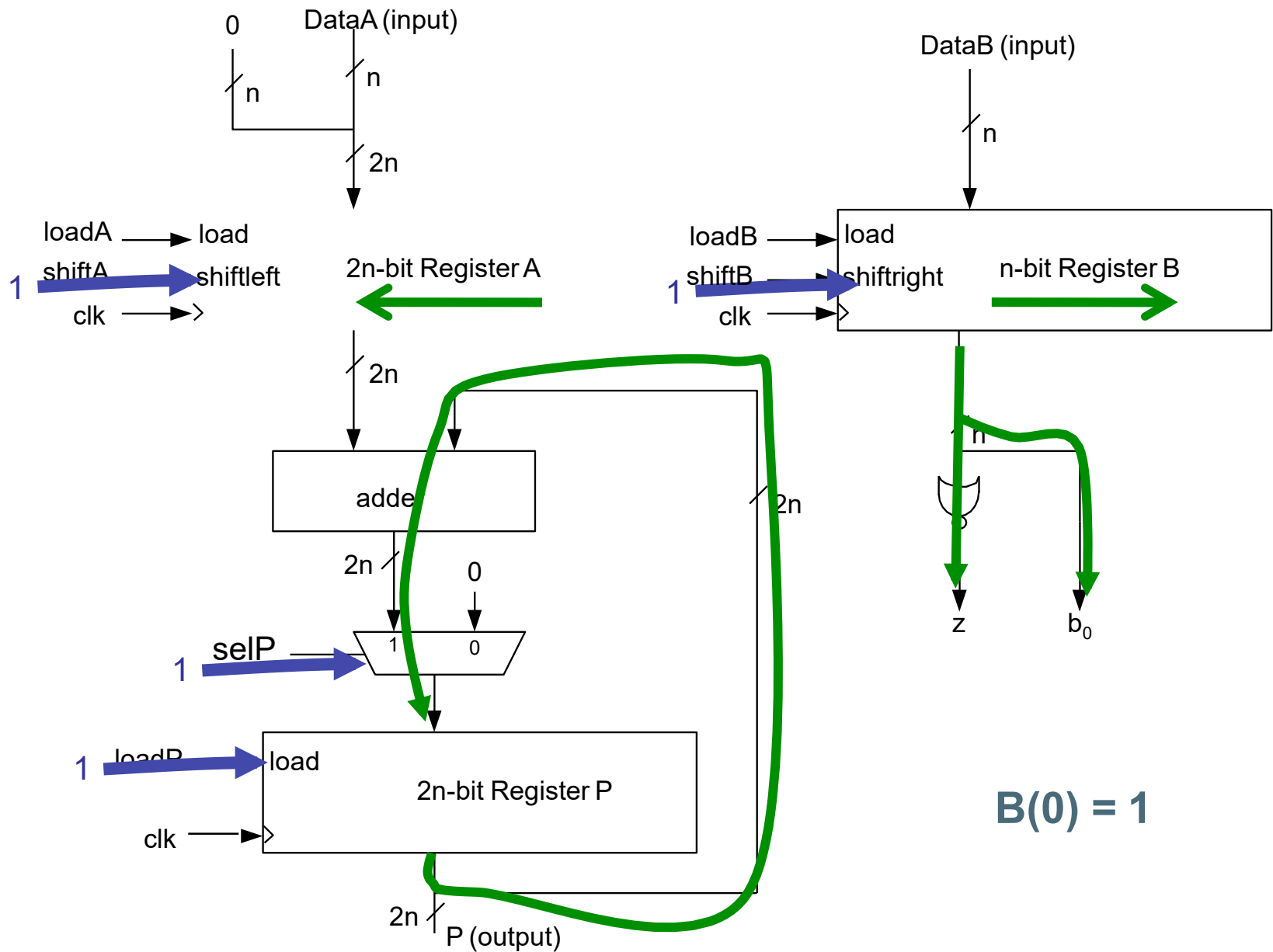

$$B(0) = 1$$

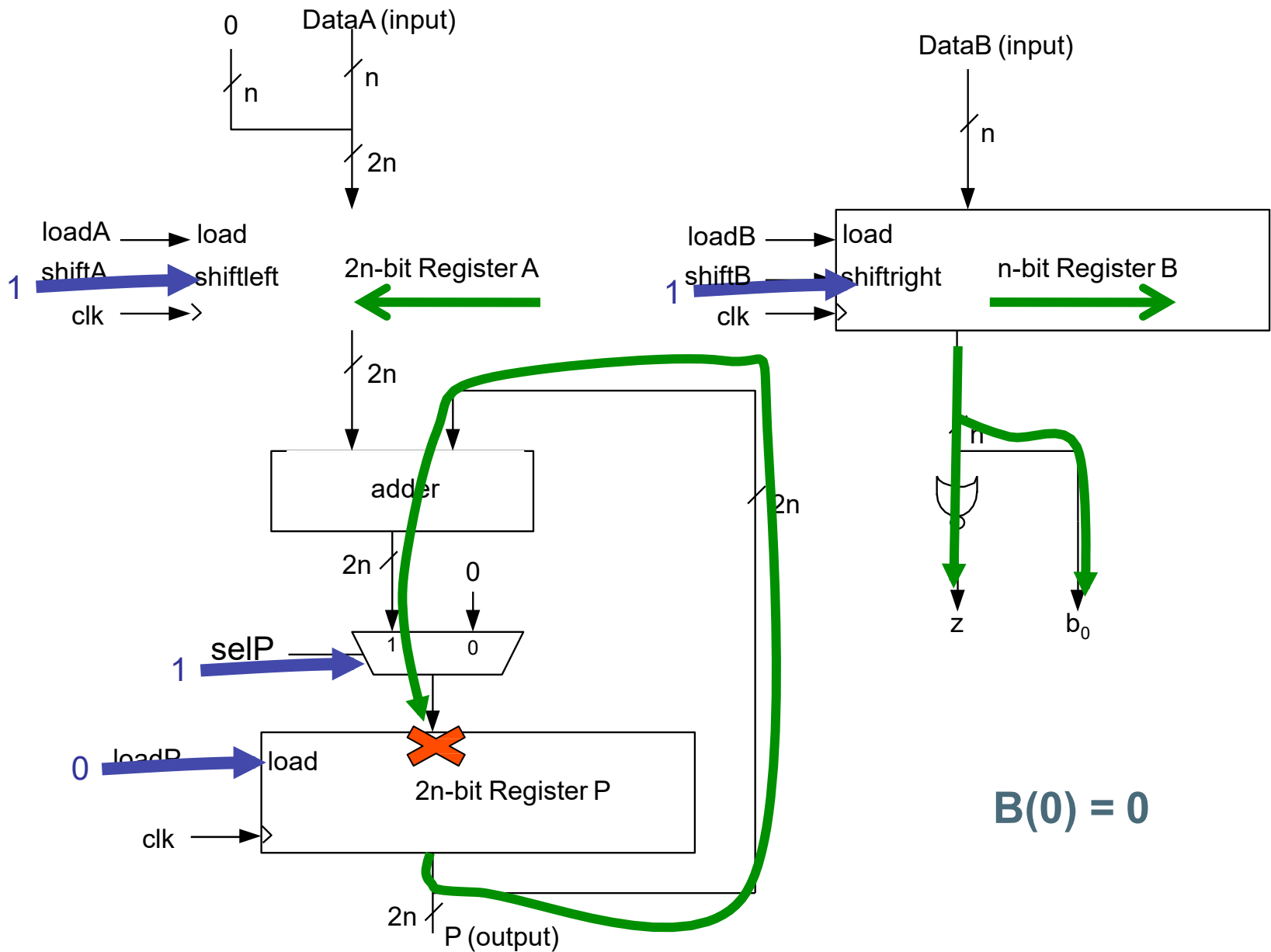

How to describe the cct?

- You can describe the Datapath and FSM in Verilog based on these schematics just like we have been doing throughout the course.
- Or, now that we understand the details, we can leverage the Synthesis tool's capabilities of inferring the datapath for us, and describe the algorithm instead.

```
module multiply (Clock, Resetn, LA, LB, s, DataA, DataB, P, Done);
```

```
  parameter n = 8;
```

```
  input Clock, Resetn, LA, LB, s;
```

```
  input [n-1:0] DataA, DataB;
```

```
  output [n+n-1:0] P;
```

```
  output reg Done;
```

```
  wire z;
```

```
  reg [n+n-1:0] A, DataP;
```

```
  wire [n+n-1:0] Sum;
```

```
  reg [1:0] y, Y;
```

```
  reg [n-1:0] B;
```

```
  reg EA, EB, EP, Psel;
```

```
  integer k;
```

```
// control circuit
```

```
  parameter S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;
```

```
  always @(s, y, z)
```

```
  begin: State_table
```

```
    case (y)
```

```
      S1: if (s == 0) Y = S1;
```

```
        else Y = S2;
```

```
      S2: if (z == 0) Y = S2;
```

```
        else Y = S3;
```

```
      S3: if (s == 1) Y = S3;
```

```
        else Y = S1;
```

```
      default: Y = 2'bxx;
```

```
    endcase
```

```
  end
```

```
  always @(posedge Clock, negedge Resetn)
```

```
  begin: State_flipflops
```

```
    if (Resetn == 0)
```

```
      y <= S1;
```

```
    else
```

```
      y <= Y;
```

```
  end
```

```
  always @(s, y, B[0])
```

```
  begin: FSM_outputs
```

```
    // defaults
```

```
    EA = 0; EB = 0; EP = 0; Done = 0; Psel = 0;
```

```
    case (y)
```

```
      S1: EP = 1;
```

```
      S2: begin
```

```
        EA = 1; EB = 1; Psel = 1;
```

```
        if (B[0]) EP = 1;
```

```
        else EP = 0;
```

```
      end
```

```
      S3: Done = 1;
```


```
    endcase
```

```
  end
```

... continued in next slide...


```
//datapath circuit
```

```
    shiftrne ShiftB (DataB, LB, EB, 0,  
Clock, B);  
        defparam ShiftB.n = 8;  
    shiftlne ShiftA ({n{1'b0}}, DataA}, LA,  
EA, 1'b0, Clock, A);  
        defparam ShiftA.n = 16;  
  
    assign z = (B == 0);  
    assign Sum = A + P;  
  
    // define the 2n 2-to-1 multiplexers  
    always @(Psel, Sum)  
        for (k = 0; k < n+n; k = k+1)  
            DataP[k] = Psel ?  
Sum[k] : 1'b0;  
  
    regne RegP (DataP, Clock, Resetn, EP,  
P);  
        defparam RegP.n = 16;  
  
endmodule
```

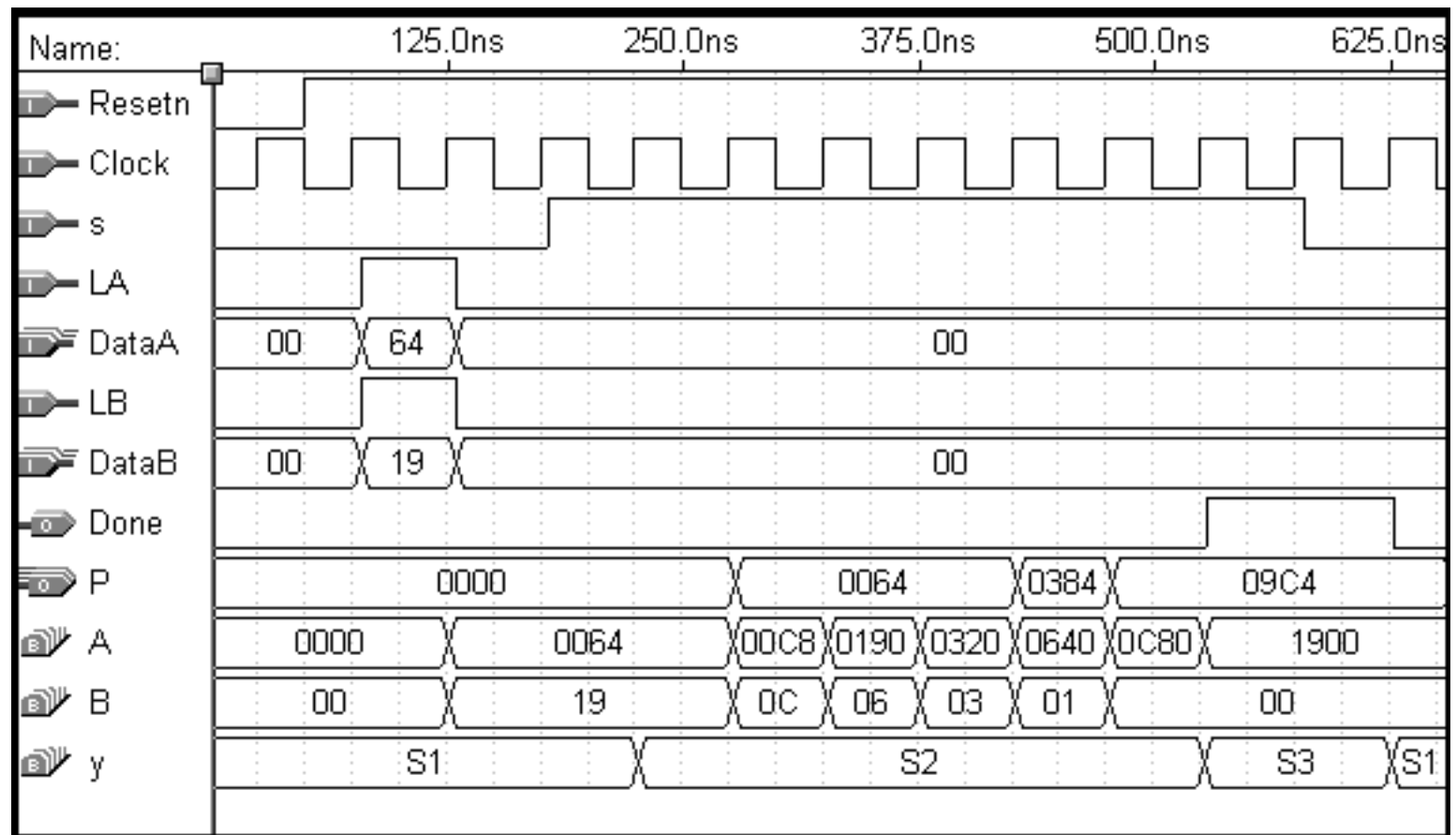

Simulation results for the multiplier circuit


F_{\max} For A Multi-Cycle Multiplier

- Multi-Cycle Multiplier F_{\max} :
 - 64 bits x 64 bits: $F_{\max} = 400$ MHz
 - Faster F_{\max} , but there is now **LATENCY** Takes up to N clock cycles to compute product
- Compare with Combinational Multiplier

Multiplier Width (in bits)	F_{\max} (MHz)
8 x 8	464
16 x 16	396
32 x 32	104
64 x 64	66

Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **S**Stephen Brown and **Z**vonko Vranesic. [**S&Z**]
 - S&Z,
 - Chapter-3
 - 3.2



THANK YOU

