



# Electronic Devices & Circuits

---

Dr. Hina Gohar Ali

[Hina.gohar@seecs.edu.pk](mailto:Hina.gohar@seecs.edu.pk)

**Office :** KBS Lab 1<sup>st</sup> floor SEECS Building

**Office Hours:** Open door policy/Appointment through emails

**Research Interest:** Photovoltaic systems, Power Electronics and Control, Renewable energy, Sliding mode control (SMC), Artificial Intelligence for PV systems

# Electronic Devices & Circuits





# Learning Process

---

## THE TEACHING/LEARNING PROCESS

### Input

Teacher  
Characteristics

Student  
Characteristics

### Classroom Processes

Teacher  
Behavior

Student  
Behavior

Other

### Output

Student  
Achievement

Other



# My Intro....

---

## Academic

2007-2010      **B.E Electronic Engineering**

NED University of Engineering & Technology, Karachi-Pakistan

2013- Jan 2015    **MS Electronic Engineering**

GIK Institute of Engineering Sciences & Technology, Topi-Pakistan

Oct 2016-2020    **Doctorate/Ph.D.** Electrical & Telecommunication Engineering (Excellent Grade)

Universitat Autònoma de Barcelona, Spain

Ph.D. Thesis: *Maximum Power Point Tracking of Photovoltaic System using Non-Linear Controllers*

## Professional Experience

Feb 2021-Present      **Assistant Professor**

SEECS, NUST Islamabad, Pakistan

May 2015-Oct 2016    **Lecturer (Adhoc BPS-18)**

B.U.I.T.E.M.S Department of Electrical Engineering, Quetta Pakistan

Jan 2013-Dec 2014    **Graduate Assistant**

GIK Institute Faculty of Electrical Engineering , Topi-Pakistan



# Profile

---



<https://www.linkedin.com/in/hina-gohar-ali-40b7a2197/>



<https://www.researchgate.net/profile/Hina-Gohar-Ali>



<https://scholar.google.com/citations?user=Z-5yLJEAAAAJ>



# Important

---

## Some Rules to be observed

---

- Please be courteous in class
- Punctuality
- Cell phones/Tabs/ Laptops are not allowed to be used
- Ask questions related to the course ...
- Drinking or eating in the class or laboratory is strictly prohibited
- *There are things that you cannot learn from reading notes*
- ...



## Important Values (to be in good books of Instructors)

---

- Discipline, Respectful & Obedient Students
- Learn Smart & Work Smart
- Focus on Concepts , Revise, Discuss
- Be kind & understand each other
- Mutual understanding, help & build each other
- No Tolerance to any kind of disrespect of Discipline Violation
- Make great memories along with learning
- Keep Good Relation everyone around
- Students really matter (the strength)
- Practice, Practice!!



# Today's Lecture

---

- About the Course Title
- Basic Concepts
- Operational Amplifiers



# Chapter 1

## Introduction to Electronics












# Data Storage Devices Timeline

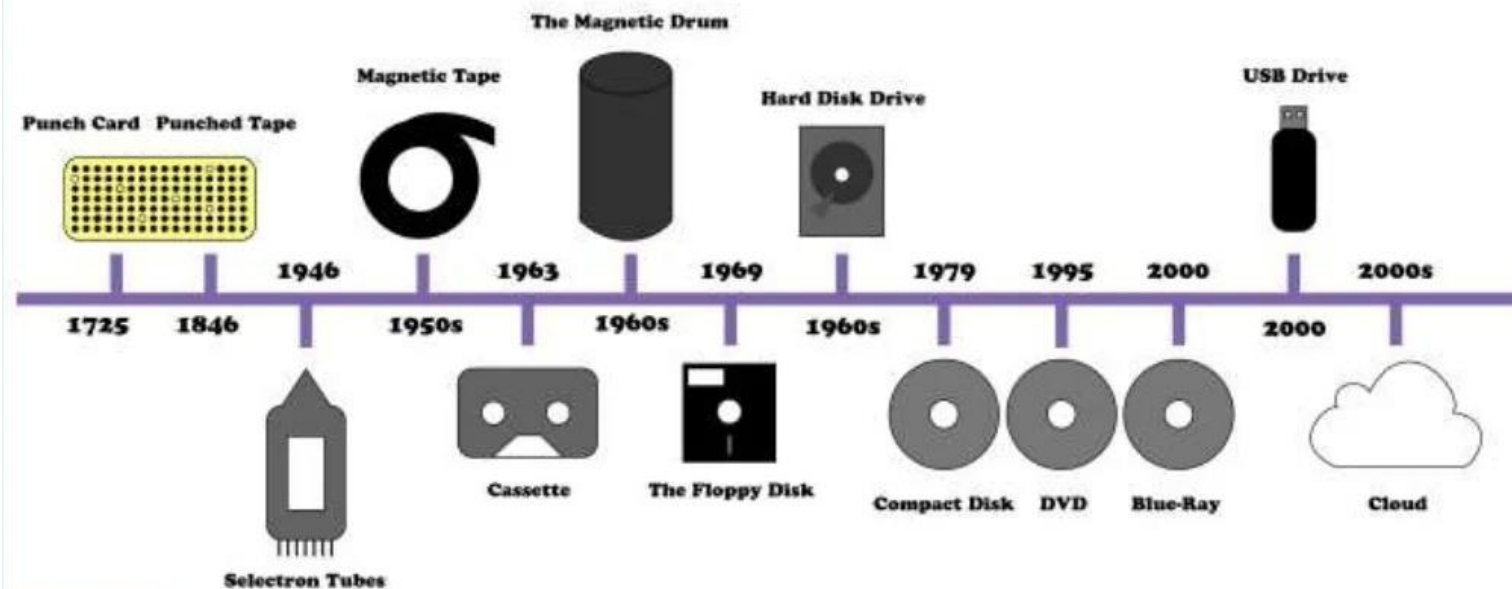

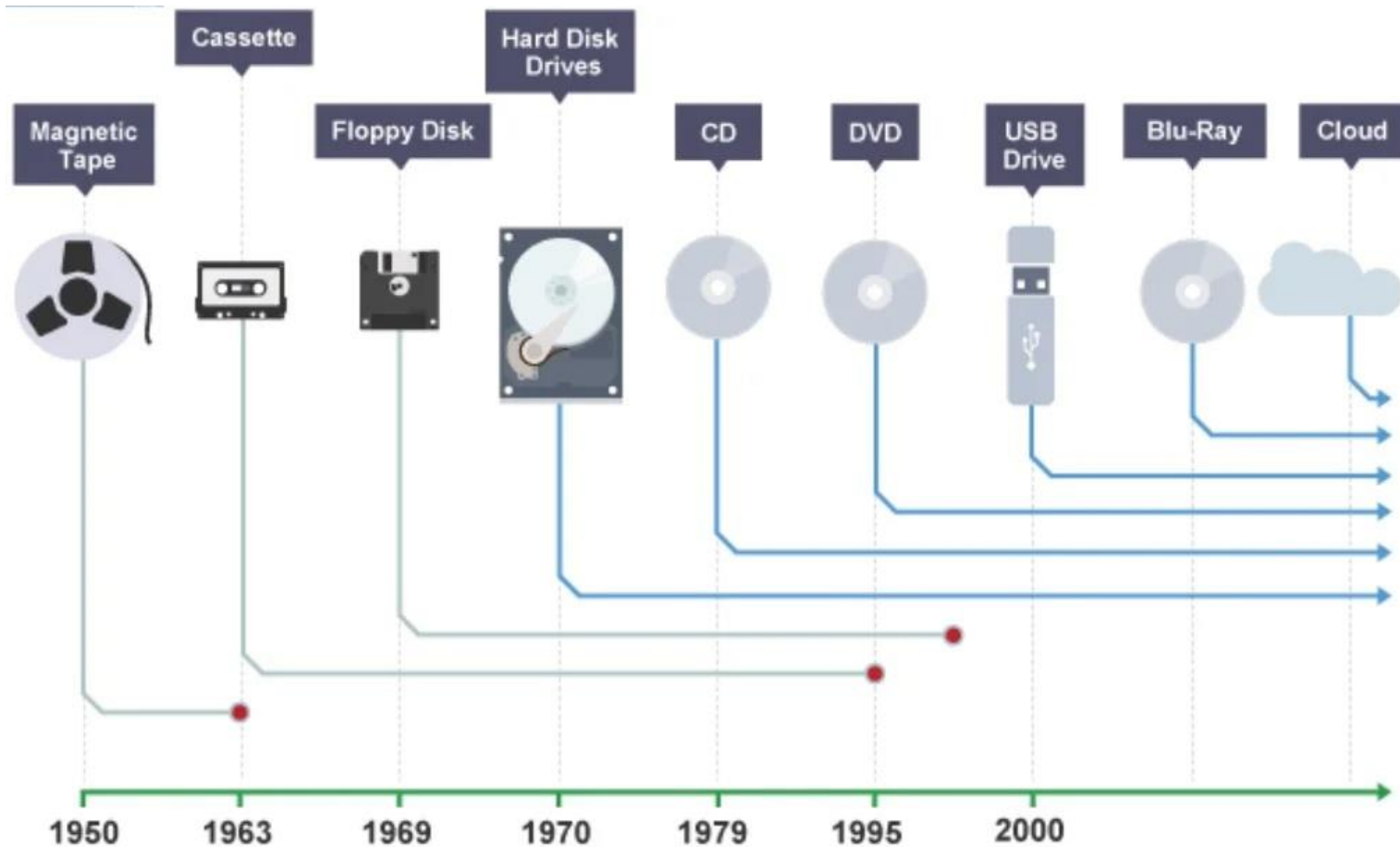

 Became obsolete

 Continuing use

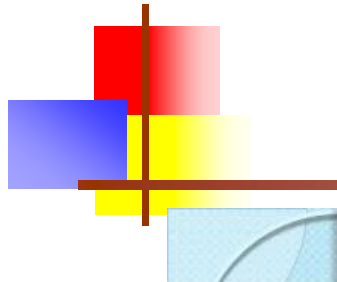


## The Sony Timeline

# The Start of the Modern Electronics Era



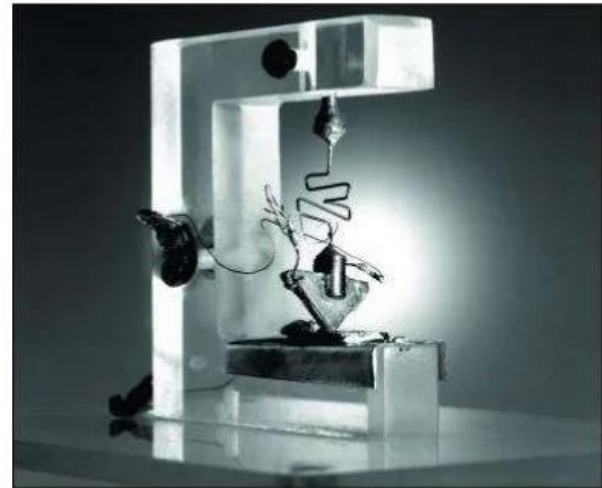
**Bardeen, Shockley, and Brattain at Bell Labs - Brattain and Bardeen invented the bipolar transistor in 1947.**



**The first germanium bipolar transistor. Roughly 50 years later, electronics account for 10% (4 trillion dollars) of the world GDP.**



# Electronics Milestones

- 
- |           |   |      |  |
|-----------|---|------|--|
| 1874      | Braun invents the solid-state rectifier.                              | 1958 | Integrated circuits developed by Kilby and Noyce     |
| 1906      | DeForest invents triode vacuum tube.                                  | 1961 | First commercial IC from Fairchild Semiconductor     |
| 1907-1927 | First radio circuits developed from diodes and triodes.               | 1963 | IEEE formed from merger of IRE and AIEE              |
| 1925      | Lilienfeld field-effect device patent filed.                          | 1968 | First commercial IC opamp                            |
| 1947      | Bardeen and Brattain at Bell Laboratories invent bipolar transistors. | 1970 | One transistor DRAM cell invented by Dennard at IBM. |
| 1952      | Commercial bipolar transistor production at Texas Instruments.        | 1971 | 4004 Intel microprocessor introduced.                |
| 1956      | Bardeen, Brattain, and Shockley receive Nobel prize.                  | 1978 | First commercial 1-kilobit memory.                   |
|           |   | 1974 | 8080 microprocessor introduced.                      |
|           |   | 1984 | Megabit memory chip introduced.                      |
|           |   | 2000 | Alferov, Kilby, and Kromer share Nobel prize         |



# Evolution of Electronic Devices

**Vacuum  
Tubes**



(a)

**Discrete  
Transistors**



(b)

**SSI and MSI  
Integrated  
Circuits**



(c)

**VLSI  
Surface-Mount  
Circuits**



(d)



# Introduction to Electronics

## Types of Electricity

- ★ Two forms of electricity ***Static*** and ***Produced***
- ★ ***Static Electricity*** is an electrical charge at rest.
- ★ ***Produced Electricity*** is produced by either magnetism, chemicals, light, heat, or pressure.



# Introduction to Electronics



**The study of electronics can be broken down into four basic steps:**

- Step 1 – Basic Electricity
- Step 2 – Electronic Components
- Step 3 – Electronic Circuits
- Step 4 – Electronic Systems



# Materials Used In Electronics

## ★ *Insulators*

- An **insulator** is a material that does not conduct electrical current under normal conditions.
- Most good insulators are compounds rather than single-element materials and have very high resistivities.
- Valence electrons are tightly bound to the atoms; therefore, there are very few free electrons in an insulator.
- Examples of insulators are rubber, plastics, glass, mica, and quartz.





# Materials Used In Electronics



## ★ *Conductors*

- A **conductor** is a material that easily conducts electrical current.
- Most metals are good conductors.
- The best conductors are single-element materials, such as copper (Cu), silver (Ag), gold (Au), and aluminum (Al), which are characterized by atoms with only one valence electron very loosely bound to the atom.



# Materials Used In Electronics

## ★ Semiconductors

- A **semiconductor** is a material that is between conductors and insulators in its ability to conduct electrical current.
- A semiconductor in its pure (intrinsic) state is neither a good conductor nor a good insulator.
- Single-element semiconductors are antimony (Sb), arsenic (As), astatine (At), boron (B), polonium (Po), tellurium (Te), silicon (Si), and germanium (Ge).



# Materials Used In Electronics

## ★ *Semiconductors*

- Compound semiconductors such as gallium arsenide, indium phosphide, gallium nitride, silicon carbide, and silicon germanium are also commonly used.
- The single-element semiconductors are characterized by atoms with four valence electrons.
- Silicon is the most commonly used semiconductor.








## Band Gap

- ★ Valence shell of an atom represents a band of energy levels and that the valence electrons are confined to that band.
- ★ When an electron acquires enough additional energy, it can leave the valence shell, become a *free electron*, and exist in what is known as the *conduction band*.
- ★ The difference in energy between the valence band and the conduction band is called an *energy gap* or **band gap**.



# Band Gap

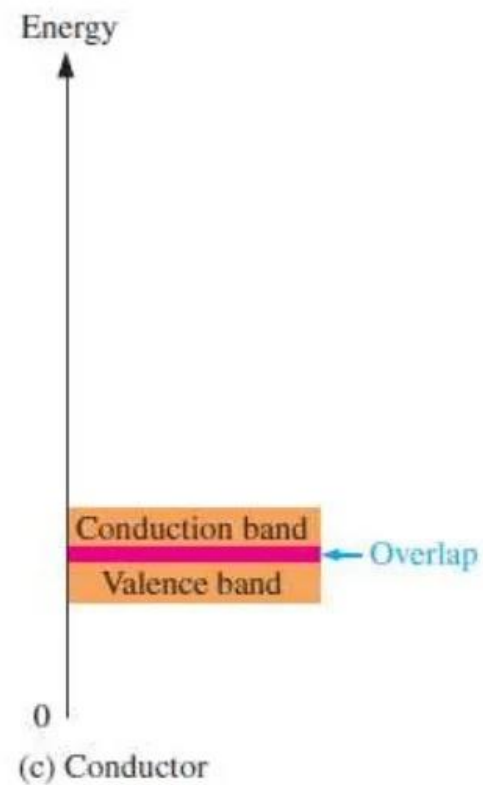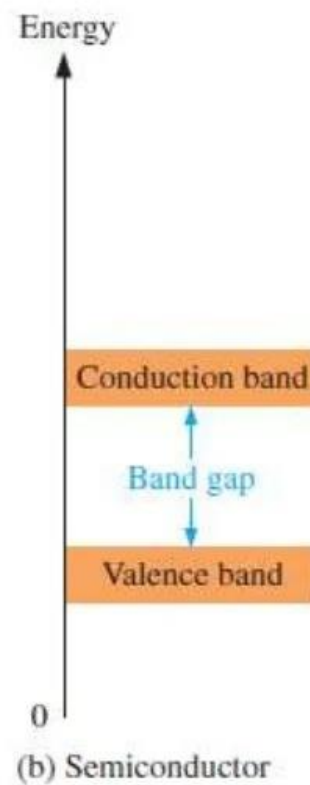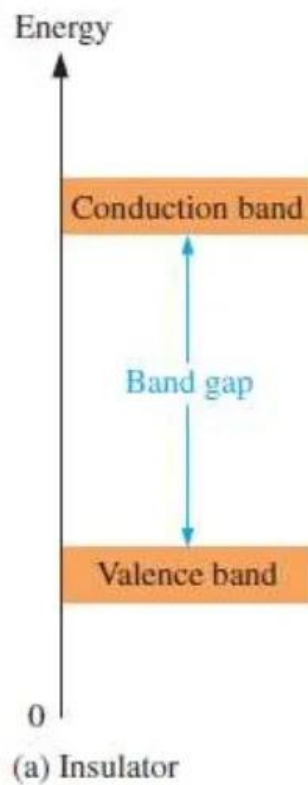


## Chapter 2



# Operational Amplifiers

---

# The Basic Op-Amp


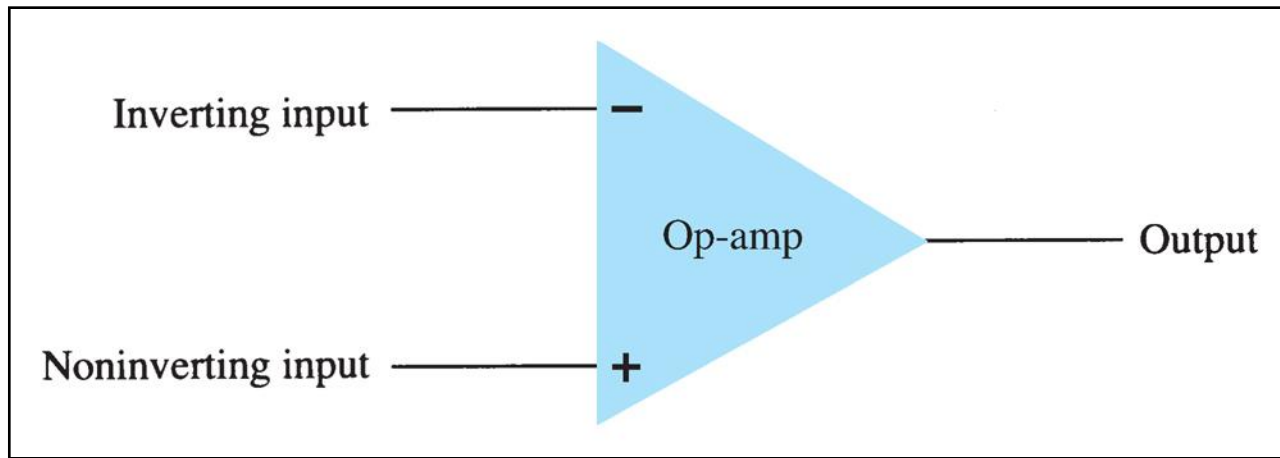


**Operational amplifier (Op-amp):** A high gain differential amplifier with a high input impedance (typically in  $M\Omega$ ) and low output impedance (less than  $100\Omega$ ).

Note the op-amp has two inputs and one output.
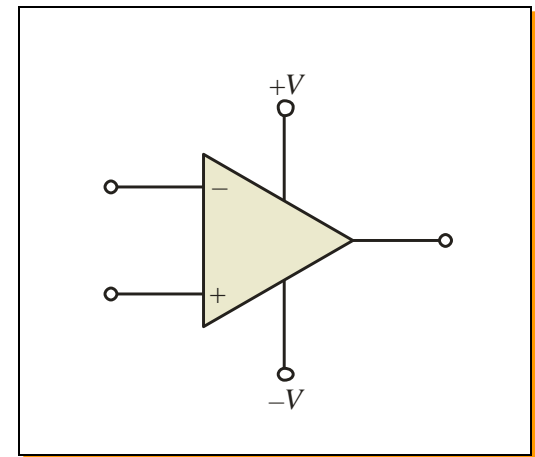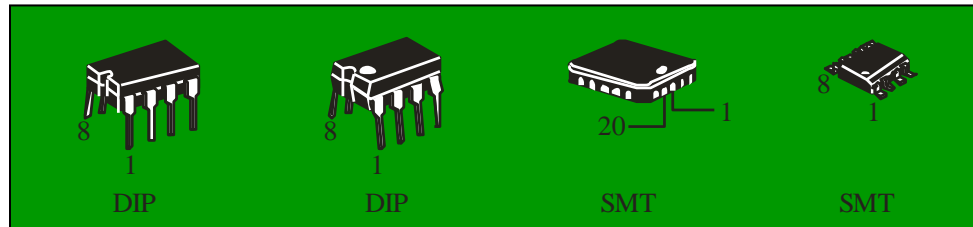
# The Basic Op-Amp

**Operational amplifiers (op-amps)** are very high gain dc coupled amplifiers with differential inputs. One of the inputs is called the inverting input ( $-$ ); the other is called the noninverting input. Usually there is a single output. Most op-amps operate from plus and minus supply voltages, which may or may not be shown on the schematic symbol.





# Op-Amp Gain

---

Op-Amps can be connected in *open-loop* or *closed-loop* configurations.

**Open-loop:** A configuration with no feedback from the op-amp output back to its input. Op-amp open-loop gain typically exceeds 10,000.

**Closed-loop:** A configuration that has a negative feedback path from the op-amp output back to its input. **Negative feedback** reduces the gain and improves many characteristics of the op-amp.


- Closed-loop gain is always lower than open-loop gain.

# Inverting Op-Amp

The input signal is applied to the **inverting (–) input**

The **non-inverting input (+)** is grounded

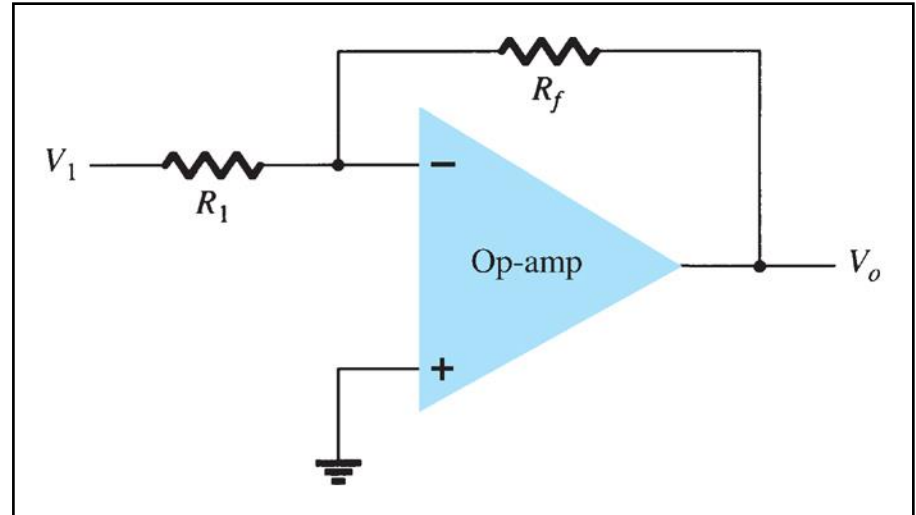The **feedback resistor** ( $R_f$ ) is connected from the output to the negative (inverting) input; providing *negative feedback*.



# Inverting Op-Amp Gain


Gain is set using external resistors:  $R_f$  and  $R_1$

$$A_v = \frac{V_o}{V_i} = \frac{R_f}{R_1}$$

Gain can be set to any value by manipulating the values of  $R_f$  and  $R_1$ .

Unity gain ( $A_v = 1$ ):
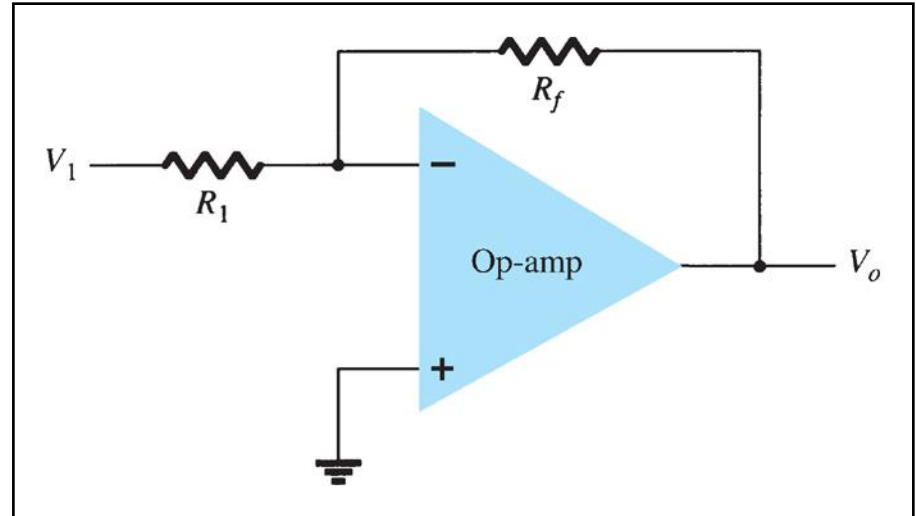
$$R_f = R_1$$
$$A_v = \frac{-R_f}{R_1} = -1$$





The negative sign denotes a  $180^\circ$  phase shift between input and output.

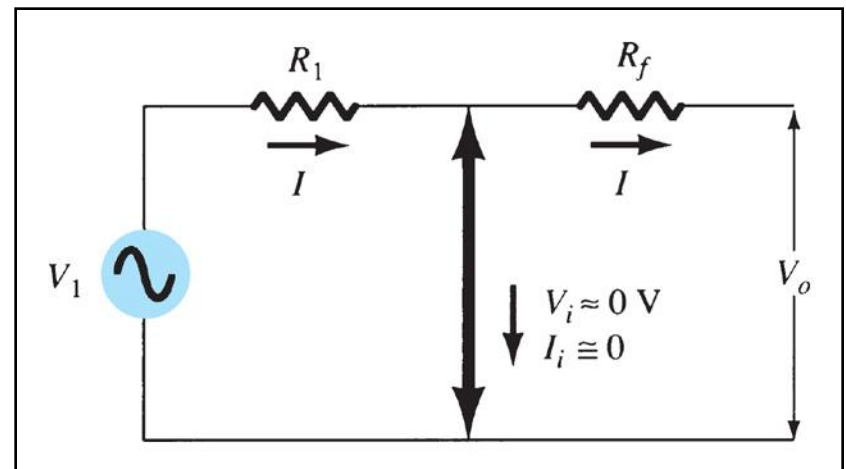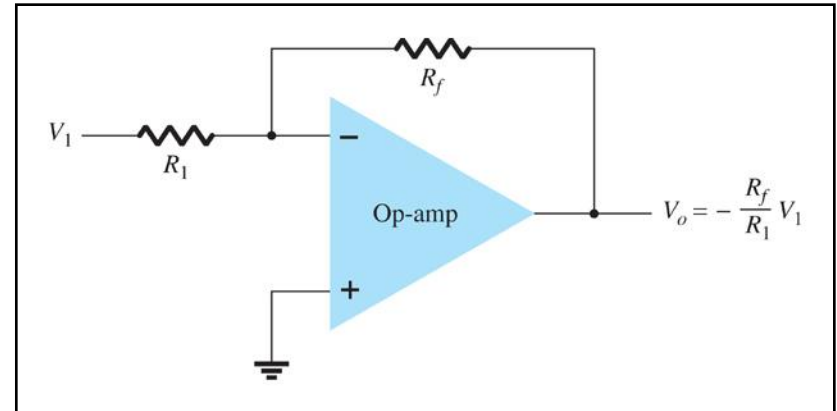
# Virtual Ground

**Virtual ground:** A term used to describe the condition where  $V_i \cong 0 \text{ V}$  (at the inverting input) when the noninverting input is grounded.

The op-amp has such high input impedance that even with a high gain there is no current through the inverting input pin, therefore all of the input current passes through  $R_f$ .





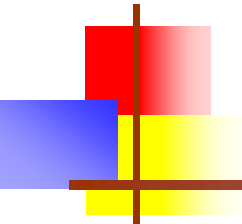

# Common Op-Amp Circuits

---

**Inverting amplifier**

**Noninverting amplifier**

**Unity follower**

**Summing amplifier**


**Integrator**

**Differentiator**

# Inverting/Noninverting Amplifiers


## Inverting Amplifier

$$V_o = -\frac{R_f}{R_1} V_1$$

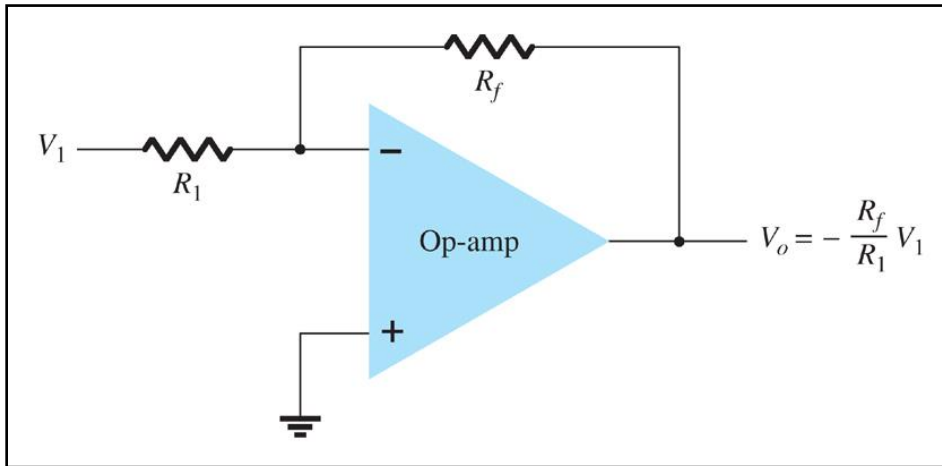

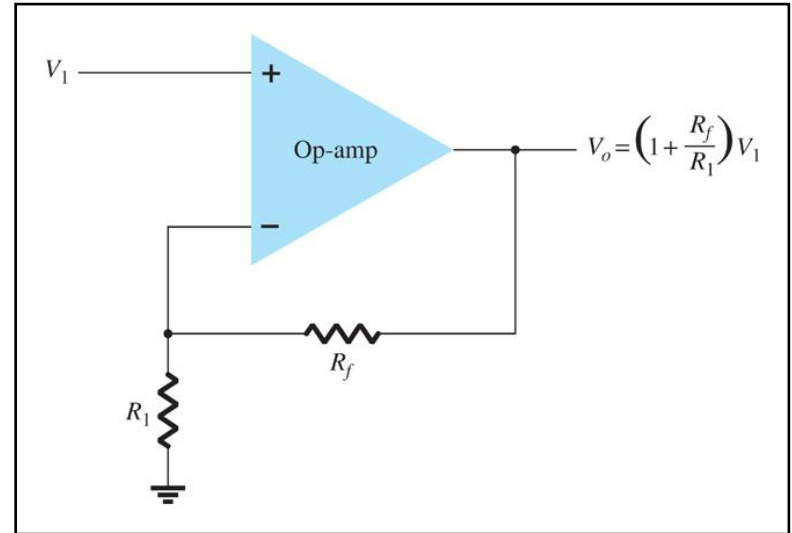
## Noninverting Amplifier

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$



# Unity Follower


$$V_o = V_1$$

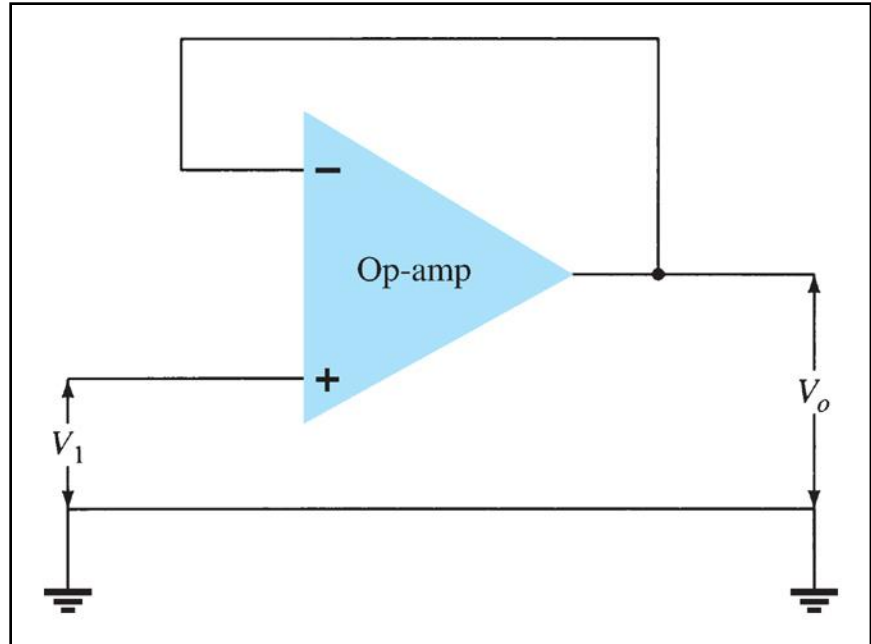
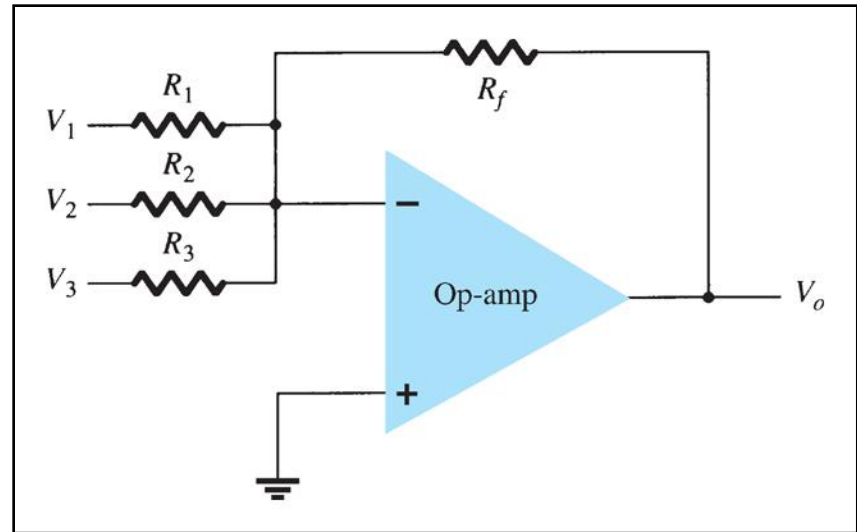
# Summing Amplifier

Because the op-amp has a high input impedance, the multiple inputs are treated as separate inputs.


$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$


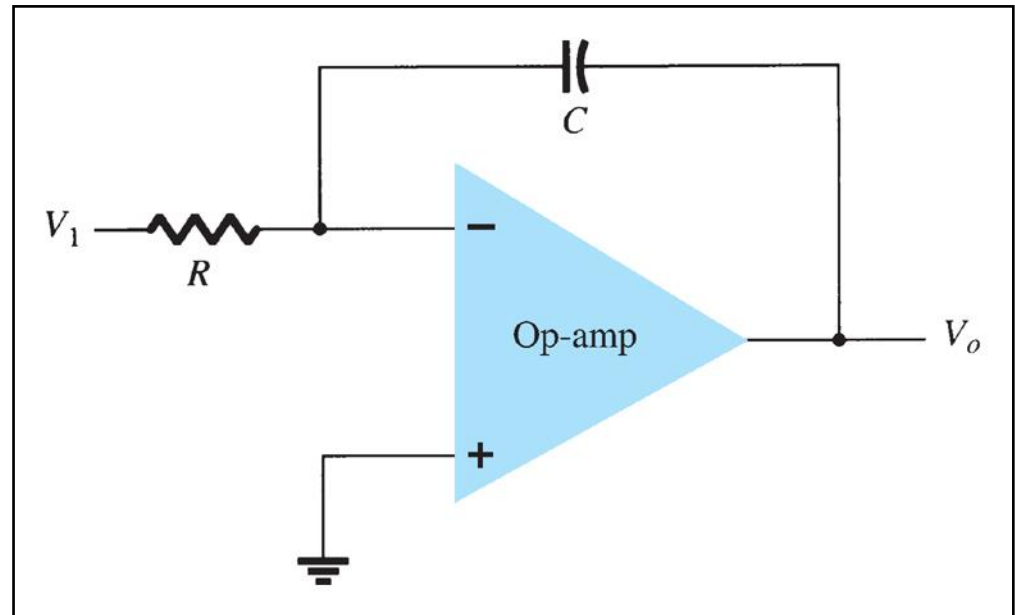
# Integrator

The output is the integral of the input; i.e., proportional to the area under the input waveform. This circuit is useful in low-pass filter circuits and sensor conditioning circuits.


$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$



# Differentiator

The differentiator takes the derivative of the input. This circuit is useful in high-pass filter circuits.

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

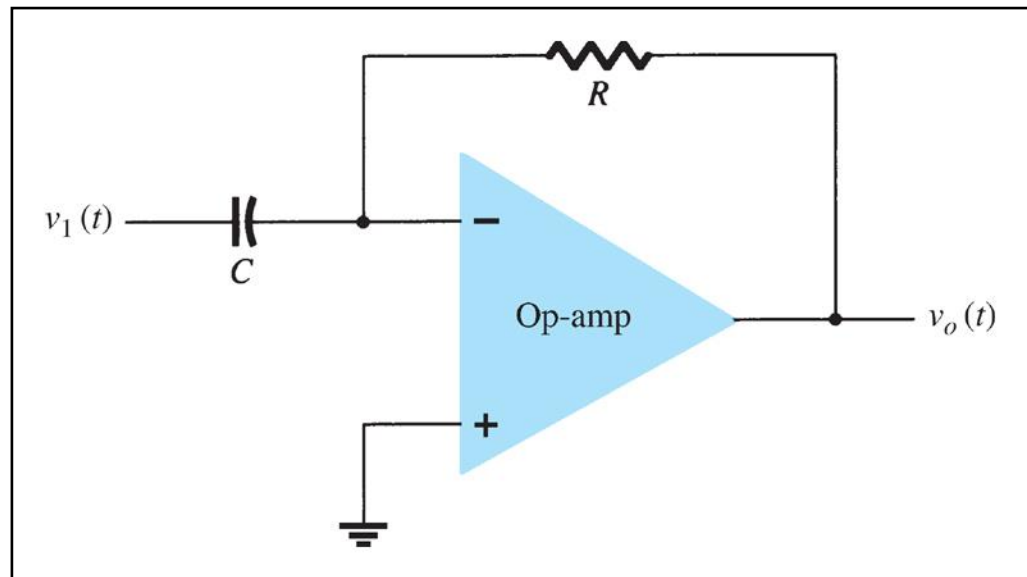



# DC-Offset Parameters

---

Even when the input voltage is zero, an op-amp can have an output **offset**. The following can cause this offset:

- Input offset voltage

- Input offset current

- Input offset voltage *and* input offset current

- Input bias current



# Input Offset Voltage ( $V_{IO}$ )

---

The specification sheet for an op-amp indicates an **input offset voltage** ( $V_{IO}$ ).

The effect of this input offset voltage on the output can be calculated with

$$V_{o(offset)} = V_{IO} \frac{R_1 + R_f}{R_1}$$





# Input Offset Current ( $I_{IO}$ )

---

If there is a difference between the dc bias currents generated by the same applied input, this also causes an output offset voltage:

The **input offset current** ( $I_{IO}$ ) is specified in the specifications for an op-amp.

The effect of  $I_{IO}$  on the output offset voltage can be calculated using:

$$V_{o(offset)} = V_{o(offset \text{ dueto } V_{IO})} + V_{o(offset \text{ dueto } I_{IO})}$$



# Total Offset Due to $V_{IO}$ and $I_{IO}$

Op-amps may have an output offset voltage due to  $V_{IO}$  and  $I_{IO}$ . The total output offset voltage equals the sum of the effects of both:

$$V_o(\text{offset}) = V_o(\text{offset due to } V_{IO}) + V_o(\text{offset due to } I_{IO})$$



# Input Bias Current ( $I_{IB}$ )

---

A parameter that is related to input offset current ( $I_{IO}$ ) is called **input bias current** ( $I_{IB}$ )

The input bias currents are calculated using:

$$I_{IB}^{-} = I_{IB} - \frac{I_{IO}}{2}$$

$$I_{IB}^{+} = I_{IB} + \frac{I_{IO}}{2}$$

The total input bias current is the average of the two:

$$I_{IB} = \frac{I_{IB}^{-} + I_{IB}^{+}}{2}$$



# Frequency Parameters

---


An op-amp is a wide-bandwidth amplifier. The following factors affect the bandwidth of the op-amp:

**Gain**

**Slew rate**
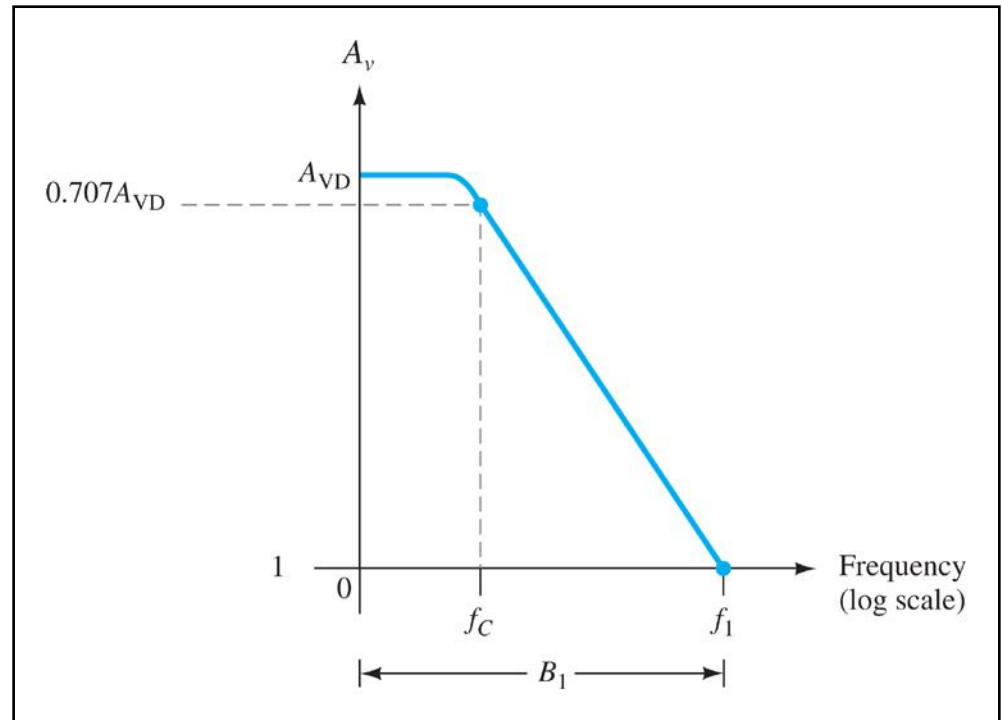
# Gain and Bandwidth

The op-amp's high frequency response is limited by its internal circuitry. The plot shown is for an open loop gain ( $A_{OL}$  or  $A_{VD}$ ). This means that the op-amp is operating at the highest possible gain with no feedback resistor.



In the open loop mode, an op-amp has a narrow bandwidth. The bandwidth widens in closed-loop mode, but the gain is lower.



# Slew Rate (SR)

---

**Slew rate (SR):** The maximum rate at which an op-amp can change output without distortion.

$$SR = \frac{\Delta V_o}{\Delta t} \quad (\text{in V}/\mu\text{s})$$

The SR rating is listed in the specification sheets as the V/ $\mu$ s rating.



# Maximum Signal Frequency

---

The slew rate determines the highest frequency of the op-amp without distortion.

$$f \leq \frac{SR}{2\pi V_p}$$

where  $V_p$  is the peak voltage



# General Op-Amp Specifications

---

Other op-amp ratings found on specification sheets are:

**Absolute Ratings**

**Electrical Characteristics**

**Performance**





# Absolute Ratings

These are  
common  
maximum ratings  
for the op-amp.

## *Absolute Maximum Ratings*

Supply voltage	$\pm 22$ V
Internal power dissipation	500 mW
Differential input voltage	$\pm 30$ V
Input voltage	$\pm 15$ V



# Electrical Characteristics

*$\mu A741$  Electrical Characteristics:  $V_{CC} = \pm 15\text{ V}$ ,  $T_A = 25^\circ\text{C}$*

Characteristic	Minimum	Typical	Maximum	Unit
$V_{IO}$ Input offset voltage		1	6	mV
$I_{IO}$ Input offset current		20	200	nA
$I_{IB}$ Input bias current		80	500	nA
$V_{ICR}$ Common-mode input voltage range	$\pm 12$	$\pm 13$		V
$V_{OM}$ Maximum peak output voltage swing	$\pm 12$	$\pm 14$		V
$A_{VD}$ Large-signal differential voltage amplification	20	200		V/mV
$r_i$ Input resistance	0.3	2		$M\Omega$
$r_o$ Output resistance		75		$\Omega$
$C_i$ Input capacitance		1.4		pF
CMRR Common-mode rejection ratio	70	90		dB
$I_{CC}$ Supply current		1.7	2.8	mA
$P_D$ Total power dissipation		50	85	mW

Note: These ratings are for specific circuit conditions, and they often include minimum, maximum and typical values.



# CMRR

---


One rating that is unique to op-amps is **CMRR** or **common-mode rejection ratio**.

Because the op-amp has two inputs that are opposite in phase (inverting input and the non-inverting input) any signal that is common to both inputs will be cancelled.

Op-amp CMRR is a measure of the ability to cancel out common-mode signals.
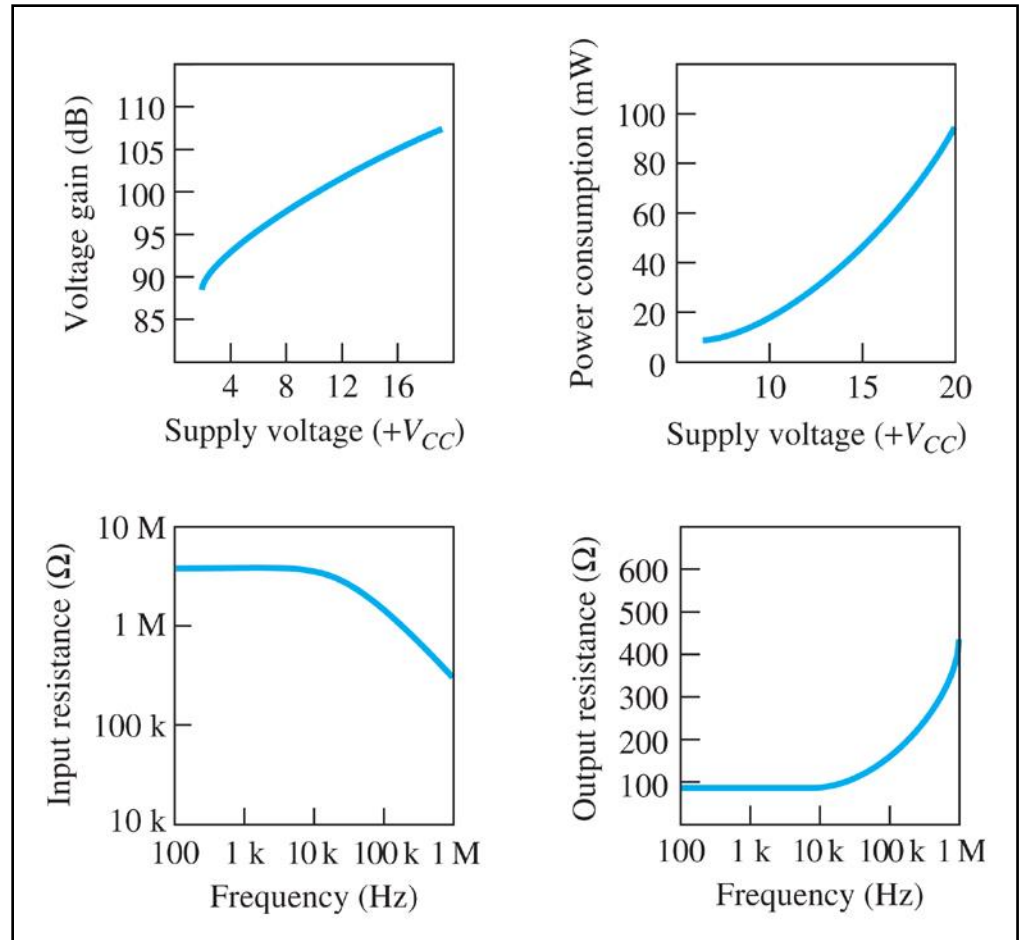
# Op-Amp Performance

The specification sheets will also include graphs that indicate the performance of the op-amp over a wide range of conditions.





# Summary

---

*That's all for Today !*