

EE-421: Digital System Design


Blocking vs Non-Blocking Revisited (in Sequential Ccts)

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Blocking vs Non-Blocking Revisited (in Sequential Ccts)


Review (1): Blocking vs Non-Blocking Statements and Statement Ordering
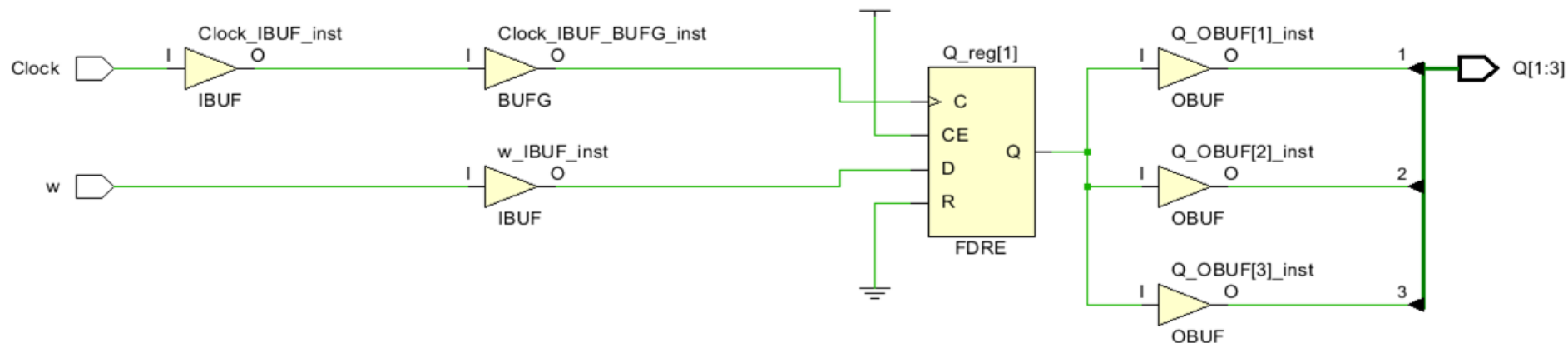
```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[3] = w;  
    Q[2] = Q[3];  
    Q[1] = Q[2];  
  end  
endmodule
```




Review (2): Blocking vs Non-Blocking Statements and Statement Ordering
 
```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[1] = Q[2];  
    Q[2] = Q[3];  
    Q[3] = w;  
  end  
endmodule
```




Review (3): Blocking vs Non-Blocking Statements and Statement Ordering
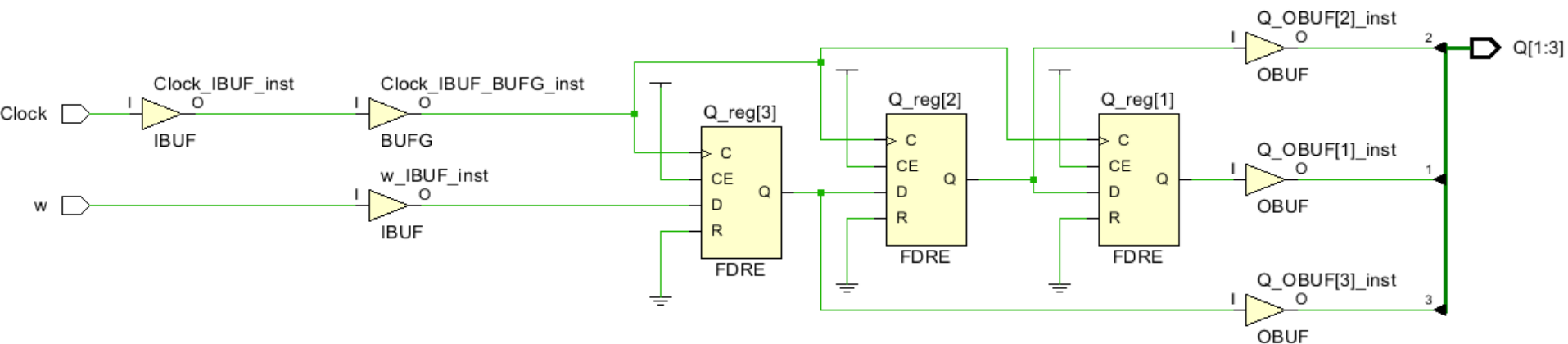
```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[1] <= Q[2];  
    Q[2] <= Q[3];  
    Q[3] <= w;  
  end  
endmodule
```




Review (4): Blocking vs Non-Blocking Statements and Statement Ordering
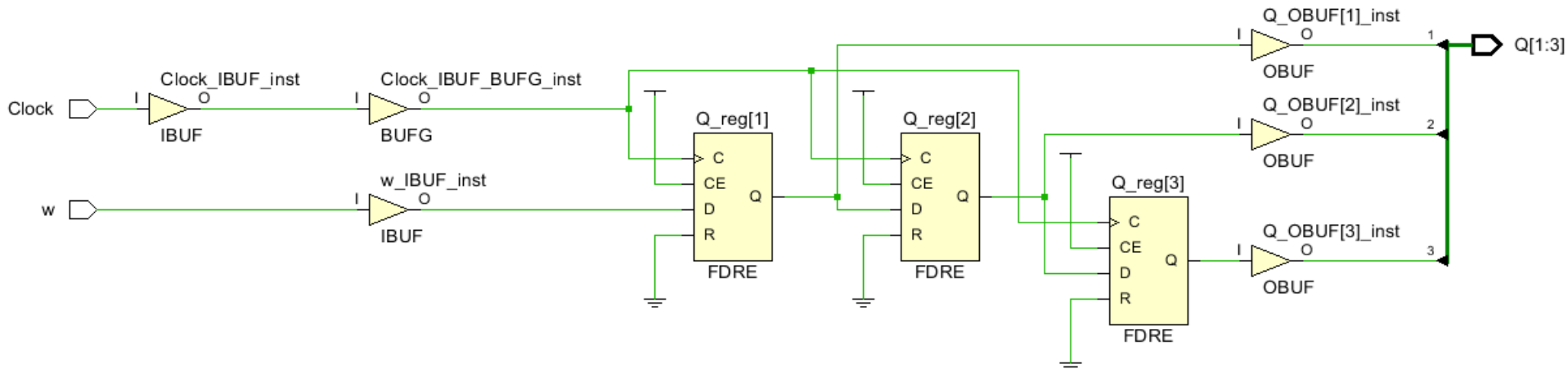
```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[2] <= Q[1];  
    Q[3] <= Q[2];  
    Q[1] <= w;  
  end  
endmodule
```



Review (5): Blocking vs Non-Blocking Statements and Statement Ordering
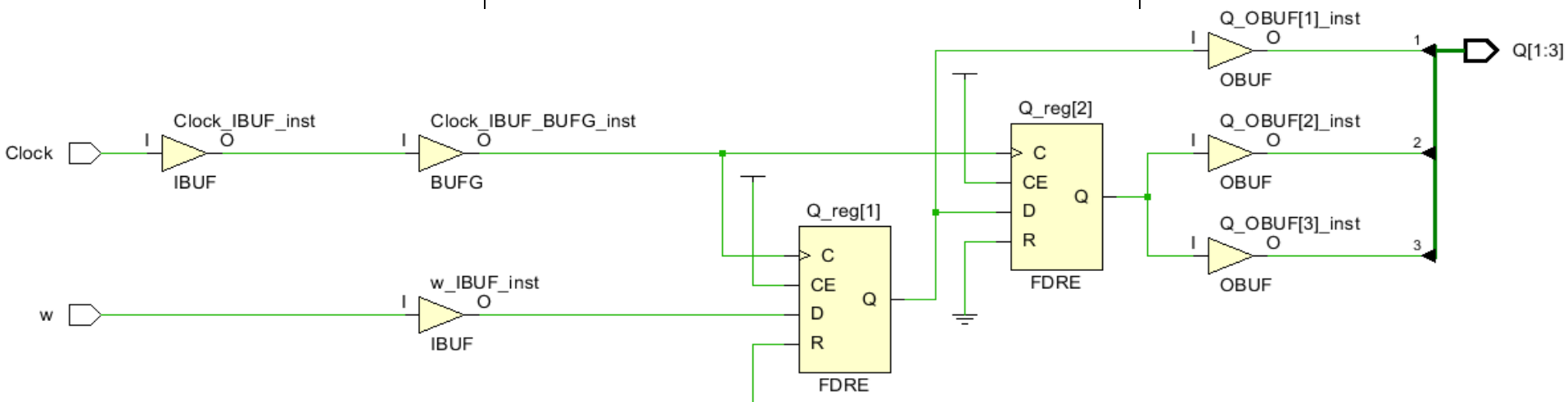
```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[2] = Q[1];  
    Q[3] = Q[2];  
    Q[1] = w;  
  end  
endmodule
```




Takeaway: Blocking vs Non-Blocking: Avoid Confusion

- To guarantee that your simulation matches the behavior of the synthesized circuit, follow these rules:
 1. Use blocking assignments to model combinational logic within an always block.
 2. Use non-blocking assignments to implement sequential logic.
 3. Do not mix blocking and non-blocking assignments in the same always block.
 - It is not possible to model both a combinational output and a sequential output in a single always block.
 4. Do not make assignments to the same variable from more than one always block

Class Activity

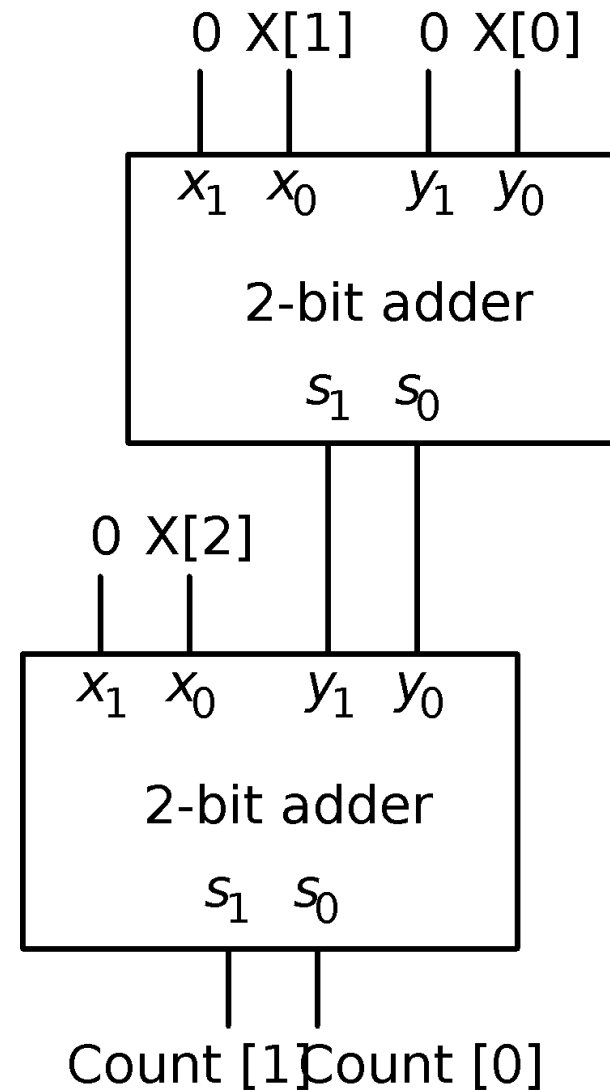- Design a circuit that counts the number of bits in an n-bit input X that have the value 1.




Blocking vs Non-Blocking

```
module bit_count (X, Count);  
  parameter n = 4;  
  parameter logn = 2;  
  input [n-1:0] X;  
  output reg [logn:0] Count;  
  integer k;
```

counts the number of bits in the n-bit input
X that have the value 1

```
  always @(X)  
  begin  
    Count = 0;  
    for (k = 0; k < n; k = k+1)  
      Count = Count + X[k];  
  end
```

 Loop unrolled as:
Count = Count + X[0];
Count = Count + X[1];
Count = Count + X[2];
.....



Blocking vs Non-Blocking

```
module bit_count (X, Count);  
  parameter n = 4;  
  parameter logn = 2;  
  input [n-1:0] X;  
  output reg [logn:0] Count;  
  integer k;  
  
  always @(X)  
  begin  
    Count <= 0;  
    for (k = 0; k < n; k = k+1)  
      Count <= Count + X[k];  
  end  
endmodule
```

Loop unrolled as:

Count <= Count + X[0];


Count <= Count + X[1];

Count <= Count + X[2];

.....

Since non-blocking assignments are involved, each subsequent assignment statement sees the starting value of Count = 0

Count <= 0 + X[2];

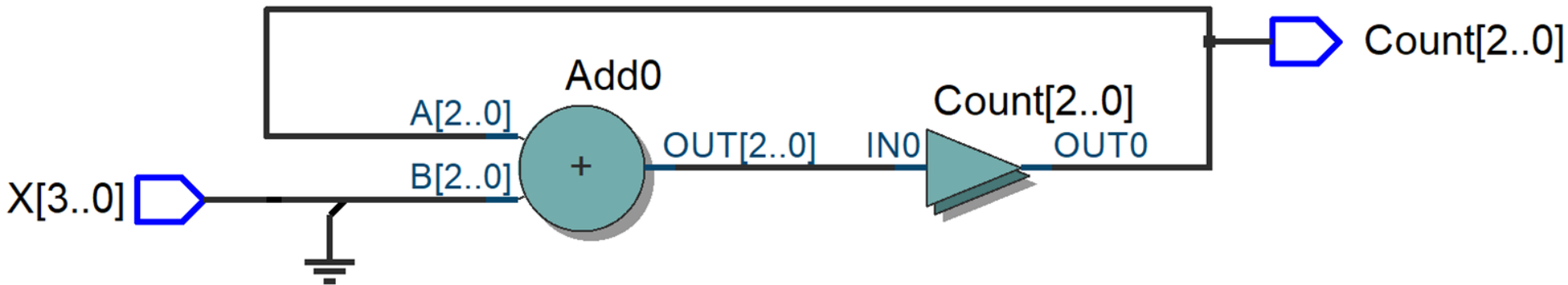

Example: Mixing Blocking and Non-Blocking

```
module bit_count (X, Count);  
    parameter n = 4;  
    parameter logn = 2;  
    input [n-1:0] X;  
    output reg [logn:0] Count;  
    integer k;  
  
    always @(X)  
    begin  
        Count = 0;  
        for (k = 0; k < n; k = k+1)  
            Count <= Count + X[k];  
    end  
endmodule
```

❗ 12127 Elaborating entity "top" for the top level hierarchy
❌ 10110 Verilog HDL error at top.v(5): variable "Count" has mixed blocking and nonblocking Procedural Assignments -- must be all blocking or all nonblocking assignments
❌ 12153 Can't elaborate top-level user hierarchy
❌ Quartus Prime Analysis & Elaboration was unsuccessful. 2 errors, 3 warnings

Takeaway: Expressing Combinational
and Sequential Ccts in Verilog


Takeaway

- Expressing Combinational or Sequential circuits using Procedural Statements:
 - Remember **THREE** patterns (discussed in the next 3-slides)
 - Purely based on observation and experience!
 - Not part of IEEE standard (**not at all**)!
 - Books might not preach that!

Always Pattern - 1

- **Combinational Logic:**

`always@(in1, in2, in3) = always @ (*)`

 


- **Simulation** – outputs are re-evaluated anytime a signal in the sensitivity list changes
- **Synthesis** – The synthesized block's output may only change when a change occurs on one of the sensitivity list signals

Always Pattern - 2

- **Sequential Logic and Synchronous Reset:**

`always@(posedge CLK)`

 


- Only the clock signal goes inside the sensitivity list.

Always Pattern - 3

- **Sequential Logic and Asynchronous Reset:**

`always@(posedge CLK or negedge RESET)`

 

- Only the clock and reset signals go inside the sensitivity list.

THANK YOU

