



Chapter6: Registers and Counters

Lecture1- An Introduction to Registers

Engr. Arshad Nazir, Asst Prof
Dept of Electrical Engineering
SEECS

Objectives

- Study Registers with Parallel Load and Shift Registers
- Design Universal Shift Registers with Parallel Load with the given specifications
- Design Serial Adders

Registers

- Clocked sequential circuits consists of:
 - a group of flip-flops and combinational gates
 - connected to form a feedback path
- Flips Flops are essential because in their absence, the circuit reduces to purely combinational circuit. (provided there is no feedback among the gates)
- Circuits that include flip flops are usually classified by the function they perform
- Two such circuits are registers and counters

Registers

- Register

- A register is a group of flip-flops, each flip-flop is capable of storing one bit of information
- A register may have combinational gates that determine how the information is transferred into the register
- An n -bit register consist of a group of n flip-flops capable of storing n bits of binary information. There are different types of registers available commercially

- Counter

- A counter is a special type of register that goes through a predetermined sequence of states.
- The gates in the counter are connected in such a way to produce the prescribed sequence of binary states

Simple Register

- The simplest **register** is one that consists of only **flip-flops** without any gates
- A n-bit register consists of n flip-flops capable of storing n bits of binary information
- Fig 6-1 shows a 4-bit register with four D-type flip-flops. The information is loaded in parallel.
- The four outputs can be sampled at any time to obtain the binary information stored in the register
- The **clear** input goes to R (reset) input of all four flip flops
- When this input goes to zero all flip- flops are **reset** (go to all 0's) asynchronously

 


Fig. 6-1 4-Bit Register

Register with Parallel Load

- **Synchronous** digital systems have a **master clock** generator that supplies a continuous train of clock pulses
- A separate **control** signal must be used to **decide** which **specific clock pulse** will have an effect on a particular register
- The **transfer** of new **information** into a register is referred to as **loading** the register
- If all the bits are loaded **simultaneously** with a common clock pulse we say that the loading is done in **parallel**
- A clock edge applied to C inputs of the register (Fig 6-1) will load all inputs in parallel
- If the content of the register be left **unchanged** then the **clock** must be **inhibited** from reaching the register

Register with Parallel Load Cont...

- The clock can be inhibited from reaching the register by controlling the clock input signal with an enabling gate. Clock pulses perform the logic
- This insertion of **gates** produce **uneven propagation delays** between the master clock and the inputs of flip flops
- To **synchronize** the system we must ensure that clock **pulses** must arrive at the **same time** anywhere in the system so that all flip-flops trigger simultaneously
- Performing logic with clock pulses, inserts variable delays and may cause the system to go out of synchronism
- For this reason it is advisable to **control** the operation of register with the **D inputs** rather than controlling the clock in the C inputs of flip flops

4-bit register with parallel load Cont...

 


Fig. 6-2 4-Bit Register with Parallel Load

Fall 2021

Register with Parallel Load Cont...

- A 4-bit register with a load control input that is directed through gates and into the D inputs of the flip-flops is shown in Fig 6-2
- The load input to the register determines the action to be taken with each clock pulse
- When the **load** input is **1**, the data in the four inputs are **transferred** into the register with next **positive edge** of the clock
- When the **load** input is **0**, the outputs of the flip flops are connected to their respective inputs
- The **feedback** connection from output to inputs is necessary because the D-flip flop doesn't have a "**no change**" condition
- With each clock edge the D input determines the next state of the register. To leave the **output unchanged** it is necessary to make the **D input** equal to **present value** of the **output**
- The clock pulses are applied to the C inputs at all times. The **load** input **determines** whether the next pulse will accept new information or leave the information in the register intact
- The transfer of information from the data inputs or the outputs of the register is done **simultaneously** with all four bits in response to clock edge

Shift Registers

- A **Shift register** is a register capable of **shifting** its binary **information** in one or both directions
- It consists of a chain of **flip flops** in **cascade**, with output of one flip flop connected to the input of next flip flop
- All flip flops receive **common clock pulses** which activate the shift from one stage to the next
- A simplest possible shift register uses only flip flops and is shown in Fig 6-3

 


Fig. 6-3 4-Bit Shift Register


Shift Registers

- The output of a given flip-flop is connected to the D input of the flip-flop at its right
- Each clock pulse **shifts** the contents of the register **one bit position** to the right
- The **serial input** determines what goes into the left-most flip flop during the shift
- The **serial output** is taken from the output of the rightmost flip flop
- If it is required to **control** the shift so that it occurs only with certain pulses but not with others then we **inhibit** the clock from the input of the register to prevent it from shifting. Shift is then controlled by connecting the clock through an AND gate with an input that controls the shift


Serial Transfer

- A digital systems can work either in **serial** transfer mode or **parallel** transfer mode
 - Serial transfer
 - Information is transferred one bit at a time
 - shifts the bits out of the source register into the destination register
 - Parallel transfer
 - All the bits of the register are transferred at the same time
- The serial transfer of information from register A to register B is done with shift registers as shown in Fig 6-4
- The serial output (SO) of register A is connected to the serial input (SI) of register B
- To **prevent the loss** of information stored in the source register, the information in register A is made to **circulate** by connecting the serial output to its serial input

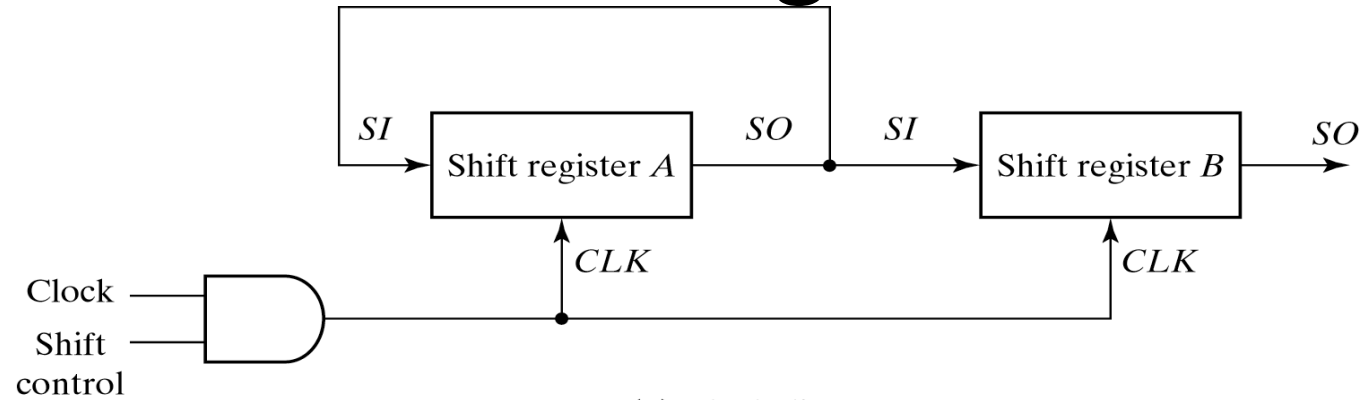Example: Serial Transfer from Register A to Register B



(a) Block diagram

 

(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B

Fall 2021

Example: Serial Transfer from Register A to Register B

- The initial content of **register B** is shifted out through its serial output and is **lost** unless it is transferred to a third shift register
- The **shift control** input determines when and how many **times** the registers are **shifted**
- This is done with an AND gate that allows clock pulse to pass into the CLK terminals only when the shift **control** is **active**
- Suppose the shift register have **four bits** each. The control unit that supervises the transfer must be designed in such a way that it enables the shift register, through the shift control signal, for a fixed time of **four clock pulses**. (as shown in timing diagram of Fig 6-4 b)
- The shift **shift control** is **synchronized** with the **clock** and changes value just after the **negative edge** of the clock
- The next four clock pulses find the shift control signal in the active state so that the output of the AND gate connected to the CLK input produces four pulses T_1 , T_2 , T_3 and T_4 . Each **rising edge** of pulse causes a **shift in both registers**

Example: Serial Transfer from Register A to Register B

- The fourth pulse changes the shift control to 0 and the shift registers are disabled
- Assume the binary contents of A before the shift is 1011 and that of B is 0010
- The serial transfer from A to B occurs in four steps as shown in Table 6-1
- With the first pulse T_1 , the **rightmost** of **A** is shifted into **leftmost** bit of **B** and is also **circulated** into the leftmost position of A
- At the same time all bits of A and B are shifted **one position** to the **right**
- The previous serial output from B in the rightmost position is lost and its value changes from 0 to 1
- The next three pulses perform identical operations, shifting the bits of A into B , one at a time
- After the fourth shift, the shift control goes to 0 and both registers A and B have the value 1011

Example: Serial Transfer from Register A to Register B

- The contents of **A** is **transferred** into **B**, while the contents of **A** remains **unchanged**
- This is a **serial transfer** where the registers have a single serial input and a single serial output. The information is transferred one bit at a time while the registers are shifted in the same direction

Table 6-1
Serial-Transfer Example

Timing Pulse	Shift Register A	Shift Register B
Initial value	1 0 1 1	0 0 1 0
After T_1	1 1 0 1	1 0 0 1
After T_2	1 1 1 0	1 1 0 0
After T_3	0 1 1 1	0 1 1 0
After T_4	1 0 1 1	1 0 1 1

Serial Addition

- Operation in digital computers are usually done in **parallel** because this is **faster** mode of operation
- **Serial** operations are **slower** but have the advantage of requiring **less equipment**
- We see here a serial adder (the parallel counterpart was discussed in section 4-4, Binary Adder)
- The two binary numbers to be added serially are stored in two shift registers
- Bits are added one pair at a time through a single full adder (FA) circuit, as shown in Fig 6-5
- The carry out of the full adder is transferred to a D flip flop
- The output of this flip flop is then used as the carry input for the next pair of significant bits
- The sum bit from the S output of the full adder could be transferred into a third shift register

Serial Addition using D Flip-Flops

- By shifting the sum into A while the bits of A are shifted out, it is possible to use one register for storing both the augends and the sum bits
- The serial input of register B can be used to transfer a new binary number while the addend bits are shifted out during the addition

 


Fig. 6-5 Serial Adder

Serial Adder using JK Flip-Flops


Table 6-2
State Table for Serial Adder

Present State Q	Inputs $x \quad y$		Next State Q	Output S	Flip-Flop Inputs	
					J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = x y$$

$$K_Q = x' y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

 

Circuit Diagram

$$J_Q = x y$$

$$K_Q = x' y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$


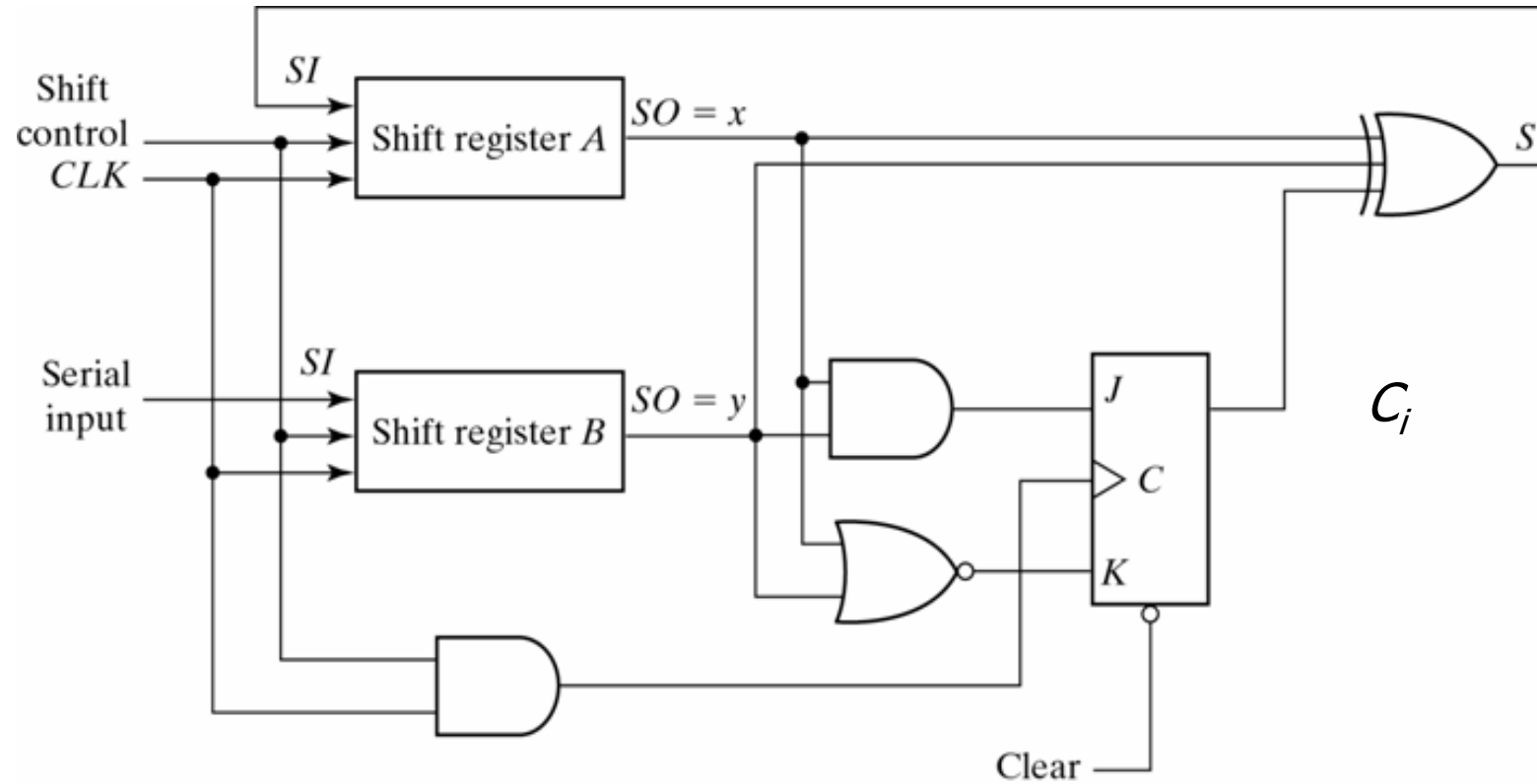


Fig. 6-6 Second form of Serial Adder

Universal Shift Register

- Shift registers can be either Unidirectional or Bidirectional.
- A universal register has both direction shifts & parallel load/out capabilities. A list of capabilities is as under:-
 - A *clear* control to clear the register to 0.
 - A *clock* input to synchronize the operations.
 - A *shift-right* control to enable the shift right operation and the *serial input* and *output* lines associated w/ the shift right.
 - A *shift-left* control to enable the shift left operation and the *serial input* and *output* lines associated w/ the shift left.
 - A *parallel-load* control to enable a parallel transfer and the *n parallel input* lines associated w/ the parallel transfer.
 - *n parallel output* lines
 - A control state that leaves the information in the register unchanged in the presence of the clock.

Example: 4-bit universal shift register

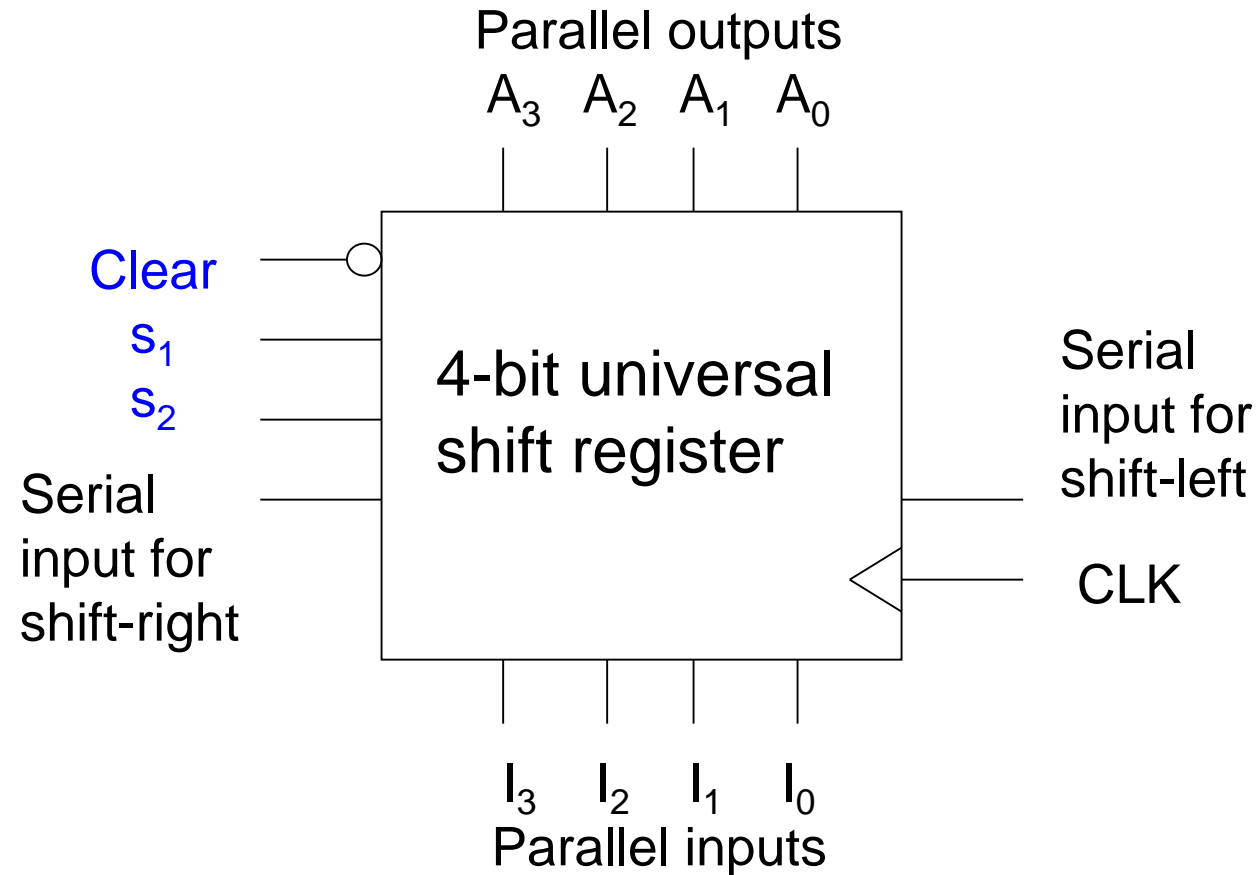

Example: 4-bit universal shift register

Function table

Clear	S_1	S_0	A_3^+	A_2^+	A_1^+	A_0^+	(Operation)
0	x	x	0	0	0	0	Clear
1	0	0	A_3	A_2	A_1	A_0	No change
1	0	1	sri	A_3	A_2	A_1	Shift right
1	1	0	A_2	A_1	A_0	sli	Shift left
1	1	1	I_3	I_2	I_1	I_0	Parallel load

Example: 4-bit universal shift register

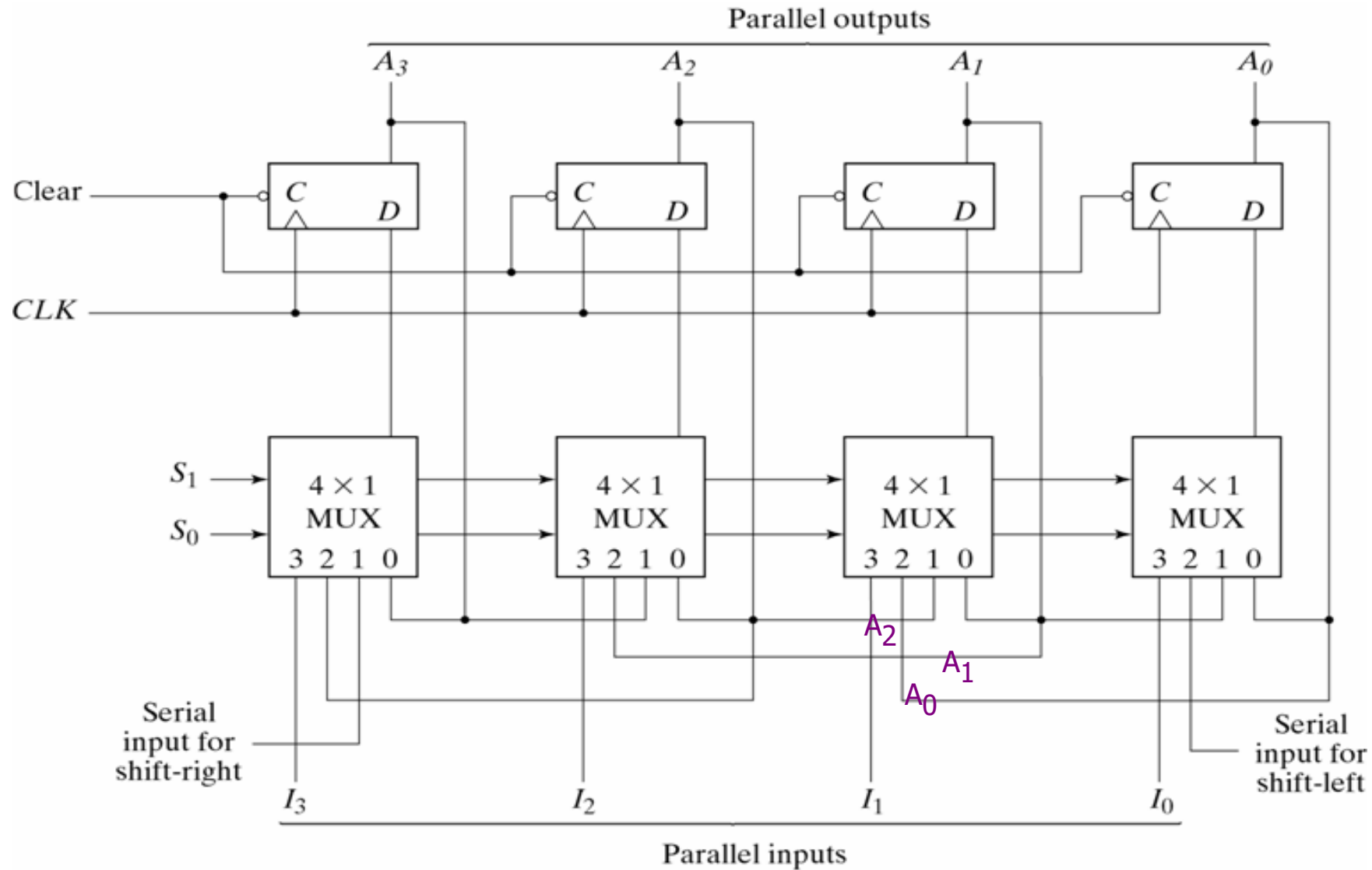


Fig. 6-7 4-Bit Universal Shift Register

The End