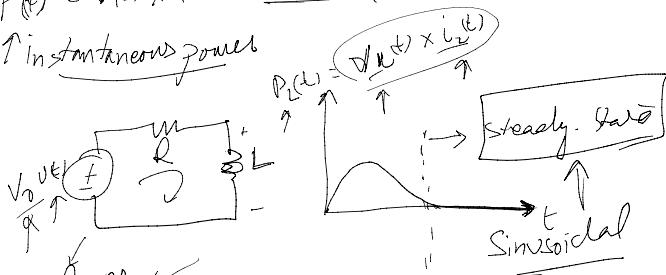


AC - Power Analysis


$$P(t) = V(t) \times i(t) \text{ Watts (W)}$$

Instantaneous power



Average Power

Real power

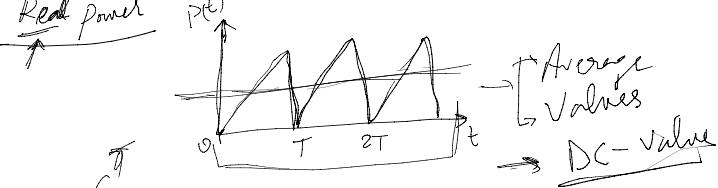

$$\frac{1}{T} \int_0^T P(t) dt = P \text{ Watts (W)}$$

Average power in SSS:

$$V(t) = V_m \cos(\omega t + \phi_v)$$

$$i(t) = I_m \cos(\omega t + \phi_i)$$

$$P(t) = V(t)i(t) = V_m \cos(\omega t + \phi_v) \times I_m \cos(\omega t + \phi_i)$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i)$$

$$P = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) \text{ Watts (W)}$$

Resistor

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R$$


$$2\omega s \propto R = \cos(\pi + j) + \cos(\pi - y)$$


Inductor / Capacitor

$$P_{ave} = 0 \text{ Watts}$$

$$P = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$$

Resistor:

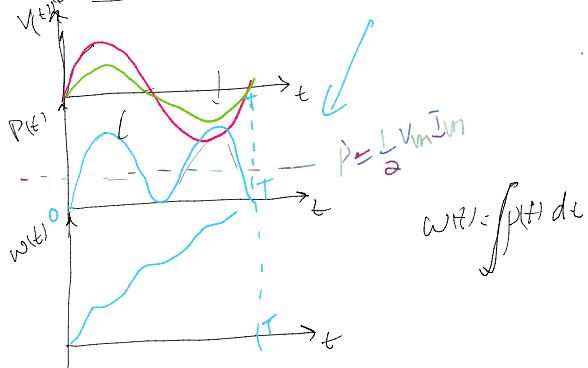


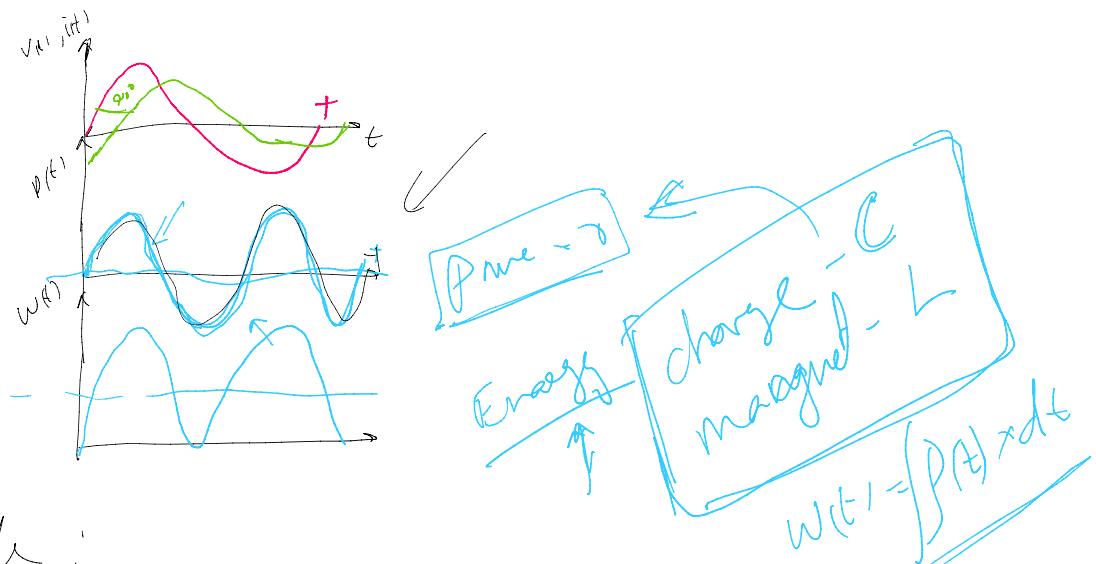

Example :

$$Z_L = 8 - 11j\Omega$$

$$\underline{V} = 5 \angle 20^\circ V$$

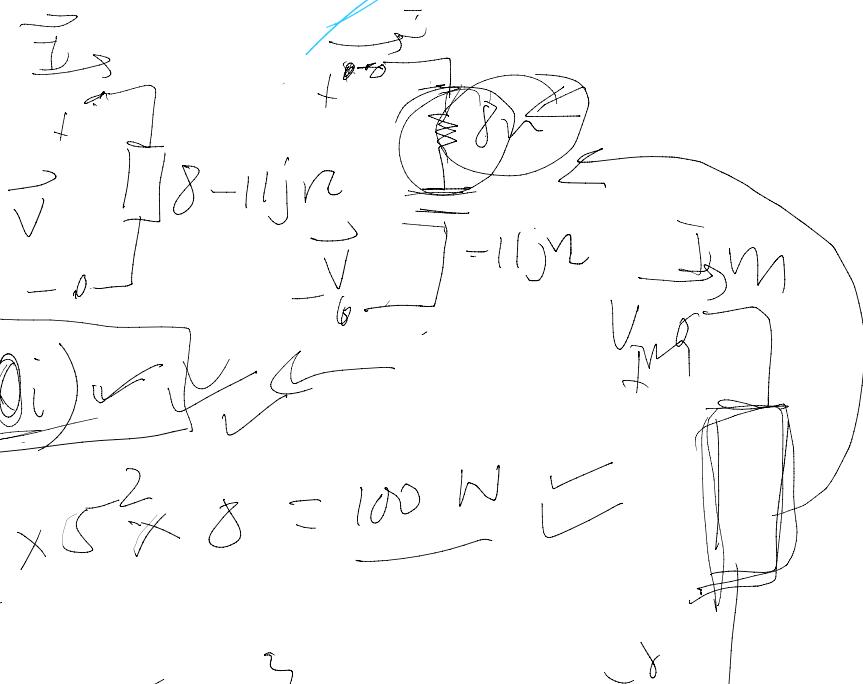

$$(1) \quad P = \frac{1}{2} V_m I_m \cos(\phi_V - \phi_i)$$

$$(2) \quad P = \frac{1}{2} I_m^2 R = \frac{1}{2} \times 5^2 \times 8 = 100 \text{ W}$$

$$V = 68.01 \angle -33.97^\circ V$$

$$P = \frac{1}{2} 68.01 \times 5 \cos(-33.97^\circ - 20^\circ)$$

$$= 100 \text{ Watts}$$

$$P = \frac{1}{2} V_m I_m \cos(\phi_V - \phi_i)$$

