

# EE-421: Digital System Design

Assignment Statements:  
Blocking (=) vs Non-Blocking (<=)

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

# Statements Ordering in an Always Block

# Always Block: Statements Order

- An important property of the always block is that:
  - the statements it contains are evaluated in the order given in the code:
    - **[STATEMENTS ORDER IS IMPORTANT]**
  - [!!!!] This contrasts with the continuous assignment statements (recall assign statement), which are evaluated concurrently and hence have no meaningful order!

# Example: Statement Ordering inside an Always block

```
module mux (w0, w1, s, f);  
  input w0, w1, s;  
  output reg f;  
  always @(w0, w1, s)  
  begin  
    f = w0;  
    if (s == 1)  
      f = w1;  
  end  
endmodule
```

Still a MUX

```
module mux (w0, w1, s, f);  
  input w0, w1, s;  
  output reg f;  
  always @(w0, w1, s)  
  begin  
    if (s == 1)  
      f = w1;  
    f = w0;  
  end  
endmodule
```

Not a MUX Anymore

**Verilog semantics specify that a signal assigned multiple values in an always construct retains the last assignment.**

# Verilog Procedural Assignment Statements

# Procedural Assignment Statements

- There are two kinds of assignments in an always block:
  1. Blocking assignments,
    - denoted by the `=` symbol
  2. Non-blocking assignments,
    - denoted by the `<=` symbol.

# Blocking and Non-Blocking Assignments

## Blocking (=)

```
always @ (a)
begin
    a = 2'b01;
    // a is 2'b01
    b = a;
    // b is now 2'b01 as well
end
```

- Each assignment is made immediately
- Process waits until the first assignment is complete, it blocks progress

## Non-blocking (<=)

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
    // all assignments are made here
    // b is not (yet) 2'b01
end
```

- All assignments are made at the end of the block
- All assignments are made in parallel, process flow is not-blocked

# Example: Blocking and Non-Blocking Assignments



## Blocking (=)

```
initial  
begin  
    a = #5 b;  
    c = #10 a;  
end
```

## Nonblocking (<=)

```
initial  
begin  
    a <= #5 b;  
    c <= #10 a;  
end
```

Assuming initially a=1 and b=2

  



# Example: Blocking Assignment

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    = a ^ b ;           // p    = 0    1  
    g    = a & b ;           // g    = 0    0  
    s    = p ^ cin ;        // s    = 0    1  
    cout = g | (p & cin) ;  // cout = 0    0  
end
```

- If **a** changes to '1'
  - All values are updated in order they are specified!

# The Same Example: Non-Blocking Assignment

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 0    1  
    g    <= a & b ;           // g    = 0    0  
    s    <= p ^ cin ;        // s    = 0    0  
    cout <= g | (p & cin) ;  // cout = 0    0  
end
```

- If **a** changes to '1'
  - All assignments are concurrent
  - When **s** is being assigned, **p** is still 0

# Summary:

## Blocking and Non-Blocking Assignments

- There are two kinds of assignments in an always block:
  1. Blocking assignments,
    - denoted by the `=` symbol
    - Executed in the order they are specified in a sequential block
  2. Non-blocking assignments,
    - denoted by the `<=` symbol
    - Allow scheduling of assignments without blocking execution of the statements that follow in a sequential block

# Synthesis of Blocking vs Non-Blocking Assignments

# Example: Blocking vs Non-Blocking


- Draw the circuit (netlist) corresponding to each of the following code snippets:

```
module top (A, f);  
  input [2:0] A;  
  output f;  
  reg f;  
  
  always @(A)  
  begin  
    f <= A[1] | A[0];  
    f <= f & (A[2] & A[1]);  
  end  
  
endmodule
```


```
module top (A, f);  
  input [2:0] A;  
  output f;  
  reg f;  
  
  always @(A)  
  begin  
    f = A[1] | A[0];  
    f = f & (A[2] & A[1]);  
  end  
  
endmodule
```

# Example: Blocking vs Non-Blocking

```
module top (A, f);  
  input [2:0] A;  
  output f;  
  reg f;  
  
  always @(A)  
  begin  
    f <= A[1] | A[0];  
    f <= f & (A[2] & A[1]);  
  end  
  
endmodule
```

 

```
module top (A, f);  
  input [2:0] A;  
  output f;  
  reg f;  
  
  always @(A)  
  begin  
    f = A[1] | A[0];  
    f = f & (A[2] & A[1]);  
  end  
  
endmodule
```

 

- There are two key aspects of the Verilog semantics relevant to this code:
  - 1. The results of non-blocking assignments are visible only after all of the statements in the always block have been evaluated.
  - 2. When there are multiple assignments to the same variable inside an always block, the **result of the last assignment** is maintained.

# Blocking vs Non-Blocking: Avoid Confusion

- Notion of “current time step” is tricky in synthesis, so to guarantee that your simulation matches the behavior of the synthesized circuit, follow these rules:
  1. Use blocking assignments to model combinational logic within an always block.
  2. Use non-blocking assignments to implement sequential logic.
  3. Do not mix blocking and non-blocking assignments in the same always block.
    - It is not possible to model both a combinational output and a sequential output in a single always block.
  4. Do not make assignments to the same variable from more than one always block:
    - Would yield multi-driver synthesis error; example ahead
      - not possible electrically, by the way!

# THANK YOU

