

EE-421: Digital System Design

Doing MATHS on an FPGA

Arithmetic Circuits for Number Crunching:
Adders,
Subtractors,
Multipliers and Dividers

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Roadmap

Arithmetic Circuits

- Addition
- Subtraction
- Multiplication
- Division



Allegory of Arithmetic, from "Margarita Philosophica," 1504 by Gregor Reisch

ADDITION and SUBTRACTION

Design Tradeoffs


There are many ways to build adders (or any function).

Which is the right implementation?

Depends on your system's requirements

Optimization Metrics:

- Speed
- Power
- Area

 

Single Cycle vs. Multi Cycle Arithmetic

Arithmetic units can be written as:

1. Combinational Blocks

- Outputs depend only on inputs
- Results available in one clock-cycle

2. Multi-Cycle

- Result is computed over multiple cycles
- Can be much smaller (require fewer logic resources)
- Can be pipelined for higher clock frequency


Common Adder Architectures

- Carry Ripple/Propagate Adder
- Carry Select Adder
- Carry Look-ahead Adder
- Carry Save Adder

Quick Review of Half and Full Adders

Review: 1-Bit (Half) Adder


A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

What if we want to add more than one bit?

Review: Full Adder

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Aside: How do we perform Subtraction?

Aside: Subtraction

Can perform subtraction with addition

$$A - B = A + (-B)$$

Recall, Two's Complement Numbers:

$$-B = \overline{B} + 1$$


(Invert all bits of **B** and add 1)

$$A - B = A + \overline{B} + 1$$

Carry Propagate/Ripple Adder

Carry Propagate Adder (CPA)

 Connect Full Adders to make Carry Propagate Adder (Ripple Adder)




- Right-most stage is least-significant bit (LSB)
- Carry-out of previous stage feeds into Carry-In of next stage
- Can extend to any number of bits
 - not entirely true, we'll see that later...

How fast is this Ripple Carry Adder?

Delay of a Full Adder

 What is the critical path delay of a Full Adder?



Assume all gates have the same
gate propagation delay t_{PD}


If inputs **A**, **B**, **C_{in}** arrive at time 0,

- **S** is ready after **t_{PD}**
A, B, C_{in} \Rightarrow XOR Gate \Rightarrow S
- **C_{out}** is ready after **$3 t_{PD}$**
A, B \Rightarrow OR \Rightarrow AND \Rightarrow OR \Rightarrow C_{out}

Critical Path Delay is $3 t_{PD}$


Delay of Carry Propagate Adder

Consider 2-bit Carry Propagate Adder

 

Delay of Carry Propagate Adder

Consider 2-bit Carry Propagate Adder

 

Inputs **A0**, **A1**, **B0**, **B1** arrive at time 0,


- **C_{out}** of first bit is ready after **3 t_{PD}**
- Delay of next **C_{out}** is ready after another **2 t_{PD}**

Critical Path Delay is 5 t_{PD}

Delay of Carry Propagate Adder

Delay for an N-bit Carry Propagate Adder is


$$2(N-1)t_{PD} + 3t_{PD}$$

 

Delay is proportional to $N \Rightarrow$ **SLOW** for large N

 Problem with Carry Propagate Adder

Carry Propagate Adders are slow because the high-order (sum) bits need to wait for the carry-in from lower-order bits




Delay is proportional to $N \Rightarrow$ SLOW for large N

When 32- or 64-bit numbers are used, this delay may become unacceptably high !!!

 
Problem with Carry Propagate Adder

When 32- or 64-bit numbers are used, this delay may become unacceptably high !!!



Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **S**tephen Brown and **Z**vonko Vranesic. [**S&Z**]
 - S&Z,
 - Chapter-3
 - 3.2



THANK YOU

