

EE-421: Digital System Design

Sequential-Circuit Building Blocks: Register and Counter

Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Register(s)

D flip-flop with Synchronous reset

```
module flipflop (D, Clock, Resetn, Q);  
  input D, Clock, Resetn;  
  output reg Q;  
  
  always @(posedge Clock)  
    if (!Resetn)  
      Q <= 0;  
    else  
      Q <= D;  
  
endmodule
```


An N-BIT Register

- Since registers of different sizes are often needed in logic circuits, it is advantageous to define a register module for which the number of flip-flops can be easily changed.

An N-BIT Register

```
module regn (D, Clock, Resetn, Q);  
    parameter n = 16;  
    input [n-1:0] D;  
    input Clock, Resetn;  
    output reg [n-1:0] Q;  
  
    always @(negedge Resetn, posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else  
            Q <= D;  
  
endmodule
```

A 4-bit Shift Register

 


(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

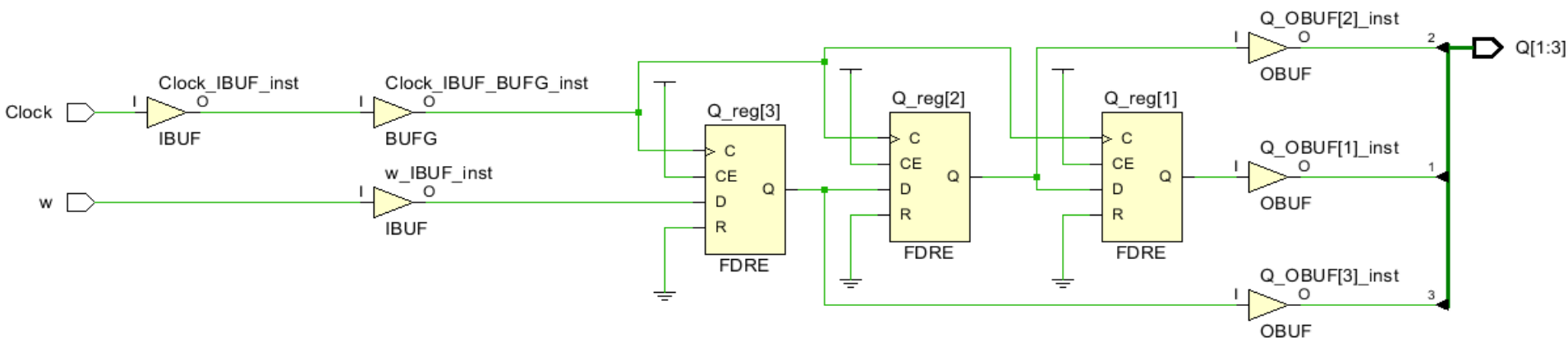
(b) A sample sequence

Expressing a 3-bit Shift Register

```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  always @(posedge Clock)  
  begin  
    Q[3] <= w;  
    Q[2] <= Q[3];  
    Q[1] <= Q[2];  
  end  
endmodule
```




A 4-bit Parallel Access Shift Register

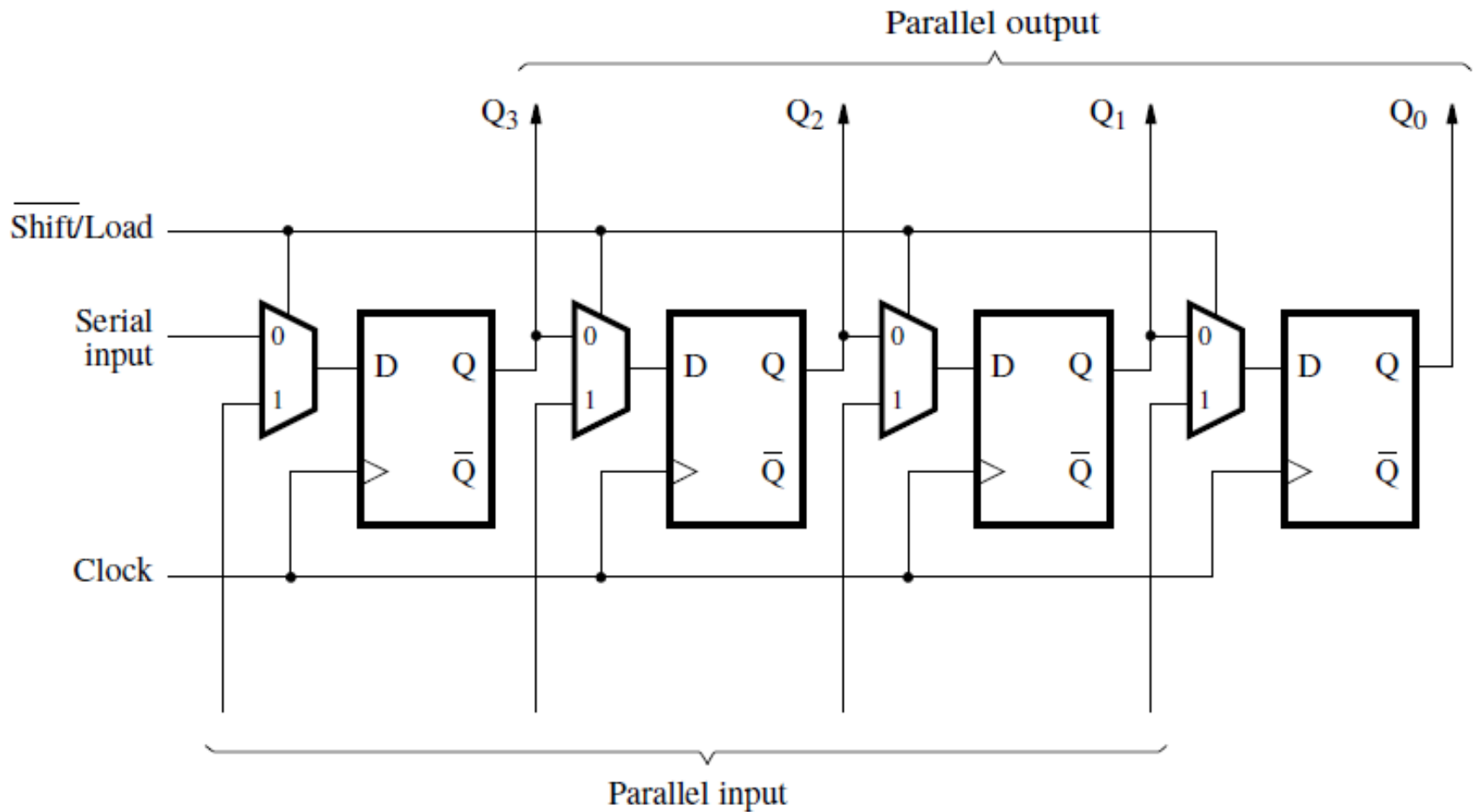


A 4-bit Parallel Access Shift Register

 - Approach-1:
 - Hierarchical approach that uses sub-circuits
 - Each subcircuit consists of a D flip-flop with a 2-to-1 multiplexer connected to the D input.



A 4-bit Parallel Access Shift Register

 
- Approach-1:
 - Hierarchical approach that uses sub-circuits
 - Each subcircuit consists of a D flip-flop with a 2-to-1 multiplexer connected to the D input.



```
module muxdff (D0, D1, Sel, Clock, Q);  
  input D0, D1, Sel, Clock;  
  output reg Q;  
  
  always @(posedge Clock)  
    if (!Sel)  
      Q <= D0;  
    else  
      Q <= D1;  
  
endmodule
```

A 4-bit Parallel Access Shift Register

 - Approach-1:
 - Hierarchical approach that uses sub-circuits
 - Each subcircuit consists of a D flip-flop with a 2-to-1 multiplexer connected to the D input.




```
module muxdff (D0, D1, Sel, Clock, Q);  
  input D0, D1, Sel, Clock;  
  output reg Q;  
  
  wire D;  
  assign D = Sel ? D1 : D0;  
  
  always @(posedge Clock)  
    Q <= D;  
  
endmodule
```

A 4-bit Parallel Access Shift Register

```
module shift4 (R, L, w, Clock, Q);  
  input [3:0] R;  
  input L, w, Clock;  
  output [3:0] Q;  
  wire [3:0] Q;
```

```
  muxdff Stage3 (w, R[3], L, Clock, Q[3]);  
  muxdff Stage2 (Q[3], R[2], L, Clock, Q[2]);  
  muxdff Stage1 (Q[2], R[1], L, Clock, Q[1]);  
  muxdff Stage0 (Q[1], R[0], L, Clock, Q[0]);
```

```
endmodule
```

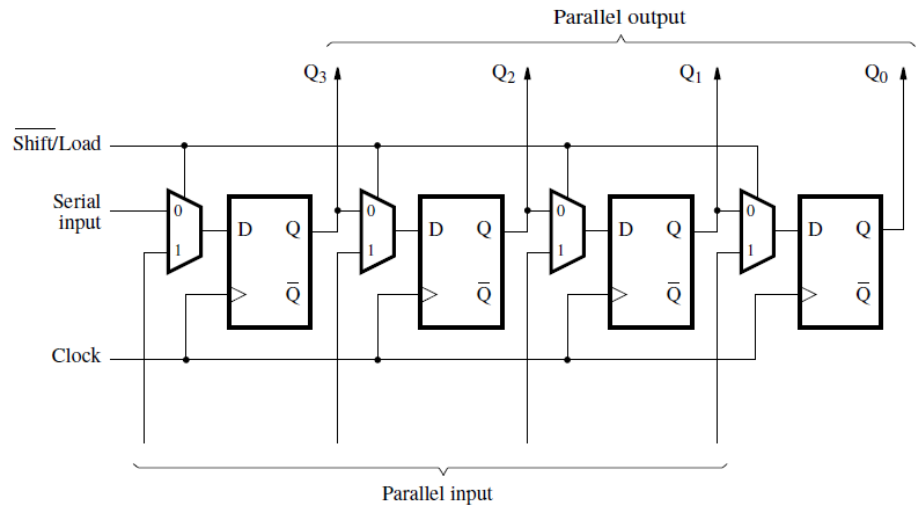

A 4-bit Parallel Access Shift Register

- Approach-2:

```
module shift4 (R, L, w, Clock, Q);  
    input [3:0] R;  
    input L, w, Clock;  
    output reg [3:0] Q;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else  
            begin  
                Q[0] <= Q[1];  
                Q[1] <= Q[2];  
                Q[2] <= Q[3];  
                Q[3] <= w;  
            end  
  
    endmodule
```

A n-bit Parallel Access Shift Register

```
module shiftn (R, L, w, Clock, Q);  
    parameter n = 16;  
    input [n-1:0] R;  
    input L, w, Clock;  
    output reg [n-1:0] Q;  
    integer k;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else  
            begin  
                for (k = 0; k < n-1; k = k+1)  
                    Q[k] <= Q[k+1];  
                Q[n-1] <= w;  
            end  
  
    endmodule
```


Counters

Synchronous Up-Counter

Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Counters Implemented as State Machine?

- Consider an 8-bit counter

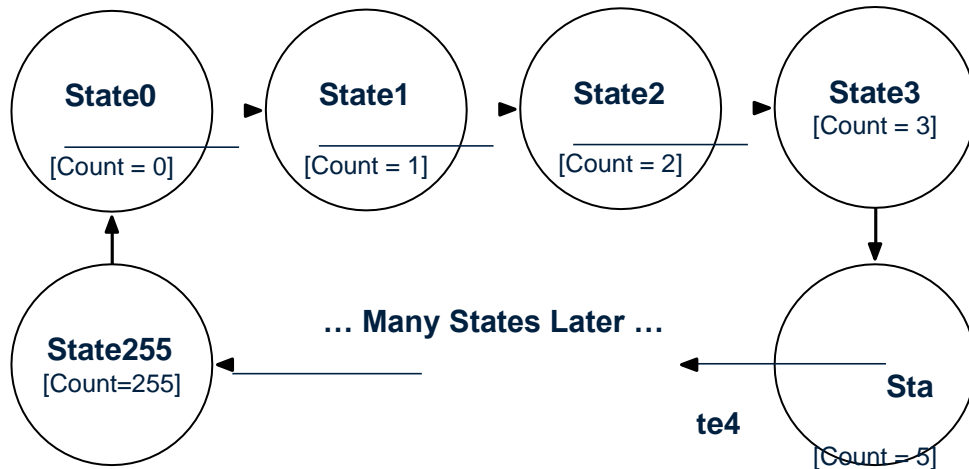

```
always @ (p_state,w)
begin
  case (p_state)
    State0: n_state = State1;
    State1: n_state = State2;
    State2: n_state = State3;
    .....
    State255: n_state = State0;
  endcase
end
```

Up-Counter

```
module upcount (Resetn, Clock, E, Q);  
    input Resetn, Clock, E;  
    output reg [3:0] Q;  
  
    always @(negedge Resetn, posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else if (E)  
            Q <= Q + 1;  
  
endmodule
```

Up-Counter with Parallel Load

```
module upcount (R, Resetn, Clock, E, L, Q);  
    input [3:0] R;  
    input Resetn, Clock, E, L;  
    output reg [3:0] Q;  
  
    always @(negedge Resetn, posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q + 1;  
  
endmodule
```

A down-counter with a Parallel Load


```
module downcount (R, Clock, E, L, Q);  
    parameter n = 8;  
    input [n-1:0] R;  
    input Clock, L, E;  
    output reg [n-1:0] Q;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q - 1;  
  
endmodule
```

Up/Down Counter

```
module updowncount (R, Clock, L, E, up_down, Q);  
    parameter n = 8;  
    input [n-1:0] R;  
    input Clock, L, E, up_down;  
    output reg [n-1:0] Q;  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q + (up_down ? 1 : -1);  
  
endmodule
```

Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **Stephen Brown** and **Zvonko Vranesic**. [**S&Z**]
 - S&Z,
 - Chapter-5
 - 5.1 – 5.11 for general review
 - 5.13 for Verilog



THANK YOU

