


EE-421: Digital System Design

Doing MATHS on an FPGA

Arithmetic Circuit:
(Revisiting) Adder for Performance
Carry Look-Ahead Adder


Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]

Carry Look-Ahead Adder (CLA)

 


Mr. Carry

Approach

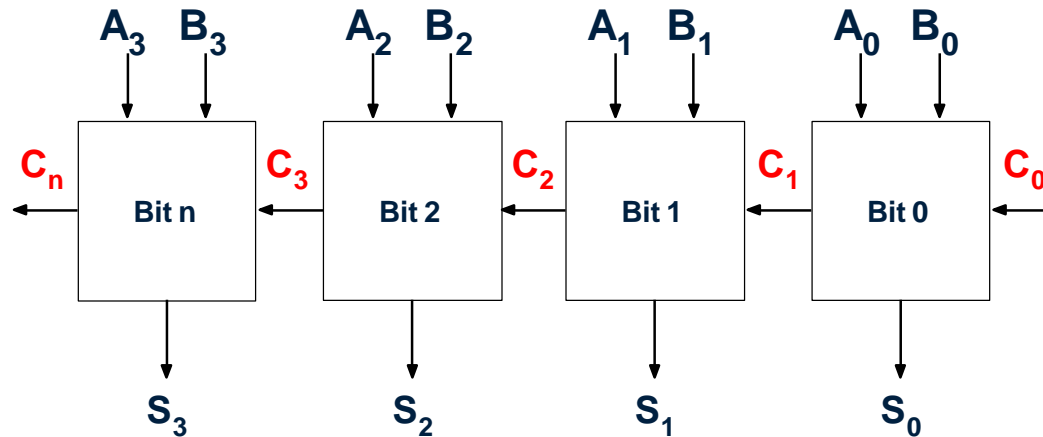

- Attempt (look-ahead) to evaluate quickly for each stage whether the carry-in from the previous stage will have a value 0 or 1:
 - If a correct evaluation can be made in a relatively short time, then the performance of the complete adder will be improved.

Approach – how?

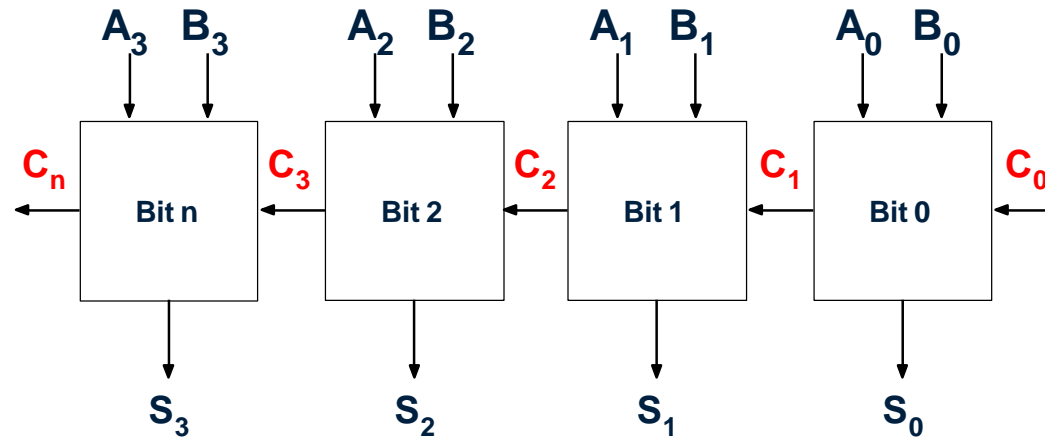

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$C_{i+1} = G_i + P_i C_i$$

G = Generate

P = Propagate

Generate Term

A_i, B_i would generate a carry if both are 1

A_i	B_i	G_i
0	0	0
0	1	0
1	0	0
1	1	1

$$G_i = A_i \text{ and } B_i$$

Propagate Term

A_i, B_i would propagate a carry if either is 1

A_i	B_i	P_i
0	0	0
0	1	1
1	0	1
1	1	1

$$P_i = A_i \text{ or } B_i$$

Approach

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = g_i + p_i c_i$$

- The function **g_i** is equal to 1 when both inputs a_i and b_i are equal to 1,
 - *regardless of the value of the incoming carry to this stage, c_i*
 - Since in this case stage i is guaranteed to generate a carry-out, **g** is called the **generate** function.
- The function **p_i** is equal to 1 when at least one of the inputs a_i and b_i is equal to 1,
 - In this case a carry-out is produced if $c_i = 1$.
 - The effect is that the carry-in of 1 is propagated through stage i ; hence p_i is called the **propagate** function.

Approach Takeaway

Pre-compute parts of carry logic

For each bit of the addition, independently calculate two terms:

- **Generate term**

$$G_i = f(A_i, B_i)$$

- **Propagate term**

$$P_i = f(A_i, B_i)$$

G_i and P_i are independent of Carry terms C_i

Then, by using the various Generate and Propagate terms, we can compute the carry terms at each bit without the ripple effect.

Approach Takeaway – (2)

$$Cout_{i+1} = \overline{G_i} \text{ or } \overline{(P_i \text{ and } Cin_i)}$$

A Carry was **GENERATED**



A Carry was **PROPAGATED**

Example: Generate Term

Does adding the i -th bits of A, B **generate** a carry?

Example: A = 011, B = 010

Look at each bit-position **INDEPENDENTLY**

Does adding bit 0 generate a Carry?

$$A + B = 01\textcolor{brown}{1} + 01\textcolor{brown}{0}$$

NO, $1 + 0 = \textcolor{brown}{0}1$ (carry NOT generated)

$$G_0 = 0$$

Does adding bit 2 generate a Carry?

$$A + B = \textcolor{brown}{0}11 + \textcolor{brown}{0}10$$

NO, $0 + 0 = \textcolor{brown}{0}0$

$$G_2 = 0$$

Does adding bit 1 generate a Carry?

$$A + B = 01\textcolor{brown}{1} + 01\textcolor{brown}{0}$$

YES, $1 + 1 = \textcolor{brown}{1}0$ (carry generated)

$$G_1 = 1$$

Example: Propagate Term

If there was a carry-in at the i -th bit, would it **propagate** to the next stage?

Example: A = 011, B = 010

Look at each bit-position **INDEPENDENTLY**

Would bit 0 propagate a Carry?

$$A + B = 011 + 010$$

YES, $1 + 0 + 1 = 10$ (carry propagated)

$$P_0 = 1$$

 hypothetical carry-in

Would bit 2 propagate a Carry?

$$A + B = 011 + 010$$

NO, $0 + 0 + 1 = 01$

$$P_2 = 0$$



hypothetical carry-in

Would bit 1 propagate a Carry?

$$A + B = 011 + 010$$

YES, $1 + 1 + 1 = 11$ (carry propagated)


$$P_1 = 1$$

 hypothetical carry-in

4-bit CLA Example

Let C_i denote the carry-in of stage i

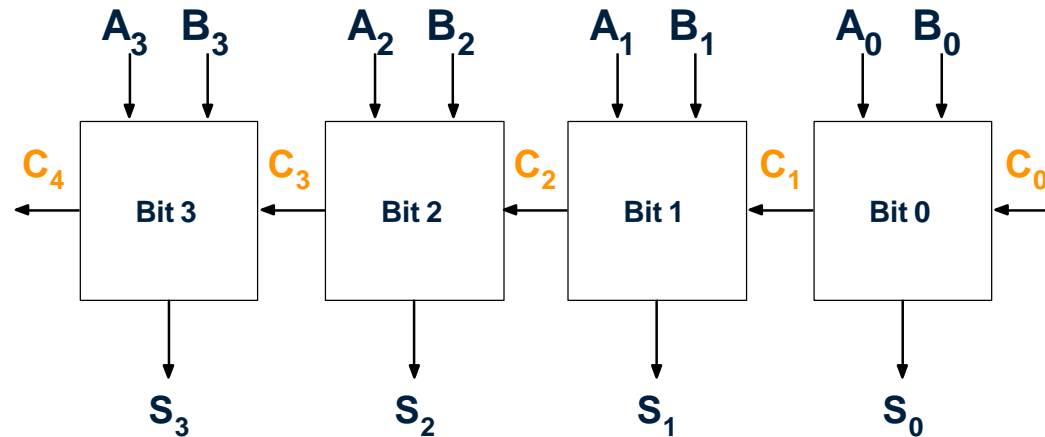this means that it is also the carry-out of the previous stage



$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1$$

$$C_3 = G_2 + P_2 \cdot C_2$$

$$C_4 = G_3 + P_3 \cdot C_3$$

Note: We are using
logical operators here:
+ means OR
. means AND

Carry Look-Ahead Logic


$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1$$

$$C_3 = G_2 + P_2 \cdot C_2$$

$$C_4 = G_3 + P_3 \cdot C_3$$

Perform Forward Substitution

 

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$

$$C_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

Carry Look-Ahead Logic


$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$

$$C_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$


AND-OR networks

 


If C_0 and all G_i and P_i terms are available at the same time,
ALL C_i terms will be ready after **2 gate delays**

No Ripple Effect!


2-bit Carry Lookahead Adder

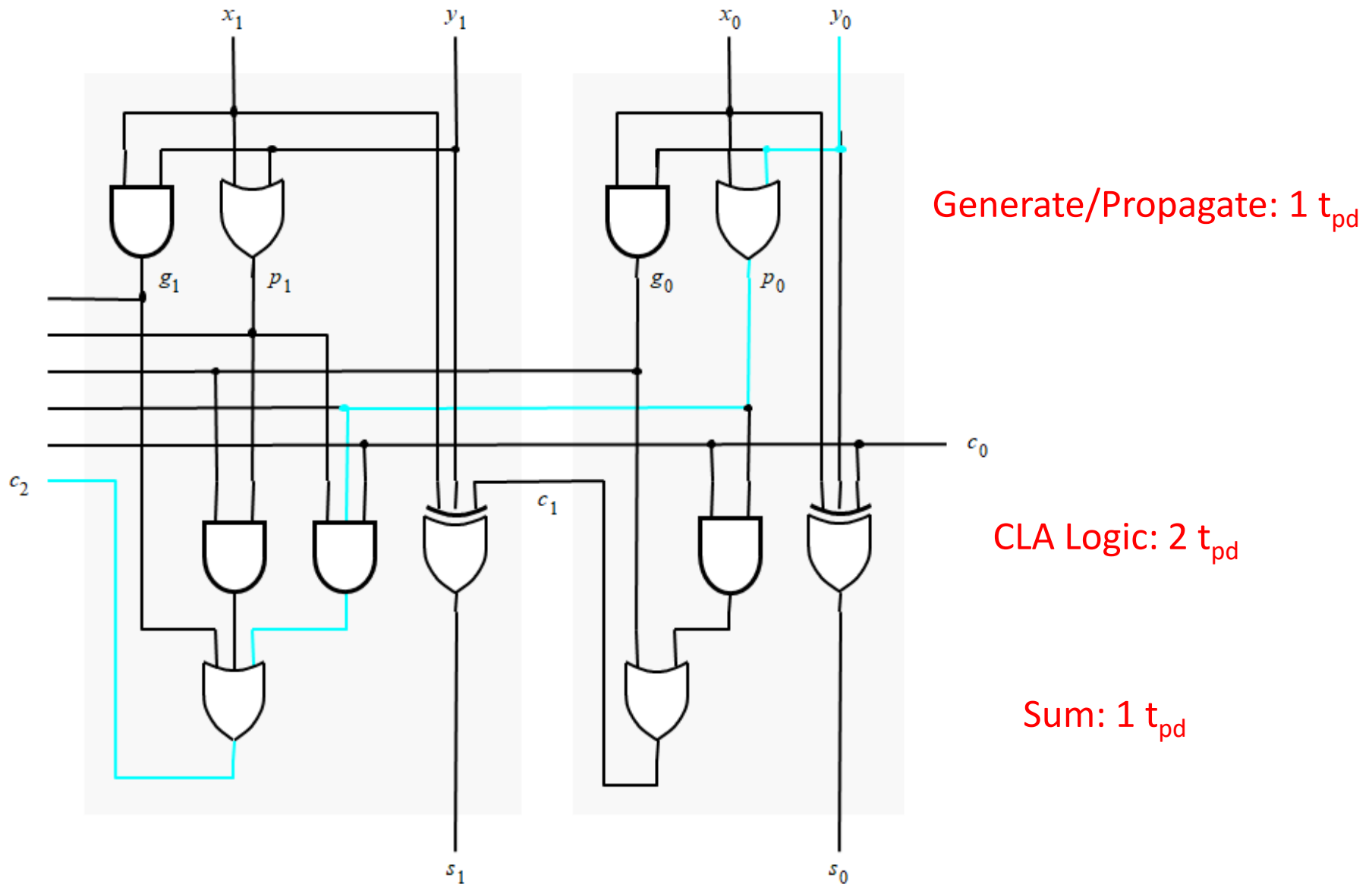


Compare: A ripple-carry adder

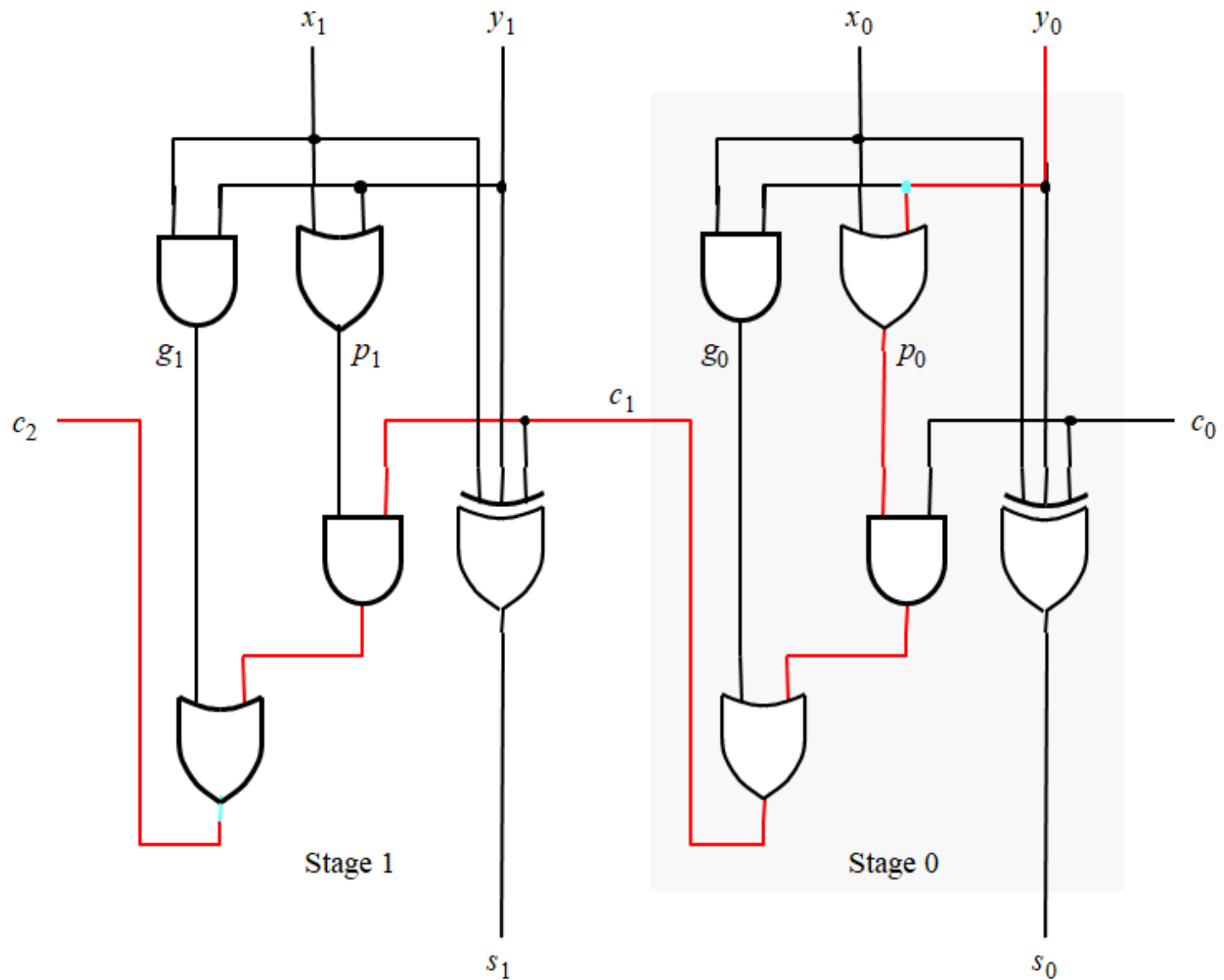


4-bit Carry Lookahead Adder

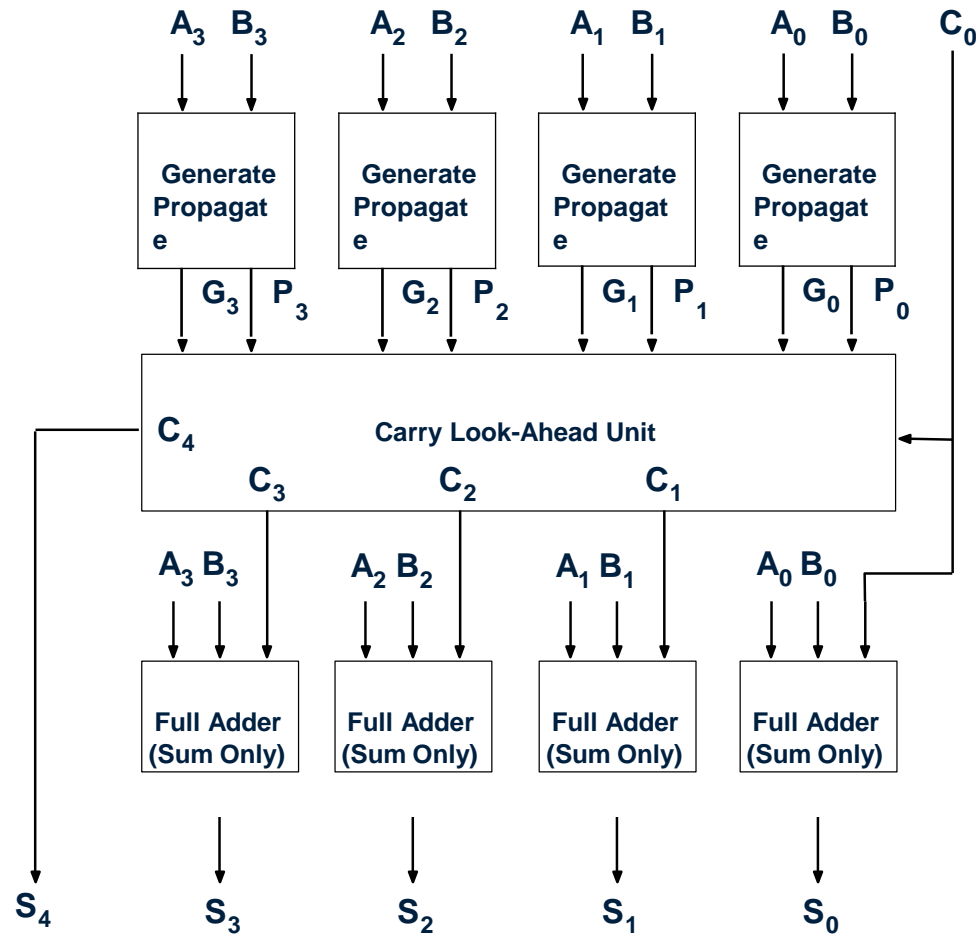

Overall Critical Path Delay

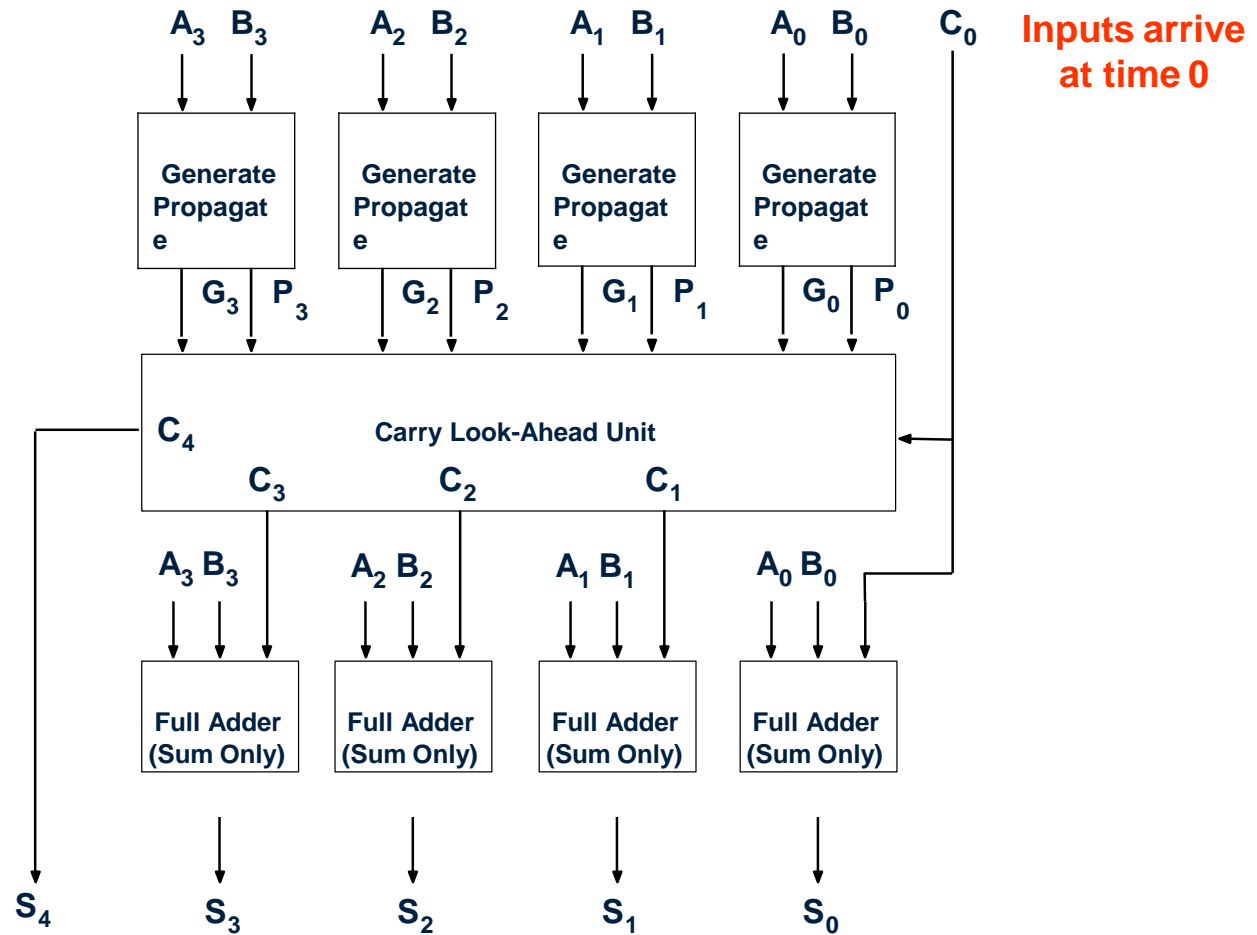


Overall Critical Path Delay

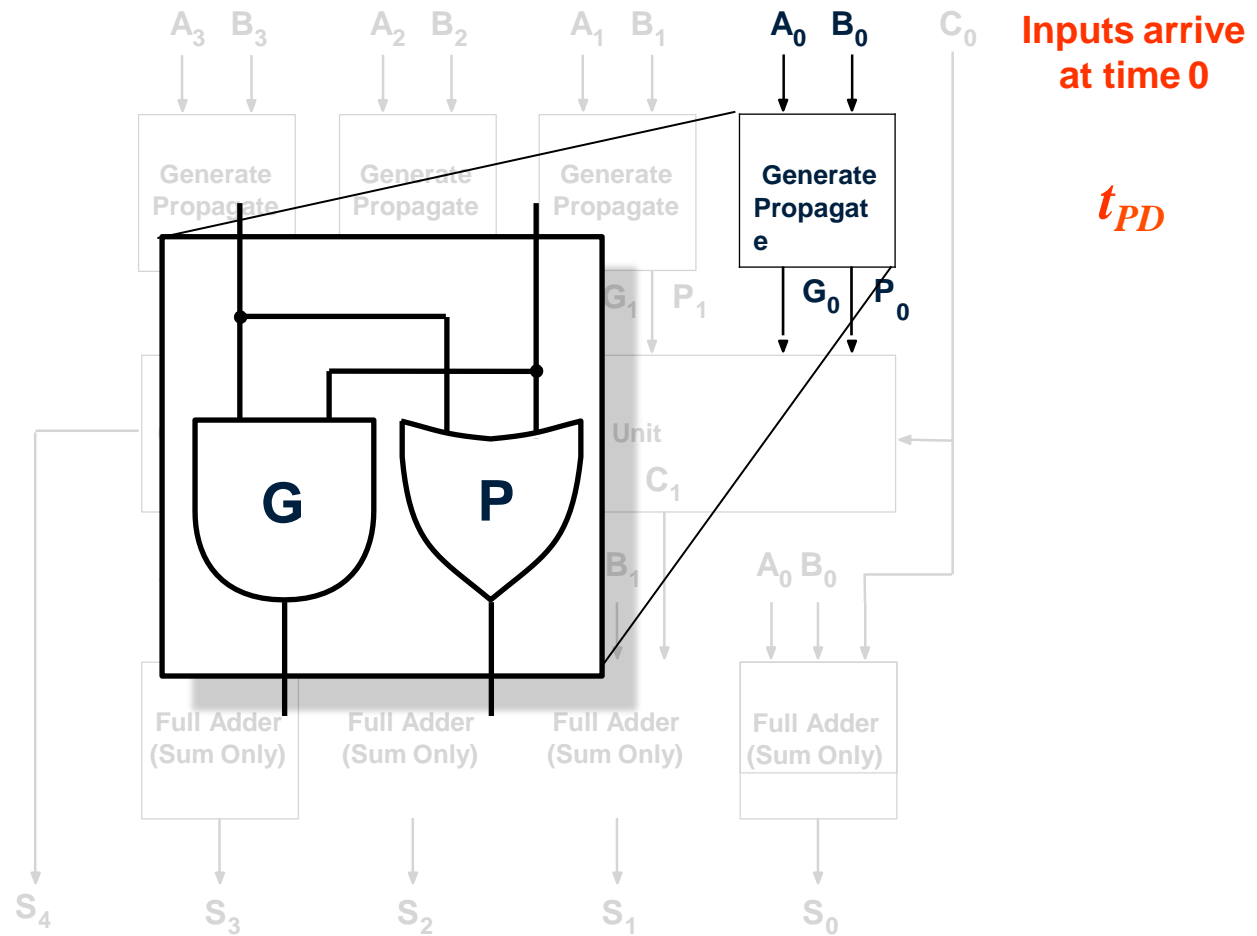


All G, P terms available after single gate delay


Overall Critical Path Delay

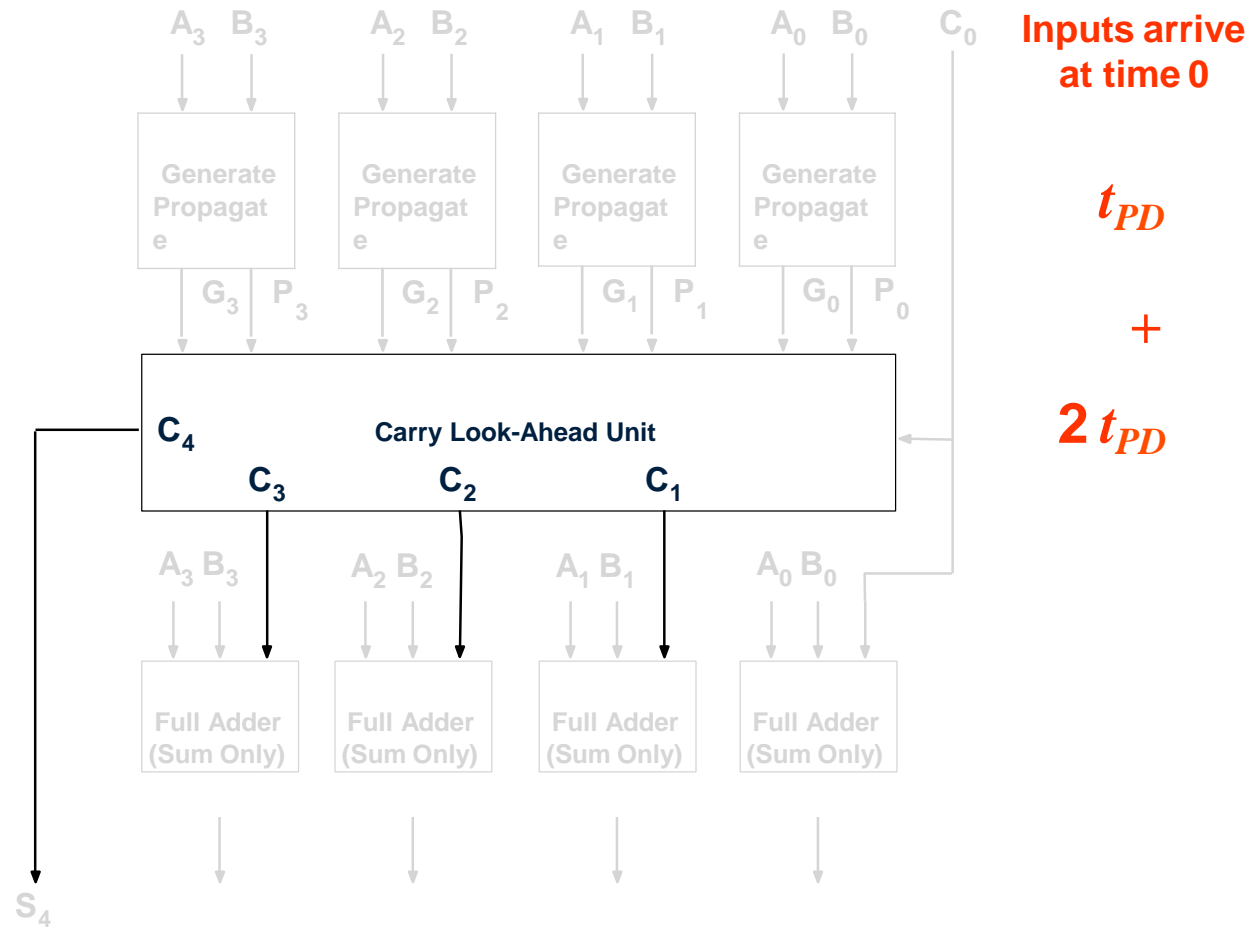

Overall Critical Path Delay

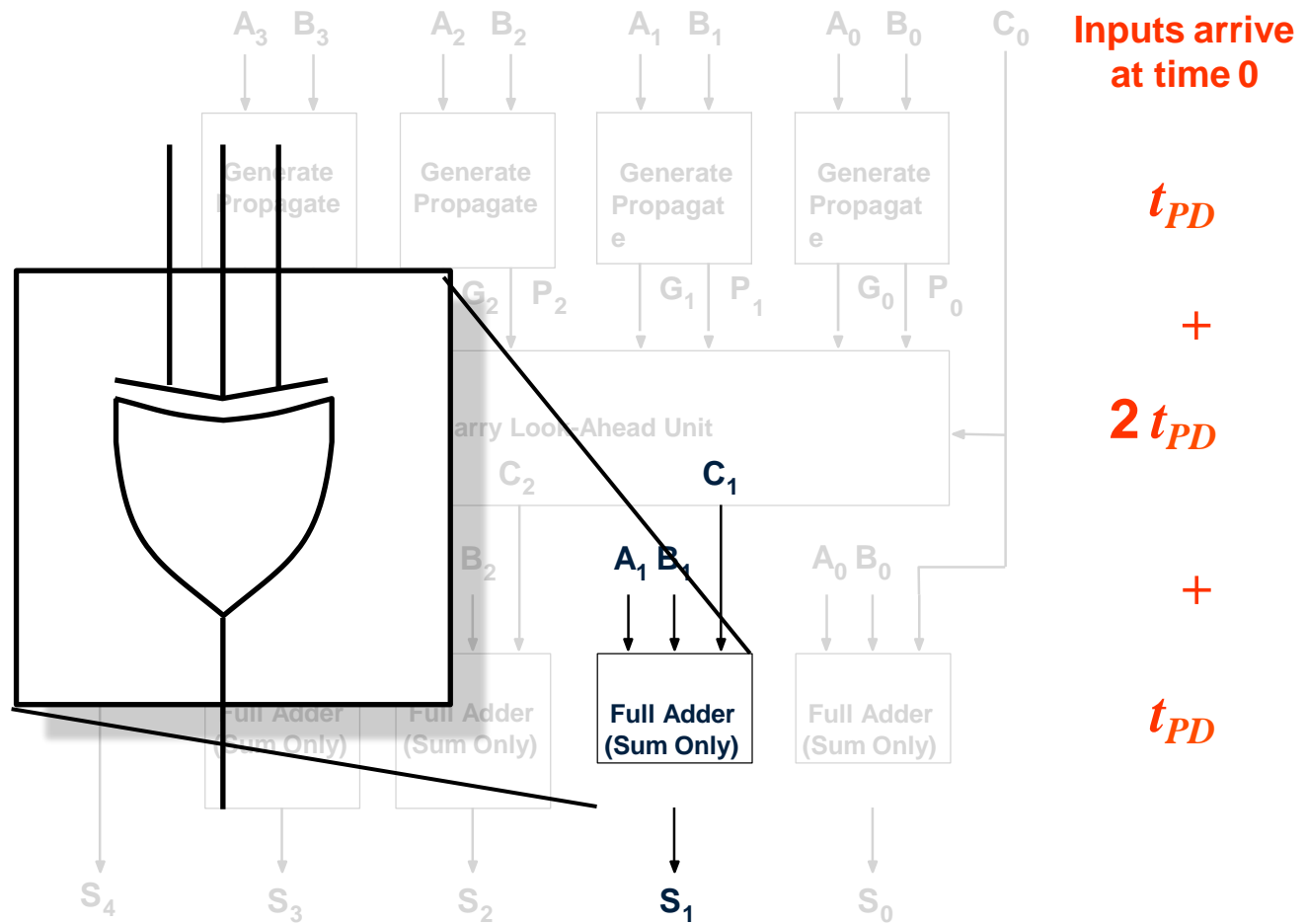

CLA: Overall Critical Path Delay

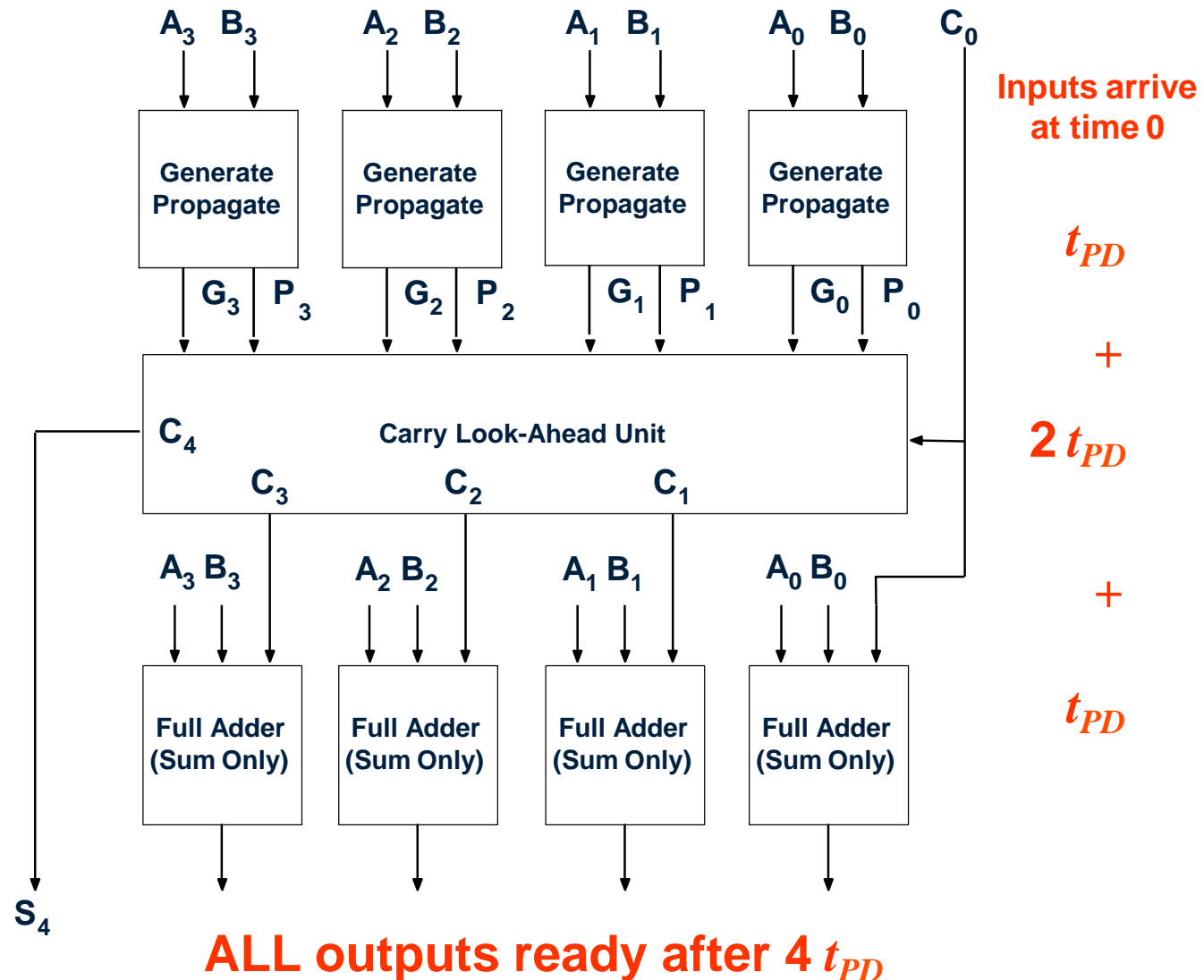

The total delay in the n-bit carry-lookahead adder is four gate delays

CLA: Overall Critical Path Delay

$A_3 \ B_3$

$A_2 \ B_2$

$A_1 \ B_1$

$A_0 \ B_0$

C_0

AWESOME!

\downarrow
 S_4

\downarrow

\downarrow

\downarrow

\downarrow

ALL outputs ready after $4 t_{PD}$

The total delay in the n-bit carry-lookahead adder is four gate delays

But there are still few wrinkles to iron out...

- What about CLA Scalability?

In theory, we could build Carry Look-Ahead Adders of any size N

However, equations get more complex very quickly, and we need wider and wider gates (slow) in the carry logic.

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0$$


$$C_3 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

$$C_4 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

**Typically do not extend beyond 4-bits
due to fan-in constraints**

Recommended Reading

 - Digital System Design with Verilog HDL, 3/e, b **S**tephen Brown and **Z**vonko Vranesic. [**S&Z**]
 - S&Z,
 - Chapter-3
 - 3.4



THANK YOU

