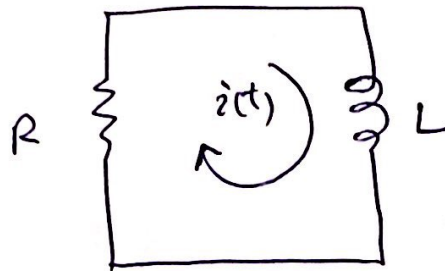


8.1 The Source-Free RL Circuit

(PP261 8th Ed HKD)

Consider the circuit:-



$$\text{Given } i(t_0) = i(0) = I_0$$

(Fig 8.1 A series RL circuit)

— Applying KVL,

$$Ri + L \frac{di}{dt} = 0$$

$$\text{or } \frac{di}{dt} + \frac{R}{L} i = 0 \quad \text{--- (A)}$$

We've to solve this differential equation to determine $i(t)$.

— Assume that the solution is:

$$i(t) = Ae^{s_1 t}$$

where A and s_1 are unknown constants.

————— contd

—contd (261)

— Now $\frac{di}{dt} = A s_1 e^{s_1 t}$

— Hence (A) becomes

$$A_1 e^{s_1 t} + \frac{R}{L} A e^{s_1 t} = 0$$

$$\text{or } Ae^{s_1 t} \left(s_1 + \frac{R}{L} \right) = 0$$

— Therefore $\delta_1 + \frac{R}{L} = 0$

$$\text{or } \mathcal{L}_1 = -\frac{R}{L}$$

Hence $i(t) = A e^{-R/L t}$

At $t=0$ $\dot{z}(t_0) = A \times 1 = I_0$ (Given)

$$S_0 \quad i(t) = I_0 e^{-R/L t}, \quad A$$

— This is the functional form of the source-free response.

— it is called "natural response"

— also called "transient response"

Note: The circuits with a single storage element are "first-order circuits".




(Example)

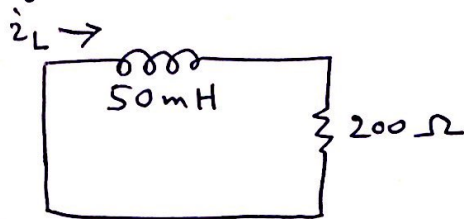Example 8.1 The Source-Free RL Circuit

(PD 263 8th Ed HKD)

If $i_L = 2 \text{ A}$ at $t = 0$, find an expression for $i_L(t)$ valid for $t > 0$ and its value at $t = 200 \mu\text{s}$.



Given $i_L(0) = 2 \text{ A}$

Solution: We have learnt that the functional form of the source-free current shall be:

$$i_L(t) = I_0 e^{-\frac{R}{L}t} \text{ A}$$

Now $R = 200 \Omega$ and $L = 50 \text{ mH}$

and $I_0 = 2 \text{ A}$ ie $i_L(0) = I_0 = 2 \text{ A}$ (Given)

$$\text{So } i_L(t) = 2 e^{-\frac{200}{50 \times 10^{-3}}t}$$

$$\text{or } i_L(t) = 2 e^{-4000t} \text{ A } t > 0$$

— $i_L(t)$ at $t = 200 \mu\text{s}$ is:

$$i_L(200 \times 10^{-6} \text{ s}) = 2 e^{-4000 \times 200 \times 10^{-6}}$$

$$= 2 e^{-0.8} = 2 \times 0.449$$


$$= 0.8987 \text{ A}$$

or

$$= 898.7 \text{ mA}$$

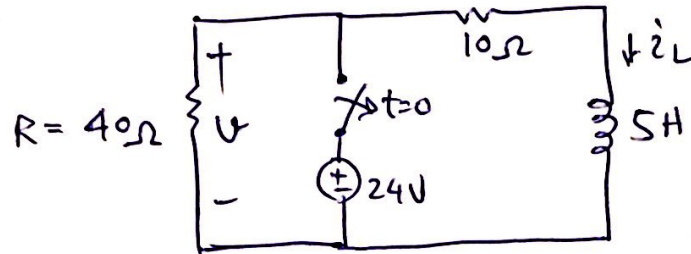
Example 8.2 The Source-Free RL circuit
(11266 8th Ed HKD)

Find the voltage labelled 'v' at $t = 200 \text{ ms}$.



Solution:

At $t \geq 0$ the circuit becomes

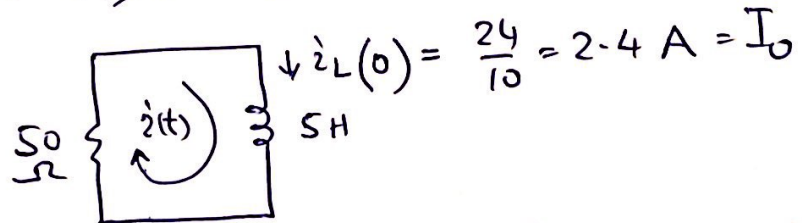

— The functional form of the response is :-

$$i(t) = I_0 e^{-R/L t}$$

$$\text{or } i(t) = 2.4 e^{-\frac{50}{5} t} = 2.4 e^{-10 t} \text{ A}$$

$$\text{So } v(200 \text{ ms}) = \left(\underset{=}{40} \times 2.4 e^{-10 \times 200 \times 10^{-3}} \right) \text{ V}$$

$$\text{or } v(200 \text{ ms}) = -96 e^{-2} = -96 \times 0.1353$$

$$\text{Hence } v(200 \text{ ms}) = -12.99 \text{ V}$$

Note: Disregard the lengthier approach in text book.