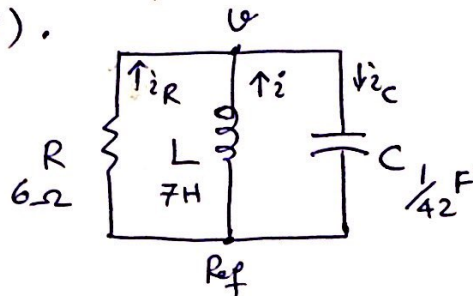


Example: The Overdamped Parallel RLC Circuit: $\alpha > \omega_0$

(PP326 8th Ed HKD)

Determine $v(t)$.



Given:

$$\left. \begin{array}{l} v(0) = 0 \text{ V} \\ \text{and } i(0) = 10 \text{ A} \end{array} \right\} \text{ (as defined in figure)}$$

Solution: We identify it as a parallel RLC circuit so;

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 6 \times \frac{1}{42}} = 3.5 \quad \left(\alpha = \frac{R}{2L} \text{ — series} \right)$$

$$\text{and } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{7 \times \frac{1}{42}}} = 2.45 \quad (\text{resonant frequency})$$

$$\text{Now } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1$$

$$\text{and } s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6$$

— As $\alpha > \omega_0$ so;

the general form of the response is:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{or } v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

— To determine A_1 and A_2 ;

we know $v(0) = 0$

$$\text{So } v(t) = v(0) = 0 = A_1 + A_2$$

_____ contd

— contd (326)

$$\text{Hence } A_1 + A_2 = 0$$

①

Also the derivative of $v(t)$

$$v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

$$\frac{dv}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$$

— At $t=0$

$$\left. \frac{dv}{dt} \right|_{t=0} = -A_1 - 6A_2$$

— We know $i_c = C \frac{dv}{dt}$

$$\text{or } \frac{dv}{dt} = \frac{1}{C} i_c$$

— Now KCL must hold at any instant in time,

$$\text{thus } i(0) + i_R(0) = i_c(0)$$

$$10 + \frac{v(0)}{R} = i_c(0)$$

$$\text{So } 10 + 0 = i_c(0)$$

$$i_c(0) = 10$$

Given:

$$\left\{ \begin{array}{l} i(0) = 10 \\ v(0) = 0 \end{array} \right. \text{ and } \}$$

$$\text{— Hence } \left. \frac{dv}{dt} \right|_{t=0} = \frac{i_c(0)}{C} = \frac{10}{\frac{1}{42}} = 420 \text{ V/s}$$

— So we get

$$-A_1 - 6A_2 = 420$$

②

— contd

— contd (327)

Now solving ① and ②

$$A_1 = 84 \quad \text{and}$$

$$A_2 = -84$$

— Therefore

$$u(t) = 84e^{-t} - 84e^{-6t}$$

$$\text{or } u(t) = 84(e^{-t} - e^{-6t}) \quad \text{V}$$

Ans