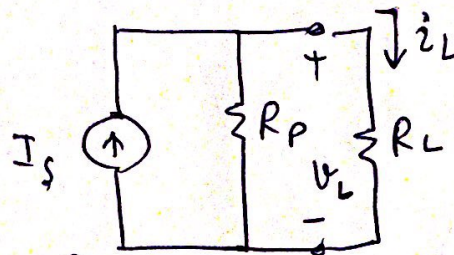


Maximum Power Transfer Theorem

A practical current source provides 10W to a 250Ω load. It provides 20W when connected to an 80Ω load. Find the value of R_L to which maximum power is delivered by this practical current source.

Solution: The circuit is :-



Now $P_L = I_L^2 R_L$ so we know $10 = I_L^2 \times 250$

and $20 = I_L^2 \times 80$

Also $P_L = \left(\frac{I_s R_p}{R_p + R_L} \right)^2 R_L$

so $10 = \left(\frac{I_s R_p}{R_p + 250} \right)^2 \times 250$ ^① and $20 = \left(\frac{I_s R_p}{R_p + 80} \right)^2 \times 80$ ^②

Dividing $\frac{20}{10} = \frac{80}{250} \left(\frac{R_p + 250}{R_p + 80} \right)^2$

$\sqrt{\frac{50}{8}} = \frac{R_p + 250}{R_p + 80}$ or $\frac{5}{2} = \frac{R_p + 250}{R_p + 80}$

so $5R_p + 400 = 2R_p + 500 \Rightarrow R_p = \frac{100}{3} \Omega$

For max power transfer

$R_L = R_p = \frac{100}{3} \Omega$