

EE-421: Digital System Design

Structural vs Behavioural Verilog

Instructor: Dr. Rehan Ahmed [rehan.ahmed@seecs.edu.pk]


Structural vs. Behavioral Implementation

Two Main Styles of HDL Implementation

- **Structural (Gate-Level)**
 - The module body contains **gate-level description** of the circuit
 - Describe how modules are interconnected
 - Each module contains other modules (instances)
 - ... and interconnections between these modules
 - Describes a hierarchy
- **Behavioral**
 - The module body contains **functional description** of the circuit
 - Contains logical and mathematical **operators**
 - **Level of abstraction is higher than gate-level**
 - Many possible gate-level realizations of a behavioral description
- **Practical circuits use a combination of both**

Structural HDL (Gate-Level)

 
Structural Specification of Logic Ccts i.e Gate-Level Primitives



```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

Structural Specification of Logic Ccts i.e Gate-Level Primitives
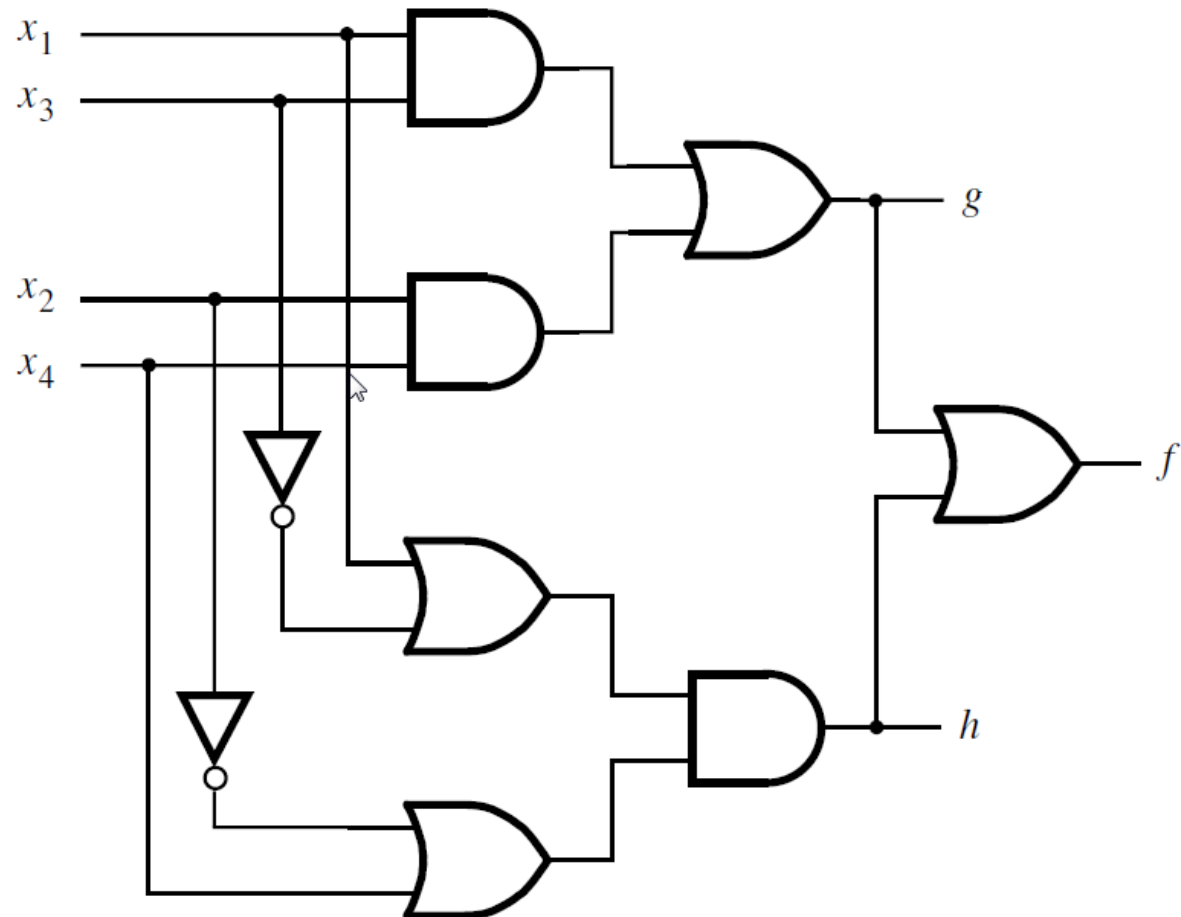
```
module example2 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  and (z1, x1, x3);  
  and (z2, x2, x4);  
  or (g, z1, z2);  
  or (z3, x1, ~x3);  
  or (z4, ~x2, x4);  
  and (h, z3, z4);  
  or (f, g, h);  
  
endmodule
```




Gate Primitives: For Reference

Name	Description	Usage
and	$f = (a \cdot b \cdots)$	and (f , a, b, \dots)
nand	$f = \overline{(a \cdot b \cdots)}$	nand (f , a, b, \dots)
or	$f = (a + b + \cdots)$	or (f , a, b, \dots)
nor	$f = \overline{(a + b + \cdots)}$	nor (f , a, b, \dots)
xor	$f = (a \oplus b \oplus \dots)$	xor (f , a, b, \dots)
xnor	$f = (a \boxplus b \boxplus \dots)$	xnor (f , a, b, \dots)
not	$f = \overline{a}$	not (f , a)
buf	$f = a$	buf (f , a)

Your Turn

 Express the following using Structural HDL




Behavioral HDL

- **Behavioral HDL to Rescue!!!**
- *Behavioral* constructs specify an operation on bits
 - High-level, more abstract
 - Specified as behavior of a logic cct, e.g., $\text{out} = (\text{a} \ \& \ \text{b}) \mid \text{c}$

Behavioral Specification of Logic Circuits

- **Using logic expressions:** $[f = s'x1 + sx2]$

```
module example3 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  assign f = (~s & x1) | (s & x2);  
  
endmodule
```

 

- The **assign** keyword provides a **continuous assignment** for the signal f :
 - whenever any signal on the right-hand side changes its state, the value of f will be **re-evaluated**.


Behavioral Specification of Logic Circuits

- **Using behavioral specification.**

```
// Behavioral specification
module example5 (x1, x2, s, f);
  input x1, x2, s;
  output f;
  reg f;


  always @(x1 or x2 or s)
    if (s == 0)
      f = x1;
    else
      f = x2;

endmodule
```

 


Behavioral HDL: Defining Functionality



```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

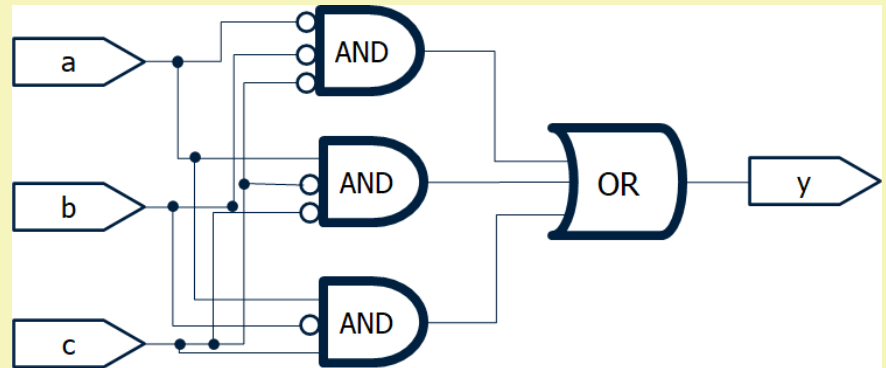

Remember: Synthesizing the “example”

 

Remember: Simulating the “example”

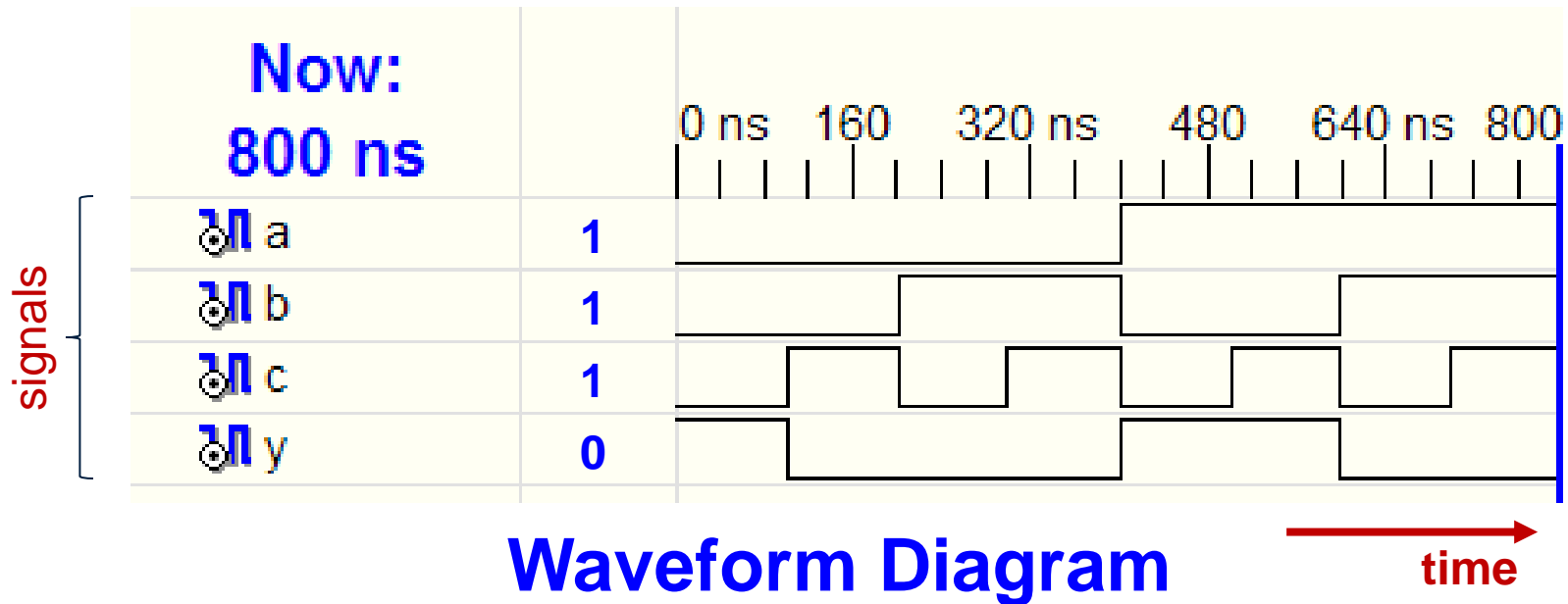 

Recommended Reading

- S&Z, 2.10 and Appendix-A