



Chapter6: Registers and Counters

Lecture4- Problem-Solving Session


Engr. Arshad Nazir, Asst Prof
Dept of Electrical Engineering
SEECS

Problem6-6: Design a four-bit shift register with parallel load, using D flip-flops. There are two control inputs: Shift and Load. When Shift=1, the contents of the register are shifted by one position. New data are transferred into the register when Load=1 and Shift=0. If both control inputs are equal to 0, the contents of the register do not change.

Problem6-7: Draw the logic diagram of a 4-bit register with four D flip-flops and four 4:1 multiplexers with mode selection inputs S1 and S0. The register operates according to the following function table.

s₁	s₀	Register Operation
0	0	No change
0	1	Complement the four outputs
1	0	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

Problem 6-13: Show that a BCD ripple counter can be constructed from a 4-bit binary ripple counter with asynchronous Clear input and a NAND gate that detects the occurrence of the count 1010.

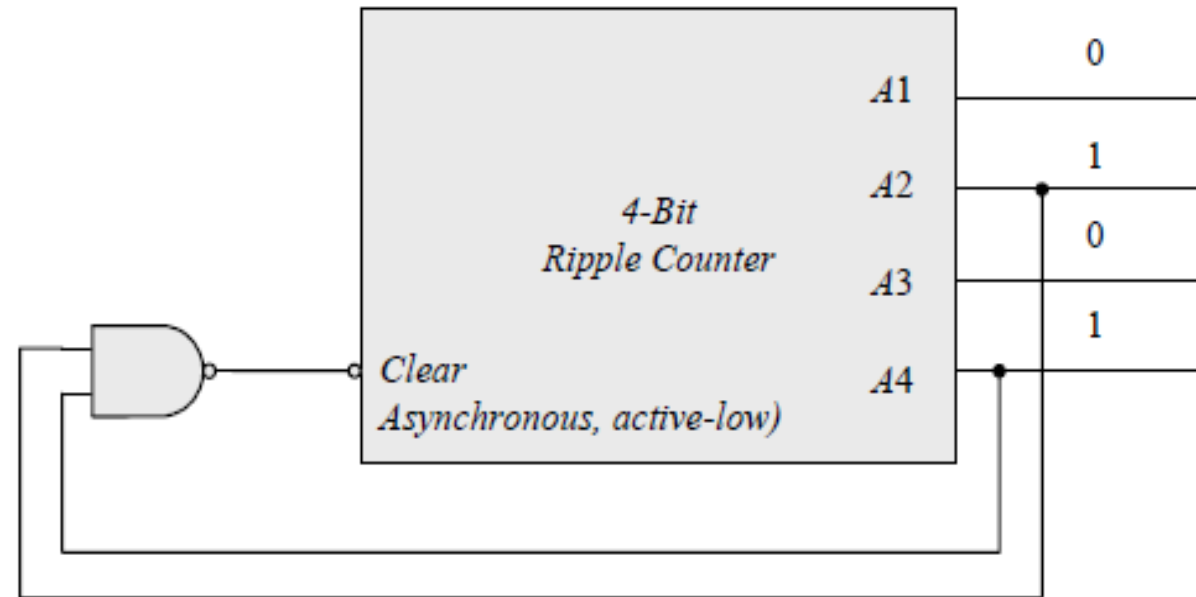

Problem 6-19: The flip-flop input equations for a BCD counter using T flip-flops are given in section 6-4. Obtain the input equations for a BCD counter that uses

(a) JK flip-flops and

(b) D flip-flops

(b) From the state table in Table 6.5:

$$D_{Q1} = Q'_1$$

$$D_{Q2} = \sum (1, 2, 5, 6)$$

$$D_{Q4} = \sum (3, 4, 5, 6)$$

$$D_{Q8} = \sum (7, 8)$$

$$\text{Don't care: } d = \sum (10, 11, 12, 13, 14, 15)$$

Simplifying with maps:

$$D_{Q2} = Q_2Q'_1 + Q'_8Q'_2Q_1$$

$$D_{Q4} = Q_4Q'_1 + Q_4Q'_2 + Q'_4Q_2Q_1$$

$$D_{Q8} = Q_8Q'_1 + Q_4Q_2Q_1$$

Problem 6-28: Design a 3-bit counter with the following repeated binary sequence: 0, 1, 2, 4, 6. Use D flip-flops. Is your counter self-correcting.

<i>Present state ABC</i>	<i>Next state ABC</i>
000	001
001	010
010	100
011	XXX
100	110
101	XXX
110	000
111	XXX

		<i>BC</i>			
<i>A</i>				<i>B</i>	
		00	01	11	10
<i>A</i>	0	m_0	m_1	m_3 X	m_2 1
	1	m_4 1	m_5 X	m_7 X	m_6

$$D_A = A \oplus B$$


		BC			
		00	01	11	10
A	0	m_0 1	m_1 x	m_3 x	m_2 1
	1	m_4 1	m_5 x	m_7 x	m_6

$$D_B = AB' + C$$

		BC			
		00	01	11	10
A	0	m_0 1	m_1	m_3 x	m_2
	1	m_4	m_5 x	m_7 x	m_6

$$D_C = A'B'C'$$

Self-correcting

 


Problem: Design a synchronous modulo-6 up-down counter with a single input line x . The counter uses a creeping code, advances following $x=0$ and regresses for $x=1$. it operates as under:-

When $x=0$: counts up through the sequence 000, 001, 011, 111, 110, 100, and repeat

When $x=1$: counts down through the sequence 000, 100, 110, 111, 011, 001, and repeat.

 - (a) Draw the state diagram
- (b) List the state transition table
- (c) Design the modulo-6 up-down counter with D flip-flops and external AND, OR, and NOT gates as required.



(a)

	$y_1^+ y_2^+ y_3^+$	
$y_1 y_2 y_3$	$x = 0$	$x = 1$
000	001	100
100	000	110
110	100	111
111	110	011
011	111	001
001	011	000

(b)

Figure State table and transition table for a modulo-6 up-down counter.

		<i>WX</i>			
		00	01	11	10
<i>yz</i>	00			1	1
	01		×	×	
	11	1	1		
	10	×	1	1	×

$$D_1 = x'y_2 + xy_3'$$

		<i>WX</i>			
		00	01	11	10
<i>yz</i>	00			1	
	01	1	×	×	
	11	1	1	1	
	10	×		1	×

$$D_2 = x'y_3 + xy_1$$

		<i>WX</i>			
		00	01	11	10
<i>yz</i>	00	1			
	01	1	×	×	
	11	1		1	1
	10	×		1	×

$$D_3 = x'y_1' + xy_2$$

 


Figure Design of Modulo-6 up-down Counter with D Flip-Flops and external gates

The End